

Network Theorems (Application to dc Networks)

3.1 INTRODUCTION

In Chapter 2, we have studied elementary network theorems like Kirchhoff's laws, mesh analysis and node analysis. There are some other methods also to analyse circuits. In this chapter, we will study superposition theorem, Thevenin's theorem, Norton's theorem, maximum power transfer theorem, reciprocity theorem, Millman's theorem, Tellegen's theorem, substitution theorem and compensation theorem. We can find currents and voltages in various parts of the circuits with these methods.

3.2 SUPERPOSITION THEOREM

It states that '*in a linear network containing more than one independent source and dependent source, the resultant current in any element is the algebraic sum of the currents that would be produced by each independent source acting alone, all the other independent sources being represented meanwhile by their respective internal resistances.*'

The independent voltage sources are represented by their internal resistances if given or simply with zero resistances, i.e., short circuits if internal resistances are not mentioned. The independent current sources are represented by infinite resistances, i.e., open circuits.

The dependent sources are not sources but dissipative components—hence they are active at all times. A dependent source has zero value only when its control voltage or current is zero.

A linear network is one whose parameters are constant, i.e., they do not change with voltage and current.

Explanation Consider the network shown in Fig. 3.1. Suppose we have to find current I_4 through resistor R_4 .

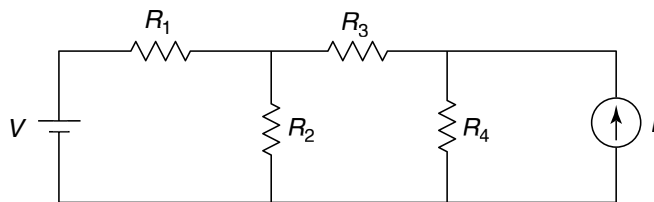


Fig. 3.1 Network to illustrate superposition theorem

3.2 Network Analysis and Synthesis

The current flowing through resistor R_4 due to constant voltage source V is found to be say I_4' (with proper direction), representing constant current source with infinite resistance, i.e., open circuit.

The current flowing through resistor R_4 due to constant current source I is found to be say I_4'' (with proper direction), representing the constant voltage source with zero resistance or short circuit.

The resultant current I_4 through resistor R_4 is found by superposition theorem.

$$I_4 = I_4' + I_4''$$

Steps to be followed in Superposition Theorem

1. Find the current through the resistance when only one independent source is acting, replacing all other independent sources by respective internal resistances.
2. Find the current through the resistance for each of the independent sources.
3. Find the resultant current through the resistance by the superposition theorem considering magnitude and direction of each current.

Example 3.1

Find the current through the $2\ \Omega$ resistor in Fig. 3.4.

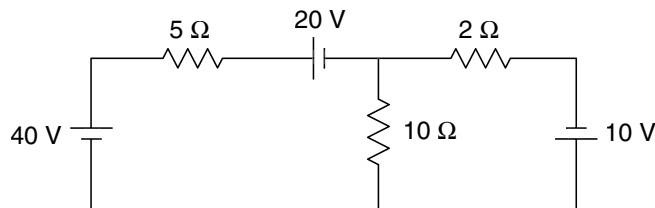


Fig. 3.4

Solution

Step I When the 40 V source is acting alone (Fig. 3.5)

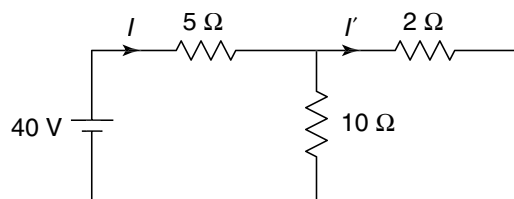


Fig. 3.5

By series parallel reduction technique (Fig. 3.6),

$$I = \frac{40}{5 + 1.67} = 6\text{ A}$$

From Fig. 3.5, by current-division rule,

$$I' = 6 \times \frac{10}{10 + 2} = 5\text{ A (} \rightarrow \text{)}$$

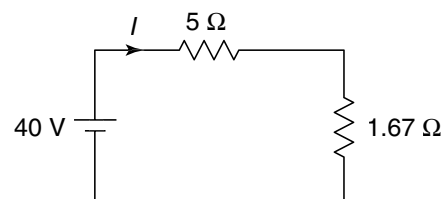


Fig. 3.6

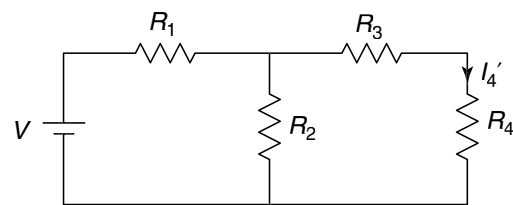


Fig. 3.2 When voltage source V is acting alone

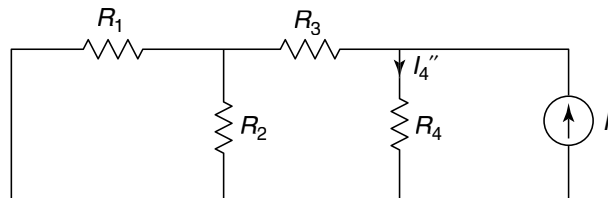


Fig. 3.3 When current source I is acting alone

Step II When the 20 V source is acting alone (Fig. 3.7)

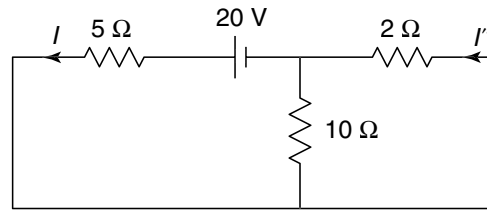


Fig. 3.7

By series–parallel reduction technique (Fig. 3.8),

$$I = \frac{20}{5 + 1.67} = 3 \text{ A}$$

From Fig. 3.7, by current-division rule,

$$I'' = 3 \times \frac{10}{10 + 2} = 2.5 \text{ A} (\leftarrow) = -2.5 \text{ A} (\rightarrow)$$

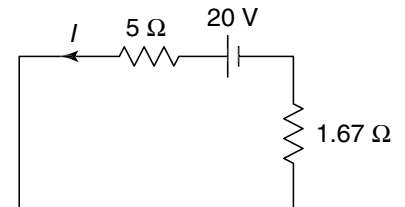


Fig. 3.8

Step III When the 10 V source is acting alone (Fig. 3.9)

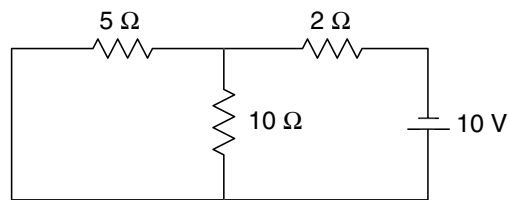


Fig. 3.9

By series–parallel reduction technique (Fig. 3.10),

$$I''' = \frac{10}{3.33 + 2} = 1.88 \text{ A} (\rightarrow)$$

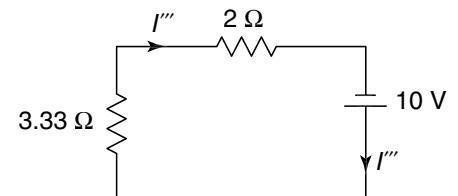


Fig. 3.10

Step IV By superposition theorem,

$$I = I' + I'' + I''' = 5 - 2.5 + 1.88 = 4.38 \text{ A} (\rightarrow)$$

Example 3.2

Find the current through the 1 Ω resistor in Fig. 3.11.

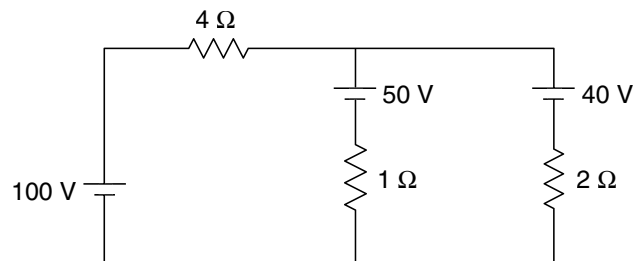


Fig. 3.11

Solution

Step I When the 100 V source is acting alone (Fig. 3.12)

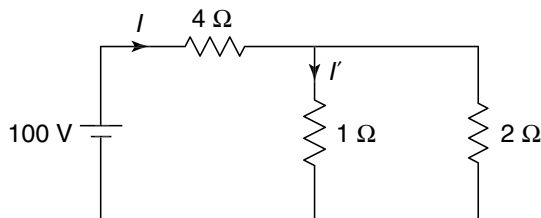


Fig. 3.12

By series-parallel reduction technique (Fig. 3.13),

$$I = \frac{100}{4 + 0.67} = 21.41 \text{ A}$$

From Fig. 3.12, by current-division rule,

$$I' = 21.41 \times \frac{2}{2+1} = 14.27 \text{ A} (\downarrow)$$

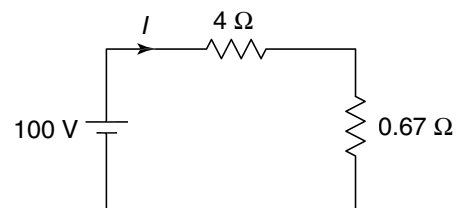


Fig. 3.13

Step II When the 50 V source is acting alone (Fig. 3.14)

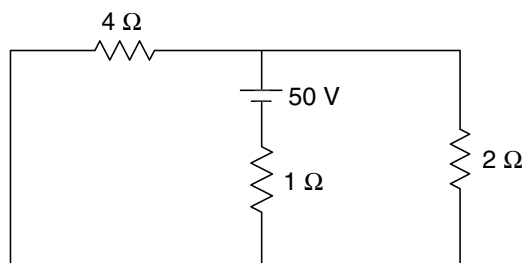


Fig. 3.14

By series-parallel reduction technique (Fig. 3.15),

$$I'' = \frac{50}{1 + 1.33} = 21.46 \text{ A} (\uparrow) = -21.46 \text{ A} (\downarrow)$$

Step III When the 40 V source is acting alone (Fig. 3.16)



Fig. 3.15

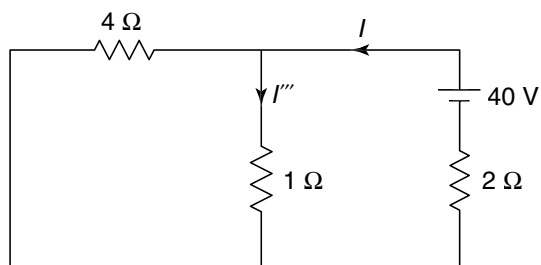


Fig. 3.16

By series–parallel reduction technique (Fig. 3.17),

$$I = \frac{40}{0.8 + 2} = 14.29 \text{ A}$$

From Fig. 3.16, by current-division rule,

$$I''' = 14.29 \times \frac{4}{4 + 1} = 11.43 \text{ A}(\downarrow)$$

Step IV By superposition theorem,

$$I = I' + I'' + I''' = 14.27 - 21.46 + 11.43 = 4.24 \text{ A}(\downarrow)$$

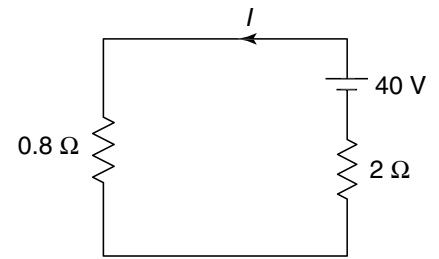


Fig. 3.17

Example 3.3

Find the current through the 8Ω resistor in Fig. 3.18.

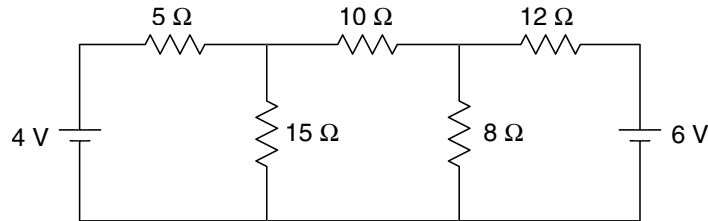


Fig. 3.18

Solution

Step I When the 4 V source is acting alone (Fig. 3.19)



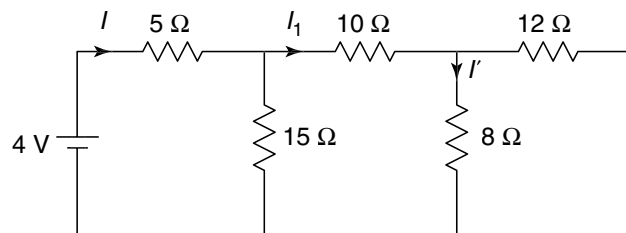


Fig. 3.19

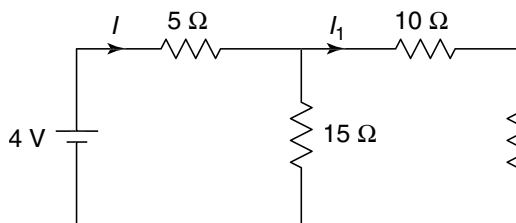By series–parallel reduction technique (Fig. 3.20),



(a)

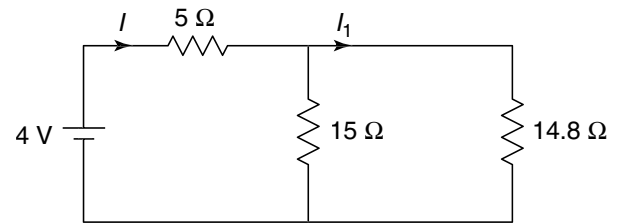

(b)


$$I = \frac{4}{5 + 7.45} = 0.32 \text{ A}$$

From Fig. 3.20(b), by current-division rule,

$$I_1 = 0.32 \times \frac{15}{15 + 14.8} = 0.16 \text{ A}$$

From Fig. 3.19, by current-division rule,
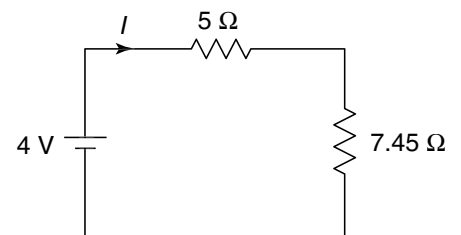
$$I' = 0.16 \times \frac{12}{12 + 8} = 0.096 \text{ A}(\downarrow)$$



(c)

Fig. 3.20

Step II When the 6 V source is acting alone (Fig. 3.21)


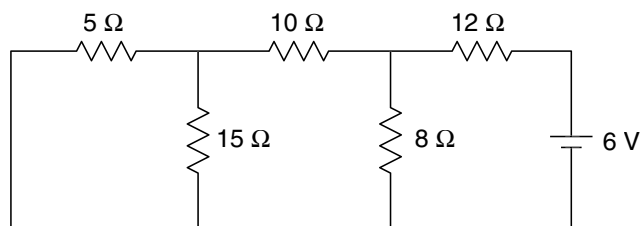


Fig. 3.21

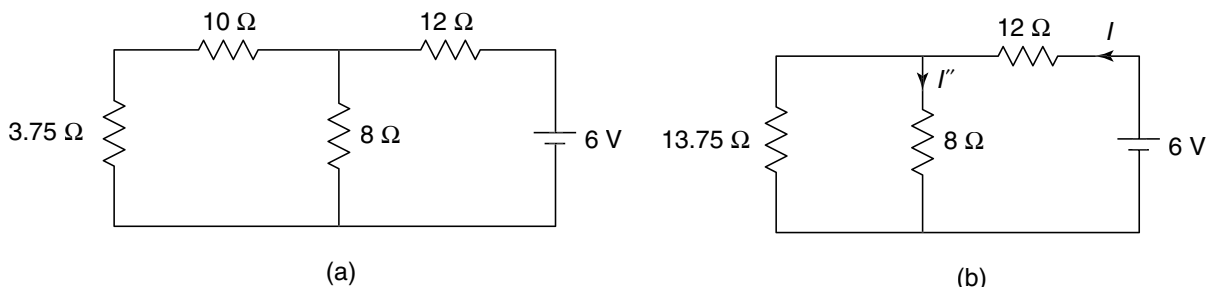By series-parallel reduction technique (Fig. 3.22),



$$I = \frac{6}{12 + 5.06} = 0.35 \text{ A}$$

From Fig. 3.22(b), by current division rule,

$$I'' = 0.35 \times \frac{13.75}{13.75 + 8} = 0.22 \text{ A (↓)}$$

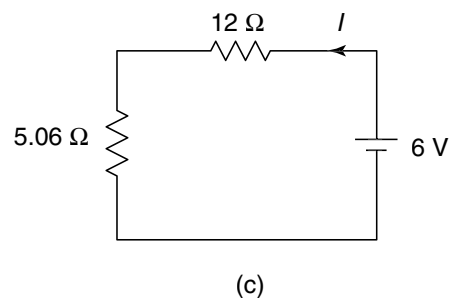


Fig. 3.22

Step III By superposition theorem,

$$I = I' + I'' = 0.096 + 0.22 = 0.316 \text{ A (↓)}$$

Example 3.4

Find the current through the 4 Ω resistor in Fig. 3.23.

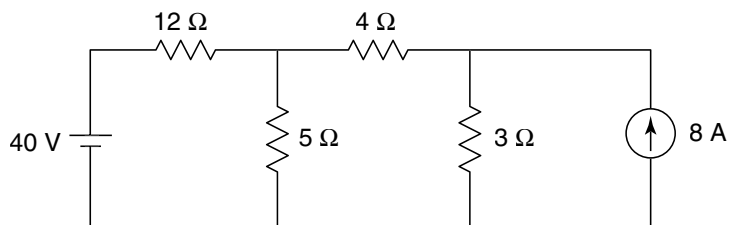


Fig. 3.23

Solution

Step I When the 40 V source is acting alone (Fig. 3.24)

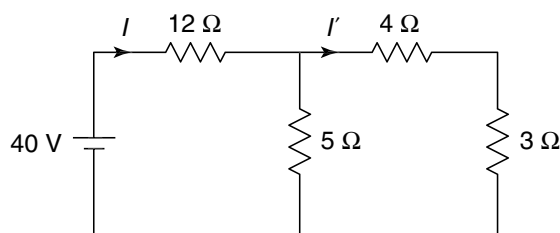


Fig. 3.24

By series–parallel reduction technique (Fig. 3.25),

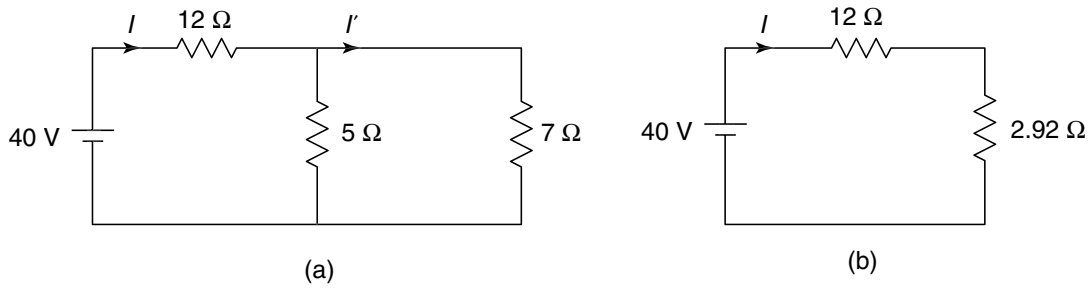


Fig. 3.25

$$I = \frac{40}{12 + 2.92} = 2.68 \text{ A}$$

From Fig. 3.25(a), by current-division rule,

$$I' = 2.68 \times \frac{5}{5 + 7} = 1.12 \text{ A} (\rightarrow) = -1.12 \text{ A} (\leftarrow)$$

Step II When the 8 A source is acting alone (Fig. 3.26)

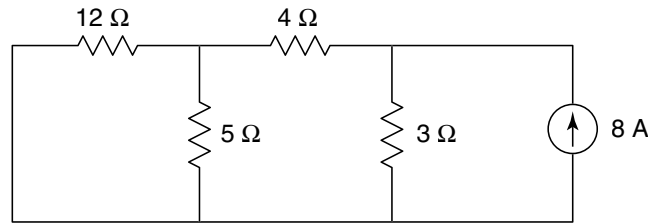


Fig. 3.26

By series–parallel reduction technique (Fig. 3.27),

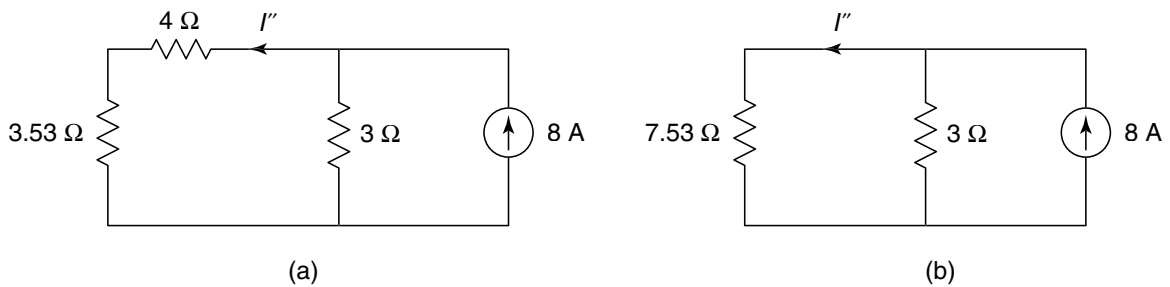
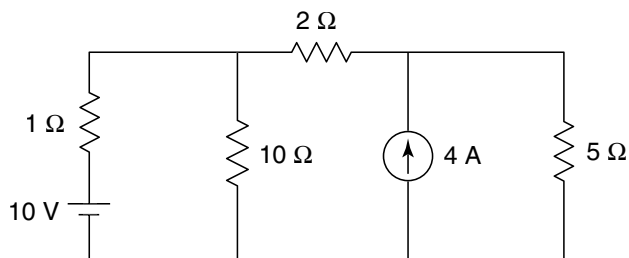
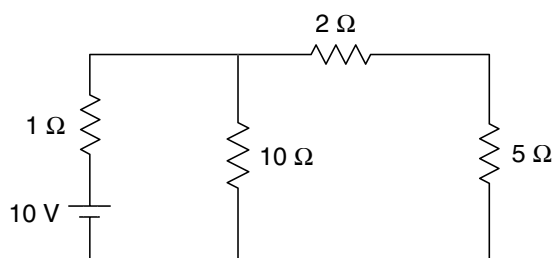


Fig. 3.27


$$I'' = 8 \times \frac{3}{7.53 + 3} = 2.28 \text{ A} (\leftarrow)$$

Step III By superposition theorem,

$$I = I' + I'' = -1.12 + 2.28 = 1.16 \text{ A} (\leftarrow)$$

Example 3.5Find the current in the $10\ \Omega$ resistor in Fig. 3.28.**Fig. 3.28****Solution****Step I** When the 10 V source is acting alone (Fig. 3.29)**Fig. 3.29**

By series-parallel reduction technique (Fig. 3.30),

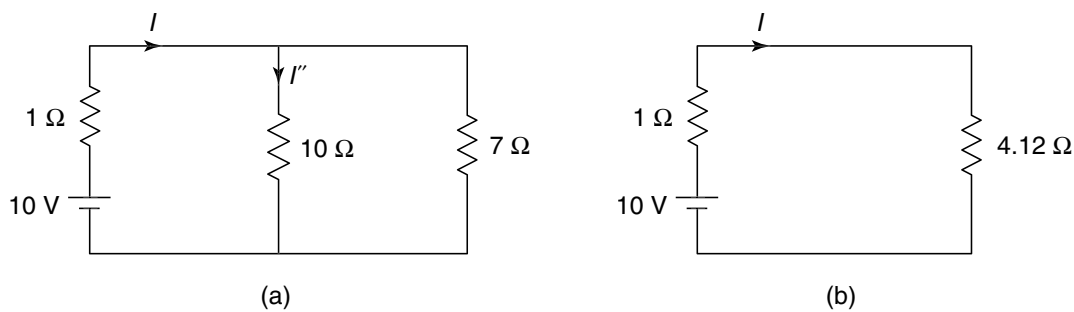**Fig. 3.30**

$$I = \frac{10}{1 + 4.12} = 1.95\text{ A}$$

From Fig. 3.30 (a), by current-division rule,

$$I' = 1.95 \times \frac{7}{7 + 10} = 0.8\text{ A}(\downarrow)$$

Step II When the 4 A source is acting alone (Fig. 3.31)

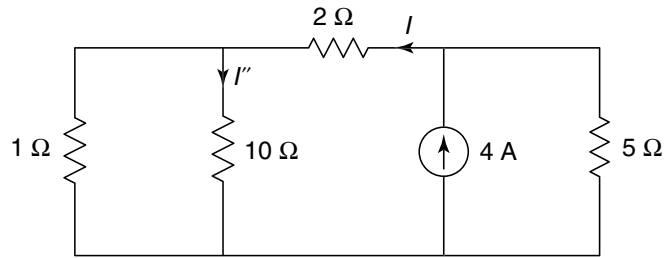


Fig. 3.31

By series-parallel reduction technique (Fig. 3.32),

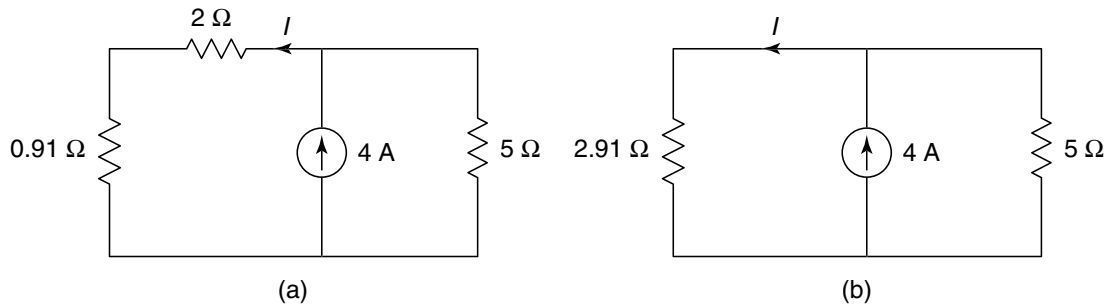


Fig. 3.32

$$I = 4 \times \frac{5}{2.91 + 5} = 2.53 \text{ A}$$

From Fig. 3.31, by current-division rule,

$$I'' = 2.53 \times \frac{1}{1 + 10} = 0.23 \text{ A} (\downarrow)$$

Step III By superposition theorem,

$$I = I' + I'' = 0.8 + 0.23 = 1.03 \text{ A} (\downarrow)$$

Example 3.6

Find the current through the 8 Ω resistor in Fig. 3.33.

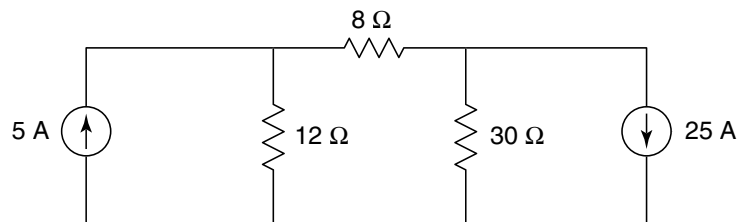


Fig. 3.33

3.10 Network Analysis and Synthesis

Solution

Step I When the 5 A source is acting alone (Fig. 3.34)

$$I' = 5 \times \frac{12}{12 + 8 + 30} = 1.2 \text{ A } (\rightarrow)$$

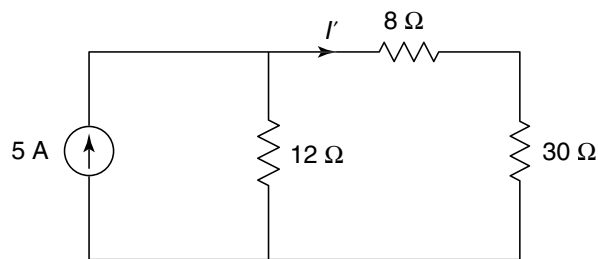


Fig. 3.34

Step II When the 25 A source is acting alone (Fig. 3.35)

$$I'' = 25 \times \frac{30}{30 + 12 + 8} = 15 \text{ A } (\rightarrow)$$

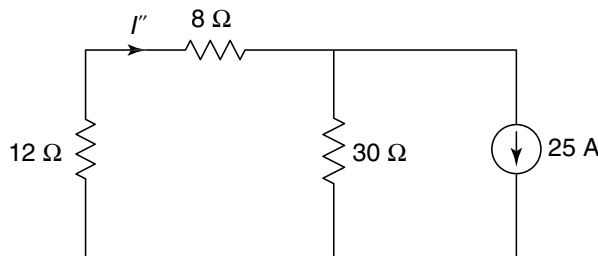


Fig. 3.35

Step III By superposition theorem,

$$I = I' + I'' = 1.2 + 15 = 16.2 \text{ A } (\rightarrow)$$

Example 3.7

Find the current through the 4 Ω resistor in Fig. 3.36.

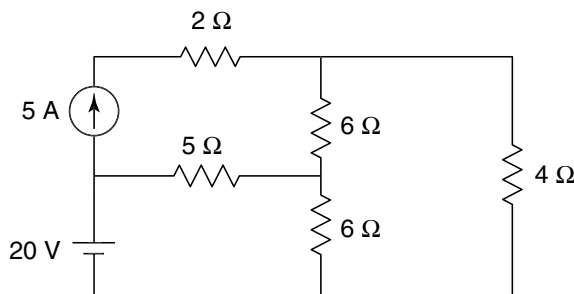


Fig. 3.36

Solution

Step I When the 5 A source is acting alone (Fig. 3.37)

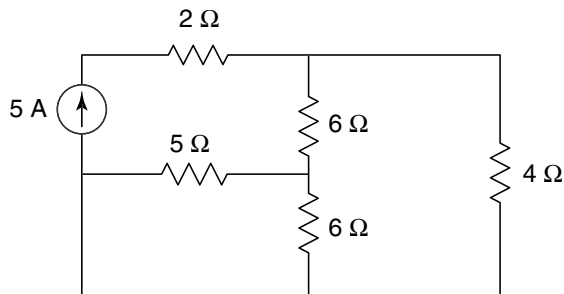
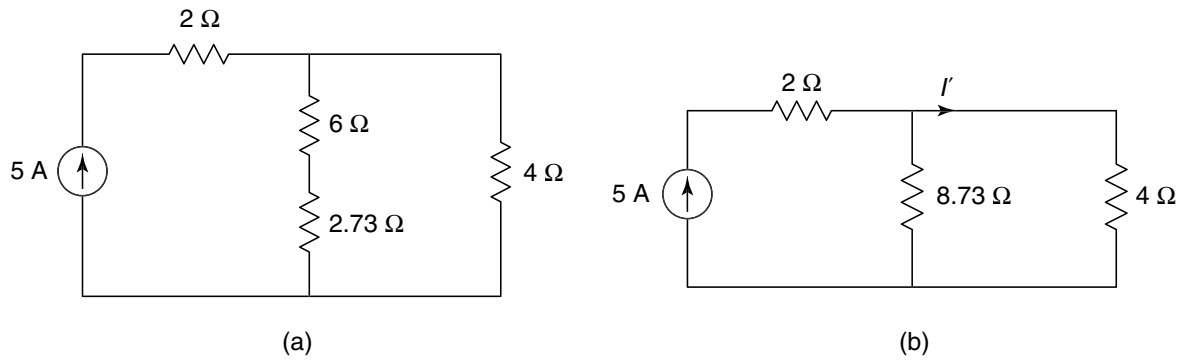



Fig. 3.37

By series-parallel reduction technique (Fig. 3.38),


**Fig. 3.38**

$$I' = 5 \times \frac{8.73}{8.73 + 4} = 3.43 \text{ A}(\downarrow)$$

Step II When the 20 V source is acting alone (Fig. 3.39)

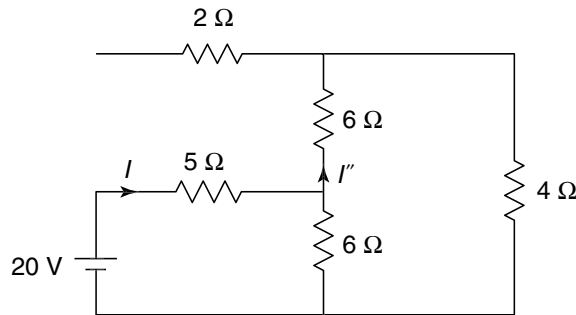**Fig. 3.39**

By series-parallel reduction technique (Fig. 3.40),

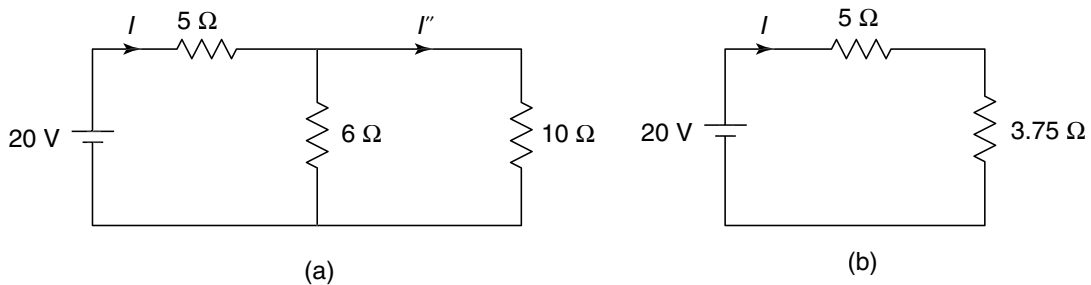**Fig. 3.40**



$$I = \frac{20}{5 + 3.75} = 2.29 \text{ A}$$

From Fig. 3.40 (a), by current-division rule,

$$I'' = 2.29 \times \frac{6}{6 + 10} = 0.86 \text{ A}(\downarrow)$$



Step III By superposition theorem

$$I = I' + I'' = 3.43 + 0.86 = 4.29 \text{ A}(\downarrow)$$

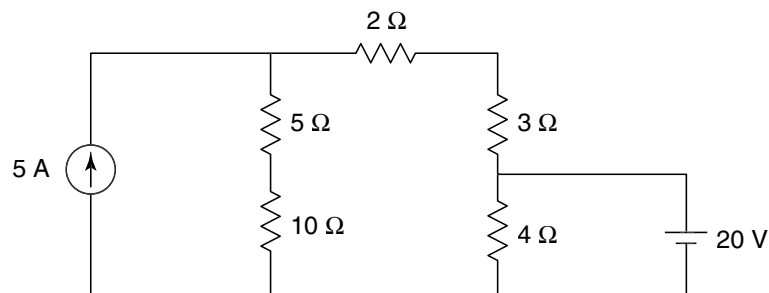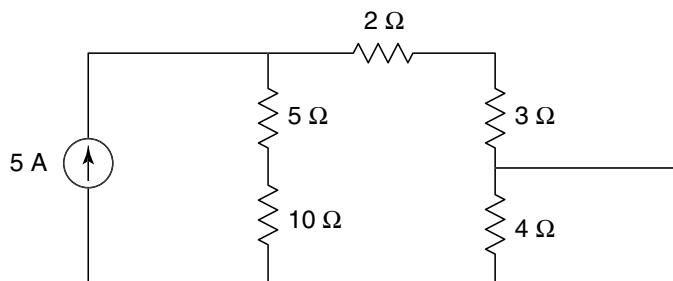
Example 3.8Find the current through the $3\ \Omega$ resistor in Fig. 3.41.**Fig. 3.41****Solution****Step I** When the 5 A source is acting alone (Fig. 3.42)**Fig. 3.42**

By series-parallel reduction technique (Fig. 3.43),

$$I' = 5 \times \frac{15}{15 + 2 + 3} = 3.75\text{ A}(\downarrow)$$

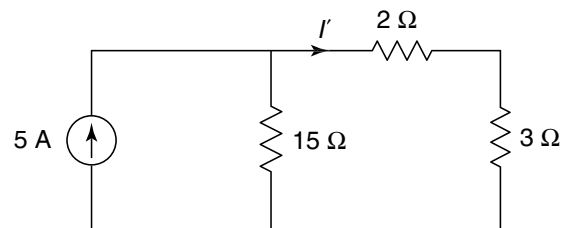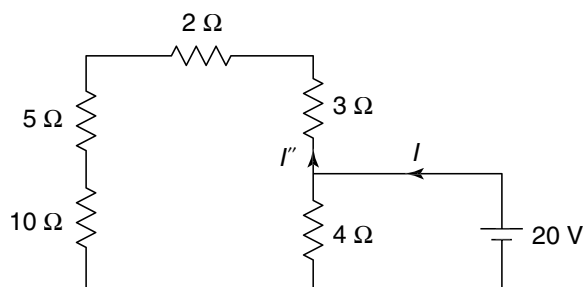**Fig. 3.43****Step II** When the 20 V source is acting alone (Fig. 3.44)**Fig. 3.44**

By series-parallel reduction technique (Fig. 3.45),

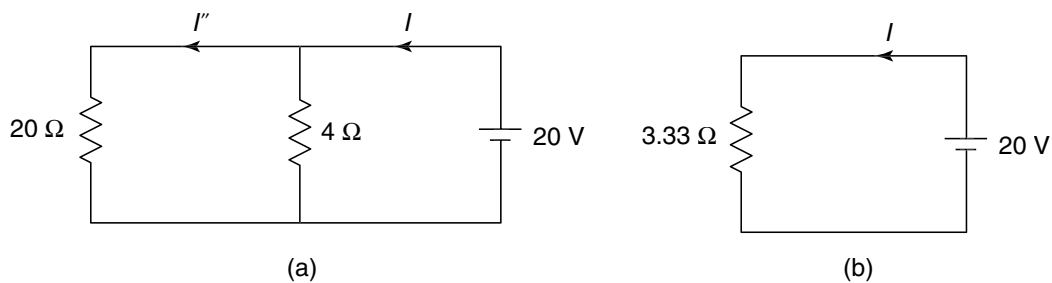**Fig. 3.45**

$$I = \frac{20}{3.33} = 6 \text{ A}$$

From Fig. 3.45(a), by current-division rule,

$$I'' = 6 \times \frac{4}{20+4} = 1 \text{ A} (\uparrow) = -1 \text{ A} (\downarrow)$$

Step III By superposition theorem,

$$I = I' + I'' = 3.75 - 1 = 2.75 \text{ A} (\downarrow)$$

Example 3.9

Find the current in the 1Ω resistors in Fig. 3.46.

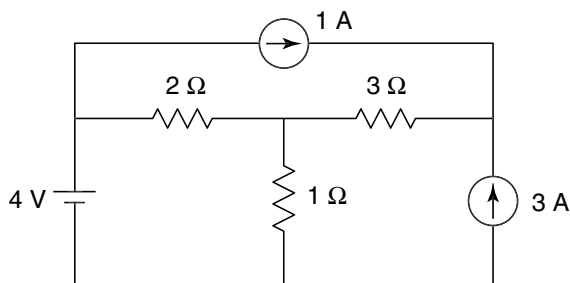


Fig. 3.46

Solution

Step I When the 4 V source is acting alone (Fig. 3.47)

$$I' = \frac{4}{2+1} = 1.33 \text{ A} (\downarrow)$$

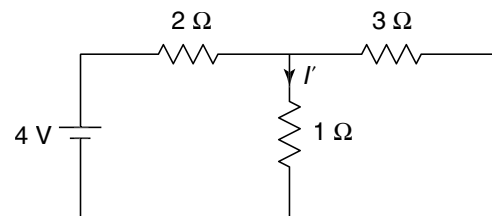


Fig. 3.47

Step II When the 3 A source is acting alone (Fig. 3.48)

By current-division rule,

$$I'' = 3 \times \frac{2}{1+2} = 2 \text{ A} (\downarrow)$$

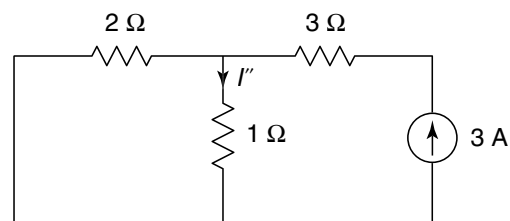


Fig. 3.48

Step III When the 1 A source is acting alone (Fig. 3.49)

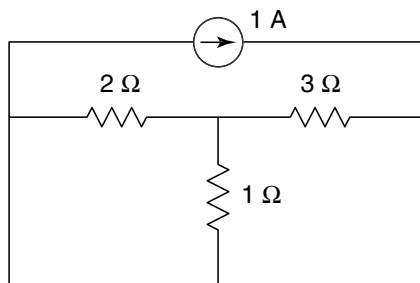


Fig. 3.49

3.14 Network Analysis and Synthesis

Redrawing the network (Fig. 3.50),

By current-division rule,

$$I''' = 1 \times \frac{2}{2+1} = 0.66 \text{ A} (\downarrow)$$

Step IV By superposition theorem,

$$I = I' + I'' + I''' = 1.33 + 2 + 0.66 = 4 \text{ A} (\downarrow)$$

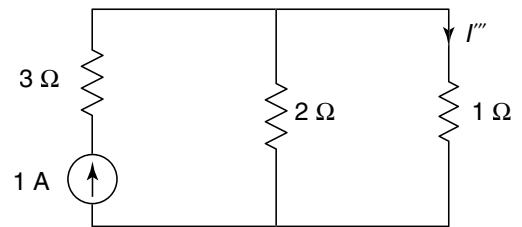


Fig. 3.50

Example 3.10

Find the voltage V_{AB} in Fig. 3.51.

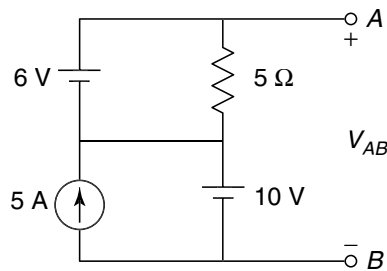


Fig. 3.51

Solution

Step I When the 6 V source is acting alone (Fig. 3.52)

$$V_{AB}' = 6 \text{ V}$$

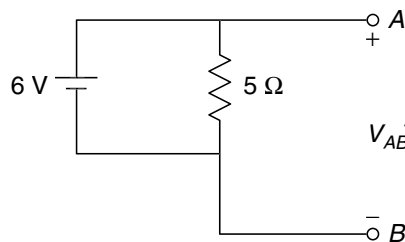


Fig. 3.52

Step II When the 10 V source is acting alone (Fig. 3.53)

Since the resistor of 5Ω is shorted, the voltage across it is zero.

$$V_{AB}'' = 10 \text{ V}$$

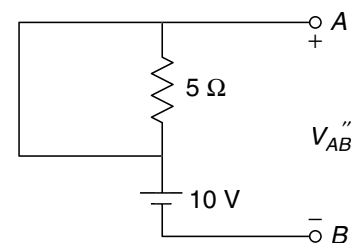


Fig. 3.53

Step III When the 5 A source is acting alone (Fig. 3.54)

Due to short circuit in both the parts,

$$V_{AB}''' = 0$$

Step IV By superposition theorem,

$$V_{AB} = V_{AB}' + V_{AB}'' + V_{AB}''' = 6 + 10 + 0 = 16 \text{ V}$$

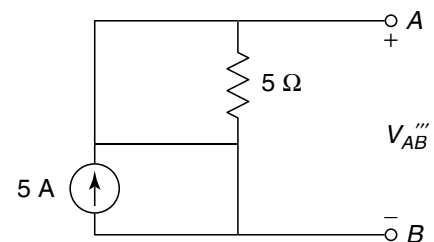
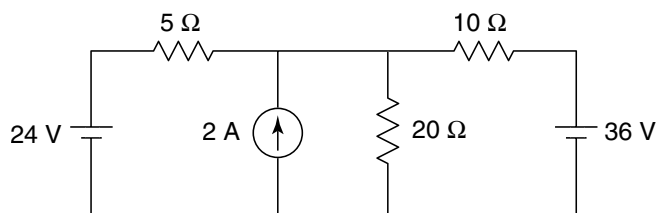
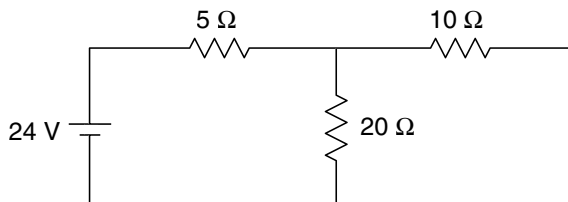
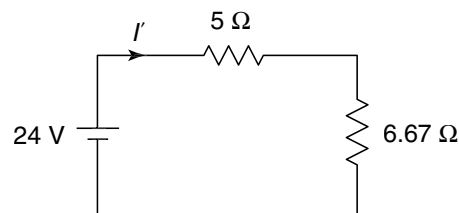


Fig. 3.54


Example 3.11Find the current through the $5\ \Omega$ resistor in Fig. 3.55.**Fig. 3.55****Solution****Step I** When the 24 V source is acting alone (Fig. 3.56)**Fig. 3.56**

By series-parallel reduction technique (Fig. 3.57),


$$I' = \frac{24}{5 + 6.67} = 2.06\text{ A}(\rightarrow) = -2.06\text{ A}(\leftarrow)$$

**Fig. 3.57****Step II** When the 2 A source is acting alone

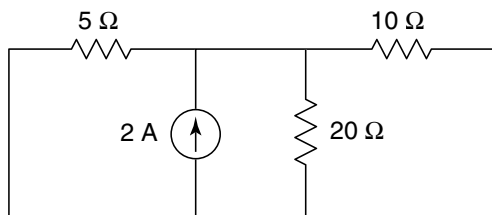By series-parallel reduction technique (Fig. 3.58),



(a)

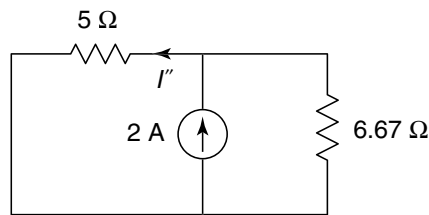

(b)


Fig. 3.58

By current-division rule,


$$I'' = 2 \times \frac{6.67}{5 + 6.67} = 1.14\text{ A}(\leftarrow)$$

Step III When the 36 V source is acting alone (Fig. 3.59)

By series-parallel reduction technique,

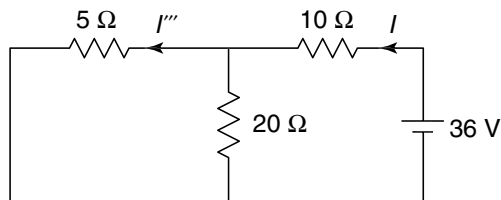

(a)

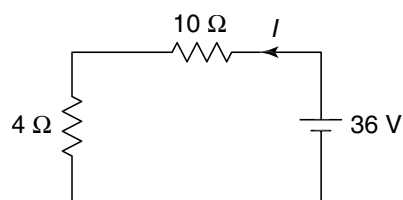

(b)

Fig. 3.59

$$I = \frac{36}{10+4} = 2.57 \text{ A}$$

By current-division rule,

$$I''' = 2.57 \times \frac{20}{20+5} = 2.06 \text{ A} (\leftarrow)$$

Step IV By superposition theorem,

$$I = I' + I'' + I''' = -2.06 + 1.14 + 2.06 = 1.14 \text{ A} (\leftarrow)$$

Example 13.12

Find the current through the 4Ω resistor in Fig. 3.60.

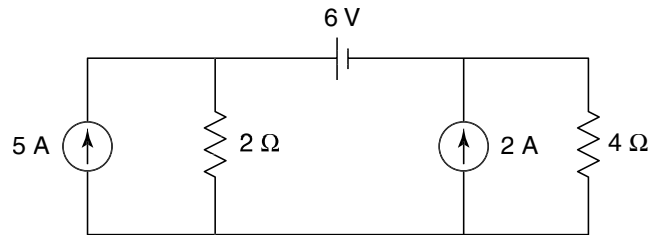


Fig. 3.60

Solution

Step I When the 5 A source is acting alone (Fig. 3.61)

By current-division rule,

$$I' = 5 \times \frac{2}{2+4} = 1.67 \text{ A} (\downarrow)$$

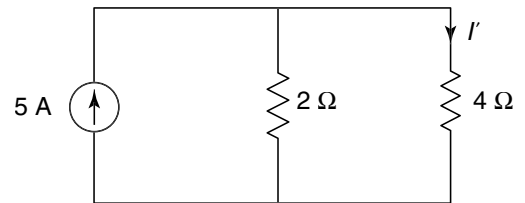


Fig. 3.61

Step II When the 2 A source is acting alone (Fig. 3.62)

By current-division rule,

$$I'' = 2 \times \frac{2}{2+4} = 0.67 \text{ A} (\downarrow)$$

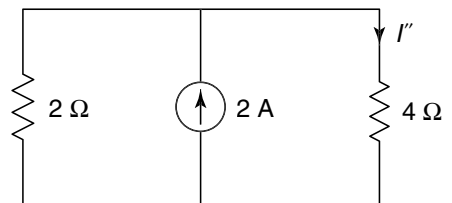


Fig. 3.62

Step III When the 6 V source is acting alone (Fig. 3.63)

Applying KVL to the mesh,

$$-2I''' - 6 - 4I''' = 0$$

$$I''' = -1 \text{ A} (\downarrow)$$

Step IV By superposition theorem,

$$I = I' + I'' + I''' = 1.67 + 0.67 - 1 = 1.34 \text{ A} (\downarrow)$$

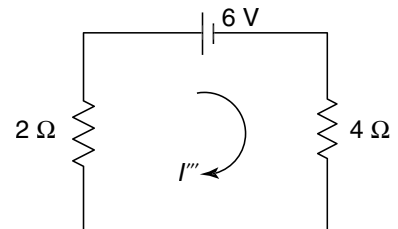


Fig. 3.63

EXAMPLES WITH DEPENDENT SOURCES

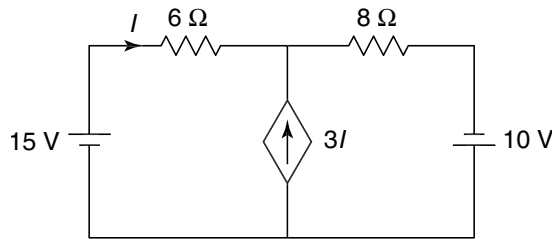
Example 3.13Find the current through the $6\ \Omega$ resistor in Fig. 3.64.

Fig. 3.64

Solution**Step I** When the 15 V source is acting alone (Fig 3.65)

From Fig. 3.65,

$$I' = I_1 \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1 = 3I' = 3I_1$$

$$4I_1 - I_2 = 0 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$15 - 6I_1 - 8I_2 = 0$$

$$6I_1 + 8I_2 = 15$$

 $\dots(iii)$

Solving Eqs (ii) and (iii),

$$I_1 = 0.39\text{ A}$$

$$I_2 = 1.59\text{ A}$$

$$I' = I_1 = 0.39\text{ A } (\rightarrow)$$

Step II When the 10 V source is acting alone (Fig 3.66)

From Fig. 3.66,

$$I'' = I_1$$

Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1 = 3I'' = 3I_1$$

$$4I_1 - I_2 = 0$$

Applying KVL to the outer path of the supermesh,

$$-6I_1 - 8I_2 + 10 = 0$$

$$6I_1 + 8I_2 = 10$$

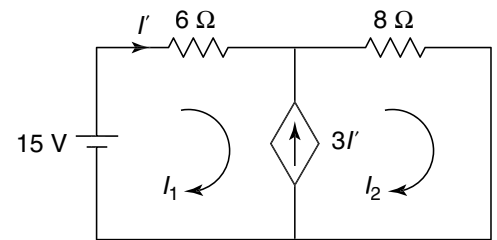
 $\dots(iii)$


Fig. 3.65

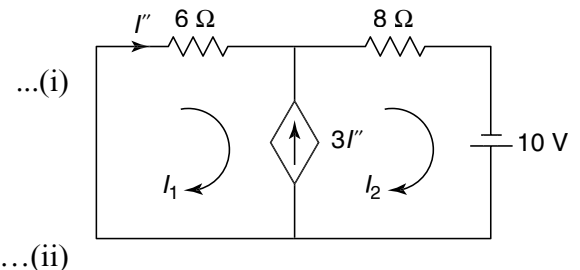


Fig. 3.66

Solving Eqs (ii) and (iii),

$$I_1 = 0.26 \text{ A}$$

$$I_2 = 1.05 \text{ A}$$

$$I'' = I_1 = 0.26 \text{ A} \quad (\rightarrow)$$

Step III By superposition theorem,

$$I = I' + I'' = 0.39 + 0.26 = 0.65 \text{ A} \quad (\rightarrow)$$

Example 3.14

Find the current I_x in Fig. 3.67.

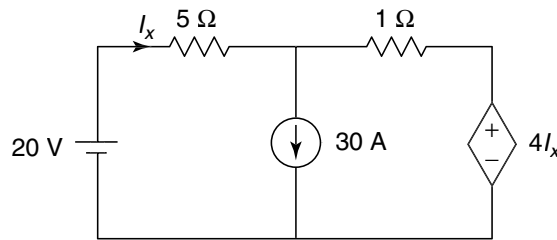


Fig. 3.67

Solution

Step I When the 30 A source is acting alone (Fig. 3.68)

From Fig. 3.68,

$$I'_x = I_1$$

Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_1 - I_2 = 30$$

Applying KVL to the outer path of the supermesh,

$$-5I_1 - 1I_2 - 4I'_x = 0$$

$$-5I_1 - I_2 - 4I_1 = 0$$

$$9I_1 + I_2 = 0$$

...(iii)

Solving Eqs (ii) and (iii),

$$I_1 = 3 \text{ A}$$

$$I_2 = -27 \text{ A}$$

$$I'_x = I_1 = 3 \text{ A} \quad (\rightarrow)$$

Step II When the 20 V source is acting alone (Fig. 3.69)

Applying KVL to the mesh,

$$20 - 5I''_x - 1I''_x - 4I''_x = 0$$

$$I''_x = 2 \text{ A} \quad (\rightarrow)$$

Step III By superposition theorem,

$$I_x = I'_x + I''_x = 3 + 2 = 5 \text{ A} \quad (\rightarrow)$$

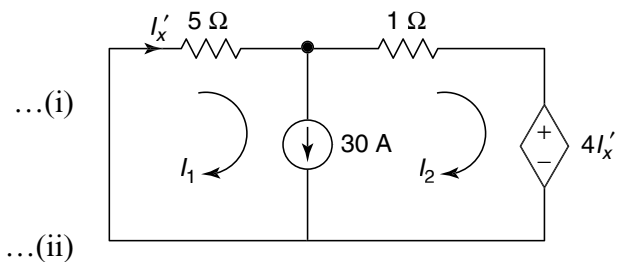


Fig. 3.68

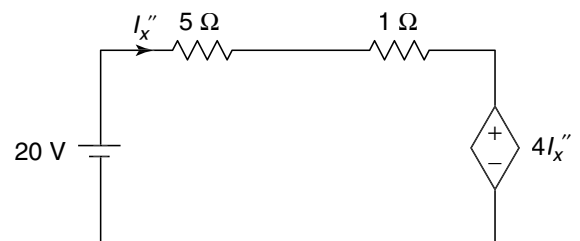
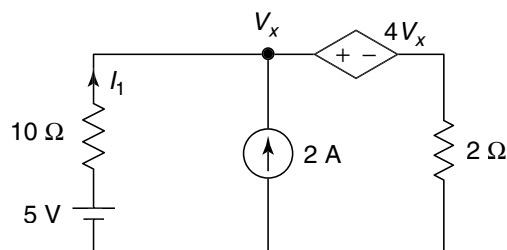


Fig. 3.69

Example 3.15Find the current I_1 in Fig. 3.70.**Fig. 3.70****Solution****Step I** When the 5 V source is acting alone (Fig 3.71)

From the figure,

$$V_x = 5 - 10I_1'$$


Applying KVL to the mesh,

$$5 - 10I_1' - 4V_x - 2I_1' = 0$$

$$5 - 10I_1' - 4(5 - 10I_1') - 2I_1' = 0$$

$$5 - 10I_1' - 20 + 40I_1' - 2I_1' = 0$$

$$I_1' = \frac{15}{28} = 0.54 \text{ A} (\uparrow)$$

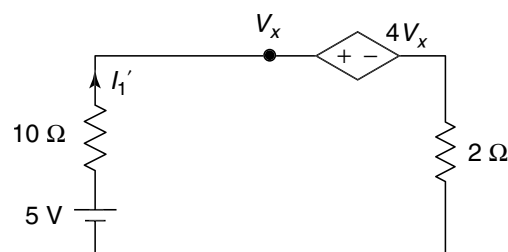**Fig. 3.71****Step II** When the 2 A source is acting alone (Fig 3.72)


From Fig . 3.72,

$$V_x = -10I_1'$$

Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1' = 2$$

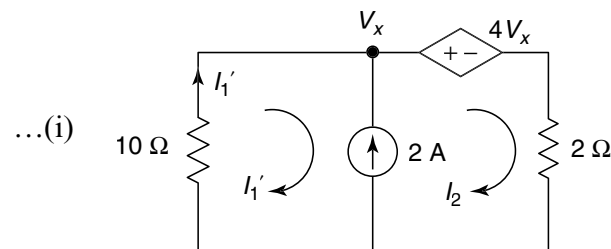**Fig. 3.72**

Applying KVL to the outer path of the supermesh,

$$-10I_1' - 4V_x - 2I_2 = 0$$

$$-10I_1' - 4(-10I_1') - 2I_2 = 0$$

$$30I_1' - 2I_2 = 0$$

...(iii)


Solving Eqs (ii) and (iii),

$$I_1 = 0.14 \text{ A} (\uparrow)$$

$$I_2 = 2.14 \text{ A}$$

Step III By superposition theorem,

$$I_1 = I_1' + I_1'' = 0.54 + 0.14 = 0.68 \text{ A} (\uparrow)$$

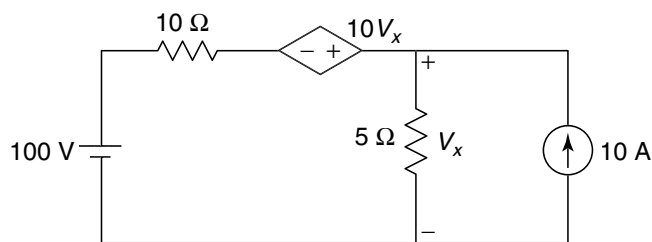Example 3.16Determine the current through the $10\ \Omega$ resistor in Fig. 3.73.**Fig. 3.73****Solution****Step I** When the 100 V source is acting alone (Fig. 3.74)

From the figure,


$$V_x = 5I'$$

Applying KVL to the mesh,

$$100 - 10I' + 10V_x - 5I' = 0$$

$$100 - 10I' + 10(5I') - 5I' = 0$$

$$I' = -2.86\text{ A } (\rightarrow)$$

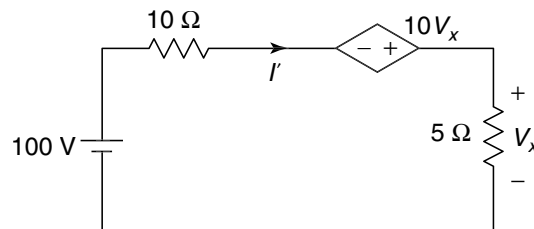**Fig. 3.74****Step II** When the 10 A source is acting alone (Fig. 3.75)

From Fig. 3.75,


$$V_x = 5(I_1 - I_2) \quad \dots(i)$$

Applying KVL to Mesh 1,

$$-10I_1 + 10V_x - 5(I_1 - I_2) = 0$$

$$-10I_1 + 10\{5(I_1 - I_2)\} - 5(I_1 - I_2) = 0$$

$$35I_1 - 45I_2 = 0 \quad \dots(ii)$$

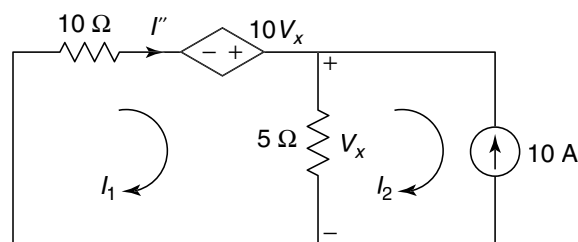**Fig. 3.75**

For Mesh 2,

$$I_2 = -10 \quad \dots(iii)$$

Solving Eqs (ii) and (iii),


$$I_1 = -12.86\text{ A}$$

$$I_2 = -10\text{ A}$$

$$I'' = I_1 = -12.86\text{ A } (\rightarrow)$$

Step III By superposition theorem,

$$I = I' + I'' = -2.86 - 12.86 = -15.72\text{ A } (\rightarrow)$$

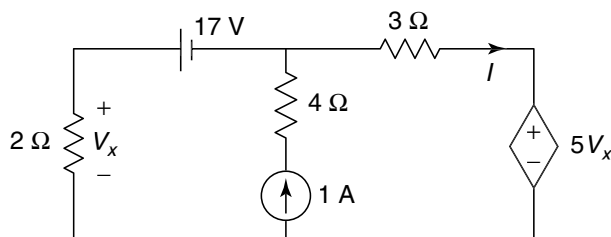Example 3.17Find the current I in the network of Fig. 3.76.**Fig. 3.76**

Solution**Step I** When the 17 V source is acting alone (Fig. 3.77)

From the figure,


$$V_x = -2I'$$

Applying KVL to the mesh,

$$-2I' - 17 - 3I' - 5V_x = 0$$

$$-2I' - 17 - 3I' - 5(-2I') = 0$$

$$I' = 3.4 \text{ A } (\rightarrow)$$

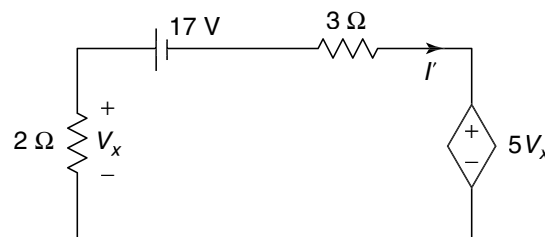**Fig. 3.77****Step II** When the 1 A source is acting alone (Fig. 3.78)


From Fig. 3.78,

$$V_x = -2I_1 \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1 = 1 \quad \dots(ii)$$

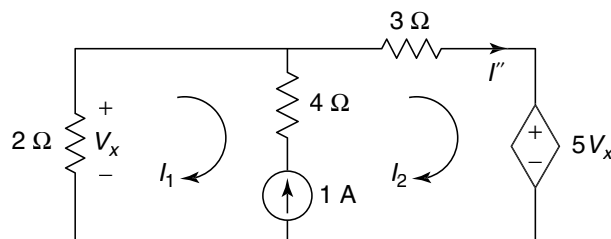**Fig. 3.78**

Applying KVL to the outer path of the supermesh,

$$-2I_1 - 3I_2 - 5V_x = 0$$

$$-2I_1 - 3I_2 - 5(-2I_1) = 0$$

$$8I_1 - 3I_2 = 0$$

 $\dots(iii)$

Solving Eqs (ii) and (iii),


$$I_1 = 0.6 \text{ A}$$

$$I_2 = 1.6 \text{ A}$$

$$I'' = I_2 = 1.6 \text{ A } (\rightarrow)$$

Step III By superposition theorem,

$$I = I' + I'' = 3.4 + 1.6 = 5 \text{ A } (\rightarrow)$$

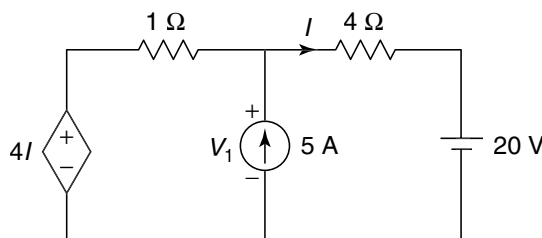
Example 3.18Find the voltage V_1 in Fig. 3.79.**Fig. 3.79****Solution****Step I** When the 5 A source is acting alone (Fig. 3.80)

From Fig. 3.80,

$$I = \frac{V_1'}{4}$$

Applying KCL at Node 1,

$$\frac{V_1' - 4I}{1} + \frac{V_1'}{4} = 5$$

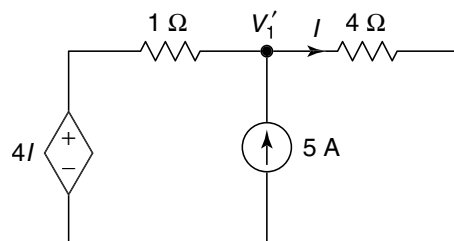**Fig. 3.80**

$$V_1' - 4\left(\frac{V_1'}{4}\right) + \frac{V_1'}{4} = 5$$

$$V_1' = 20 \text{ V}$$

Step II When the 20 V source is acting alone (Fig. 3.81)

Applying KVL to the mesh,

$$4I - I - 4I - 20 = 0$$

$$I = -20 \text{ A}$$

$$V_1'' = 4I - 1(I) = 3I = 3(-20) = -60 \text{ V}$$

Step III By superposition theorem,

$$V_1 = V_1' + V_1'' = 20 - 60 = -40 \text{ V}$$

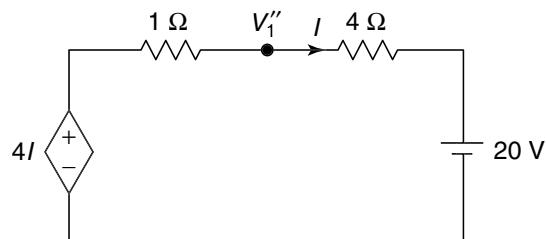


Fig. 3.81

Example 3.19

Find the current in the 6 Ω resistor in Fig. 3.82.

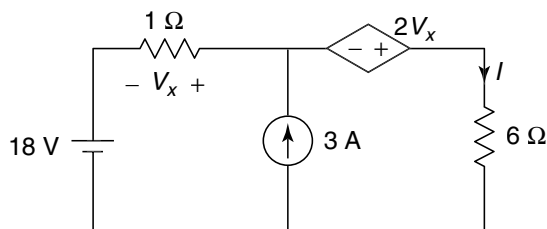


Fig. 3.82

Solution

Step I When the 18 V source is acting alone (Fig. 3.83)

From Fig. 3.83,

$$V_x = -I'$$

Applying KVL to the mesh,

$$18 - I' + 2V_x - 6I' = 0$$

$$18 - I' - 2I' - 6I' = 0$$

$$I' = 2 \text{ A (↓)}$$

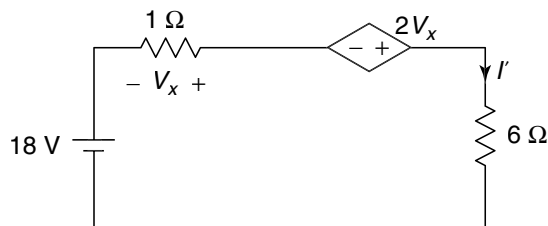


Fig. 3.83

Step II When the 3 A source is acting alone (Fig. 3.84)

From Fig. 3.84,

$$V_x = -1 I_1 = -I_1 \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1 = 3 \quad \dots(ii)$$

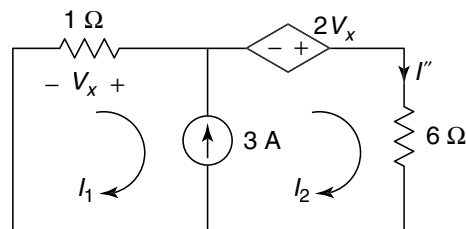


Fig. 3.84

Applying KVL to the outerpath of the supermesh,

$$-1I_1 + 2V_x - 6I_2 = 0$$

$$-I_1 + 2(-I_1) - 6I_2 = 0$$

$$3I_1 + 6I_2 = 0$$

...(iii)

Solving Eqs (ii) and (iii),

$$I_1 = -2 \text{ A}$$

$$I_2 = 1 \text{ A}$$

$$I'' = I_2 = 1 \text{ A } (\downarrow)$$

Step III By superposition theorem,

$$I_{6\Omega} = I' + I'' = 2 + 1 = 3 \text{ A } (\downarrow)$$

Example 3.20

Find the current I_y in Fig. 3.85.

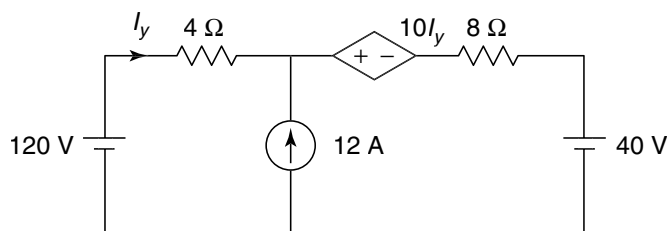


Fig. 3.85

Solution

Step I When the 120 V source is acting alone (Fig. 3.86)

Applying KVL to the mesh,

$$120 - 4I_y' - 10I_y' - 8I_y' = 0$$

$$I_y' = 5.45 \text{ A } (\rightarrow)$$

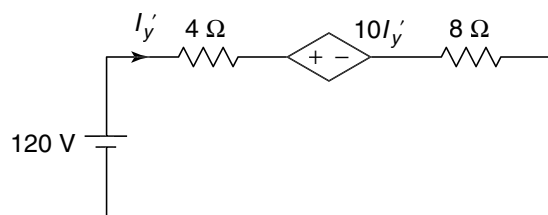


Fig. 3.86

Step II When the 12 A source is acting alone (Fig. 3.87)

From Fig. 3.87,

$$I_y'' = I_1 \quad \dots(i)$$

Mesher 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1 = 12 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$-4I_1 - 10I_y'' - 8I_2 = 0$$

$$-4I_1 - 10I_1 - 8I_2 = 0$$

$$14I_1 + 8I_2 = 0$$

...(iii)

Solving Eqs (ii) and (iii),

$$I_1 = -4.36 \text{ A}$$

$$I_2 = 7.64 \text{ A}$$

$$I_y'' = I_1 = -4.36 \text{ A } (\rightarrow)$$

Step III When the 40 V source is acting alone (Fig. 3.88)

Applying KVL to the mesh,

$$-4I_y''' - 10I_y''' - 8I_y''' - 40 = 0$$

$$I_y''' = -\frac{40}{22} = -1.82 \text{ A } (\rightarrow)$$

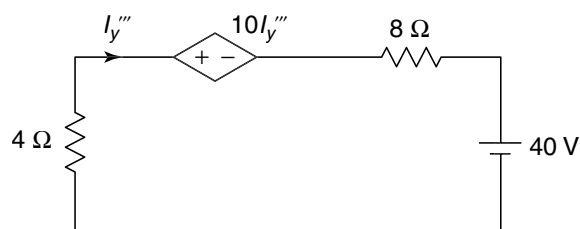


Fig. 3.88

Step IV By superposition theorem,

$$I_y = I'_y + I''_y + I'''_y = 5.45 - 4.36 - 1.82 = -0.73 \text{ A } (\rightarrow)$$

Example 3.21

Find the voltage V_x in Fig. 3.89.

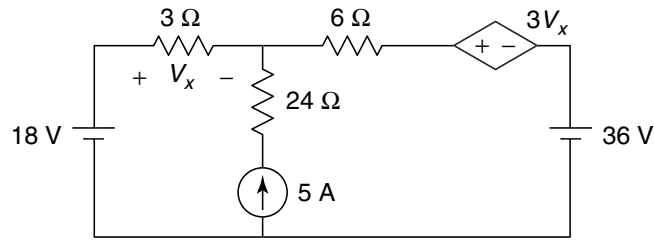


Fig. 3.89

Solution

Step I When the 18 V source is acting alone (Fig. 3.90)

From Fig. 3.90,

$$V'_x = 3I$$

Applying KVL to the mesh,

$$18 - 3I - 6I - 3V'_x = 0$$

$$18 - 3I - 6I - 3(3I) = 0$$

$$I = 1 \text{ A}$$

$$V'_x = 3 \text{ V}$$

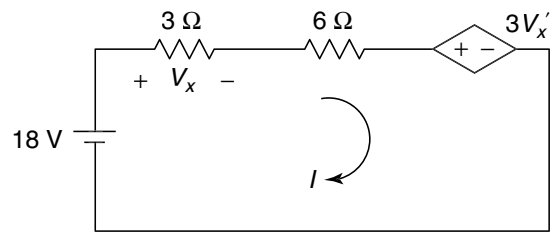


Fig. 3.90

Step II When the 5 A source is acting alone (Fig. 3.91)

From Fig. 3.91,

$$V''_x = -3I_1$$

Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1 = 5$$

Applying KVL to the outer path of the supermesh,

$$-3I_1 - 6I_2 - 3V''_x = 0$$

$$-3I_1 - 6I_2 - 3(3I_1) = 0$$

$$12I_1 + 6I_2 = 0$$

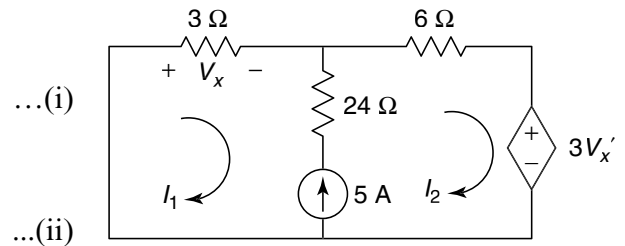


Fig. 3.91

Solving Eqs (ii) and (iii),

$$I_1 = -1.67 \text{ A}$$

$$I_2 = 3.33 \text{ A}$$

$$V''_x = 3I_1 = 3(-1.67) = -5 \text{ V}$$

Step III When the 36 V source is acting alone (Fig. 3.92)

From the figure,

$$V'''_x = -3I$$

Applying KVL to the mesh,

$$36 + 3V'''_x - 6I - 3I = 0$$

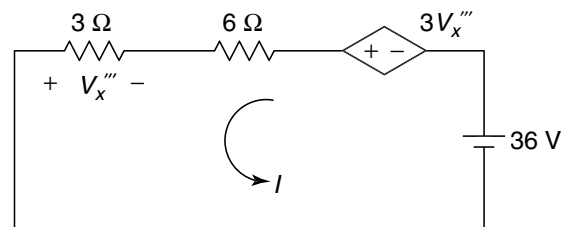


Fig. 3.92

$$36 + 3V_x''' - 6\left(\frac{-V_x'''}{3}\right) - 3\left(\frac{-V_x'''}{3}\right) = 0$$

$$36 + 3V_x''' + 2V_x''' + V_x''' = 0$$

$$V_x''' = -6 \text{ V}$$

Step IV By superposition theorem,

$$V_x = V_x' + V_x'' + V_x''' = 3 - 5 - 6 = -8 \text{ V}$$

Example 3.22

Find the voltage V in the network of Fig. 3.93.

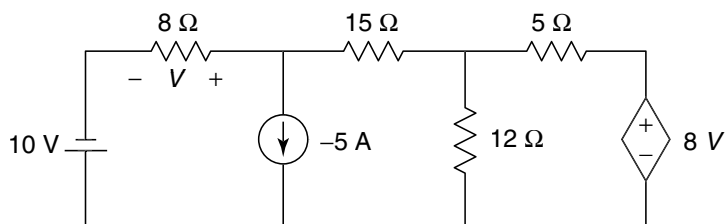


Fig. 3.93

Solution

Step I When the 10 V source is acting alone (Fig. 3.94)

From Fig. 3.94,

$$V' = -8I_1 \quad \dots(i)$$

Applying KVL to Mesh 1,

$$-10 - 8I_1 - 15I_1 - 12(I_1 - I_2) = 0$$

$$35I_1 - 12I_2 = -10 \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$-12(I_2 - I_1) - 5I_2 - 8V' = 0$$

$$-12I_2 + 12I_1 - 5I_2 - 8(-8I_1) = 0$$

$$76I_1 - 17I_2 = 0 \quad \dots(iii)$$

Solving Eqs (ii) and (iii),

$$I_1 = 0.54 \text{ A}$$

$$I_2 = 2.4 \text{ A}$$

$$V' = -8I_1 = -8(0.54) = -4.32 \text{ V}$$

Step II When the -5 A source is acting alone (Fig. 3.95)

From Fig. 3.95,

$$V'' = -8I_1 \quad \dots(i)$$

Mesher 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_1 - I_2 = -5 \quad \dots(ii)$$

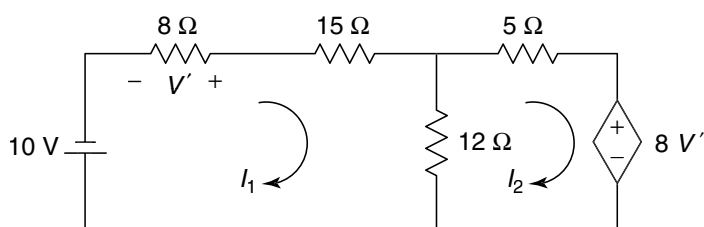


Fig. 3.94

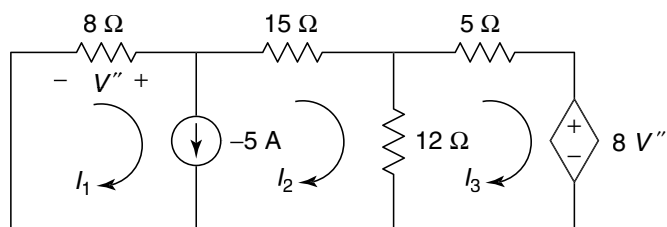


Fig. 3.95

3.26 Network Analysis and Synthesis

Applying KVL to the outer path of the supermesh,

$$-8I_1 - 15I_2 - 12(I_2 - I_3) = 0$$

$$-8I_1 - 27I_2 + 12I_3 = 0$$

...(iii)

Applying KVL to Mesh 3,

$$-12(I_3 - I_2) - 5I_3 - 8V'' = 0$$

$$-12I_3 + 12I_2 - 5I_3 - 8(-8I_1) = 0$$

$$64I_1 + 12I_2 - 17I_3 = 0$$

...(iv)

Solving Eqs (ii), (iii) and (iv),

$$I_1 = 4.97 \text{ A}$$

$$I_2 = 9.97 \text{ A}$$

$$I_3 = 25.74 \text{ A}$$

$$V'' = -8I_1 = -8(-4.97) = -39.76 \text{ V}$$

Step III By superposition theorem,

$$V = V' + V'' = -4.32 - 39.76 = -44.08 \text{ V}$$

Example 3.23

For the network shown in Fig. 3.96, find the voltage V_0 .

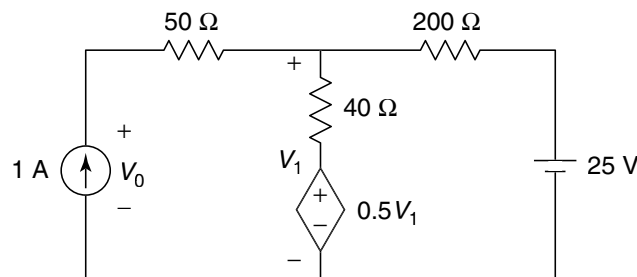


Fig. 3.96

Solution

Step I When the 1 A source is acting alone (Fig. 3.97)

From Fig. 3.97,

$$V_1 = 200I_2 \quad \dots(i)$$

For Mesh 1,

$$I_1 = 1 \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$0.5V_1 - 40(I_2 - I_1) - 200I_2 = 0$$

$$0.5(200I_2) - 40I_2 + 40I_1 - 200I_2 = 0$$

$$40I_1 - 140I_2 = 0$$

...(iii)

Solving Eqs (ii) and (iii),

$$I_1 = 1 \text{ A}$$

$$I_2 = 0.29 \text{ A}$$

$$V_0' - 50I_1 - 200I_2 = 0$$

$$V_0' - 50(1) - 200(0.29) = 0$$

$$V_0' = 108 \text{ V}$$

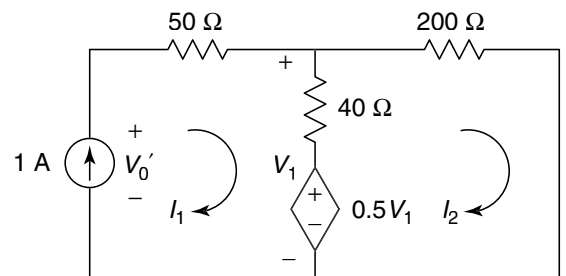


Fig. 3.97

Step II When the 25 V source is acting alone (Fig. 3.98)

From Fig. 3.98,

$$V_1 - 200I - 25 = 0$$

$$V_1 = 200I + 25 \quad \dots(i)$$

Applying KVL to Mesh 1,

$$0.5V_1 - 40I - 200I - 25 = 0$$

$$0.5(200I + 25) - 40I - 200I - 25 = 0$$

$$I = -0.09 \text{ A}$$

$$V_0'' = V_1 = 200I + 25 = 200(-0.09) + 25 = 7 \text{ V}$$

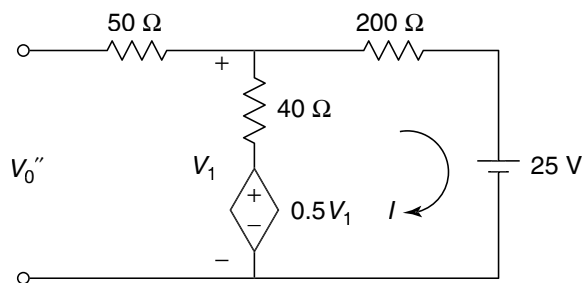


Fig. 3.98

Step III By superposition theorem,

$$V_0 = V_0' + V_0'' = 108 + 7 = 115 \text{ V}$$

Example 3.24

For the network shown in Fig. 3.99, find the voltage V_x .

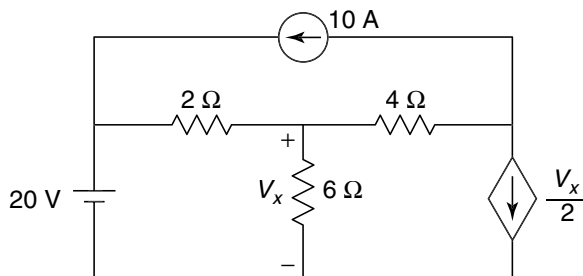


Fig. 3.99

Solution

Step I When the 20 V source is acting alone (Fig. 3.100)

From Fig. 3.100,

$$V_x' = 6(I_1 - I_2) \quad \dots(i)$$

Applying KVL to Mesh 1,

$$20 - 2I_1 - 6(I_1 - I_2) = 0$$

$$8I_1 - 6I_2 = 20$$

For Mesh 2,

$$I_2 = \frac{V_x'}{2} = \frac{6(I_1 - I_2)}{2} = 3I_1 - 3I_2$$

$$3I_1 - 4I_2 = 0$$

Solving Eqs (ii) and (iii),

$$I_1 = 5.71 \text{ A}$$

$$I_2 = 4.29 \text{ A}$$

$$V_x' = 6(I_1 - I_2) = 6(5.71 - 4.29) = 8.52 \text{ V}$$

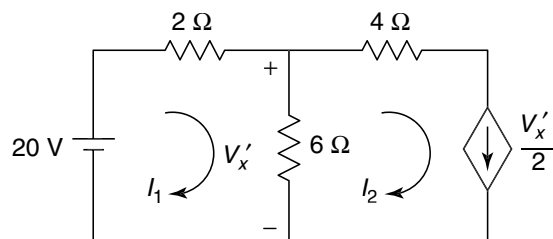


Fig. 3.100

...(ii)

...(iii)

3.28 Network Analysis and Synthesis

Step II When the 10 A source is acting alone (Fig. 3.101)

From Fig. 3.101,

$$V_x'' = 6(I_1 - I_2)$$

Applying KVL to Mesh 1,

$$-2(I_1 - I_3) - 6(I_1 - I_2) = 0$$

$$8I_1 - 6I_2 - 2I_3 = 0$$

For Mesh 2,

$$I_2 = \frac{V_x''}{2} = \frac{6(I_1 - I_2)}{2} = 3I_1 - 3I_2$$

$$3I_1 - 4I_2 = 0$$

For Mesh 3,

$$I_3 = -10$$

Solving Eqs (ii), (iii) and (iv),

$$I_1 = -5.71 \text{ A}$$

$$I_2 = -4.29 \text{ A}$$

$$I_3 = -10 \text{ A}$$

$$V_x'' = 6(I_1 - I_2) = 6(-5.71 + 4.29) = -8.52 \text{ V}$$

Step III By superposition theorem,

$$V_x = V_x' + V_x'' = 8.52 - 8.52 = 0$$

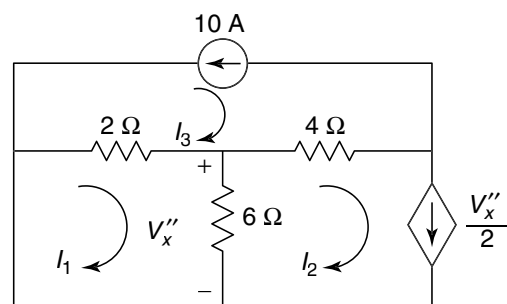


Fig. 3.101

...(iii)

...(iv)

Example 3.25

Calculate the current I in the network shown in Fig. 3.102.

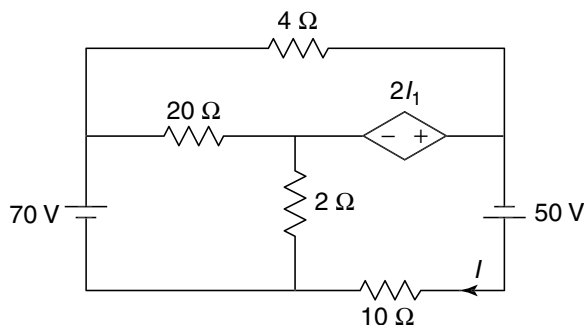


Fig. 3.102

Solution

Step I When the 70 V source is acting alone (Fig. 3.103)

From Fig. 3.103,

$$I' = I_3$$

Applying KVL to Mesh 1,

$$-4I_1 - 2I_1 - 20(I_1 - I_2) = 0$$

$$26I_1 - 20I_2 = 0$$

Applying KVL to Mesh 2,

$$70 - 20(I_2 - I_1) - 2(I_2 - I_3) = 0$$

$$-20I_1 + 22I_2 - 2I_3 = 70$$

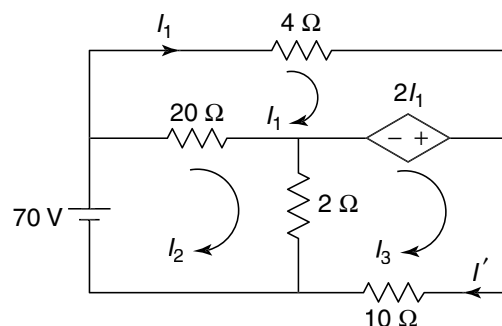


Fig. 3.103

...(iii)

Applying KVL to Mesh 3,

$$-2(I_3 - I_2) + 2I_1 - 10I_3 = 0$$

$$2I_1 + 2I_2 - 12I_3 = 0$$

...(iv)

Solving Eqs (ii), (iii) and (iv),

$$I_1 = 8.94 \text{ A}$$

$$I_2 = 11.62 \text{ A}$$

$$I_3 = 3.43 \text{ A}$$

$$I' = I_3 = 3.43 \text{ A} (\leftarrow)$$

Step II When the 50 V source is acting alone (Fig. 3.104)

From Fig. 3.104,

$$I'' = I_3 \quad \dots(i)$$

Applying KVL to Mesh 1,

$$-4I_1 - 2I_1 - 20(I_1 - I_2) = 0$$

$$26I_1 - 20I_2 = 0 \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$-20(I_2 - I_1) - 2(I_2 - I_3) = 0$$

$$-20I_1 + 22I_2 - 2I_3 = 0$$

...(iii)

Applying KVL to Mesh 3,

$$-2(I_3 - I_2) + 2I_1 + 50 - 10I_3 = 0$$

$$2I_1 + 2I_2 - 12I_3 = -50$$

...(iv)

Solving Eqs (ii), (iii), and (iv),

$$I_1 = 1.06 \text{ A}$$

$$I_2 = 1.38 \text{ A}$$

$$I_3 = 4.57 \text{ A}$$

$$I'' = I_3 = 4.57 \text{ A} (\leftarrow)$$

Step III By superposition theorem,

$$I = I' + I'' = 3.43 + 4.57 = 8 \text{ A} (\leftarrow)$$

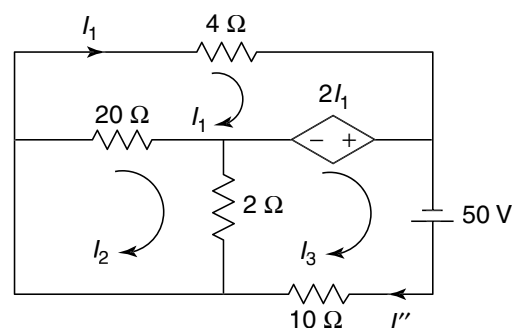


Fig. 3.104

Example 3.26

Find the voltage V_0 in the network of Fig. 3.105.

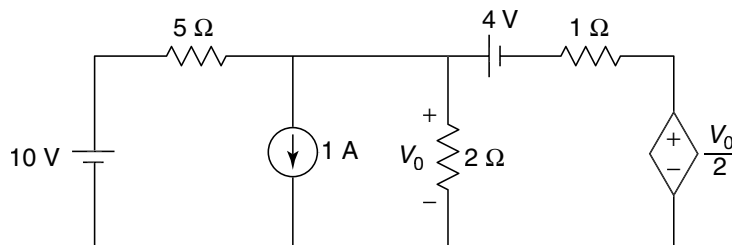


Fig. 3.105

Solution

Step I When the 10 V source is acting alone (Fig. 3.106)

Applying KCL at the node,

$$\frac{V_0' - 10}{5} + \frac{V_0'}{2} + \frac{V_0' - \frac{V_0'}{2}}{1} = 0$$

$$\left(\frac{1}{5} + \frac{1}{2} + \frac{1}{2}\right)V_0' = 2$$

$$V_0' = 1.67 \text{ V}$$

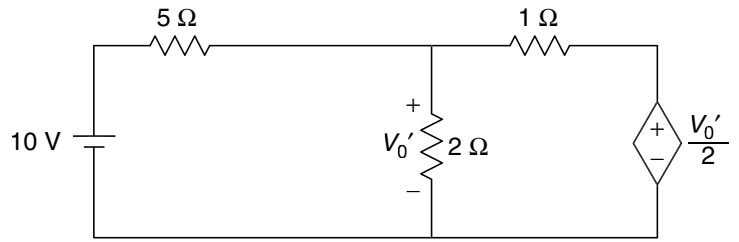


Fig. 3.106

Step II When the 1A current source is acting alone (Fig. 3.107)

Applying KCL at the node,

$$\frac{V_0''}{5} + 1 + \frac{V_0''}{2} + \frac{V_0'' - \frac{V_0''}{2}}{1} = 0$$

$$\left(\frac{1}{5} + \frac{1}{2} + \frac{1}{2}\right)V_0'' = -1$$

$$V_0'' = -0.83 \text{ V}$$

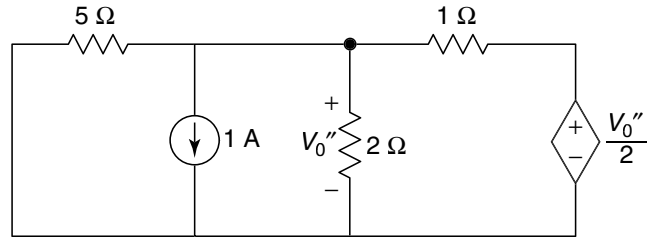


Fig. 3.107

Step III When the 4 V source is acting alone (Fig. 3.108)

Applying KCL at the node,

$$\frac{V_0'''}{5} + \frac{V_0'''}{2} + \frac{V_0''' - 4 - \frac{V_0'''}{2}}{1} = 0$$

$$\left(\frac{1}{5} + \frac{1}{2} + \frac{1}{2}\right)V_0''' = 4$$

$$V_0''' = 3.33 \text{ V}$$

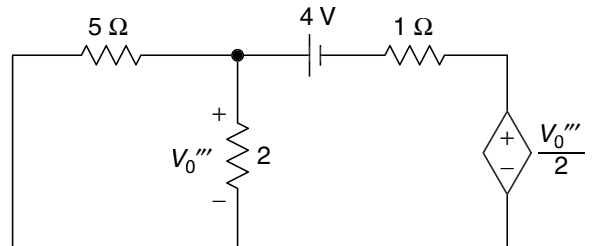


Fig. 3.108

Step IV By superposition theorem,

$$V_0 = V_0' + V_0'' + V_0''' = 1.67 - 0.83 + 3.33 = 4.17 \text{ V}$$

3.3 THEVENIN'S THEOREM

It states that ‘any two terminals of a network can be replaced by an equivalent voltage source and an equivalent series resistance. The voltage source is the voltage across the two terminals with load, if any, removed. The series resistance is the resistance of the network measured between two terminals with load removed and constant voltage source being replaced by its internal resistance (or if it is not given with zero resistance, i.e., short circuit) and constant current source replaced by infinite resistance, i.e., open circuit.’

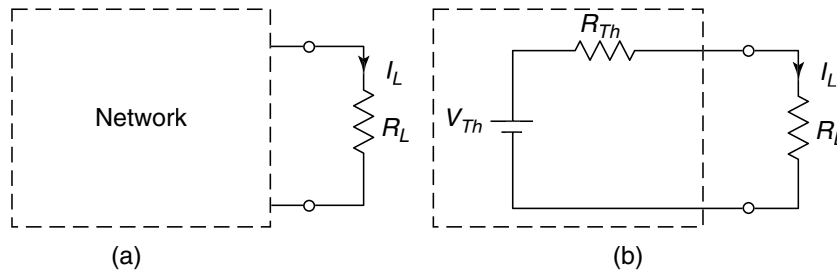


Fig. 3.109 Network illustrating Thevenin's theorem

Explanation Consider a simple network as shown in Fig. 3.110.

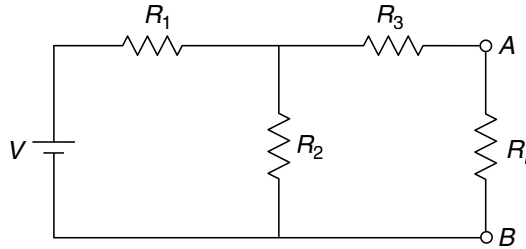


Fig. 3.110 Network

For finding load current through R_L , first remove the load resistor R_L from the network and calculate open circuit voltage V_{Th} across points A and B as shown in Fig. 3.111.

$$V_{Th} = \frac{R_2}{R_1 + R_2} V$$

For finding series resistance R_{Th} , replace the voltage source by a short circuit and calculate resistance between points A and B as shown in Fig. 3.112.

$$R_{Th} = R_3 + \frac{R_1 R_2}{R_1 + R_2}$$

Thevenin's equivalent network is shown in Fig. 3.113.

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

If the network contains both independent and dependent sources, Thevenin's resistance R_{Th} is calculated as,

$$R_{Th} = \frac{V_{Th}}{I_N}$$

where I_N is the short-circuit current which would flow in a short circuit placed across the terminals A and B . Dependent sources are active at all times. They have zero values only when the control voltage or current is zero. R_{Th} may be negative in

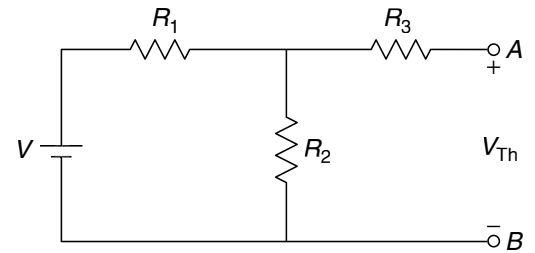


Fig. 3.111 Calculation of V_{Th}

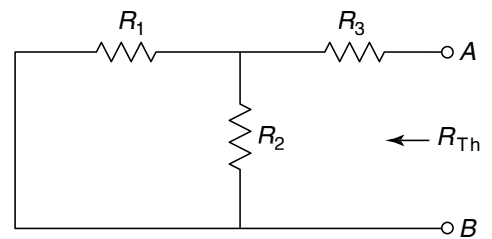


Fig. 3.112 Calculation of R_{Th}

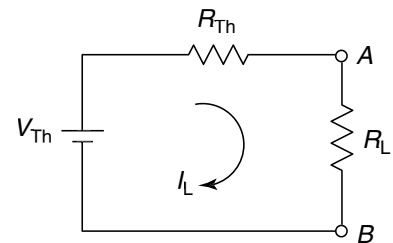


Fig 3.113 Thevenin's equivalent network

3.32 Network Analysis and Synthesis

some cases which indicates negative resistance region of the device, i.e., as voltage increases, current decreases in the region and vice-versa.

If the network contains only dependent sources then

$$V_{Th} = 0$$

$$I_N = 0$$

For finding R_{Th} in such a network, a known voltage V is applied across the terminals A and B and current is calculated through the path AB .

$$R_{Th} = \frac{V}{I}$$

or a known current source I is connected across the terminals A and B and voltage is calculated across the terminals A and B .

$$R_{Th} = \frac{V}{I}$$

Thevenin's equivalent network for such a network is shown in Fig. 3.114.

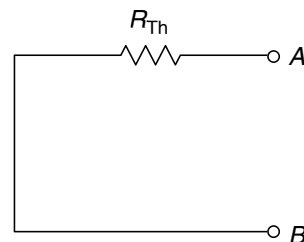


Fig. 3.114 Thevenin's equivalent network

Steps to be Followed in Thevenin's Theorem

1. Remove the load resistance R_L .
2. Find the open circuit voltage V_{Th} across points A and B .
3. Find the resistance R_{Th} as seen from points A and B .
4. Replace the network by a voltage source V_{Th} in series with resistance R_{Th} .
5. Find the current through R_L using Ohm's law.

$$I_L = \frac{V_{Th}}{R_{Th} + R_L}$$

Example 3.27

Find the current through the $2\ \Omega$ resistor in Fig. 3.115.

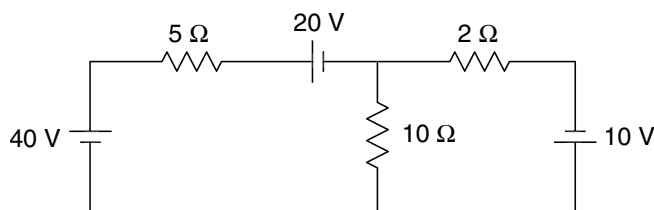


Fig. 3.115

Solution

Step I Calculation of V_{Th} (Fig. 3.116)

Applying KVL to the mesh,

$$40 - 5I - 20 - 10I = 0$$

$$15I = 20$$

$$I = 1.33\text{ A}$$

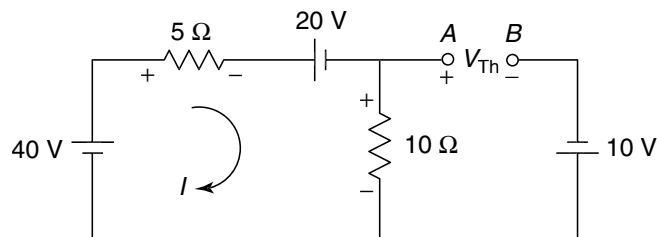


Fig. 3.116

Writing the V_{Th} equation,

$$10I - V_{Th} + 10 = 0$$

$$V_{Th} = 10I + 10 = 10(1.33) + 10 = 23.33 \text{ V}$$

Step II Calculation of R_{Th} (Fig. 3.117)

$$R_{Th} = 5 \parallel 10 = 3.33 \Omega$$

Step III Calculation of I_L (Fig. 3.118)

$$I_L = \frac{23.33}{3.33 + 2} = 4.38 \text{ A}$$

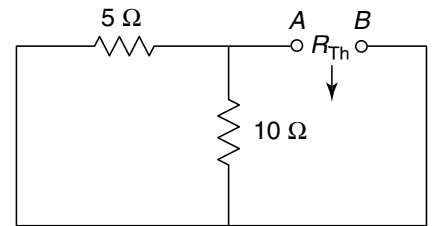


Fig. 3.117

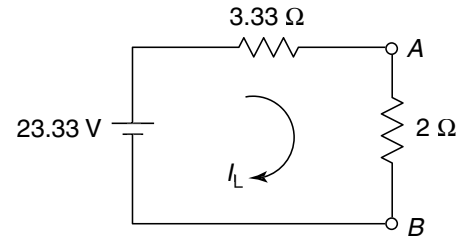


Fig. 3.118

Example 3.28

Find the current through the 8Ω resistor in Fig. 3.119.

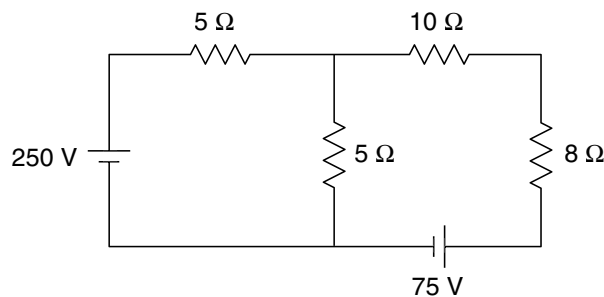


Fig. 3.119

Solution

Step I Calculation of V_{Th} (Fig. 3.120)

$$I = \frac{250}{5 + 5} = 25 \text{ A}$$

Writing the V_{Th} equation,

$$250 - 5I - V_{Th} - 75 = 0$$

$$V_{Th} = 175 - 5I = 175 - 5(25) = 50 \text{ V}$$

Step II Calculation of R_{Th} (Fig. 3.121)

$$R_{Th} = (5 \parallel 5) + 10 = 12.5 \Omega$$

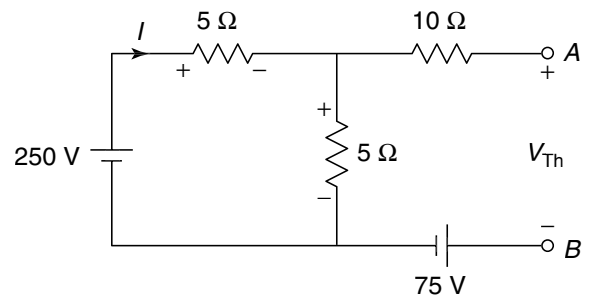


Fig. 3.120

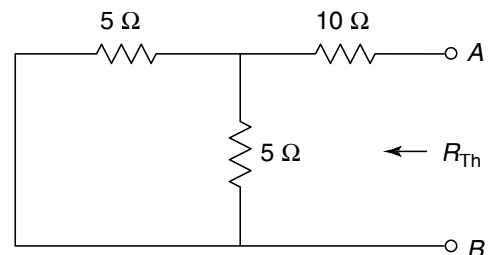


Fig. 3.121

Step III Calculation of I_L (Fig. 3.122)

$$I_L = \frac{50}{12.5 + 8} = 2.44 \text{ A}$$

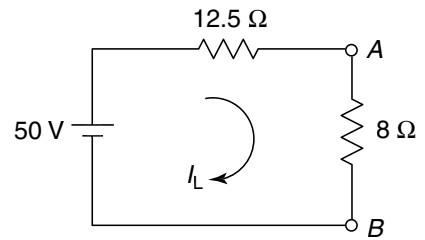


Fig. 3.122

Example 3.29 Find the current through the 2Ω resistor connected between terminals A and B in the Fig. 3.123.

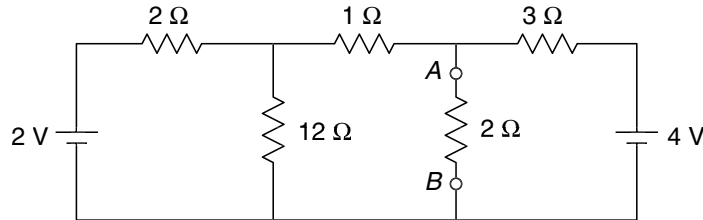


Fig. 3.123

Solution

Step I Calculation of V_{Th} (Fig. 3.124)

Applying KVL to Mesh 1,

$$\begin{aligned} 2 - 2I_1 - 12(I_1 - I_2) &= 0 \\ 14I_1 - 12I_2 &= 2 \quad \dots(i) \end{aligned}$$

Applying KVL to Mesh 2,

$$\begin{aligned} -12(I_2 - I_1) - 1I_2 - 3I_2 - 4 &= 0 \\ -12I_1 + 16I_2 &= -4 \quad \dots(ii) \end{aligned}$$

Solving Eqs (i) and (ii),

$$I_2 = -0.4 \text{ A}$$

Writing the V_{Th} equation,

$$\begin{aligned} V_{Th} - 3I_2 - 4 &= 0 \\ V_{Th} &= 4 + 3I_2 = 4 + 3(-0.4) = 2.8 \text{ V} \end{aligned}$$

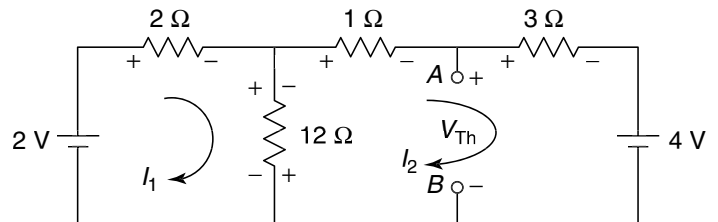


Fig. 3.124

Step II Calculation of R_{Th} (Fig. 3.125)

$$R_{Th} = [(2 \parallel 12) + 1] \parallel 3 = 1.43 \Omega$$

Step III Calculation of I_L (Fig. 3.126)

$$I_L = \frac{2.8}{1.43 + 2} = 0.82 \text{ A}$$

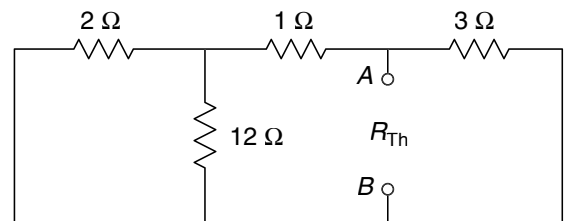


Fig. 3.125

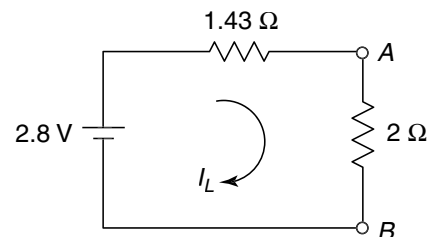
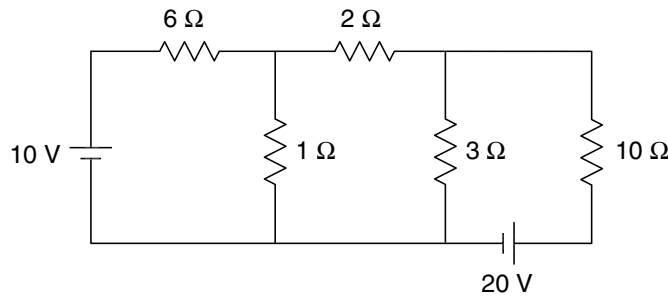


Fig. 3.126

Example 3.30Find the current through the $10\ \Omega$ resistor in Fig. 3.127.**Fig. 3.127****Solution****Step I** Calculation of V_{Th} (Fig. 3.128)

Applying KVL to Mesh 1,

$$10 - 6I_1 - 1(I_1 - I_2) = 0$$

$$7I_1 - I_2 = 10 \quad \dots(i)$$

Applying KVL to Mesh 2,

$$-1(I_2 - I_1) - 2I_2 - 3I_2 = 0$$

$$-I_1 + 6I_2 = 0 \quad \dots(ii)$$

Solving Eqs (i) and (ii),

$$I_2 = 0.24\text{ A} \quad \dots(ii)$$

Writing the V_{Th} equation,

$$3I_2 - V_{Th} - 20 = 0$$

$$V_{Th} = 3I_2 - 20 = 3(0.24) - 20 = -19.28\text{ V}$$





$$= 19.28\text{ V (terminal B is positive w.r.t A)}$$

Step II Calculation of R_{Th} (Fig. 3.129)

$$R_{Th} = [(6 \parallel 1) + 2] \parallel 3 = 1.47\ \Omega$$

Step III Calculation of I_L (Fig. 3.130)

$$I_L = \frac{19.28}{1.47 + 10} = 1.68\text{ A (}\uparrow\text{)}$$

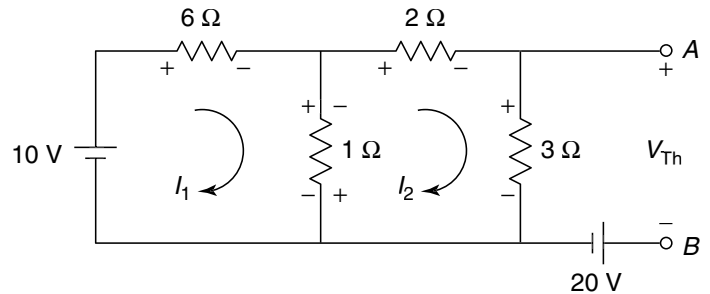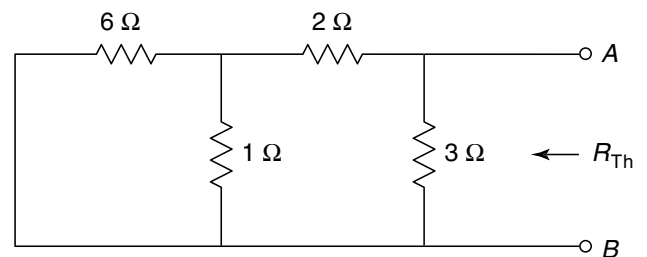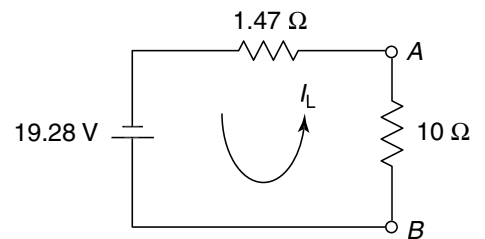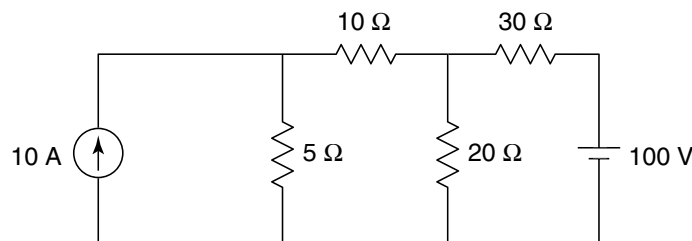**Fig. 3.128****Fig. 3.129****Fig. 3.130****Example 3.31**Find the current through the $10\ \Omega$ resistor in Fig. 3.131.**Fig. 3.131**

Solution

Step I Calculation of V_{Th} (Fig. 3.132)

For Mesh 1,

$$I_1 = 10$$

Applying KVL to Mesh 2,

$$100 - 30I_2 - 20I_2 = 0$$

$$I_2 = 2 \text{ A}$$

Writing the V_{Th} equation,

$$5I_1 - V_{Th} - 20I_2 = 0$$

$$V_{Th} = 5I_1 - 20I_2 = 5(10) - 20(2) = 10 \text{ V}$$

Step II Calculation of R_{Th} (Fig. 3.133)

$$R_{Th} = 5 + (20 \parallel 30) = 17 \Omega$$

Step III Calculation of I_L (Fig. 3.134)

$$I_L = \frac{10}{17 + 10} = 0.37 \text{ A}$$

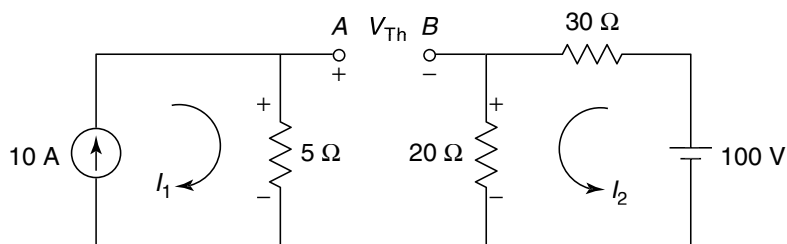


Fig. 3.132

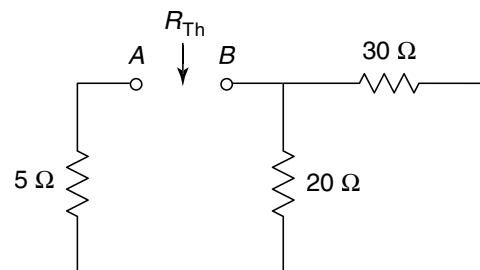


Fig. 3.133

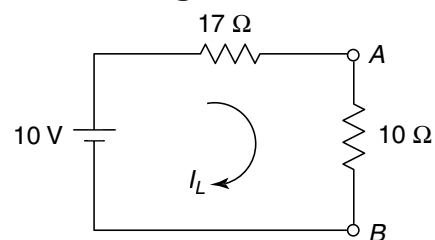


Fig. 3.134

Example 3.32

Find the current through the 40Ω resistor in Fig. 3.135.

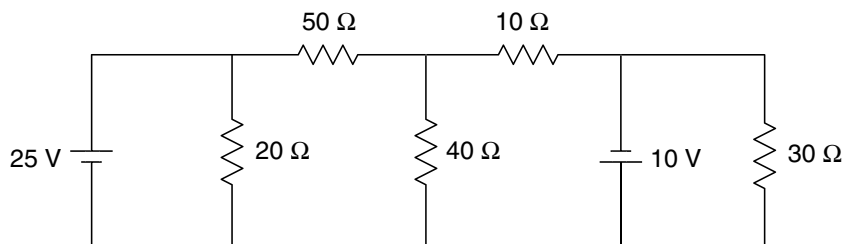


Fig. 3.135

Solution

Step I Calculation of V_{Th} (Fig. 3.136)

Since the 20Ω resistor is connected across the 25 V source, the resistor becomes redundant.

$$V_{20\Omega} = 25 \text{ V}$$

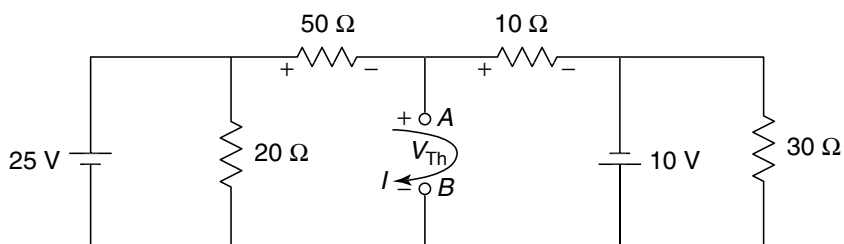


Fig. 3.136

Applying KVL to the mesh,

$$25 - 50I - 10I + 10 = 0$$

$$I = 0.58 \text{ A}$$

Writing the V_{Th} equation,

$$V_{Th} - 10I + 10 = 0$$

$$V_{Th} = 10(I) - 10 = 10(0.58) - 10 = -4.2 \text{ V}$$

$$= 4.2 \text{ V (terminal } B \text{ is positive w.r.t } A)$$

Step II Calculation of R_{Th} (Fig. 3.137)

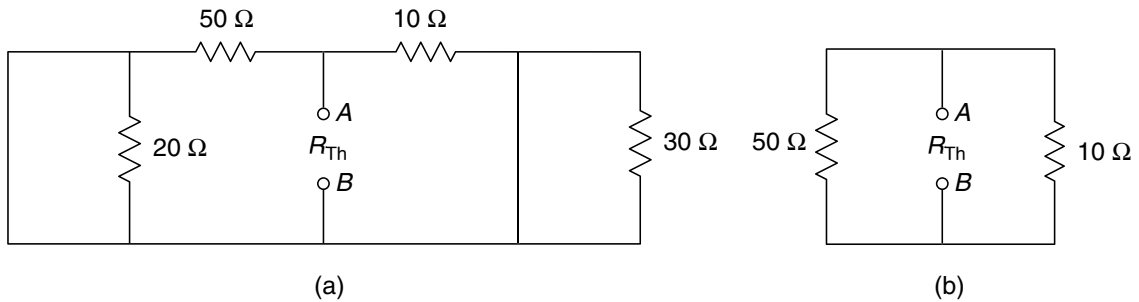


Fig. 3.137

$$R_{Th} = 50 \parallel 10 = 8.33 \Omega$$

Step III Calculation of I_L (Fig. 3.138)

$$I_L = \frac{4.2}{8.33 + 40} = 0.09 \text{ A} (\uparrow)$$

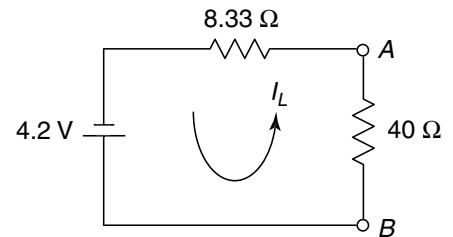


Fig. 3.138

Example 3.33

Find the current through the 10Ω resistor in Fig. 3.139.

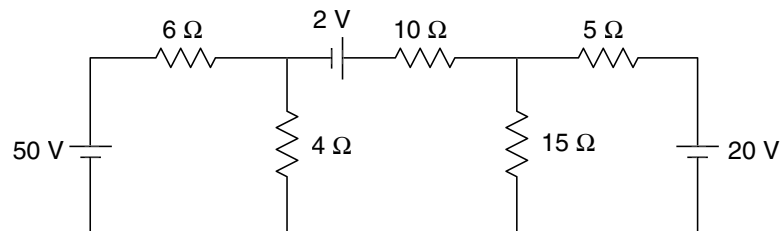


Fig. 3.139

Solution

Step I Calculation of V_{Th} (Fig. 3.140)

$$I_1 = \frac{50}{6 + 4} = 5 \text{ A}$$

$$I_2 = \frac{20}{5 + 15} = 1 \text{ A}$$

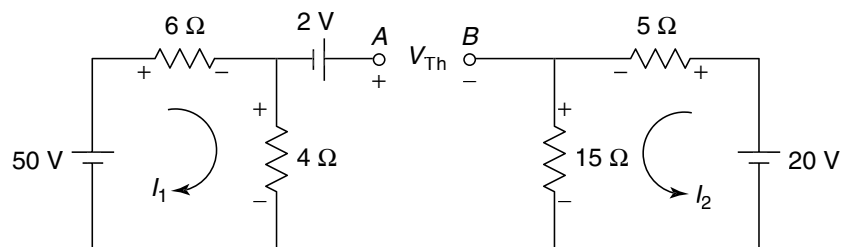


Fig. 3.140

3.38 Network Analysis and Synthesis

Writing the V_{Th} equation,

$$4I_1 + 2 - V_{Th} - 15I_2 = 0$$

$$V_{Th} = 4I_1 + 2 - 15I_2 = 4(5) + 2 - 15(1) = 7 \text{ V}$$

Step II Calculation of R_{Th} (Fig. 3.141)

$$R_{Th} = (6 \parallel 4) + (5 \parallel 15) = 6.15 \Omega$$

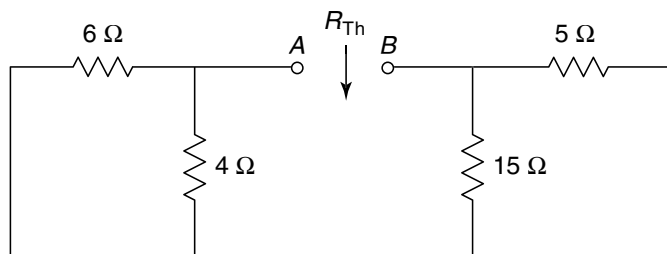


Fig. 3.141

Step III Calculation of I_L (Fig. 3.142)

$$I_L = \frac{7}{6.15 + 10} = 0.43 \text{ A}$$

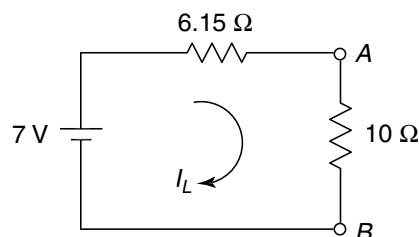


Fig. 3.142

Example 3.34

Determine the current through the 24Ω resistor in Fig. 3.143.

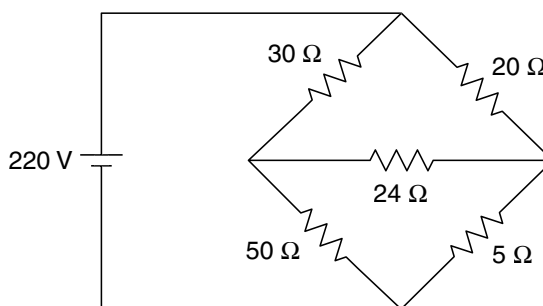


Fig. 3.143

Solution

Step I Calculation of V_{Th} (Fig. 3.144)

$$I_1 = \frac{220}{30 + 50} = 2.75 \text{ A}$$

$$I_2 = \frac{220}{20 + 5} = 8.8 \text{ A}$$

Writing the V_{Th} equation,

$$V_{Th} + 30I_1 - 20I_2 = 0$$

$$V_{Th} = 20I_2 - 30I_1 = 20(8.8) - 30(2.75) = 93.5 \text{ V}$$

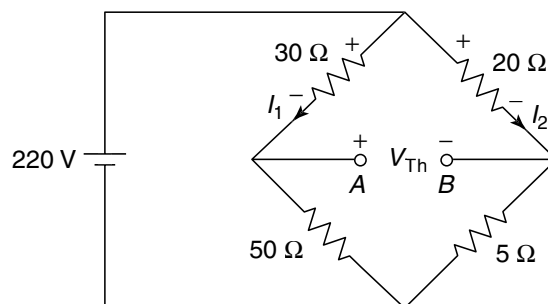


Fig. 3.144

Step II Calculation of R_{Th} (Fig. 3.145)

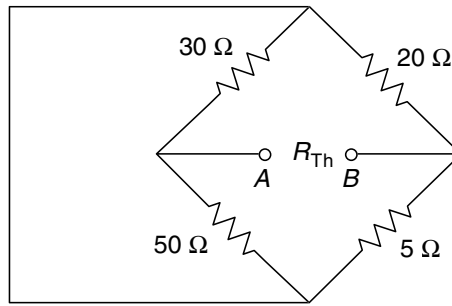


Fig. 3.145

Redrawing the circuit (Fig. 3.146),

$$R_{Th} = (30 \parallel 50) + (20 \parallel 5) = 22.75 \, \Omega$$

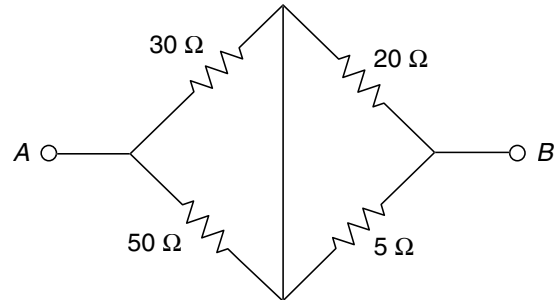


Fig. 3.146

Step III Calculation of I_L (Fig. 3.147)

$$I_L = \frac{93.5}{22.75 + 24} = 2 \, \text{A}$$

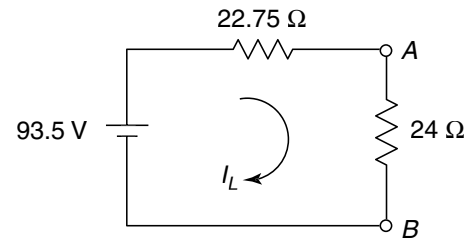


Fig. 3.147

Example 3.35

Find the current through the $3 \, \Omega$ resistor in Fig. 3.148.

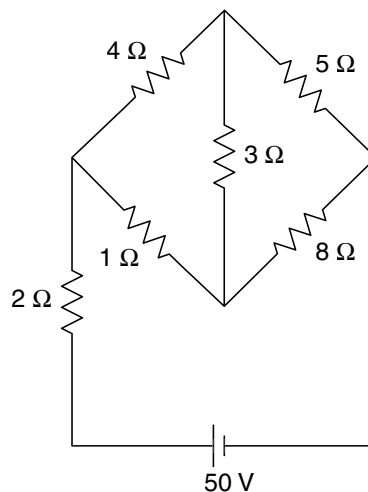


Fig. 3.148

Solution

Step I Calculation of V_{Th} (Fig. 3.149)

Applying KVL to Mesh 1,

$$\begin{aligned} 50 - 2I_1 - 1(I_1 - I_2) - 8(I_1 - I_2) &= 0 \\ 11I_1 - 9I_2 &= 50 \end{aligned} \quad \dots(i)$$

Applying KVL to Mesh 2,

$$\begin{aligned} -4I_2 - 5I_2 - 8(I_2 - I_1) - 1(I_2 - I_1) &= 0 \\ -9I_1 + 18I_2 &= 0 \end{aligned} \quad \dots(ii)$$

Solving Eqs (i) and (ii),

$$\begin{aligned} I_1 &= 7.69 \text{ A} \\ I_2 &= 3.85 \text{ A} \end{aligned}$$

Writing the V_{Th} equation,

$$V_{Th} - 5I_2 - 8(I_2 - I_1) = 0$$

$$\begin{aligned} V_{Th} &= 5I_2 + 8(I_2 - I_1) = 5(3.85) + 8(3.85 - 7.69) = -11.47 \text{ V} \\ &= 11.47 \text{ V (the terminal B is positive w.r.t. A)} \end{aligned}$$

Step II Calculation of R_{Th} (Fig. 3.150)

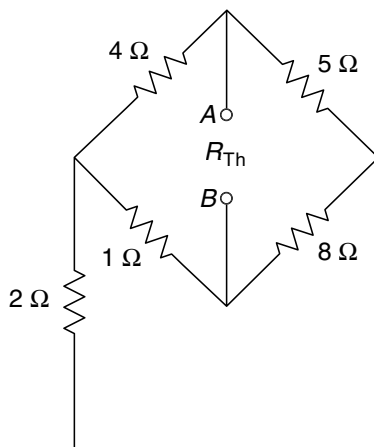


Fig. 3.150

Redrawing the network (Fig. 3.151),

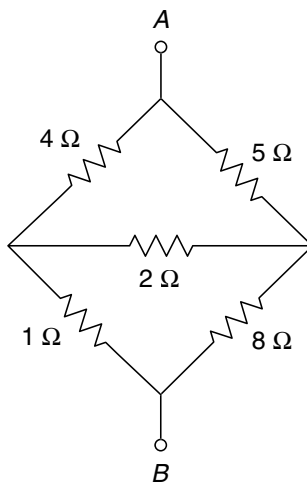


Fig. 3.151

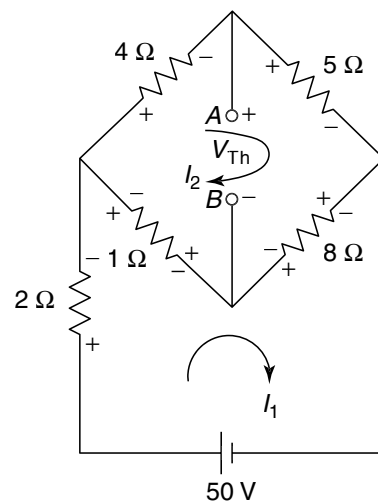


Fig. 3.149

Converting the upper delta into equivalent star network (Fig. 3.152),

$$R_1 = \frac{4 \times 2}{4 + 2 + 5} = 0.73 \, \Omega$$

$$R_2 = \frac{4 \times 5}{4 + 2 + 5} = 1.82 \, \Omega$$

$$R_3 = \frac{5 \times 2}{4 + 2 + 5} = 0.91 \, \Omega$$

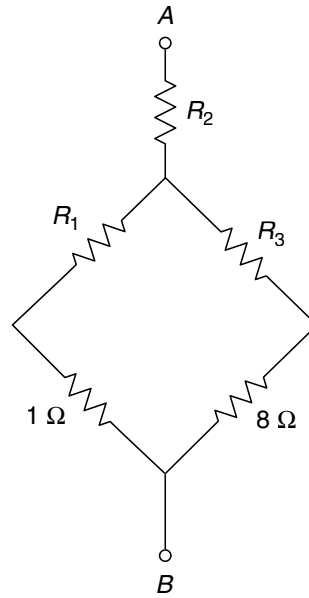


Fig. 3.152

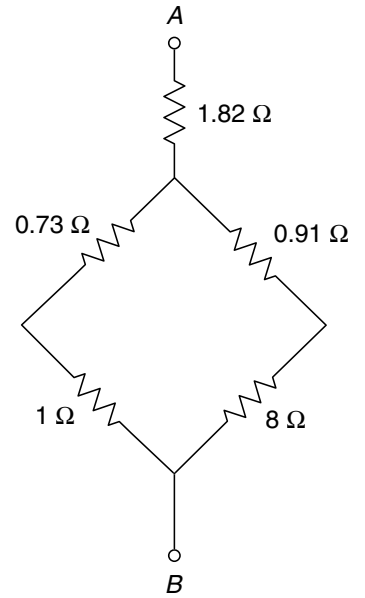


Fig. 3.153

Simplifying the network (Fig. 3.153),

$$R_{Th} = 1.82 + (1.73 \parallel 8.91) = 3.27 \, \Omega$$

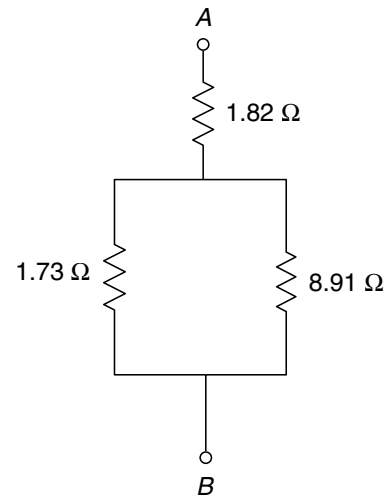


Fig. 3.154

Step III Calculation of I_L (Fig. 3.155)

$$I_L = \frac{11.47}{3.27 + 3} = 1.83 \, \text{A} (\uparrow)$$

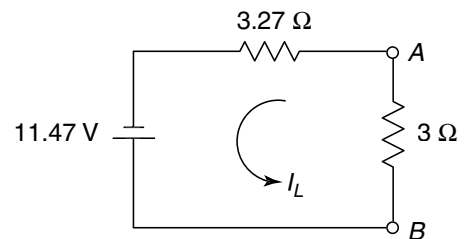
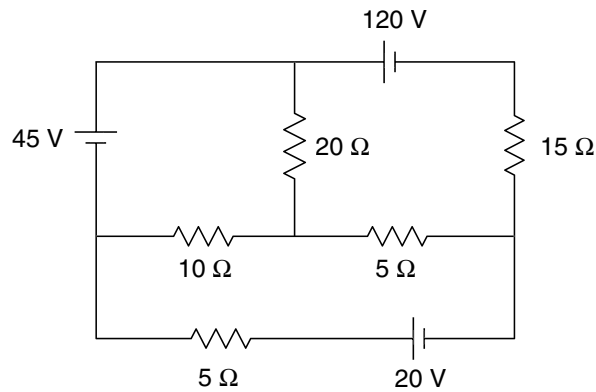


Fig. 3.155

Example 3.36Find the current through the $20\ \Omega$ resistor in Fig. 3.156.**Fig. 3.156****Solution****Step I** Calculation of V_{Th} (Fig. 3.157)

Applying KVL to Mesh 1,

$$45 - 120 - 15I_1 - 5(I_1 - I_2) - 10(I_1 - I_2) = 0 \quad \dots(i)$$

$$30I_1 - 15I_2 = -75$$

Applying KVL to Mesh 2,

$$20 - 5I_2 - 10(I_2 - I_1) - 5(I_2 - I_1) = 0 \quad \dots(ii)$$

$$-15I_1 + 20I_2 = 20$$

Solving Eqs (i) and (ii),



$$I_1 = -3.2\text{ A}$$

$$I_2 = -1.4\text{ A}$$

Writing the V_{Th} equation,

$$45 - V_{Th} - 10(I_1 - I_2) = 0$$

$$V_{Th} = 45 - 10(I_1 - I_2) = 45 - 10[-3.2 - (-1.4)] = 63\text{ V}$$

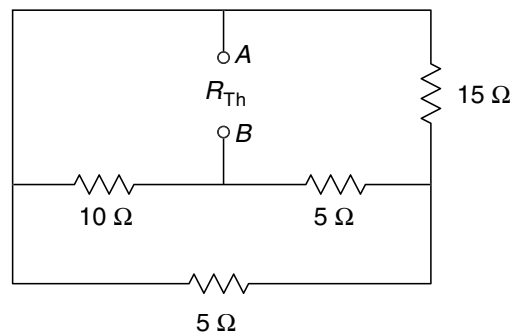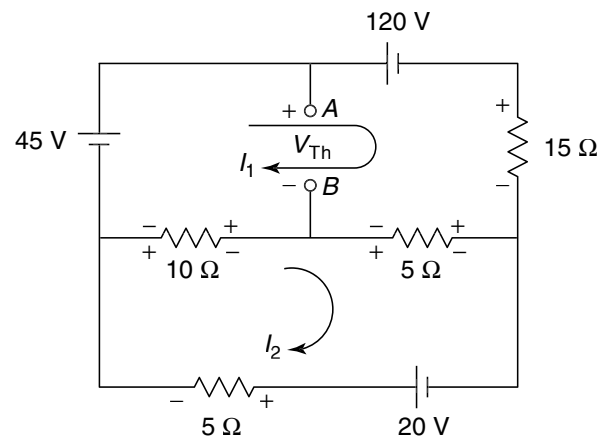Step II Calculation of R_{Th} (Fig. 3.158)**Fig. 3.158****Fig. 3.157**

Converting the delta formed by resistors of $10\ \Omega$, $5\ \Omega$ and $5\ \Omega$ into an equivalent star network (Fig. 3.159),

$$R_1 = \frac{10 \times 5}{20} = 2.5\ \Omega$$

$$R_2 = \frac{10 \times 5}{20} = 2.5\ \Omega$$

$$R_3 = \frac{5 \times 5}{20} = 1.25\ \Omega$$

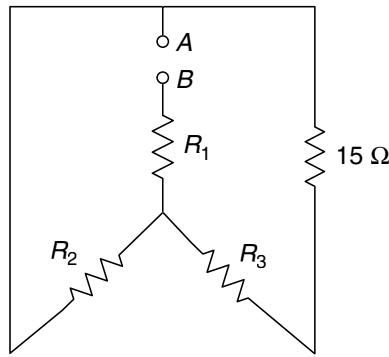


Fig. 3.159

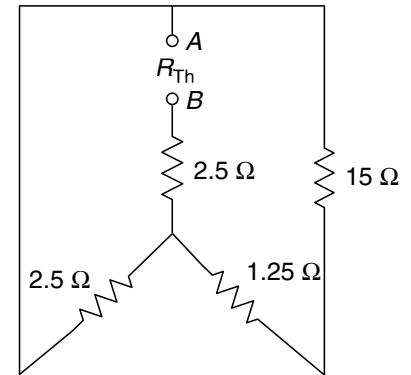


Fig. 3.160

Simplifying the network (Fig. 3.160),

$$R_{Th} = (16.25 \parallel 2.5) + 2.5 = 4.67\ \Omega$$

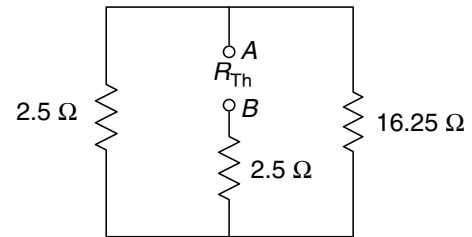


Fig. 3.161

Step III Calculation of I_L

$$I_L = \frac{63}{4.67 + 20} = 2.55\text{ A}$$

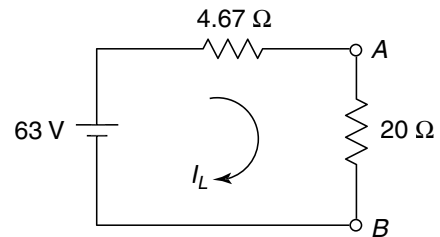


Fig. 3.162

Example 3.37

Find the current through the $3\ \Omega$ resistor in Fig. 3.163.

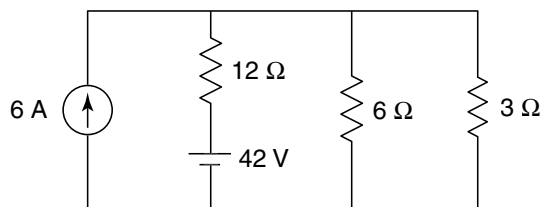


Fig. 3.163

Solution

Step I Calculation of V_{Th} (Fig. 3.164)

For Mesh 1,

$$I_1 = 6$$

Applying KVL to Mesh 2,

$$42 - 12(I_2 - I_1) - 6I_2 = 0$$

$$-12I_1 + 18I_2 = 42$$

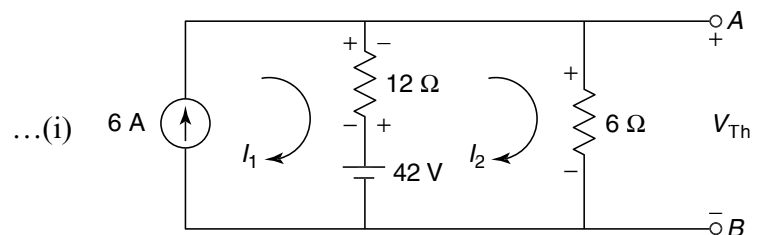


Fig. 3.164

3.44 Network Analysis and Synthesis

Solving Eqs (i) and (ii),

$$I_2 = 6.33 \text{ A}$$

Writing the V_{Th} equation,

$$V_{Th} = 6I_2 = 38 \text{ V}$$

Step II Calculation of R_{Th} (Fig. 3.165)

$$R_{Th} = 6 \parallel 12 = 4 \Omega$$

Step III Calculation of I_L (Fig. 3.166)

$$I_L = \frac{38}{4+3} = 5.43 \text{ A}$$

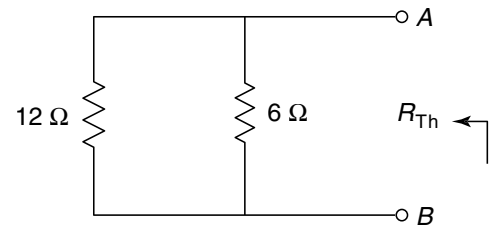


Fig. 3.165

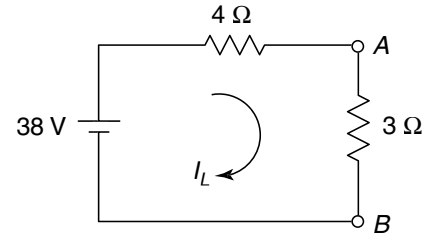


Fig. 3.166

Example 3.38

Find the current through the 30Ω resistor in Fig. 3.167.

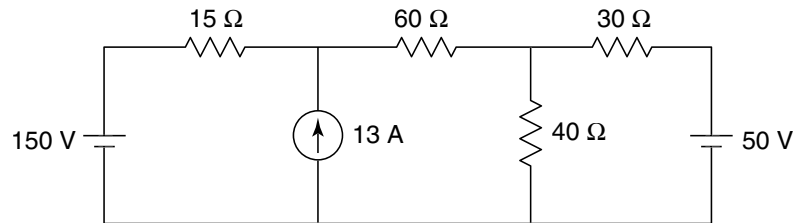


Fig. 3.167

Solution

Step I Calculation of V_{Th} (Fig. 3.168)

Meshes 1 and 2 form a supermesh.

Writing current equation for supermesh,

$$I_2 - I_1 = 13 \quad \dots(i)$$

Writing voltage equation for supermesh,

$$150 - 15I_1 - 60I_2 - 40I_2 = 0$$

$$15I_1 + 100I_2 = 150 \quad \dots(ii)$$

Solving Eqs (i) and (ii),

$$I_1 = -10 \text{ A}$$

$$I_2 = 3 \text{ A}$$

Writing the V_{Th} equation,

$$40I_2 - V_{Th} - 50 = 0$$

$$V_{Th} = 40I_2 - 50 = 40(3) - 50 = 70 \text{ V}$$

Step II Calculation of R_{Th} (Fig. 3.169)

$$R_{Th} = 75 \parallel 40 = 26.09 \Omega$$

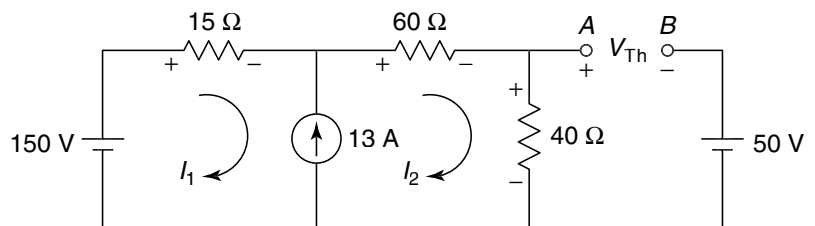


Fig. 3.168

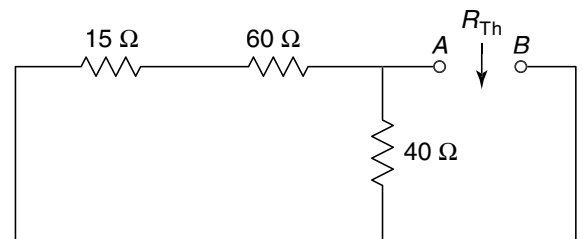


Fig. 3.169

Step III Calculation of I_L (Fig. 3.170)

$$I_L = \frac{70}{26.09 + 30} = 1.25 \text{ A}$$

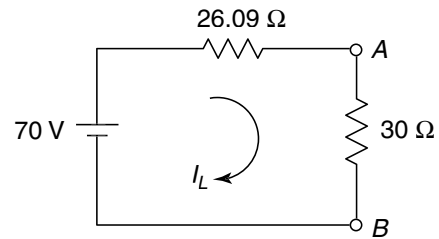


Fig. 3.170

Example 3.39

Find the current through the 20Ω resistor in Fig. 3.171.

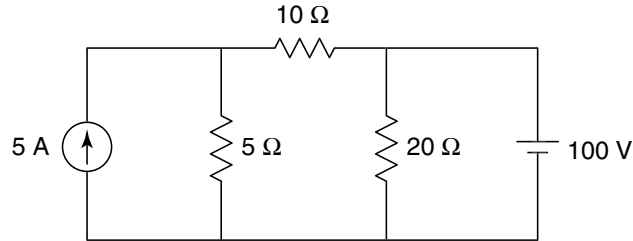


Fig. 3.171

Solution

Step I Calculation of V_{Th} (Fig. 3.172)

$$V_{Th} = 100 \text{ V}$$

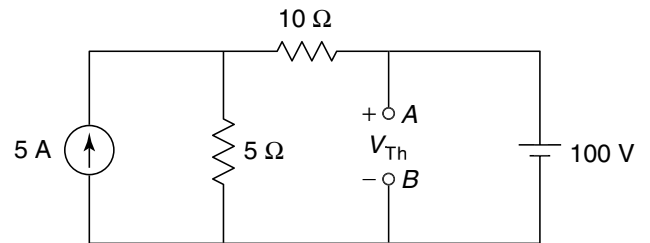


Fig. 3.172

Step II Calculation of R_{Th} (Fig. 3.173)

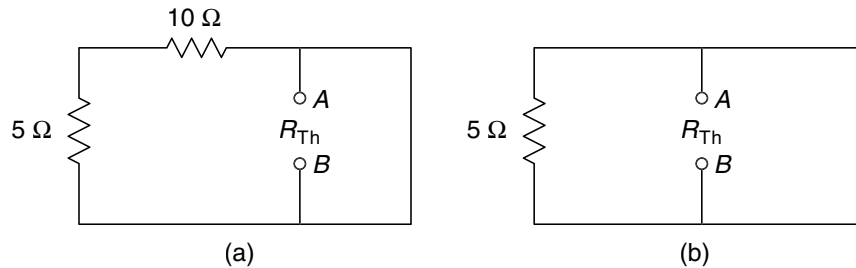


Fig. 3.173

$$R_{Th} = 0$$

Step III Calculation of I_L (Fig. 3.174)

$$I_L = \frac{100}{20} = 5 \text{ A}$$

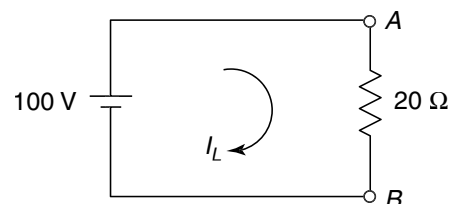
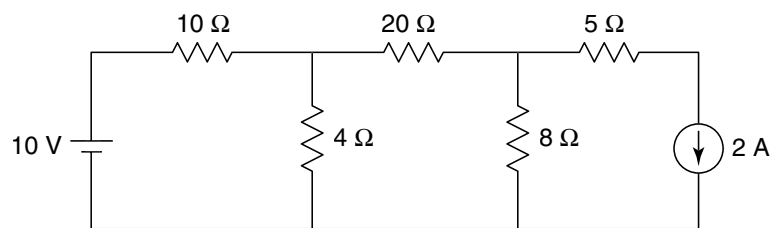


Fig. 3.174

Example 3.40Find the current through the $20\ \Omega$ resistor in Fig. 3.175.**Fig. 3.175****Solution****Step I** Calculation of V_{Th} (Fig. 3.176)



$$I_1 = \frac{10}{10 + 4} = 0.71\text{ A}$$

$$I_2 = 2\text{ A}$$

Writing the V_{Th} equation,

$$4I_1 - V_{Th} + 8I_2 = 0$$


$$V_{Th} = 4(0.71) + 8(2) = 18.84\text{ V}$$

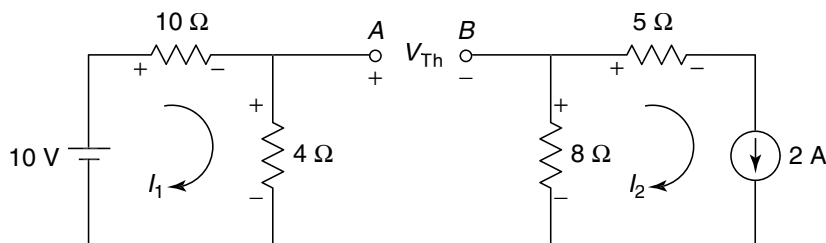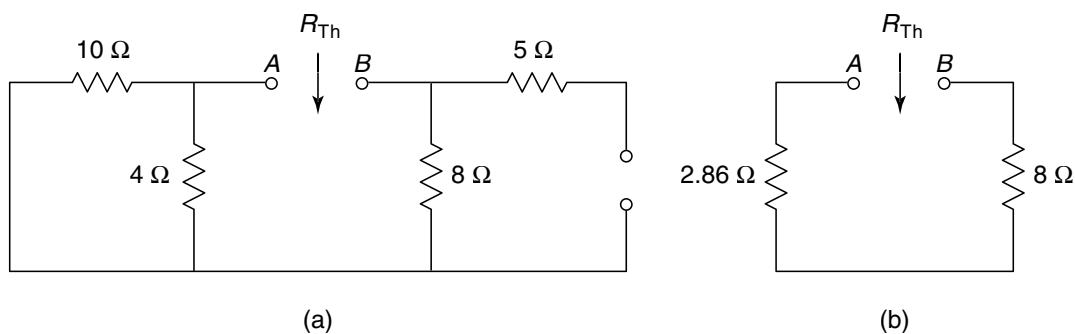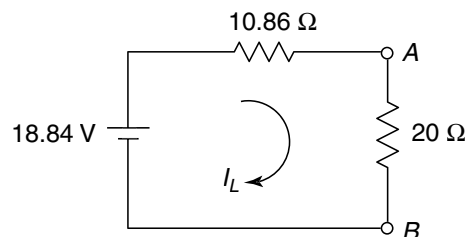
**Fig. 3.176****Step II** Calculation of R_{Th} (Fig. 3.177).**Fig. 3.177**

$$R_{Th} = 10.86\ \Omega$$

Step III Calculation of I_L (Fig. 3.178)

$$I_L = \frac{18.84}{10.86 + 20} = 0.61\text{ A}$$

**Fig. 3.178**

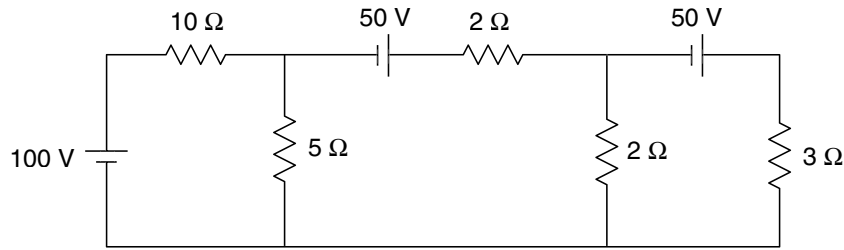Example 3.41Find the current through the $5\ \Omega$ resistor in Fig. 3.179.**Fig. 3.179****Solution****Step I** Calculation of V_{Th} (Fig. 3.180)

Applying KVL to Mesh 1,

$$100 - 10I_1 + 50 - 2I_1 - 2(I_1 - I_2) = 0$$

$$14I_2 - 2I_2 = 150$$

...(i)

Applying KVL to Mesh 2,

$$-2(I_2 - I_1) + 50 - 3I_2 = 0$$

$$-2I_1 + 5I_2 = 50 \quad \dots(ii)$$

Solving Eqs (i) and (ii),

$$I_1 = 12.88\text{ A}$$



$$I_2 = 15.15\text{ A}$$

Writing the V_{Th} equation,


$$100 - 10I_1 - V_{Th} = 0$$

$$V_{Th} = 100 - 10(12.88) = -28.8\text{ V}$$

$$= 28.8\text{ V (terminal B is positive w.r.t. A)}$$

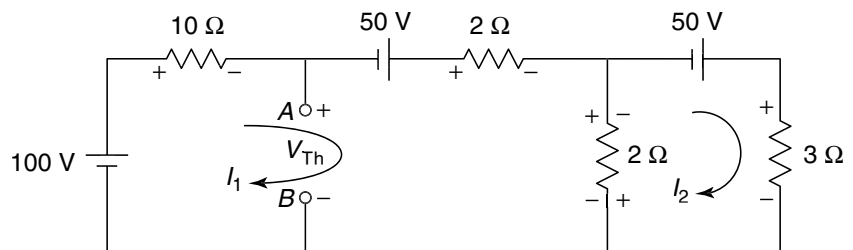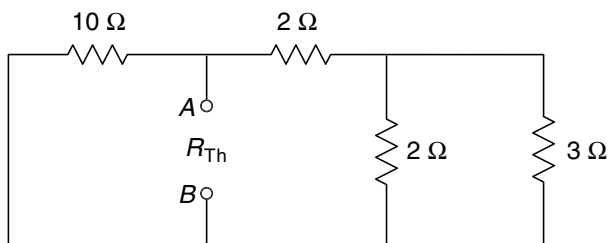
**Fig. 3.180****Step II** Calculation of R_{Th} (Fig. 3.181)

(a)

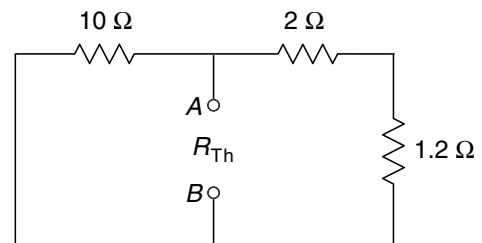

(b)
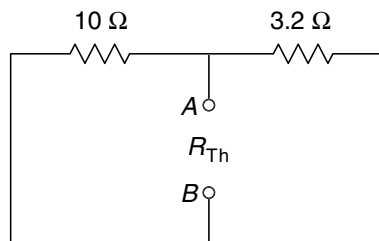
$$R_{Th} = 10 \parallel 3.2 = 2.42\ \Omega$$



(c)

Fig. 3.181

Step III Calculation of I_L (Fig. 3.182)

$$I_L = \frac{28.8}{2.42 + 5} = 3.88 \text{ A } (\uparrow)$$

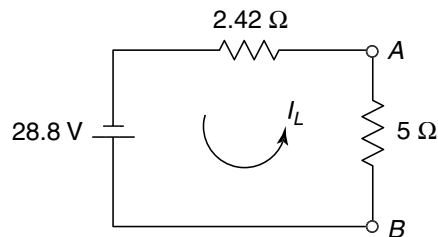


Fig. 3.182

Example 3.42

Find the current through the 10Ω resistor in Fig. 3.183.

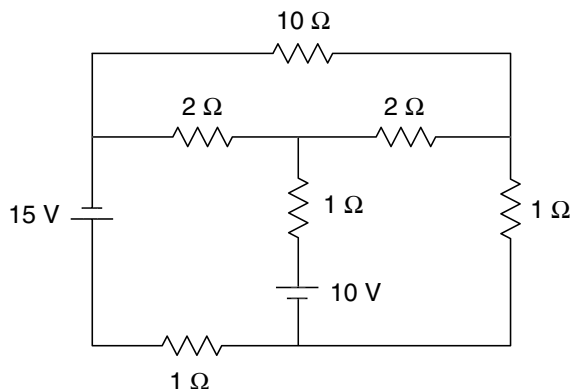


Fig. 3.183

Solution

Step I Calculation of V_{Th} (Fig. 3.183)

Applying KVL to Mesh 1,

$$\begin{aligned} -15 - 2I_1 - 1(I_1 - I_2) - 10 - 1I_1 &= 0 \\ 4I_1 - I_2 &= -25 \end{aligned} \quad \dots(i)$$

Applying KVL to Mesh 2,

$$\begin{aligned} 10 - 1(I_2 - I_1) - 2I_2 - 1I_2 &= 0 \\ -I_1 + 4I_2 &= 10 \end{aligned} \quad \dots(ii)$$

Solving Eqs (i) and (ii),

$$\begin{aligned} I_1 &= -6 \text{ A} \\ I_2 &= 1 \text{ A} \end{aligned}$$

Writing the V_{Th} equation,

$$\begin{aligned} -V_{Th} + 2I_2 + 2I_1 &= 0 \\ V_{Th} &= 2I_1 + 2I_2 = 2(-6) + 2(1) = -10 \text{ V} \\ &= 10 \text{ V (the terminal B is positive w.r.t. A)} \end{aligned}$$

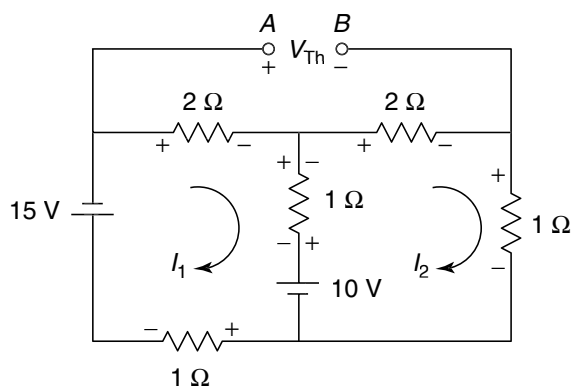


Fig. 3.184

Step II Calculation of R_{Th} (Fig. 3.185)

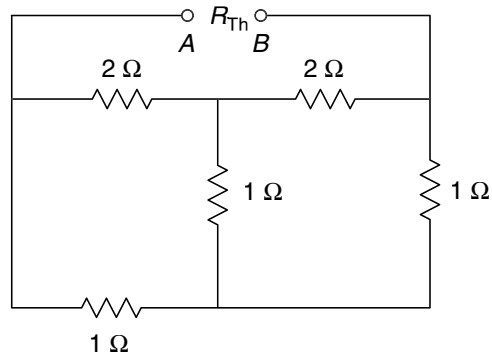


Fig. 3.185

Converting the star network formed by resistors of $2\ \Omega$, $2\ \Omega$ and $1\ \Omega$ into an equivalent delta network (Fig. 3.186),

$$R_1 = 2 + 2 + \frac{2 \times 2}{1} = 8\ \Omega$$

$$R_2 = 2 + 1 + \frac{2 \times 1}{2} = 4\ \Omega$$

$$R_3 = 2 + 1 + \frac{2 \times 1}{2} = 4\ \Omega$$

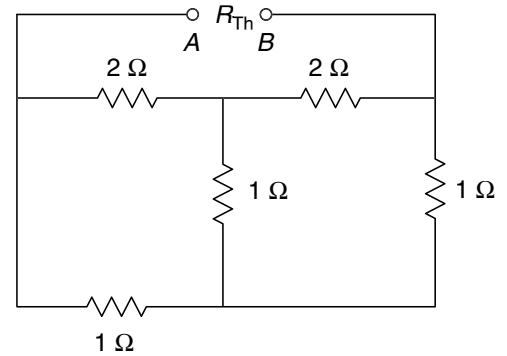


Fig. 3.186

Simplifying the network (Fig. 3.187),

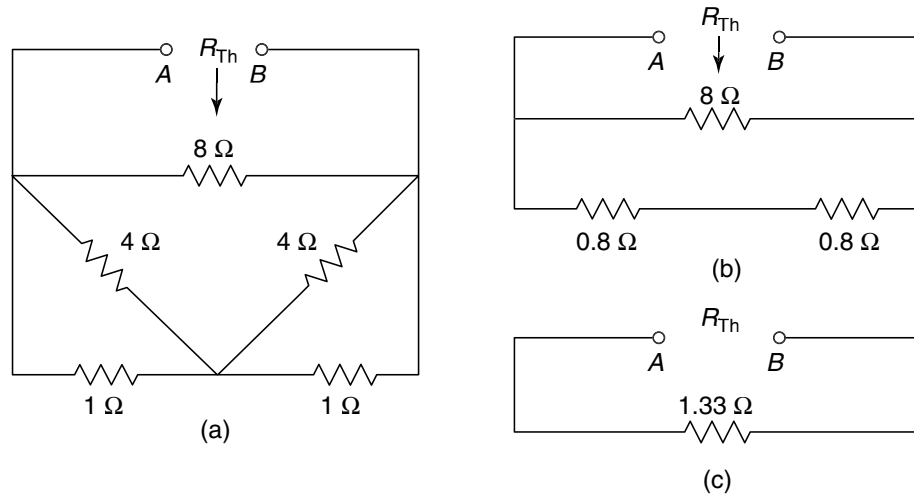


Fig. 3.187

$$R_{Th} = 1.33\ \Omega$$

Step III Calculation of I_L (Fig. 3.188)

$$I_L = \frac{10}{1.33 + 10} = 0.88 \text{ A } (\uparrow)$$

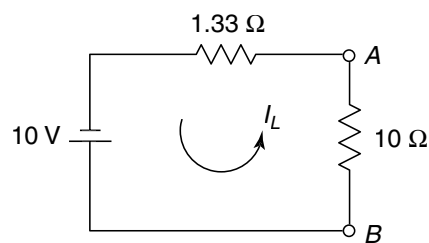


Fig. 3.188

Example 3.43

Find the current through the $1\ \Omega$ resistor in Fig. 3.189.

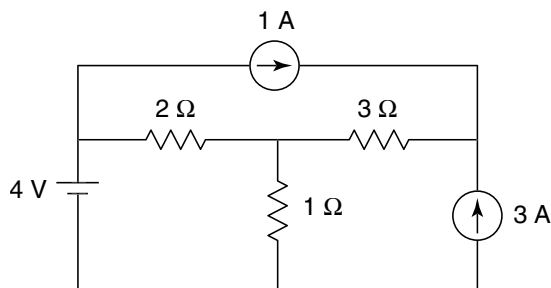


Fig. 3.189

Solution

Step I Calculation of V_{Th} (Fig. 3.190)

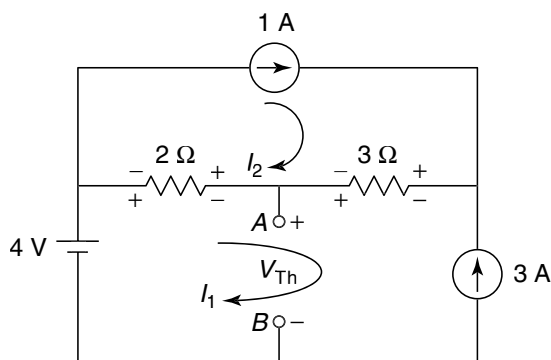


Fig. 3.190

Writing the current equations for Meshes 1 and 2,

$$I_1 = -3$$

$$I_2 = 1$$

Writing the V_{Th} equation,

$$4 - 2(I_1 - I_2) - V_{Th} = 0$$

$$V_{Th} = 4 - 2(I_1 - I_2) = 4 - 2(-4) = 12 \text{ V}$$

Step II Calculation of R_{Th} (Fig. 3.191)

$$R_{Th} = 2\ \Omega$$

Step III Calculation of I_L (Fig. 3.192)

$$I_L = \frac{12}{2 + 1} = 4 \text{ A}$$

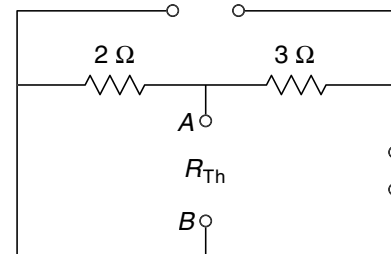


Fig. 3.191

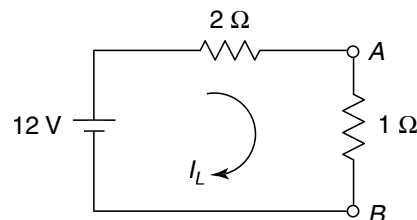
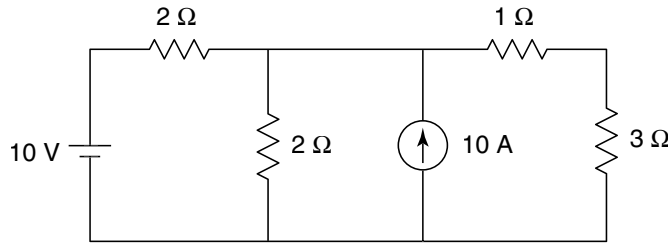
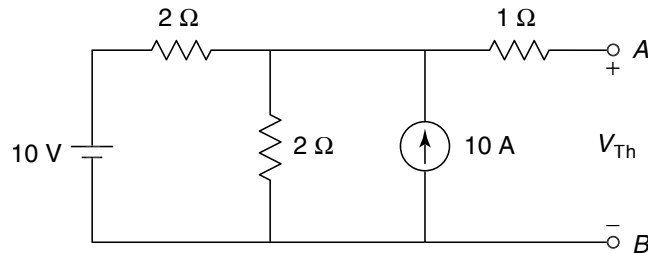
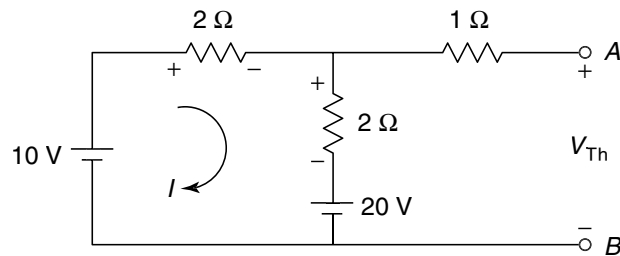


Fig. 3.192

Example 3.44Find the current through the $3\ \Omega$ resistor in Fig. 3.193.**Fig. 3.193****Solution****Step I** Calculation of V_{Th} (Fig. 3.194)**Fig. 3.194**

By source transformation (Fig. 3.195),

**Fig. 3.195**

Applying KVL to the mesh,

$$\begin{aligned} 10 - 2I - 2I - 20 &= 0 \\ 4I &= -10 \\ I &= -2.5\text{ A} \end{aligned}$$

Writing the V_{Th} equation,



$$\begin{aligned} 10 - 2I - V_{Th} &= 0 \\ V_{Th} &= 10 - 2I = 10 - 2(-2.5) = 15\text{ V} \end{aligned}$$

Step II Calculation of R_{Th} (Fig. 3.196)

$$R_{Th} = (2 \parallel 2) + 1 = 1 + 1 = 2\ \Omega$$

Step III Calculation of I_L (Fig. 3.197)

$$I_L = \frac{15}{2+3} = 3\text{ A}$$

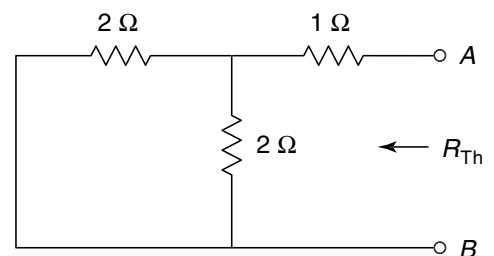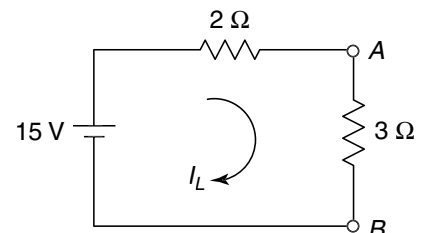**Fig. 3.196****Fig. 3.197**

EXAMPLES WITH DEPENDENT SOURCES

Example 3.45

Obtain the Thevenin equivalent network for the given network of Fig. 3.198 at terminals A and B.

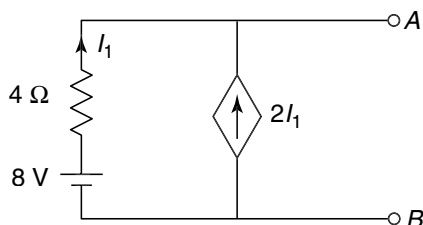


Fig. 3.198

Solution

Step I Calculation of V_{Th} (Fig. 3.199)

From Fig. 3.199,

$$I_1 = -2I_1$$

$$3I_1 = 0$$

$$I_1 = 0$$

Writing the V_{Th} equation,

$$8 - 0 - V_{Th} = 0$$

$$V_{Th} = 8 \text{ V}$$

Step II Calculation of I_N (Fig. 3.200),

Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1 = 2I_1$$

$$3I_1 - I_2 = 0 \quad \dots(i)$$

Applying KVL to the outer path of the supermesh,

$$8 - 4I_1 = 0$$

$$I_1 = 2 \quad \dots(ii)$$

Solving Eqs (i) and (ii),

$$I_2 = 6 \text{ A}$$

$$I_N = I_2 = 6 \text{ A}$$

Step III Calculation of R_{Th}

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{8}{6} = 1.33 \text{ } \Omega$$

Step IV Thevenin's Equivalent Network (Fig. 3.201)

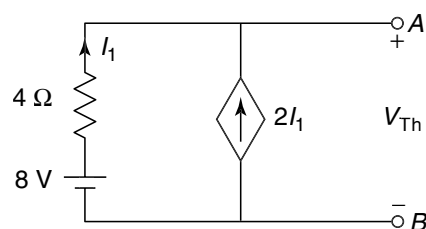


Fig. 3.199

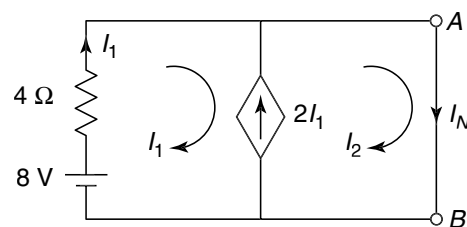


Fig. 3.200

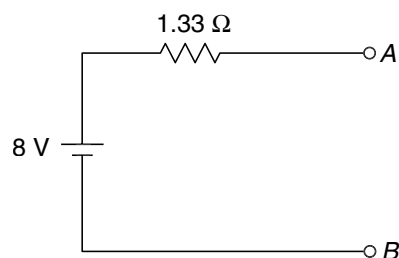
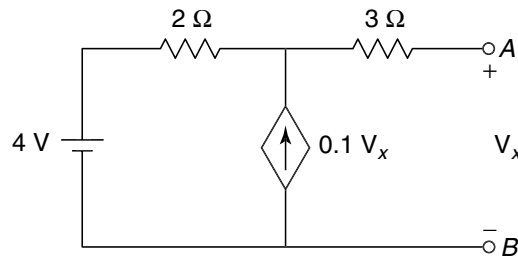


Fig. 3.201

Example 3.46

Find Thevenin's equivalent network of Fig. 3.202.

**Fig. 3.202****Solution****Step I** Calculation of V_{Th} (Fig. 3.203)

$$V_x = V_{Th}$$

$$I_1 = -0.1 V_x$$

Writing the V_{Th} equation,



$$4 - 2I_1 - V_x = 0$$

$$4 - 2(-0.1V_x) - V_x = 0$$

$$4 - 0.8V_x = 0$$

$$V_x = 5 \text{ V}$$

$$V_x = V_{Th} = 5 \text{ V}$$

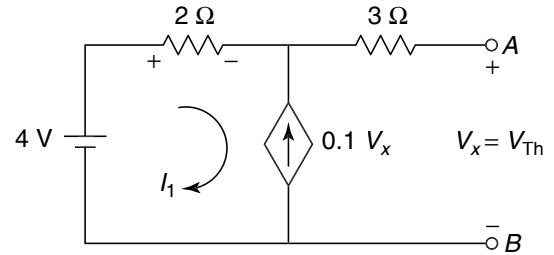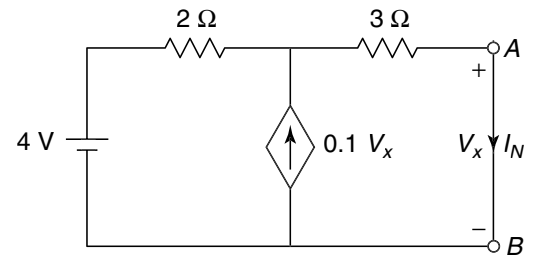
**Fig. 3.203****Fig. 3.204****Step II** Calculation of I_N (Fig. 3.204)

From Fig. 3.204,


$$V_x = 0$$

The dependent source $0.1 V_x$ depends on the controlling variable V_x . When $V_x = 0$, the dependent source vanishes, i.e., $0.1 V_x = 0$ as shown in Fig. 3.205.

$$I_N = \frac{4}{2+3} = 0.8 \text{ A}$$

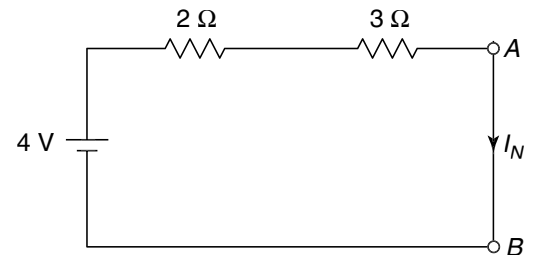
**Fig. 3.205****Step III** Calculation of R_{Th}

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{5}{0.8} = 6.25 \Omega$$

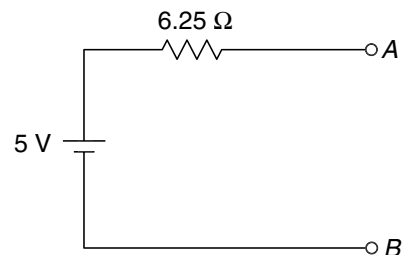Step IV Thevenin's Equivalent Network (Fig. 3.206)**Fig. 3.206**

Example 3.47

Obtain the Thevenin equivalent network of Fig. 3.207 for the terminals A and B.

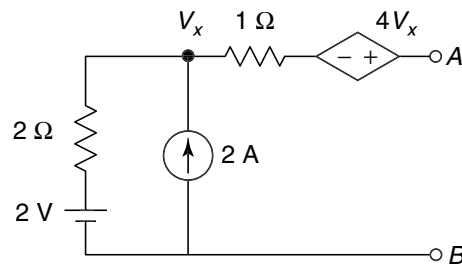**Fig. 3.207****Solution****Step I** Calculation of V_{Th} (Fig. 3.208)

From Fig. 3.208,

$$2 - 2I_1 - V_x = 0$$

$$V_x = 2 - 2I_1$$

For Mesh 1,

$$I_1 = -2 \text{ A}$$

$$V_x = 2 - 2(-2) = 6 \text{ V}$$

Writing the V_{Th} equation,

$$2 - 2I_1 - 0 + 4V_x - V_{Th} = 0$$

$$2 - 2(-2) - 0 + 4(6) - V_{Th} = 0$$

$$V_{Th} = 30 \text{ V}$$

Step II Calculation of I_N (Fig. 3.209)

From Fig. 3.209,

$$V_x = 2 - 2I_1$$

Meshes 1 and 2 will form a supermesh,

Writing current equation for the supermesh

$$I_2 - I_1 = 2$$

Applying KVL to the outer path of the supermesh,

$$2 - 2I_1 - 1I_2 + 4V_x = 0$$

$$2 - 2I_1 - I_2 + 4(2 - 2I_1) = 0$$

$$10I_1 + I_2 = 10$$

Solving Eqs (ii) and (iii),




$$I_1 = 0.73 \text{ A}$$

$$I_2 = 2.73 \text{ A}$$

$$I_N = I_2 = 2.73 \text{ A}$$


Step III Calculation of R_{Th}

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{30}{2.73} = 10.98 \Omega$$

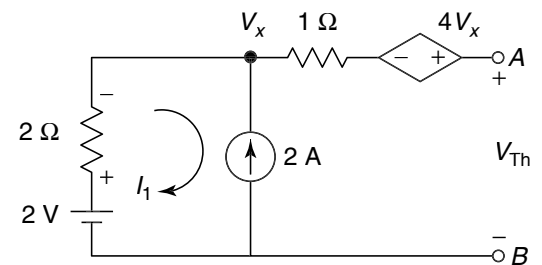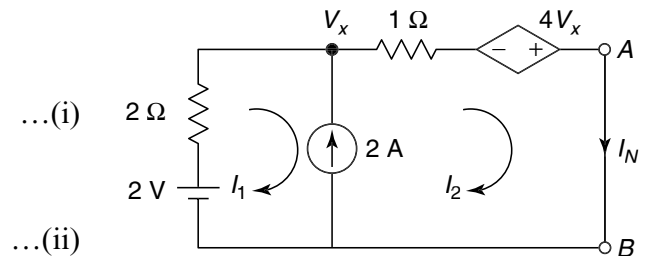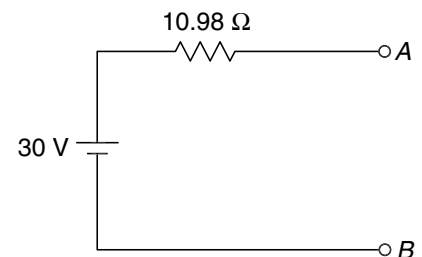Step IV Thevenin's Equivalent Network (Fig. 3.210)**Fig. 3.208****Fig. 3.209****Fig. 3.210**

Example 3.48

Find the Thevenin equivalent network of Fig. 3.211 for the terminals A and B.

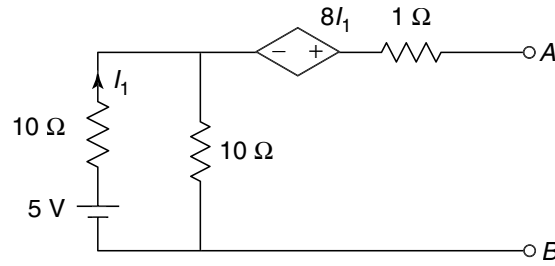**Fig. 3.211****Solution****Step I** Calculation of V_{Th} (Fig. 3.212)

Applying KVL to the mesh,

$$5 - 10I_1 - 10I_1 = 0$$

$$I_1 = \frac{5}{20} = 0.25 \text{ A}$$

Writing the V_{Th} equation,

$$5 - 10I_1 + 8I_1 - 0 - V_{Th} = 0$$

$$V_{Th} = 5 - 2I_1 = 5 - 2(0.25) = 4.5 \text{ V}$$

Step II Calculation of I_N (Fig. 3.213)

Applying KVL to Mesh 1,

$$5 - 10I_1 - 10(I_1 - I_2) = 0$$

$$20I_1 - 10I_2 = 5$$

Applying KVL to Mesh 2,

$$-10(I_2 - I_1) + 8I_1 - 1I_2 = 0$$

$$18I_1 - 11I_2 = 0 \quad \dots(ii)$$

Solving Eqs (i) and (ii),




$$I_1 = 1.375 \text{ A}$$


$$I_2 = 2.25 \text{ A}$$

$$I_N = I_2 = 2.25 \text{ A}$$

Step III Calculation of R_{Th}

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{4.5}{2.25} = 2 \Omega$$

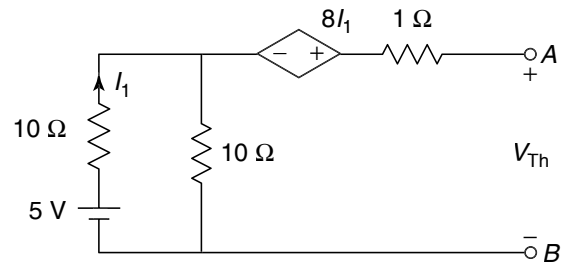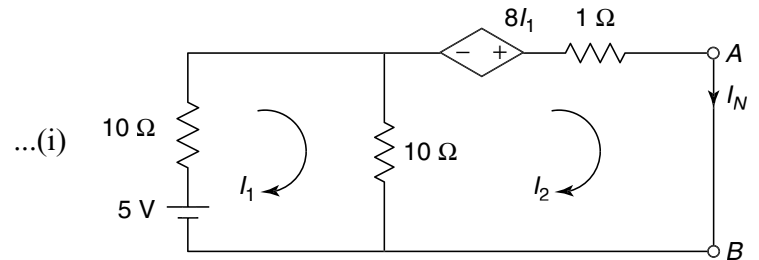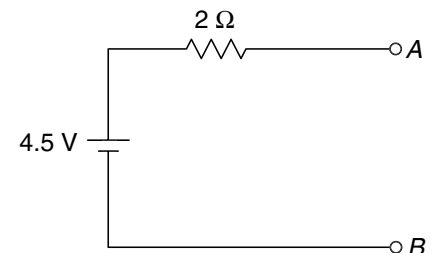Step IV Thevenin's Equivalent Network (Fig. 3.214)**Fig. 3.212****Fig. 3.213****Fig. 3.214**

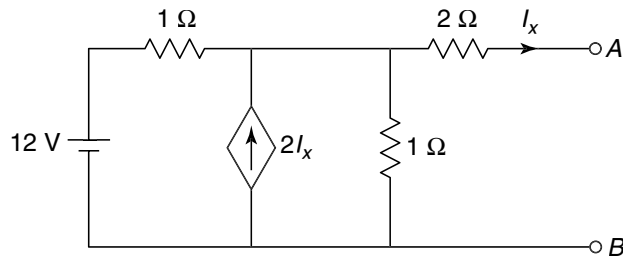Example 3.49Find V_{Th} and R_{Th} between terminals A and B of the network shown in Fig. 3.215.**Fig. 3.215****Solution****Step I** Calculation of V_{Th} (Fig. 3.216)

$$I_x = 0$$

The dependent source $2I_x$ depends on the controlling variable I_x . When $I_x = 0$, the dependent source vanishes, i.e., $2I_x = 0$ as shown in Fig. 3.216.

Writing the V_{Th} equation,

$$V_{Th} = 12 \times \frac{1}{1+1} = 6 \text{ V}$$

Step II Calculation of I_N (Fig. 3.217)

From Fig. 3.217,

$$I_x = \frac{V_1}{2}$$

Applying KCL at Node 1,

$$\frac{V_1 - 12}{1} + \frac{V_1}{1} + \frac{V_1}{2} = 2I_x$$



$$V_1 + V_1 + \frac{V_1}{2} - 12 = 2 \left(\frac{V_1}{2} \right)$$

$$V_1 = 8 \text{ V}$$

$$I_N = \frac{V_1}{2} = \frac{8}{2} = 4 \text{ A}$$

Step III Calculation of R_{Th}

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{6}{4} = 1.5 \Omega$$

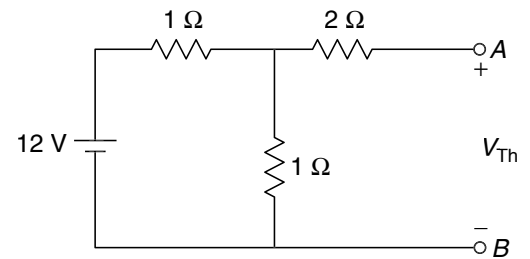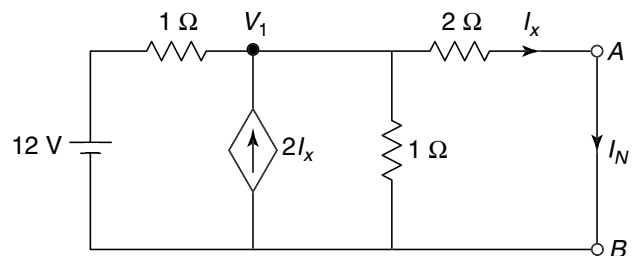**Fig. 3.216****Fig. 3.217****Example 3.50**Obtain the Thevenin equivalent network of Fig. 3.218 for the given network at terminals a and b .

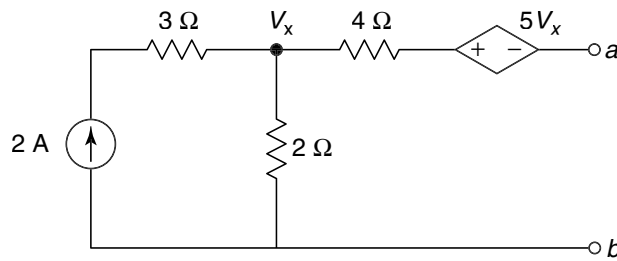


Fig. 3.218

Solution**Step I** Calculation of V_{Th} (Fig. 3.219)Applying KCL at Node x ,

$$2 = \frac{V_x}{2}$$

$$V_x = 4 \text{ V}$$

Writing the V_{Th} equation,

$$V_{Th} = V_x - 5V_x = -4V_x$$

$$= -16 \text{ V} \quad (\text{the terminal } a \text{ is negative w.r.t. } b)$$

Step II Calculation of I_N (Fig. 3.220)Applying KCL at Node x ,

$$2 = \frac{V_x}{2} + \frac{V_x - 5V_x}{4}$$

$$2 = \frac{V_x}{2} - V_x = -\frac{V_x}{2}$$

$$V_x = -4 \text{ V}$$

$$I_N = \frac{V_x - 5V_x}{4} = -V_x = 4 \text{ A}$$

Step III Calculation of R_{Th}

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{-16}{4} = -4 \Omega$$

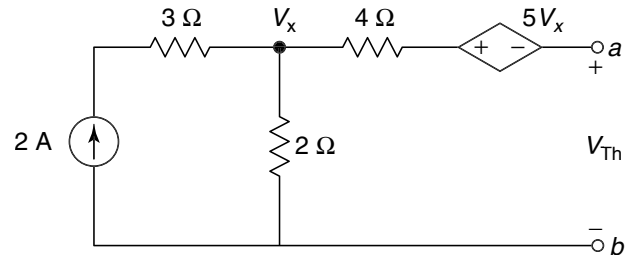
Step IV Thevenin's Equivalent Network (Fig. 3.221)

Fig. 3.219

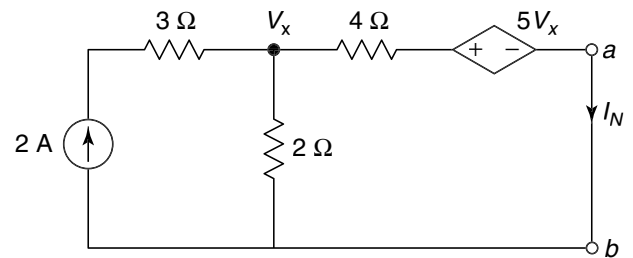


Fig. 3.220

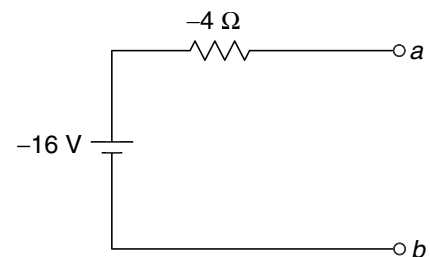


Fig. 3.221

Example 3.51

Obtain the Thevenin equivalent network of Fig. 3.222 for the given network.

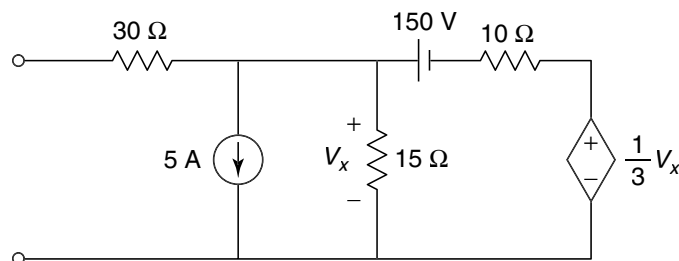


Fig. 3.222

Solution

Step I Calculation of V_{Th} (Fig. 3.223)

From Fig. 3.223

$$V_x = V_{Th}$$

Applying KCL at the node,

$$\frac{V_x - 150 - \frac{1}{3}V_x}{10} + \frac{V_x}{15} + 5 = 0$$

$$V_x = 75 \text{ V}$$

$$V_{Th} = 75 \text{ V}$$

Step II Calculation of I_N (Fig. 3.224)

Applying KCL at Node x ,

$$\frac{V_x}{30} + 5 + \frac{V_x}{15} + \frac{V_x - 150 - \frac{1}{3}V_x}{10} = 0$$

$$\frac{V_x}{30} + \frac{V_x}{15} + \frac{V_x}{10} - \frac{V_x}{30} = 15 - 5$$

$$V_x = 60 \text{ V}$$

$$I_N = \frac{V_x}{30} = \frac{60}{30} = 2 \text{ A}$$

Step III Calculation of R_{Th}

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{75}{2} = 37.5 \Omega$$

Step IV Thevenin's Equivalent Network (Fig. 3.225)

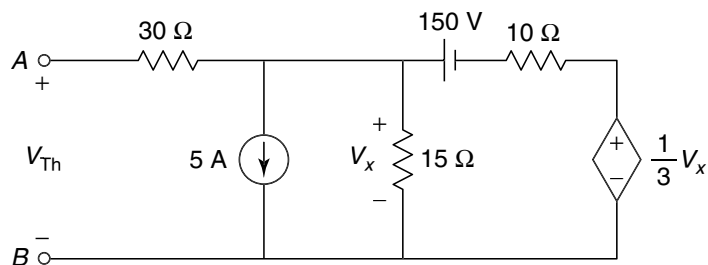


Fig. 3.223

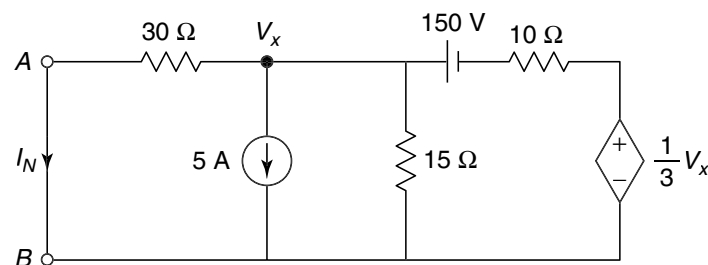


Fig. 3.224

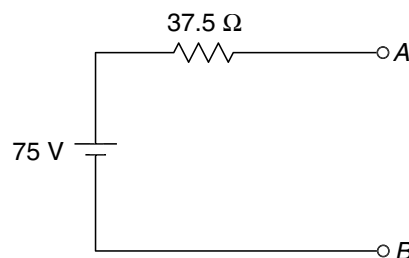


Fig. 3.225

Example 3.52

Find the Thevenin's equivalent network of the network to the left of A-B in the Fig. 3.226.

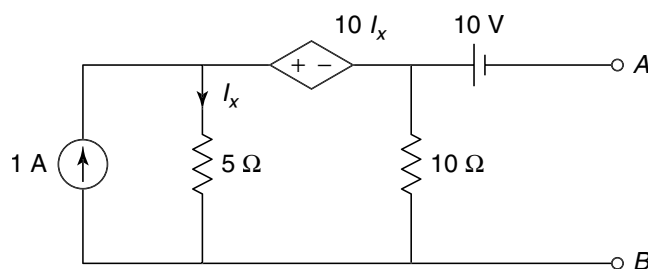


Fig. 3.226

Solution

Step I Calculation of V_{Th} (Fig. 3.227)

From Fig. 3.227,

$$I_x = I_1 - I_2 \quad \dots(i)$$

For Mesh 1,

$$I_1 = 1 \quad \dots(ii)$$

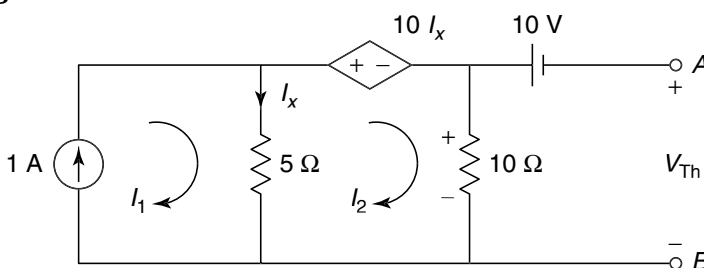


Fig. 3.227

Applying KVL to Mesh 2,

$$-5(I_2 - I_1) - 10I_x - 10I_2 = 0$$

$$-5(I_2 - I_1) - 10(I_1 - I_2) - 10I_2 = 0$$

$$5I_1 + 5I_2 = 0$$

...(iii)

Solving Eqs (ii) and (iii),

$$I_1 = 1 \text{ A}$$

$$I_2 = -1 \text{ A}$$

$$I_x = I_1 - I_2 = 1 - (-1) = 2 \text{ A}$$

Writing the V_{Th} equation,

$$10I_2 - 10 - V_{Th} = 0$$

$$10(-1) - 10 - V_{Th} = 0$$

$$V_{Th} = -20 \text{ V}$$

Step II Calculation of I_N (Fig. 3.228)

From Fig. 3.228,

$$I_x = I_1 - I_2 \quad \dots(i)$$

For Mesh 1,

$$I_1 = 1 \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$-5(I_2 - I_1) - 10I_x - 10(I_2 - I_3) = 0$$

$$-5(I_2 - I_1) - 10(I_1 - I_2) - 10(I_2 - I_3) = 0$$

$$-5I_1 - 5I_2 + 10I_3 = 0$$

...(iii)

Applying KVL to Mesh 3,

$$-10(I_3 - I_2) - 10 = 0$$

$$10I_2 - 10I_3 = 10$$

...(iv)

Solving Eqs (ii), (iii) and (iv),

$$I_1 = 1 \text{ A}$$

$$I_2 = 3 \text{ A}$$

$$I_3 = 2 \text{ A}$$

$$I_N = I_3 = 2 \text{ A}$$

Step III Calculation of R_{Th}

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{-20}{2} = -10 \Omega$$

Step IV Thevenin's Equivalent Network (Fig. 3.229)

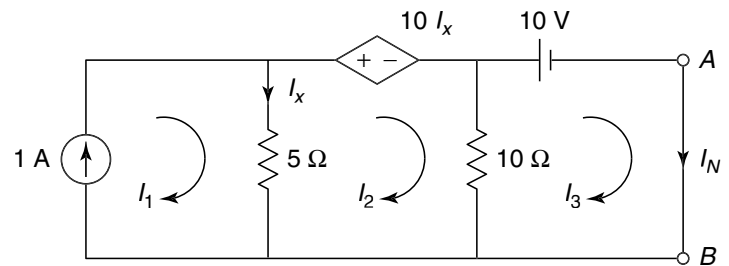


Fig. 3.228

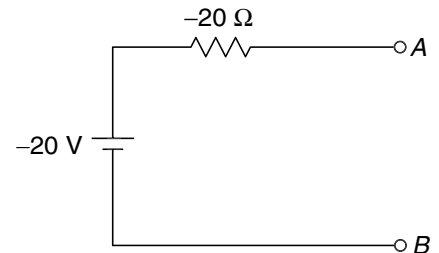


Fig. 3.229

Example 3.53

Find Thevenin's equivalent network at terminals A and B in the network of Fig. 3.230.

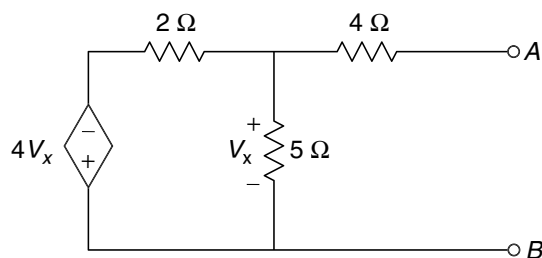


Fig. 3.230

Solution

Since the network does not contain any independent source,

$$V_{Th} = 0$$

$$I_N = 0$$

But the R_{Th} can be calculated by applying a known voltage source of 1 V at the terminals A and B as shown in Fig. 3.231.

$$R_{Th} = \frac{V}{I} = \frac{1}{I}$$

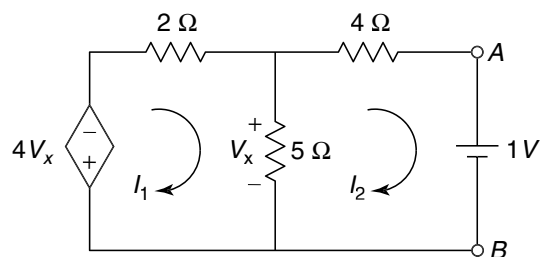


Fig. 3.231

From Fig. 3.231,

$$V_x = 5(I_1 - I_2)$$

...(i)

Applying KVL to Mesh 1,

$$-4V_x - 2I_1 - 5(I_1 - I_2) = 0$$

$$-4[5(I_1 - I_2)] - 2I_1 - 5I_1 + 5I_2 = 0$$

$$-27I_1 + 25I_2 = 0$$

...(ii)

Applying KVL to Mesh 2,

$$-5(I_2 - I_1) - 4I_2 - 1 = 0$$

$$5I_1 - 9I_2 = 1$$

...(iii)

Solving Eqs (ii) and (iii),

$$I_1 = -0.21 \text{ A}$$

$$I_2 = -0.23 \text{ A}$$

Hence, current supplied by voltage source of 1 V is 0.23 A.

$$R_{Th} = \frac{1}{0.23} = 4.35 \Omega$$

Hence, Thevenin's equivalent network is shown in Fig. 3.232.

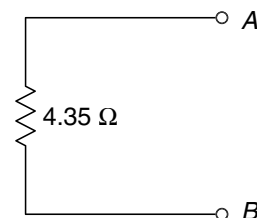


Fig. 3.232

Example 3.54

Find the current in the 9Ω resistor in Fig. 3.233.

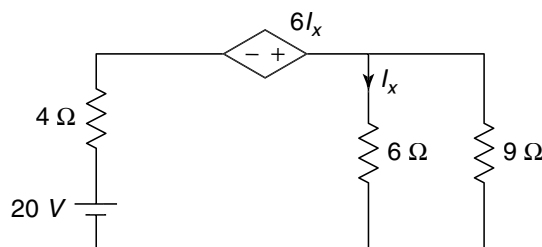


Fig. 3.233

Solution**Step I** Calculation of V_{Th} (Fig. 3.234)

Applying KVL to the mesh,

$$20 - 4I_x + 6I_x - 6I_x = 0$$

$$I_x = 5 \text{ A}$$

Writing the V_{Th} equation,

$$6I_x - V_{Th} = 0$$

$$6(5) - V_{Th} = 0$$

$$V_{Th} = 30 \text{ V}$$


Step II Calculation of I_N (Fig. 3.235).

From Fig. 3.235,

$$I_x = 0$$

The dependent source $6I_x$ depends on the controlling variable I_x . When $I_x = 0$, the dependent source vanishes, i.e., $6I_x = 0$ as shown in Fig. 3.236.





$$I_N = \frac{20}{4} = 5 \text{ A}$$

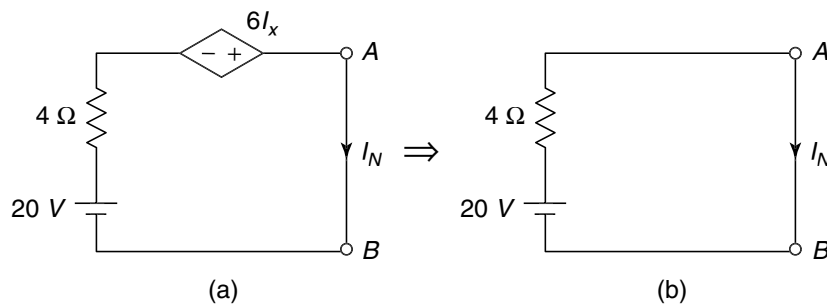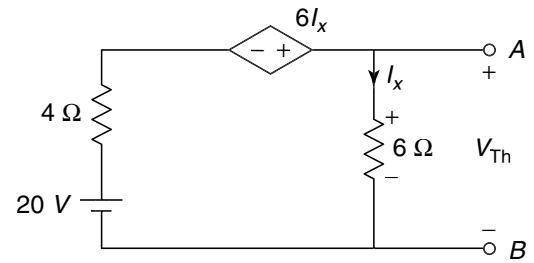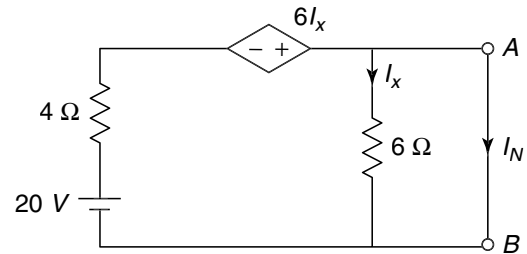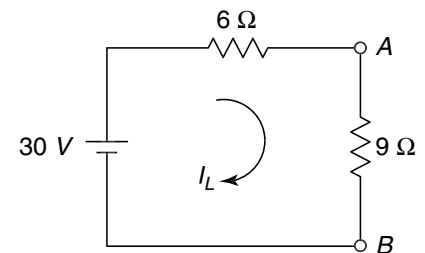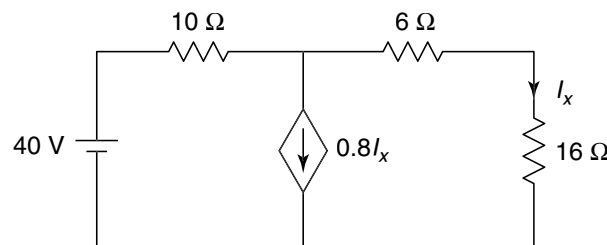**Fig. 3.236****Step III** Calculation of R_{Th}

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{30}{5} = 6 \Omega$$

Step IV Calculation of I_L (Fig. 3.237)

$$I_L = \frac{30}{6+9} = 2 \text{ A}$$

**Fig. 3.234****Fig. 3.235****Fig. 3.237****Example 3.55**Determine the current in the 16Ω resistor in Fig. 3.238.**Fig 3.238**

Solution

Step I Calculation of V_{Th} (Fig. 3.239)

From Fig. 3.239,

$$I_x = 0$$

The dependent source $0.8I_x$ depends on the controlling variable I_x . When $I_x = 0$, the dependent source vanishes, as shown in Fig. 3.240.

i.e.,

$$0.8I_x = 0$$

$$V_{Th} = 40 \text{ V}$$

Step II Calculation of I_N (Fig. 3.241)

From Fig. 3.241,

$$I_x = I_2$$

Meshes 1 and 2 will form a supermesh,

Writing current equation for the supermesh,

$$I_1 - I_2 = 0.8 I_x = 0.8 I_2$$

$$I_1 - 1.8 I_2 = 0$$

Applying KVL to the outer path of the supermesh,

$$40 - 10 I_1 - 6 I_2 = 0$$

$$10 I_1 + 6 I_2 = 40$$

Solving Eqs (ii) and (iii),

$$I_1 = 3 \text{ A}$$

$$I_2 = \frac{5}{3} \text{ A}$$

$$I_N = I_2 = \frac{5}{3} \text{ A}$$

Step III Calculation of R_{Th}

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{40}{\frac{5}{3}} = 24 \Omega$$

Step IV Calculation of I_L (Fig. 3.242)

$$I_L = \frac{40}{24 + 16} = 1 \text{ A}$$

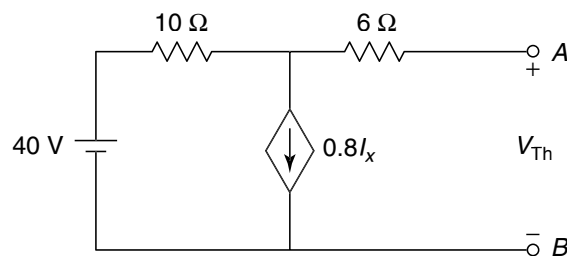


Fig. 3.239

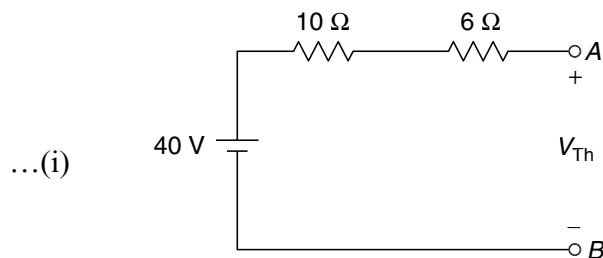


Fig. 3.240

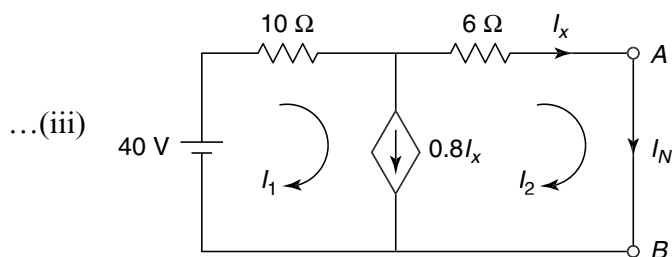


Fig. 3.241

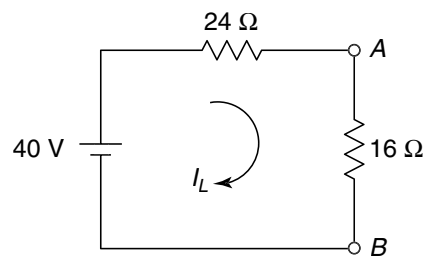


Fig. 3.242

Example 3.56

Find the current in the 6Ω resistor in Fig. 3.243.

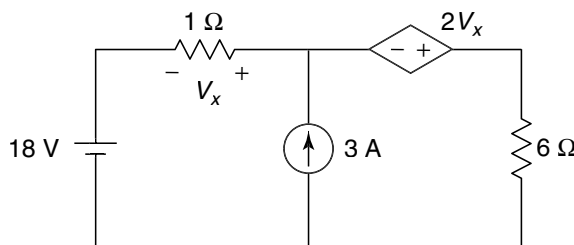


Fig. 3.243

Solution**Step I** Calculation of V_{Th} (Fig. 3.244)

From Fig. 3.244,

$$V_x = -1I_1 = -I_1 \quad \dots(i)$$

For Mesh 1,

$$I_1 = -3 \text{ A} \quad \dots(ii)$$

$$V_x = 3 \text{ V}$$

Writing the V_{Th} equation,

$$18 - 1I_1 + 2V_x - V_{Th} = 0$$

$$18 + 3 + 2(3) - V_{Th} = 0$$

$$V_{Th} = 27 \text{ V}$$

Step II Calculation of I_N (Fig. 3.245)

From Fig. 3.245,

$$V_x = -I_1 \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh,
Writing current equation for supermesh,

$$I_2 - I_1 = 3 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$18 - 1I_1 + 2V_x = 0$$

$$18 - I_1 + 2(-I_1) = 0 \quad \dots(iii)$$

$$I_1 = 6 \text{ A}$$

Solving Eqs (ii) and (iii),

$$I_2 = 9 \text{ A}$$





$$I_N = I_2 = 9 \text{ A}$$

Step III Calculation of R_{Th}

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{27}{9} = 3 \Omega$$

Step IV Calculation of I_L (Fig. 3.246)

$$I_L = \frac{27}{3+6} = 3 \text{ A}$$

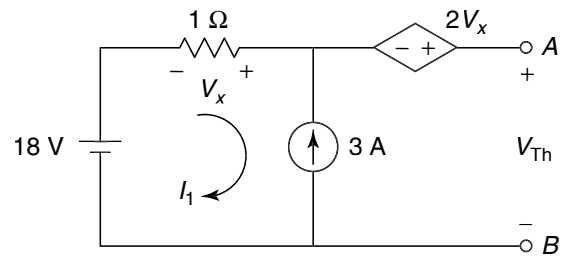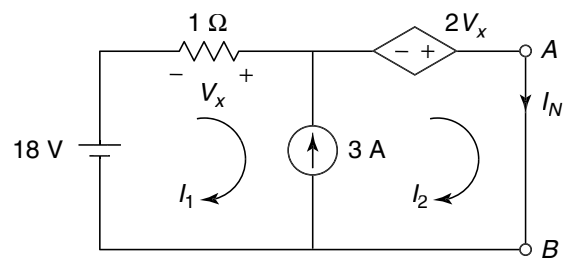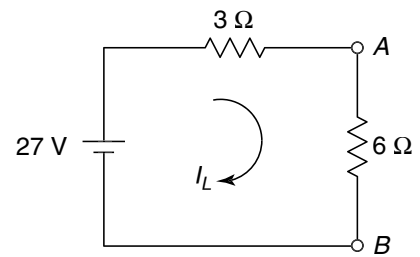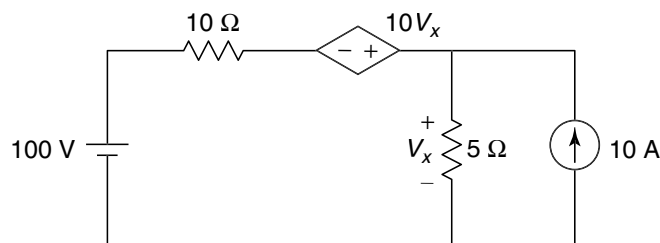**Fig. 3.244****Fig. 3.245****Fig. 3.246****Example 3.57**Find the current in the 10Ω resistor.**Fig. 3.247**

Solution

Step I Calculation of V_{Th} (Fig. 3.248)

From the figure,

$$V_x = 10 \times 5 = 50 \text{ V}$$

Writing the V_{Th} equation,

$$100 - V_{Th} + 10V_x - V_x = 0$$

$$100 - V_{Th} + 9V_x = 0$$

$$100 - V_{Th} + 9(50) = 0$$

$$V_{Th} = 550 \text{ V}$$

Step II Calculation of I_N (Fig. 3.249)

From Fig. 3.249,

$$V_x = 5(I_N + 10)$$

Applying KVL to Mesh 1,

$$100 + 10V_x - V_x = 0$$

$$V_x = -\frac{100}{9}$$

$$-\frac{100}{9} = 5I_N + 50$$

$$I_N = -\frac{550}{45} \text{ A}$$

Step III Calculation of R_{Th}

$$R_{Th} = \frac{550}{-\frac{550}{45}} = -45 \Omega$$

Step IV Calculation of I_L (Fig. 3.250)

$$I_L = \frac{550}{-45 + 10} = -\frac{110}{7} \text{ A}$$

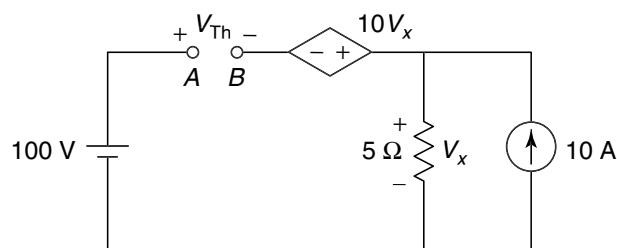


Fig. 3.248

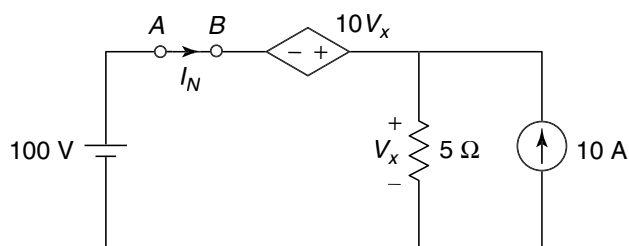


Fig. 3.249

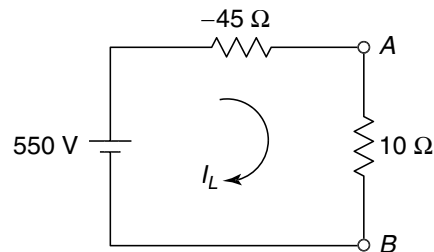


Fig. 3.250

3.4 NORTON'S THEOREM

It states that 'any two terminals of a network can be replaced by an equivalent current source and an equivalent parallel resistance.' The constant current is equal to the current which would flow in a short circuit placed across the terminals. The parallel resistance is the resistance of the network when viewed from these open-circuited terminals after all voltage and current sources have been removed and replaced by internal resistances.

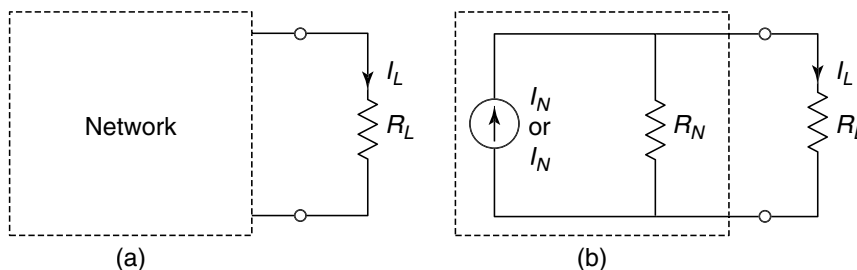


Fig. 3.251 Network illustrating Norton's theorem

Explanation Consider a simple network as shown in Fig.3.252

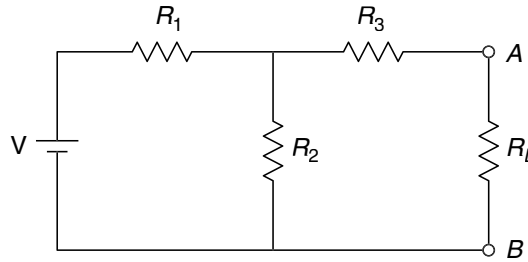


Fig. 3.252 Network

For finding load current through R_L , first remove the load resistor R_L from the network and calculate short circuit current I_{SC} or I_N which would flow in a short circuit placed across terminals A and B as shown in Fig. 3.253.

For finding parallel resistance R_N , replace the voltage source by a short circuit and calculate resistance between points A and B as shown in Fig. 3.254.

$$R_N = R_3 + \frac{R_1 R_2}{R_1 + R_2}$$

Norton's equivalent network is shown in Fig.3.255.

$$I_L = I_N \frac{R_N}{R_N + R_L}$$

If the network contains both independent and dependent sources, Norton's resistance R_N is calculated as

$$R_N = \frac{V_{Th}}{I_N}$$

where V_{Th} is the open-circuit voltage across terminals A and B . If the network contains only dependent sources, then

$$V_{Th} = 0$$

$$I_N = 0$$

To find R_{Th} in such network, a known voltage V or current I is applied across the terminals A and B , and the current I or the voltage V is calculated respectively.

$$R_N = \frac{V}{I}$$

Norton's equivalent network for such a network is shown in Fig. 3.256.

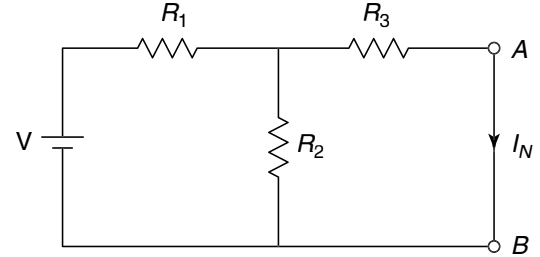


Fig. 3.253 Calculation of I_N

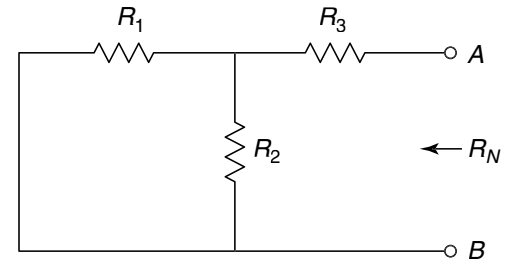


Fig. 3.254 Calculation of R_N

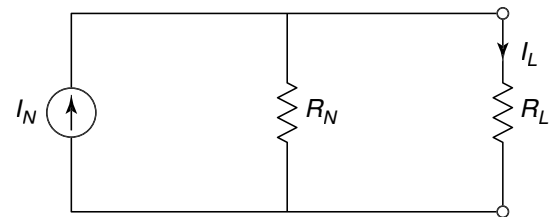


Fig. 3.255 Norton's equivalent network

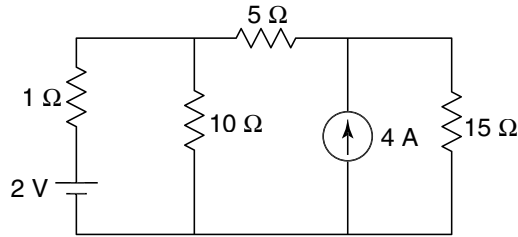


Fig. 3.256 Norton's equivalent network

Steps to be followed in Norton's Theorem

1. Remove the load resistance R_L and put a short circuit across the terminals.
2. Find the short-circuit current I_{SC} or I_N .
3. Find the resistance R_N as seen from points A and B .
4. Replace the network by a current source I_N in parallel with resistance R_N .
5. Find current through R_L by current-division rule.

$$I_L = \frac{I_N R_N}{R_N + R_L}$$

Example 3.58Find the current through the $10\ \Omega$ resistor in Fig. 3.257.**Fig. 3.257****Solution****Step I** Calculation of I_N (Fig. 3.258)

Applying KVL to Mesh 1,

$$2 - 1I_1 = 0$$

$$I_1 = 2$$

Meshes 2 and 3 will form a supermesh.

Writing the current equation for the supermesh,

$$I_3 - I_2 = 4 \quad \dots(ii)$$

Applying KVL to the supermesh,

$$-5I_2 - 15I_3 = 0 \quad \dots(iii)$$

Solving Eqs (i), (ii) and (iii),

$$I_1 = 2\text{ A}$$

$$I_2 = -3\text{ A}$$

$$I_3 = 1\text{ A}$$




$$I_N = I_1 - I_2 = 2 - (-3) = 5\text{ A}$$


Step II Calculation of R_N (Fig. 3.259)

$$R_N = 1 \parallel (5 + 15) = 0.95\ \Omega$$

Step III Calculation of I_L (Fig. 3.260)

$$I_L = 5 \times \frac{0.95}{0.95 + 10} = 0.43\text{ A}$$

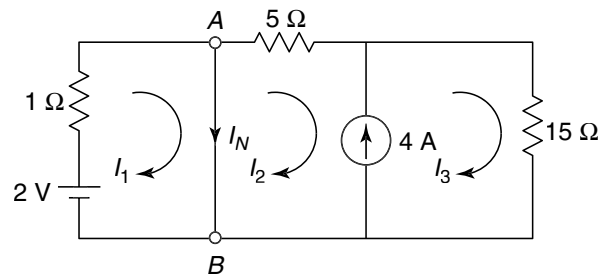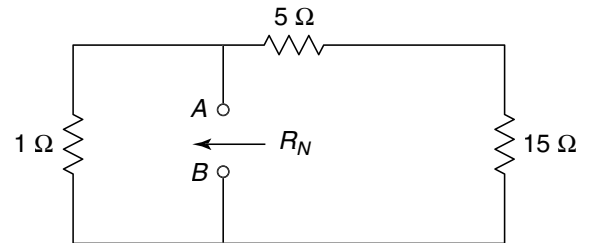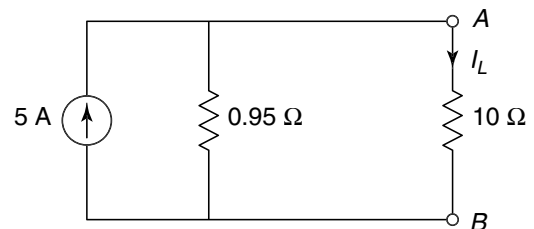**Fig. 3.258****Fig. 3.259****Fig. 3.260**

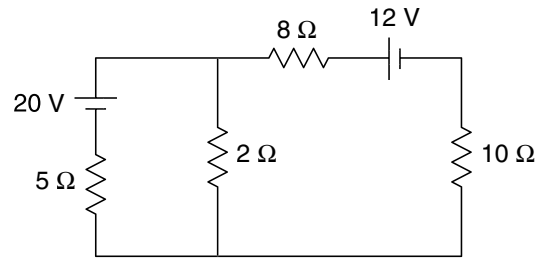Example 3.59Find the current through the $10\ \Omega$ resistor in Fig. 3.258.**Fig. 3.261****Solution****Step I** Calculation of I_N (Fig. 3.262)

Applying KVL to Mesh 1,

$$\begin{aligned} -5I_1 + 20 - 2(I_1 - I_2) &= 0 \\ 7I_1 - 2I_2 &= 20 \end{aligned} \quad \dots(i)$$

Applying KVL to Mesh 2,

$$\begin{aligned} -2(I_2 - I_1) - 8I_2 - 12 &= 0 \\ -2I_1 + 10I_2 &= -12 \end{aligned}$$

Solving Eqs (i) and (ii),





$$\begin{aligned} I_2 &= -0.67\text{ A} \\ I_N = I_2 &= -0.67\text{ A} \end{aligned}$$

Step II Calculation of R_N (Fig. 3.263)

$$R_N = (5 \parallel 2) + 8 = 9.43\ \Omega$$

Step III Calculation of I_L (Fig. 3.264)

$$I_L = 0.67 \times \frac{9.43}{9.43 + 10} = 0.33\text{ A} (\uparrow)$$

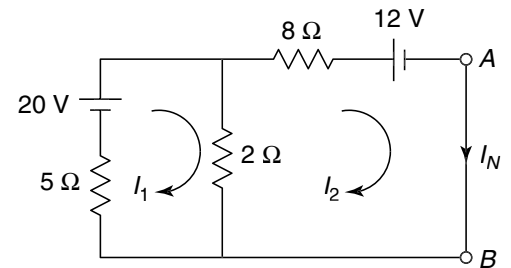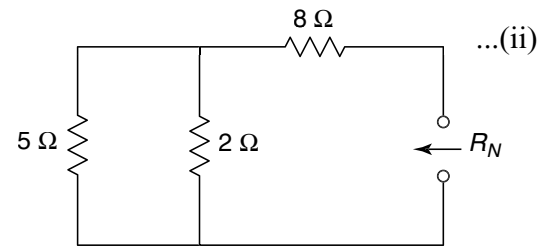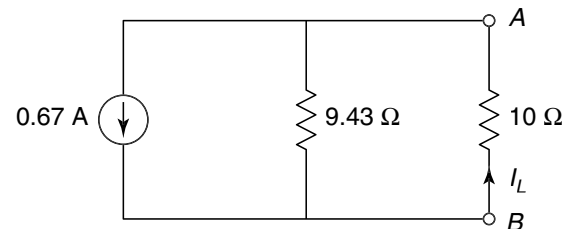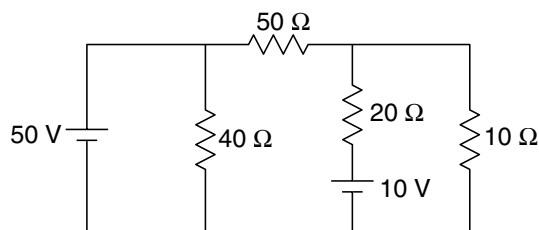**Fig. 3.262****Fig. 3.263****Fig. 3.264****Example 3.60**Find the current in the $10\ \Omega$ resistor in Fig. 3.265.**Fig. 3.265**

Solution

Step I Calculation of I_N (Fig. 3.266)

The resistance of $40\ \Omega$ becomes redundant as it is connected across the 50 V source (Fig. 3.267).

Applying KVL to Mesh 1,

$$\begin{aligned} 50 - 50I_1 - 20(I_1 - I_2) - 10 &= 0 \\ 70I_1 - 20I_2 &= 40 \end{aligned} \quad \dots(i)$$

Applying KVL to Mesh 2,

$$\begin{aligned} 10 - 20(I_2 - I_1) &= 0 \\ -20I_1 + 20I_2 &= 0 \end{aligned} \quad \dots(ii)$$

Solving Eqs (i) and (ii),

$$\begin{aligned} I_1 &= 1\text{ A} \\ I_2 &= 1.5\text{ A} \\ I_N &= I_2 = 1.5\text{ A} \end{aligned}$$

Step II Calculation of R_N (Fig. 3.268)

$$R_N = 50 \parallel 20 = 14.28\ \Omega$$

Step III Calculation of I_L (Fig. 3.269)

$$I_L = 1.5 \times \frac{14.28}{14.28 + 10} = 0.88\text{ A}$$

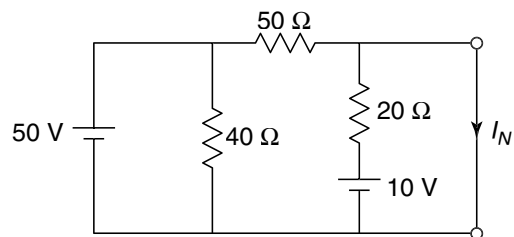


Fig. 3.266

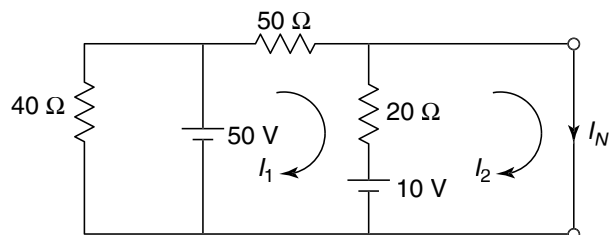


Fig. 3.267

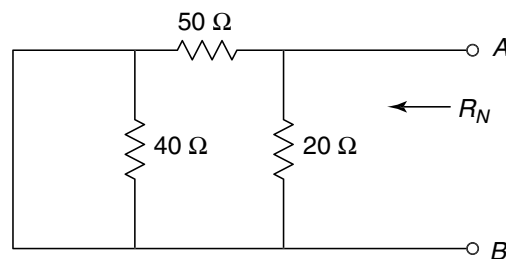


Fig. 3.268

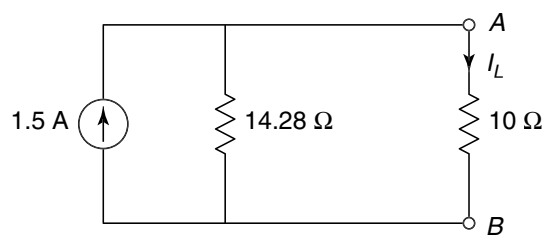


Fig. 3.269

Example 3.61

Find the current through the $10\ \Omega$ resistor in Fig. 3.270.

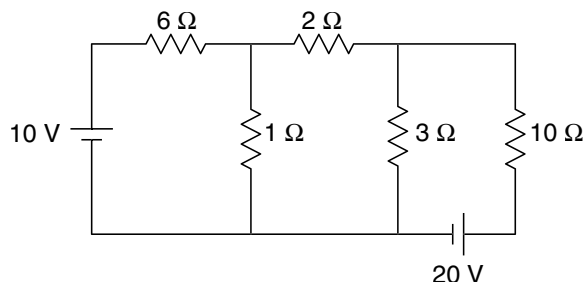


Fig. 3.270

Solution**Step I** Calculation of I_N (Fig. 3.271)

Applying KVL to Mesh 1,

$$10 - 6I_1 - 1(I_1 - I_2) = 0$$

$$7I_1 - I_2 = 10$$

...(i)

Applying KVL to Mesh 2,

$$-1(I_2 - I_1) - 2I_2 - 3(I_2 - I_3) = 0$$

$$-I_1 + 6I_2 - 3I_3 = 0$$

...(ii)

Applying KVL to Mesh 3,

$$-3(I_3 - I_2) - 20 = 0$$



$$3I_2 - 3I_3 = 20$$

...(iii)

Solving Eqs (i), (ii) and (iii),

$$I_3 = -13.17 \text{ A}$$



$$I_N = I_3 = -13.17 \text{ A}$$

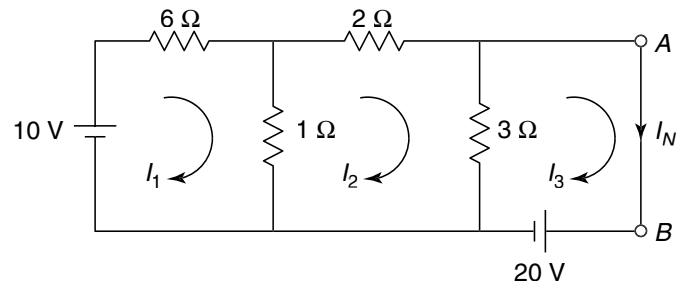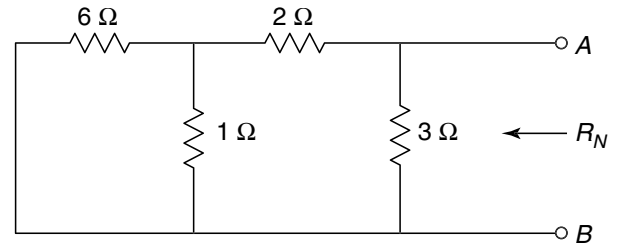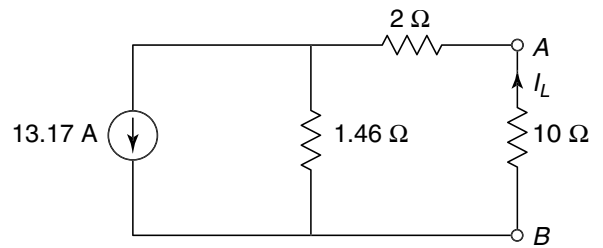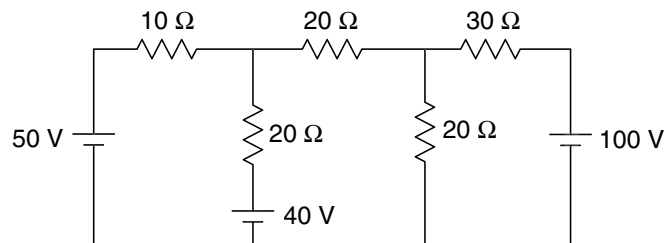**Fig. 3.271****Fig. 3.272****Step II** Calculation of R_N (Fig. 3.272)

$$R_N = [(6 \parallel 1) + 2] \parallel 3 = 1.46 \Omega$$

Step III Calculation of I_L (Fig. 3.273)

$$I_L = 13.17 \times \frac{1.46}{1.46 + 10} = 1.68 \text{ A} (\uparrow)$$

**Fig. 3.273****Example 3.62**Find the current through the 10Ω resistor in Fig. 3.274.**Fig. 3.274****Solution****Step I** Calculation of I_N (Fig. 3.274)

Applying KVL to Mesh 1,

$$50 - 20(I_1 - I_2) - 40 = 0$$


$$20I_1 - 20I_2 = 10$$

...(i)

Applying KVL to Mesh 2,

$$40 - 20(I_2 - I_1) - 20I_2 - 20(I_2 - I_3) = 0$$

$$-20I_1 + 60I_2 - 20I_3 = 40 \quad \dots(\text{ii})$$

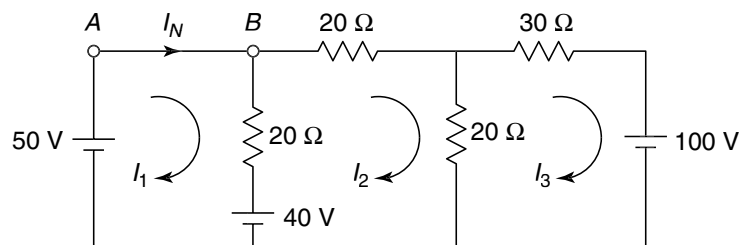**Fig. 3.275**

3.70 Network Analysis and Synthesis

Applying KVL to Mesh 3,

$$-20(I_3 - I_2) - 30I_3 - 100 = 0$$

$$-20I_2 + 50I_3 = -100$$

...(iii)

Solving Eqs (i), (ii) and (iii),

$$I_1 = 0.81 \text{ A}$$

$$I_N = I_1 = 0.81 \text{ A}$$

Step II Calculation of R_N (Fig. 3.276)

$$R_N = [(20 \parallel 30) + 20] \parallel 20 = 12.3 \Omega$$

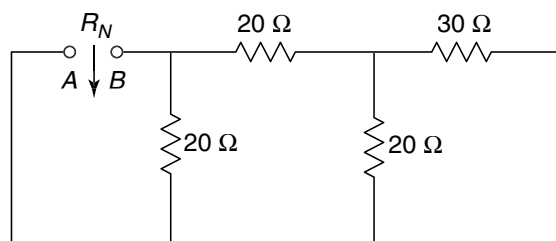


Fig. 3.276

Step III Calculation of I_L (Fig. 3.277)

$$I_L = 0.81 \times \frac{12.3}{12.3 + 10} = 0.45 \text{ A}$$

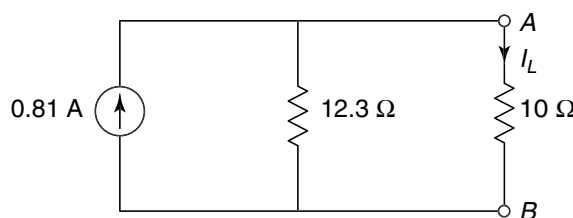


Fig. 3.277

Example 3.63

Obtain Norton's equivalent network as seen by R_L in Fig. 3.278.

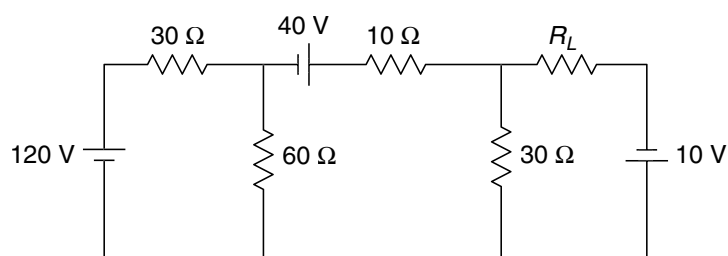


Fig. 3.278

Solution

Step I Calculation of I_N (Fig. 3.279)

Applying KVL to Mesh 1,

$$120 - 30I_1 - 60(I_1 - I_2) = 0$$

$$90I_1 - 60I_2 = 120 \quad \dots(i)$$

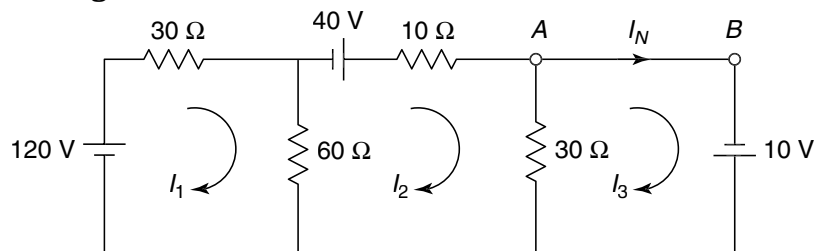


Fig. 3.279

Applying KVL to Mesh 2,

$$\begin{aligned} -60(I_2 - I_1) + 40 - 10I_2 - 30(I_2 - I_3) &= 0 \\ -60I_1 + 100I_2 - 30I_3 &= 40 \end{aligned} \quad \dots(\text{ii})$$

Applying KVL to Mesh 3,

$$\begin{aligned} -30(I_3 - I_2) + 10 &= 0 \\ 30I_2 - 30I_3 &= -10 \end{aligned} \quad \dots(\text{iii})$$

Solving Eqs (i), (ii) and (iii),

$$I_3 = 4.67 \text{ A}$$

$$I_N = I_3 = 4.67 \text{ A}$$

Step II Calculation of R_N (Fig. 3.280)

$$R_N = [(30 \parallel 60) + 10] \parallel 30 = 15 \Omega$$

Step III Norton's equivalent network (Fig. 3.281)

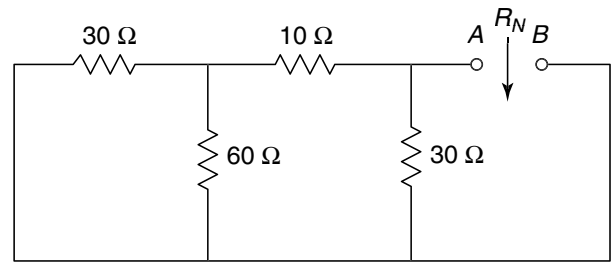


Fig. 3.280

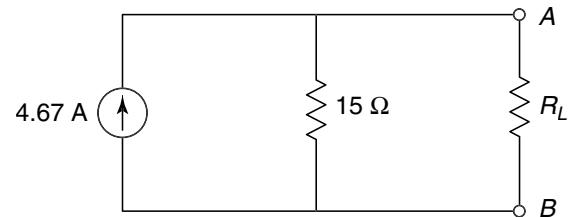


Fig. 3.281

Example 3.64

Find the current through the 8Ω resistor in Fig. 3.282.

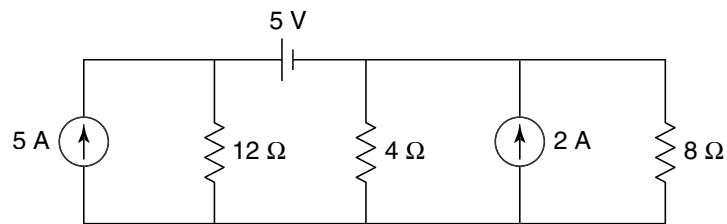


Fig. 3.282

Solution

Step I Calculation of I_N (Fig. 3.283)

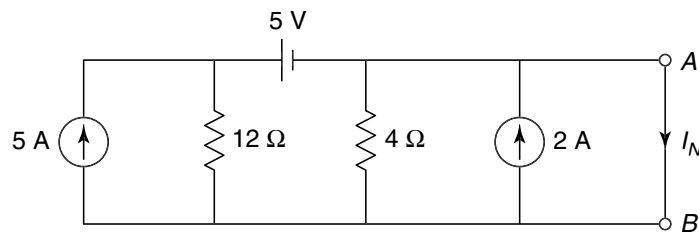


Fig. 3.283

The resistor of the 4Ω gets shorted as it is in parallel with the short circuit. Simplifying the network by source transformation (Fig. 3.284),

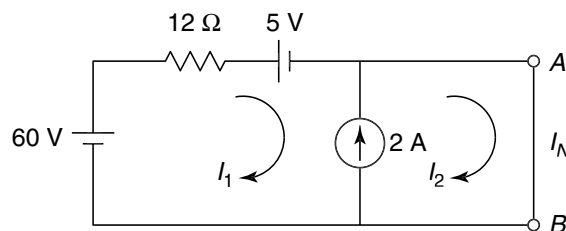


Fig. 3.284

3.72 Network Analysis and Synthesis

Meshes 1 and 2 will form a supermesh.

Writing the current equation for the supermesh,

$$I_2 - I_1 = 2$$

Applying KVL to the supermesh,

$$60 - 12I_1 - 5 = 0$$

$$12I_1 = 55$$

Solving Eqs (i) and (ii),

$$I_1 = 4.58 \text{ A}$$

$$I_2 = 6.58 \text{ A}$$

$$I_N = I_2 = 6.58 \text{ A}$$

Step II Calculation of R_N (Fig. 3.285)

$$R_N = 12 \parallel 4 = 3 \Omega$$

Step III Calculation of I_L (Fig. 3.286)

$$I_L = 6.58 \times \frac{3}{3+8} = 1.79 \text{ A}$$

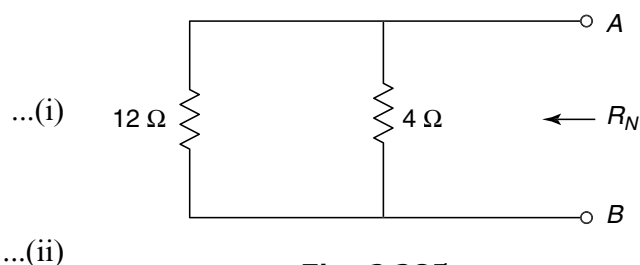


Fig. 3.285

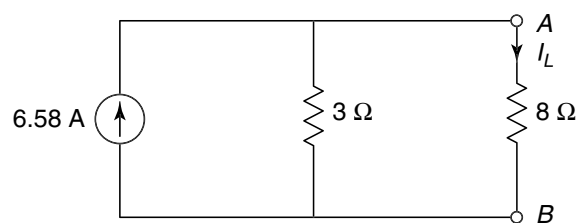


Fig. 3.286

Example 3.65

Find the current through the 1 Ω resistor in Fig. 3.287.

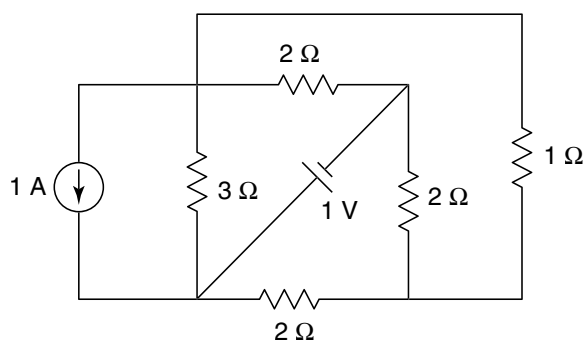


Fig. 3.287

Solution

Step I Calculation of I_N (Fig. 3.288)

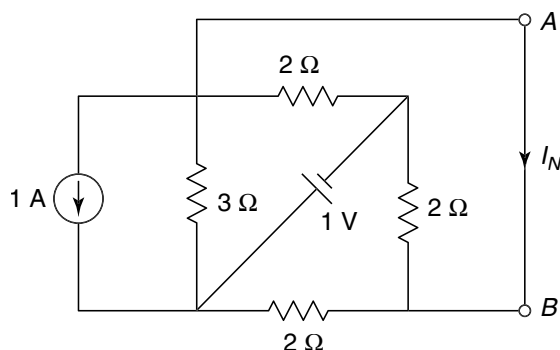


Fig. 3.288

By source transformation (Fig. 3.289),

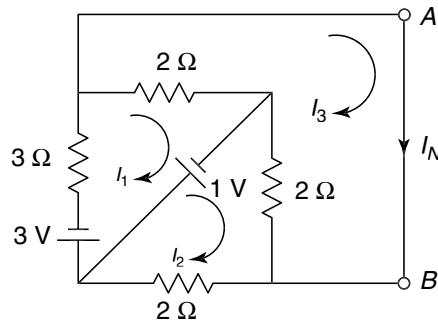


Fig. 3.289

Applying KVL to Mesh 1,

$$\begin{aligned} -3 - 3I_1 - 2(I_1 - I_3) + 1 &= 0 \\ 5I_1 - 2I_3 &= -2 \end{aligned} \quad \dots(i)$$

Applying KVL to Mesh 2,

$$\begin{aligned} -1 - 2(I_2 - I_3) - 2I_2 &= 0 \\ 4I_2 - 2I_3 &= -1 \end{aligned} \quad \dots(ii)$$

Applying KVL to Mesh 3,

$$\begin{aligned} -2(I_3 - I_1) - 2(I_3 - I_2) &= 0 \\ -2I_1 - 2I_2 + 4I_3 &= 0 \end{aligned} \quad \dots(iii)$$

Solving Eqs (i), (ii) and (iii),


$$\begin{aligned} I_1 &= -0.64 \text{ A} \\ I_2 &= -0.55 \text{ A} \\ I_3 &= -0.59 \text{ A} \\ I_N = I_3 &= -0.59 \text{ A} \end{aligned}$$

Step II Calculation of R_N (Fig. 3.290)


$$R_N = 2.2 \Omega$$

Step III Calculation of I_L (Fig. 3.291)

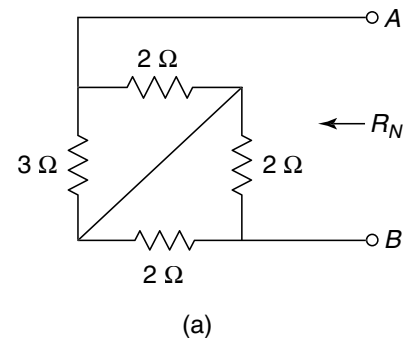
$$I_L = 0.59 \times \frac{2.2}{2.2 + 1} = 0.41 \text{ A}$$



(a)

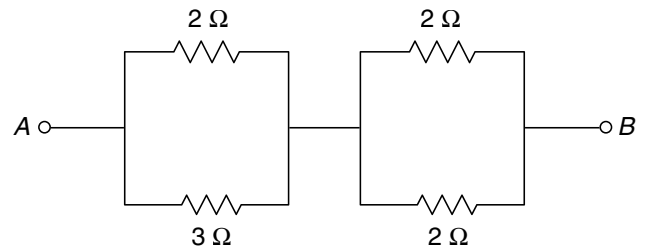

(b)

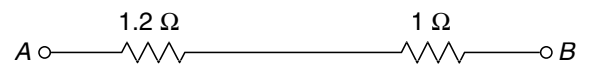

(c)

Fig. 3.290

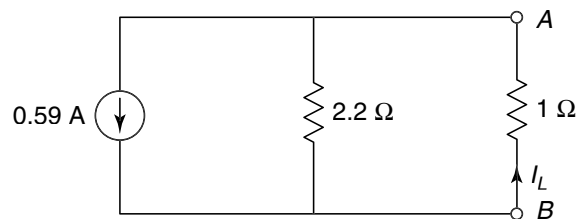
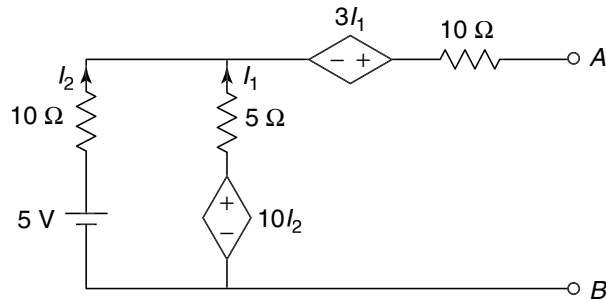


Fig. 3.291

EXAMPLES WITH DEPENDENT SOURCES

Example 3.66

Find Norton's equivalent network across terminals A and B of Fig. 3.292.

**Fig. 3.292****Solution****Step I** Calculation of V_{Th} (Fig. 3.293)

From Fig. 3.293,

$$I_2 = I_x$$

$$I_1 = -I_x$$

Applying KVL to the mesh,

$$5 - 10I_x - 5I_x - 10I_2 = 0$$

$$5 - 10I_x - 5I_x - 10I_x = 0$$

$$I_x = 0.2 \text{ A}$$


$$I_1 = -0.2 \text{ A}$$

Writing the V_{Th} equation,

$$5 - 10I_x + 3I_1 - V_{Th} = 0$$

$$5 - 10(0.2) + 3(-0.2) - V_{Th} = 0$$

$$V_{Th} = 2.4 \text{ V}$$

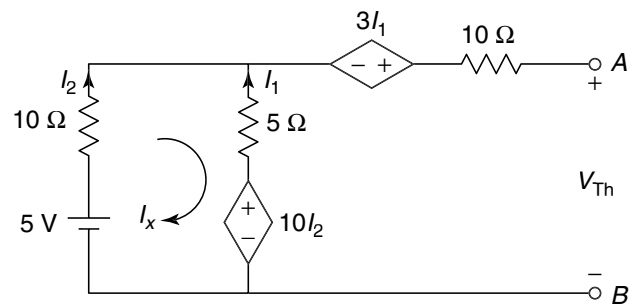**Fig. 3.293****Step II** Calculation of I_N (Fig. 3.294)

From Fig. 3.294,

$$I_2 = I_x \quad \dots(i)$$

$$I_1 = I_y - I_x \quad \dots(ii)$$

Applying KVL to Mesh 1,

$$5 - 10I_x - 5(I_x - I_y) - 10I_2 = 0$$

$$5 - 10I_x - 5I_x + 5I_y - 10I_x = 0$$


$$25I_x - 5I_y = 5 \quad \dots(iii)$$

Applying KVL to Mesh 2,

$$10I_2 - 5(I_y - I_x) + 3I_1 - 10I_y = 0$$

$$10I_x - 5I_y + 5I_x + 3(I_y - I_x) - 10I_y = 0$$

$$12I_x - 12I_y = 0 \quad \dots(iv)$$

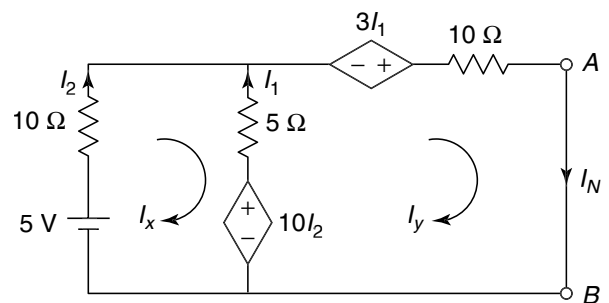**Fig. 3.294**

Solving Eqs (iii) and (iv),

$$I_x = 0.25 \text{ A}$$

$$I_y = 0.25 \text{ A}$$

$$I_N = I_y = 0.25 \text{ A}$$

Step III Calculation of R_N

$$R_N = \frac{V_{Th}}{I_N} = \frac{2.4}{0.25} = 9.6 \Omega$$

Step IV Norton's Equivalent Network (Fig. 3.295)

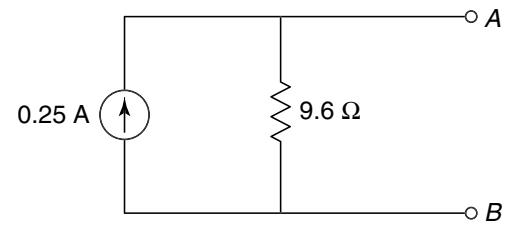


Fig. 3.295

Example 3.67

For the network shown in Fig. 3.296, find Norton's equivalent network.

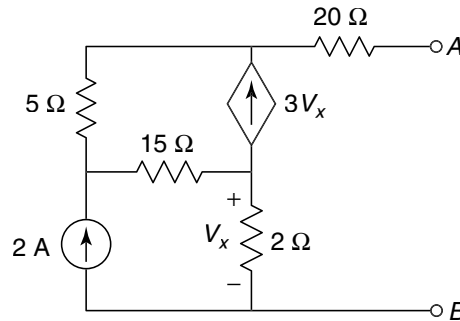


Fig. 3.296

Solution

Step I Calculation of V_{Th} (Fig. 3.297)

From Fig. 3.297,

$$V_x = 2I_2 \quad \dots(i)$$

For Mesh 1,

$$I_1 = -3V_x = -3(2I_2) = -6I_2 \quad \dots(ii)$$

For Mesh 2,

$$I_2 = 2 \quad \dots(iii)$$

$$I_1 = -6I_2 = -6(2) = -12 \text{ A}$$

Writing the V_{Th} equation,

$$V_{Th} - 0 + 5I_1 + 15(I_1 - I_2) - 2I_2 = 0$$

$$V_{Th} + 5(-12) + 15(-12 - 2) - 2(2) = 0$$

$$V_{Th} = 274 \text{ V}$$

Step II Calculation of I_N (Fig. 3.298)

From Fig. 3.298,

$$V_x = 2(I_2 - I_3) \quad \dots(i)$$

For Mesh 2,

$$I_2 = 2 \quad \dots(ii)$$

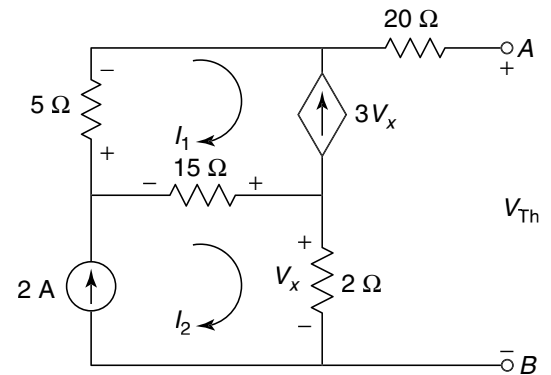


Fig. 3.297

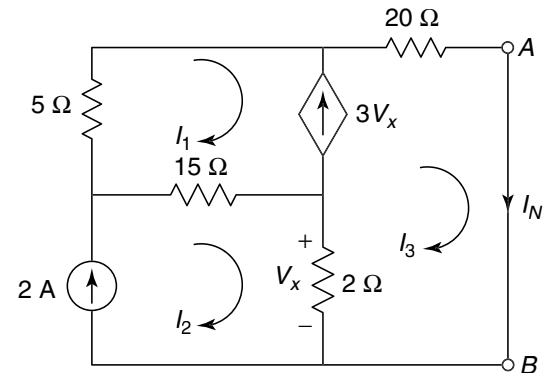


Fig. 3.298

3.76 Network Analysis and Synthesis

Meshes 1 and 3 will form a supermesh.

Writing the current equation for the supermesh,

$$I_3 - I_1 = 3V_x = 3[2(I_2 - I_3)] = 6I_2 - 6I_3$$

$$I_1 + 6I_2 - 7I_3 = 0$$

...(iii)

Applying KVL to the outer path of the supermesh,

$$-5I_1 - 20I_3 - 2(I_3 - I_2) - 15(I_1 - I_2) = 0$$

$$-20I_1 + 17I_2 - 22I_3 = 0$$

...(iv)

Solving Eqs (ii), (iii) and (iv),

$$I_1 = -0.16 \text{ A}$$

$$I_2 = 2 \text{ A}$$

$$I_3 = 1.69 \text{ A}$$

$$I_N = I_3 = 1.69 \text{ A}$$

Step III Calculation of R_N

$$R_N = \frac{V_{Th}}{I_N} = \frac{274}{1.69} = 162.13 \text{ } \Omega$$

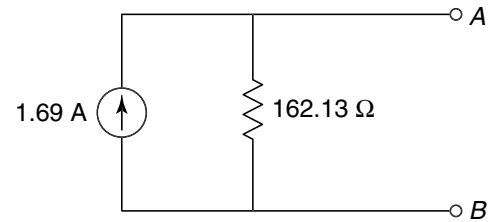


Fig. 3.299

Step IV Norton's Equivalent Network (Fig. 3.299)

Example 3.68

Obtain Norton's equivalent network across A-B in the network of Fig. 3.300.

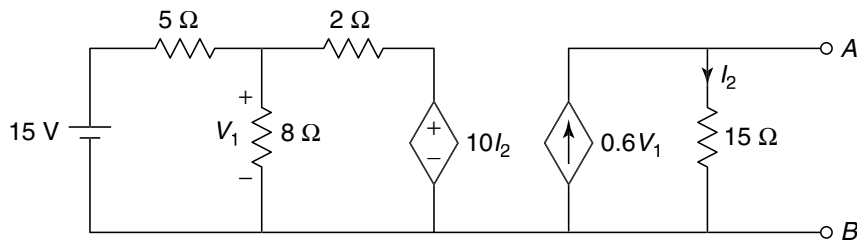


Fig. 3.300

Solution

Step I Calculation of V_{Th}
(Fig. 3.301)

From Fig. 3.301,

$$V_1 = 8(I_x - I_y) \quad \dots(i)$$

Applying KVL to Mesh 1,

$$15 - 5I_x - 8(I_x - I_y) = 0$$

$$13I_x - 8I_y = 15$$

...(ii)

Applying KVL to Mesh 2,

$$-8(I_y - I_x) - 2I_y - 10I_2 = 0$$

$$8I_x - 10I_y - 10I_2 = 0$$

...(iii)

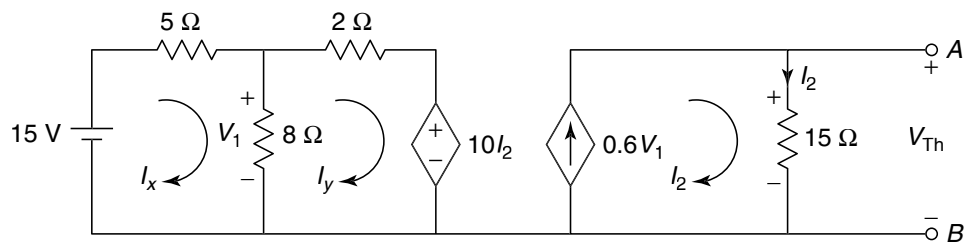


Fig. 3.301

For Mesh 3,

$$I_2 = 0.6V_1 = 0.6[8(I_x - I_y)]$$

$$4.8I_x - 4.8I_y - I_2 = 0 \quad \dots(\text{iv})$$

Solving Eqs (ii), (iii) and (iv),

$$I_x = 3.28 \text{ A}$$

$$I_y = 3.45 \text{ A}$$

$$I_2 = -0.83 \text{ A}$$

Writing the V_{Th} equation,

$$15I_2 - V_{\text{Th}} = 0$$

$$15(-0.83) - V_{\text{Th}} = 0$$

$$V_{\text{Th}} = -12.45 \text{ V}$$

Step II Calculation of I_N (Fig. 3.302)

From Fig. 3.302,

$$I_2 = 0$$

The dependent source of $10I_2$ depends on the controlling variable I_2 . When $I_2 = 0$, the dependent source vanishes, i.e. $10I_2 = 0$ as shown in Fig. 3.303.

From Fig. 3.303,

$$V_1 = 8(I_x - I_y) \quad \dots(\text{i})$$

Applying KVL to Mesh 1,

$$15 - 5I_x - 8(I_x - I_y) = 0$$

$$13I_x - 8I_y = 15 \quad \dots(\text{ii})$$

Applying KVL to Mesh 2,

$$-8(I_y - I_x) - 2I_y = 0$$

$$-8I_x + 10I_y = 0 \quad \dots(\text{iii})$$

Solving Eqs (ii) and (iii),

$$I_x = 2.27 \text{ A}$$

$$I_y = 1.82 \text{ A}$$

$$V_1 = 8(I_x - I_y) = 8(2.27 - 1.82) = 3.6 \text{ V}$$

For Mesh 3,

$$I_N = 0.6V_1 = 0.6(3.6) = 2.16 \text{ A}$$

Step III Calculation of R_N

$$R_N = \frac{V_{\text{Th}}}{I_N} = \frac{-12.45}{2.16} = -5.76 \Omega$$

Step IV Norton's Equivalent Network (Fig. 3.304)

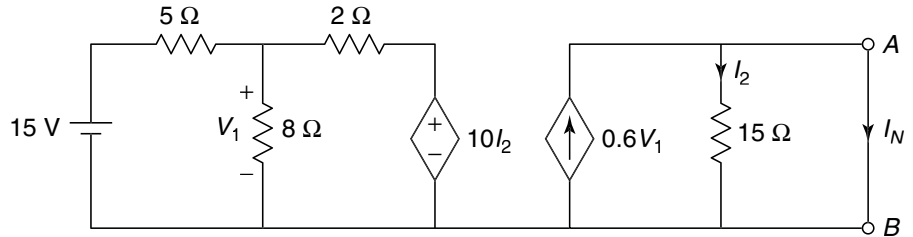


Fig. 3.302

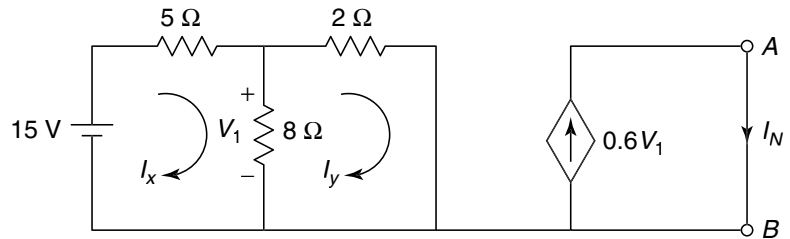


Fig. 3.303

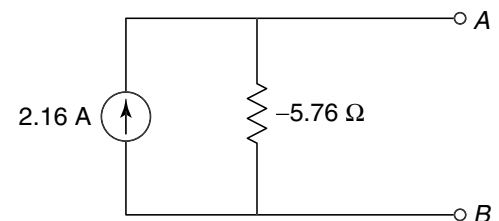
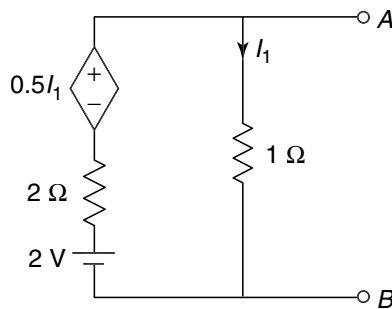


Fig. 3.304

Example 3.69

Find Norton's equivalent network of Fig. 3.305.

**Fig. 3.305****Solution****Step I** Calculation of V_{Th} (Fig. 3.306)

Applying KVL to the mesh,

$$2 - 2I_1 + 0.5I_1 - 1I_1 = 0$$

$$2 - 2.5I_1 = 0$$

$$I_1 = 0.8 \text{ A}$$

Writing the V_{Th} equation,

$$1I_1 - V_{Th} = 0$$

$$1(0.8) - V_{Th} = 0$$

$$V_{Th} = 0.8 \text{ V}$$

Step II Calculation of I_N (Fig. 3.307)When a short circuit is placed across the 1Ω resistor, it gets shorted.





$$I_1 = 0$$

The dependent source of $0.5I_1$ depends on the controlling variable I_1 . When $I_1 = 0$, the dependent source vanishes, i.e. $0.5 I_1 = 0$ as shown in Fig. 3.308.

$$I_N = \frac{2}{2} = 1 \text{ A}$$


Step III Calculation of R_N

$$R_N = \frac{V_{Th}}{I_N} = \frac{0.8}{1} = 0.8 \Omega$$

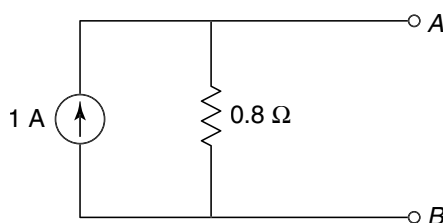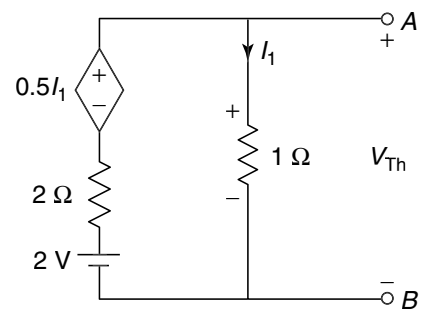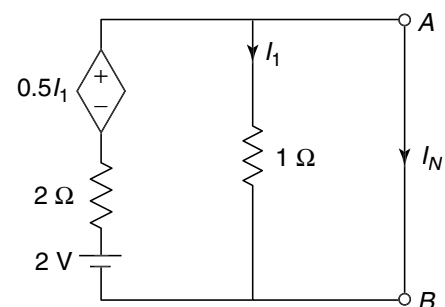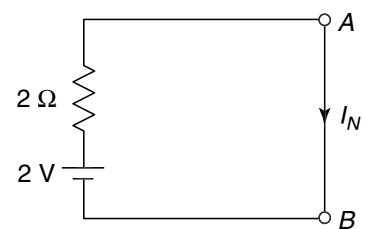Step IV Norton's Equivalent Network (Fig. 3.309)**Fig. 3.309****Fig. 3.306****Fig. 3.307****Fig. 3.308**

Example 3.70

Find Norton's equivalent network at the terminals A and B of Fig. 3.310.

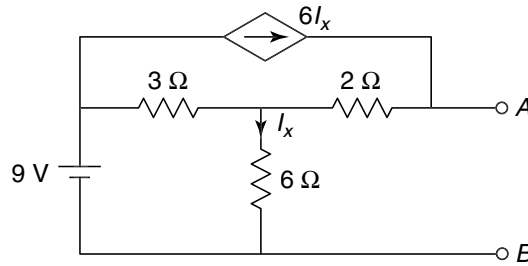**Fig. 3.310****Solution****Step I** Calculation of V_{Th} (Fig. 3.311)

From Fig. 3.311,

$$I_x = I_1 \quad \dots(i)$$

Applying KVL to Mesh 1,

$$9 - 3(I_1 - I_2) - 6I_1 = 0$$

$$9I_1 - 3I_2 = 9 \quad \dots(ii)$$

For Mesh 2,

$$I_2 = 6I_x = 6I_1$$

$$6I_1 - I_2 = 0 \quad \dots(iii)$$

Solving Eqs (ii) and (iii),

$$I_1 = -1 \text{ A}$$

$$I_2 = -6 \text{ A}$$

Writing the V_{Th} equation,

$$9 - 3(I_1 - I_2) + 2I_2 - V_{Th} = 0$$

$$9 - 3(-1 + 6) + 2(-6) - V_{Th} = 0$$

$$V_{Th} = -18 \text{ V}$$

Step II Calculation of I_N (Fig. 3.312)

From Fig. 3.312,

$$I_x = I_1 - I_3 \quad \dots(i)$$

Applying KVL to Mesh 1,

$$9 - 3(I_1 - I_2) - 6(I_1 - I_3) = 0$$

$$9I_1 - 3I_2 - 6I_3 = 9 \quad \dots(ii)$$

For Mesh 2,



$$I_2 = 6I_x = 6(I_1 - I_3)$$

$$6I_1 - I_2 - 6I_3 = 0 \quad \dots(iii)$$

Applying KVL to Mesh 3,

$$-6(I_3 - I_1) - 2(I_3 - I_2) = 0$$

$$-6I_1 - 2I_2 + 8I_3 = 0 \quad \dots(iv)$$

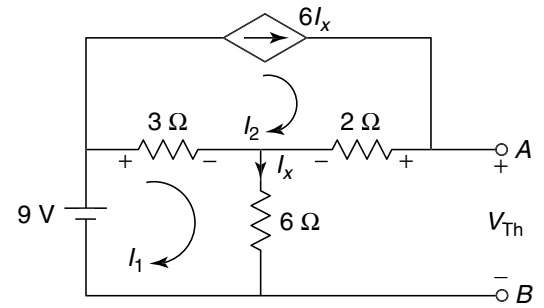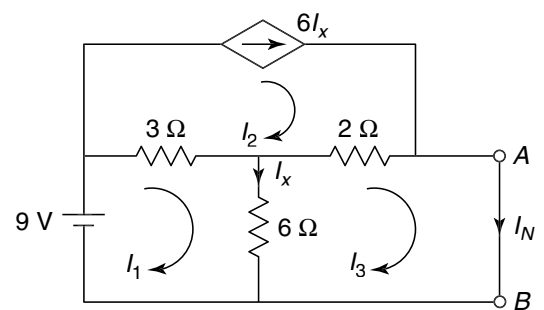**Fig. 3.311****Fig. 3.312**

Solving Eqs (ii), (iii) and (iv),

$$\begin{aligned} I_1 &= 5 \text{ A} \\ I_2 &= 3 \text{ A} \\ I_3 &= 4.5 \text{ A} \\ I_N &= I_3 = 4.5 \text{ A} \end{aligned}$$

Step III Calculation of R_N

$$R_N = \frac{V_{Th}}{I_N} = \frac{-18}{4.5} = -4 \Omega$$

Step IV Norton's Equivalent Network (Fig. 3.313)

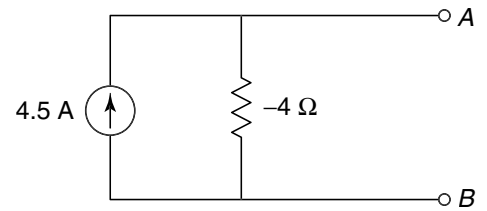


Fig. 3.313

Example 3.71

Find Norton's equivalent network to the left of terminal A-B in Fig. 3.314.

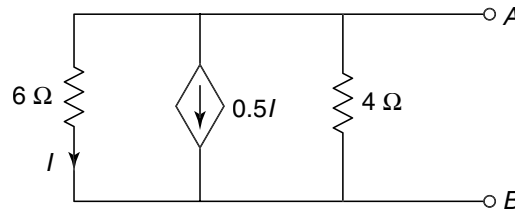


Fig. 3.314

Solution Since the network does not contain any independent source,

$$V_{Th} = 0$$

$$I_N = 0$$

But R_N can be calculated by applying a known current source of 1 A at the terminals A and B as shown in Fig. 3.315.

From Fig. 3.315,

$$I = \frac{V}{6}$$

Applying KCL at the node,

$$\frac{V}{6} + 0.5I + \frac{V}{4} = 1$$

$$\frac{V}{6} + 0.5\left(\frac{V}{6}\right) + \frac{V}{4} = 1$$

$$\left(\frac{1}{6} + \frac{0.5}{6} + \frac{1}{4}\right)V = 1$$

$$V = 2$$

$$R_N = \frac{V}{1} = \frac{2}{1} = 2 \Omega$$

Hence, Norton's equivalent network is shown in Fig. 3.316.

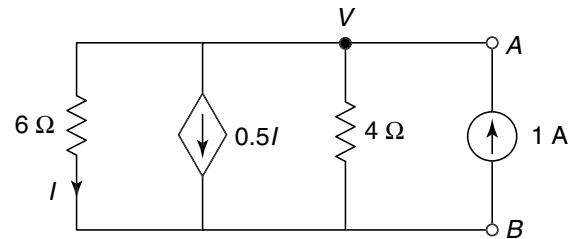


Fig. 3.315

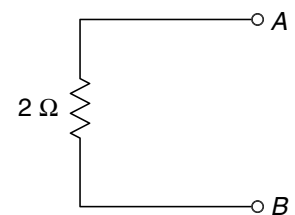
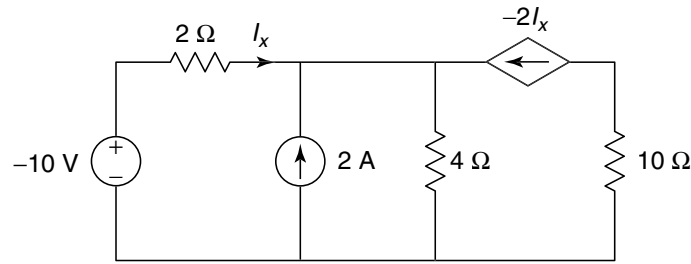


Fig. 3.316

Example 3.72Find the current through the $2\ \Omega$ resistor in the network shown in Fig. 3.317.**Fig. 3.317****Solution****Step I** Calculation of V_{Th} (Fig. 3.318)

From Fig. 3.318,

$$I_x = 0$$

The dependent source of $-2I_x$ depends on the controlling variable I_x . When $I_x = 0$, the dependent source vanishes, i.e. $-2I_x = 0$ as shown in Fig. 3.319.



$$I_1 = 2$$

Writing the V_{Th} equation,

$$-10 - V_{Th} - 4I_1 = 0$$

$$-10 - V_{Th} - 4(2) = 0$$

$$V_{Th} = -18\text{ V}$$

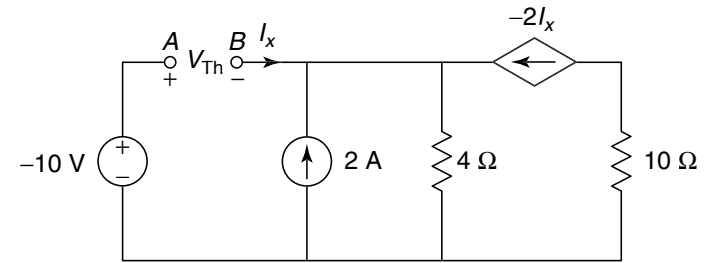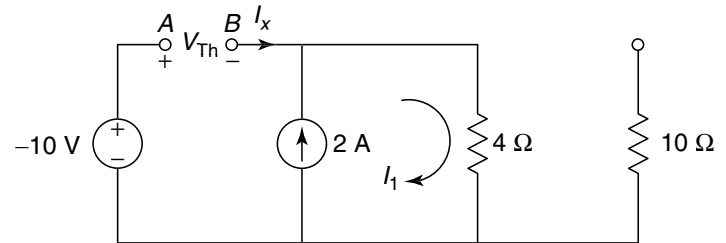**Fig. 3.318****Fig. 3.319****Step II** Calculation of I_N (Fig. 3.320)

From Fig. 3.320,

$$I_x = I_1 \quad \dots(i)$$

Mesh 1 and 2 will form a supermesh.

Writing the current equation for the supermesh,

$$I_2 - I_1 = 2 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,


$$-10 - 4(I_2 - I_3) = 0$$

$$-4I_2 + 4I_3 = 10 \quad \dots(iii)$$

For Mesh 3,

$$I_3 = -(-2I_x) = 2I_x = 2I_1$$

$$2I_1 - I_3 = 0 \quad \dots(iv)$$

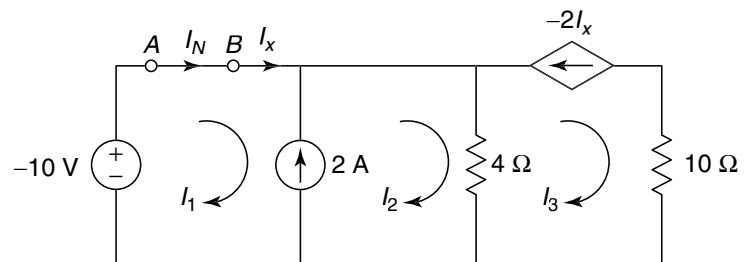**Fig. 3.320**

Solving Eqs (ii), (iii) and (iv),

$$\begin{aligned} I_1 &= 4.5 \text{ A} \\ I_2 &= 6.5 \text{ A} \\ I_3 &= 9 \text{ A} \\ I_N &= I_1 = 4.5 \text{ A} \end{aligned}$$

Step III Calculation of R_N

$$R_N = \frac{V_{Th}}{I_N} = \frac{-18}{4.5} = -4 \Omega$$

Step IV Calculation of I_L (Fig. 3.321)

$$I_L = 4.5 \times \frac{-4}{-4 + 2} = 9 \text{ A}$$

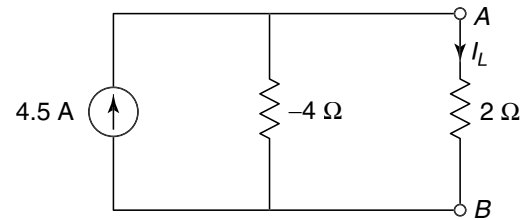


Fig. 3.321

Example 3.73

Find the current through the 2Ω resistor in the network of Fig. 3.322.

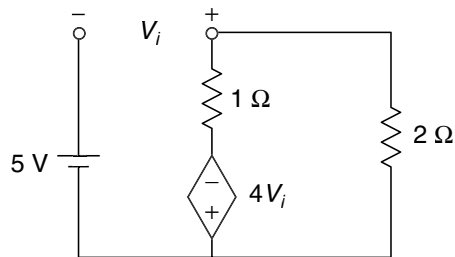


Fig. 3.322

Solution

Step I Calculation of V_{Th} (Fig. 3.323)

From Fig. 3.323,

$$\begin{aligned} 5 + V_i + 4V_i &= 0 \\ V_i &= -1 \text{ V} \end{aligned}$$

Writing the V_{Th} equation,

$$\begin{aligned} -4V_i - V_{Th} &= 0 \\ V_{Th} &= -4V_i = -4(-1) = 4 \text{ V} \end{aligned}$$

Step II Calculation of I_N (Fig. 3.324)

From Fig. 3.324,

$$\begin{aligned} 5 + V_i &= 0 \\ V_i &= -5 \text{ V} \end{aligned}$$

Applying KVL to the mesh,

$$\begin{aligned} -4V_i - 1I_N &= 0 \\ I_N &= -4V_i = -4(-5) = 20 \text{ A} \end{aligned}$$

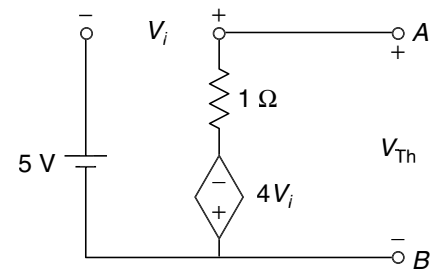


Fig. 3.323

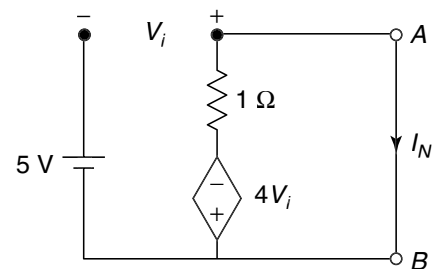


Fig. 3.324

Step III Calculation of R_N

$$R_N = \frac{V_{Th}}{I_N} = \frac{4}{20} = 0.2 \, \Omega$$

Step IV Calculation of I_L (Fig. 3.325)

$$I_L = 20 \times \frac{0.2}{0.2 + 2} = 1.82 \, \text{A}$$

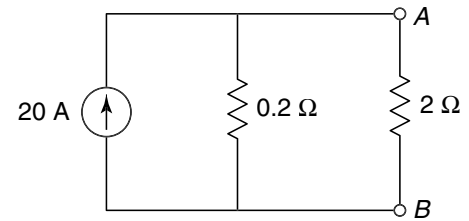


Fig. 3.325

Example 3.74

Find the current in the $2 \, \Omega$ resistor in the network of Fig. 3.326.

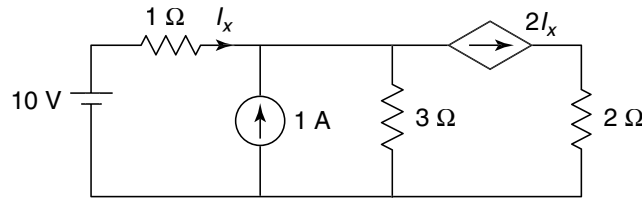


Fig. 3.326

Solution

Step I Calculation of V_{Th} (Fig. 3.327)

Meshes 1 and 2 will form a supermesh.

Writing current equation for the supermesh,

$$I_2 - I_1 = 1 \quad \dots(i)$$

Applying KVL to the outer path of the supermesh,

$$10 - 1I_1 - 3I_2 = 0$$

$$I_1 + 3I_2 = 10 \quad \dots(ii)$$

Solving Eqs (i) and (ii),

$$I_1 = 1.75 \, \text{A}$$

$$I_2 = 2.75 \, \text{A}$$

Writing the V_{Th} equation,

$$3I_2 - V_{Th} = 0$$

$$3(2.75) - V_{Th} = 0$$

$$V_{Th} = 8.25 \, \text{V}$$

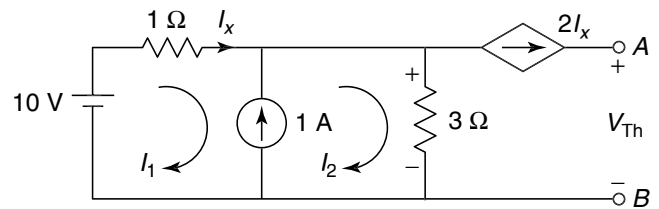


Fig. 3.327

Step II Calculation of I_N (Fig. 3.328)

From Fig. 3.328,

$$I_x = I_1 \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh.

Writing the current equation for the supermesh,

$$I_2 - I_1 = 1 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$10 - 1I_1 - 3(I_2 - I_3) = 0$$

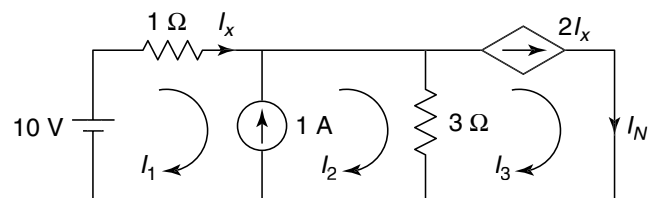


Fig. 3.328

$$I_1 + 3I_2 - 3I_3 = 10 \quad \dots(\text{iii})$$

For Mesh 3,

$$\begin{aligned} I_3 &= 2I_x = 2I_1 \\ 2I_1 - I_3 &= 0 \quad \dots(\text{iv}) \end{aligned}$$

Solving Eqs (ii), (iii) and (iv),

$$\begin{aligned} I_1 &= -3.5 \text{ A} \\ I_2 &= -2.5 \text{ A} \\ I_3 &= -7 \text{ A} \\ I_N &= I_3 = -7 \text{ A} \end{aligned}$$

Step III Calculation of R_N

$$R_N = \frac{V_{Th}}{I_N} = \frac{8.25}{-7} = -1.18 \Omega$$

Step IV Calculation of I_L (Fig. 3.329)

$$I_L = -7 \times \frac{-1.18}{-1.18 + 2} = 10.07 \text{ A}$$

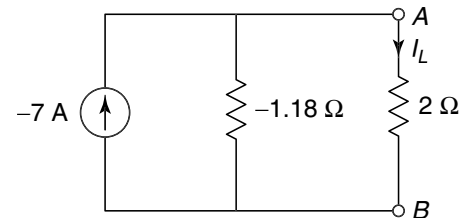


Fig. 3.329

Example 3.75

Find the current through the 10Ω resistor for the network of Fig. 3.330.

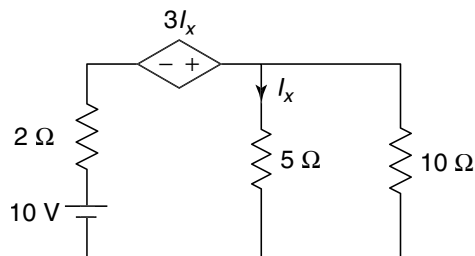


Fig. 3.330

Solution

Step I Calculation of V_{Th} (Fig. 3.331)

Applying KVL to the mesh,

$$\begin{aligned} 10 - 2I_x + 3I_x - 5I_x &= 0 \\ I_x &= 2.5 \text{ A} \end{aligned}$$

Writing the V_{Th} equation,

$$\begin{aligned} 5I_x - V_{Th} &= 0 \\ 5(2.5) - V_{Th} &= 0 \\ V_{Th} &= 12.5 \text{ V} \end{aligned}$$

Step II Calculation of I_N (Fig. 3.332)

From Fig. 3.332,

$$I_x = 0$$

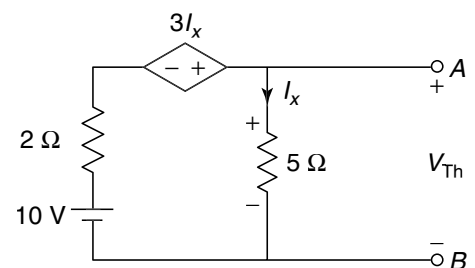


Fig. 3.331

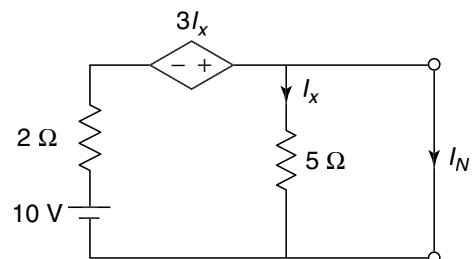


Fig. 3.332

The dependent source of $3 I_x$ depends on the controlling variable I_x . When $I_x = 0$, the dependent source $3 I_x$ vanishes, i.e. $3 I_x = 0$ as shown in Fig. 3.333.

$$I_N = \frac{10}{2} = 5 \text{ A}$$

Step III Calculation of R_N

$$R_N = \frac{V_{Th}}{I_N} = \frac{12.5}{5} = 2.5 \Omega$$

Step IV Calculation of I_L (Fig. 3.334)

$$I_L = 5 \times \frac{2.5}{2.5 + 10} = 1 \text{ A}$$

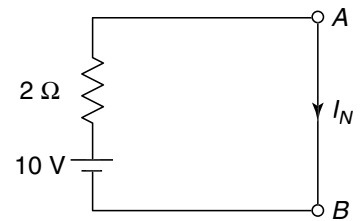


Fig. 3.333

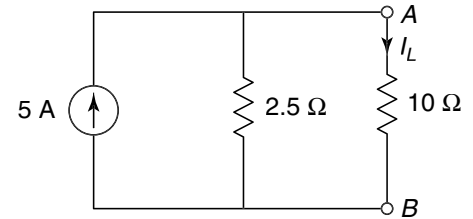


Fig. 3.334

Example 3.76

Find the current through the 5Ω resistor in the network of Fig. 3.335.

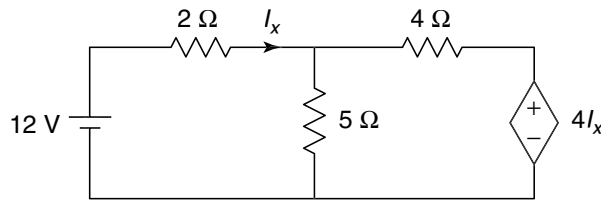


Fig. 3.335

Solution

Step I Calculation of V_{Th} (Fig. 3.336)

Applying KVL to the mesh,

$$\begin{aligned} 12 - 2I_x - 4I_x - 4I_x &= 0 \\ 12 - 10I_x &= 0 \\ I_x &= 1.2 \text{ A} \end{aligned}$$

Writing the V_{Th} equation,

$$\begin{aligned} 12 - 2I_x - V_{Th} &= 0 \\ 12 - 2(1.2) - V_{Th} &= 0 \\ V_{Th} &= 9.6 \text{ V} \end{aligned}$$

Step II Calculation of I_N (Fig. 3.337)

From Fig. 3.337,

$$I_x = I_1 \quad \dots(i)$$

Applying KVL to Mesh 1,

$$\begin{aligned} 12 - 2I_1 &= 0 \\ I_1 &= 6 \text{ A} \quad \dots(ii) \end{aligned}$$

Applying KVL to Mesh 2,

$$\begin{aligned} -4I_2 - 4I_x &= 0 \\ -4I_2 - 4I_1 &= 0 \quad \dots(iii) \end{aligned}$$

Solving Eqs (ii) and (iii),

$$\begin{aligned} I_2 &= -6 \text{ A} \\ I_N = I_1 - I_2 &= 6 - (-6) = 12 \text{ A} \end{aligned}$$

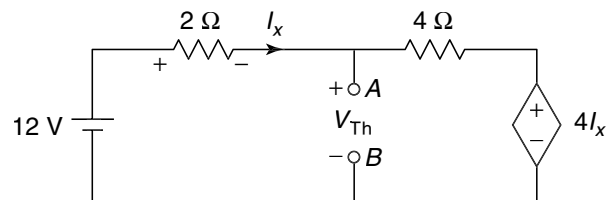


Fig. 3.336

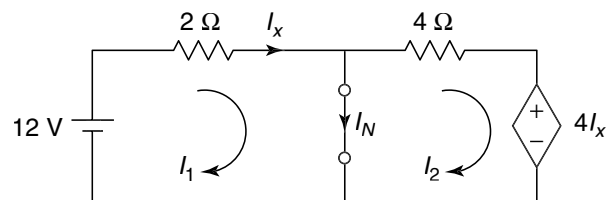


Fig. 3.337

Step III Calculation of R_N

$$R_N = \frac{V_{Th}}{I_N} = \frac{9.6}{12} = 0.8 \Omega$$

Step IV Calculation of I_L (Fig. 3.338)

$$I_L = 12 \times \frac{0.8}{0.8 + 5} = 1.66 \text{ A}$$

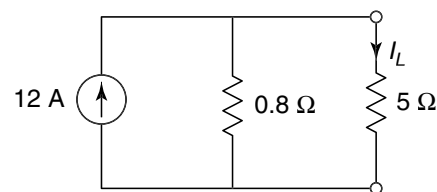


Fig. 3.338

Example 3.77

Find the current through the 10Ω resistor for the network of Fig. 3.339.

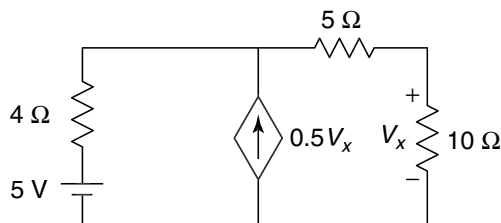


Fig. 3.339

Solution

Step I Calculation of V_{Th} (Fig. 3.340)

For the mesh,

$$I = -0.5V_x = -0.5V_{Th}$$

Writing the V_{Th} equation,

$$5 - 4I - 0 - V_{Th} = 0$$

$$5 - 4(-0.5V_{Th}) - V_{Th} = 0$$

$$V_{Th} = -5 \text{ V}$$

Step II Calculation of I_N (Fig. 3.341)

From Fig. 3.341,

$$V_x = 0$$

The dependent source of $0.5V_x$ depends on the controlling variable V_x . When $V_x = 0$, the dependent source vanishes, i.e. $0.5V_x = 0$ as shown in Fig. 3.342.

$$I_N = \frac{5}{4 + 5} = \frac{5}{9} \text{ A}$$

Step III Calculation of R_N

$$R_N = \frac{V_{Th}}{I_N} = \frac{-5}{\frac{5}{9}} = -9 \Omega$$

Step IV Calculation of I_L (Fig. 3.343)

$$I_L = \frac{5}{9} \times \frac{-9}{-9 + 10} = -5 \text{ A}$$

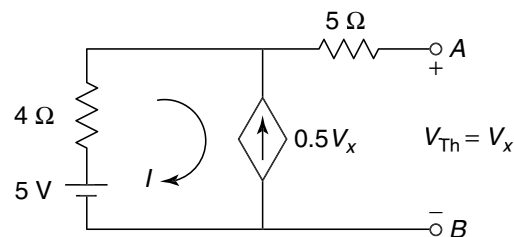


Fig. 3.340

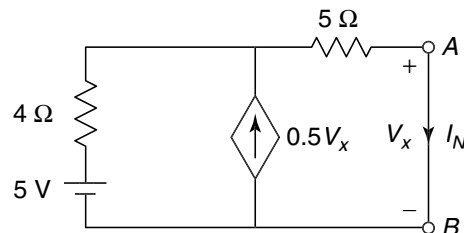


Fig. 3.341

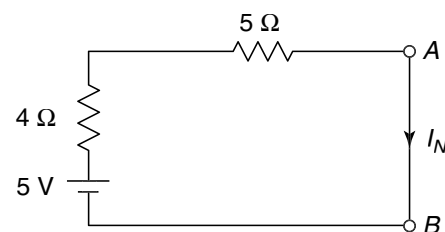


Fig. 3.342

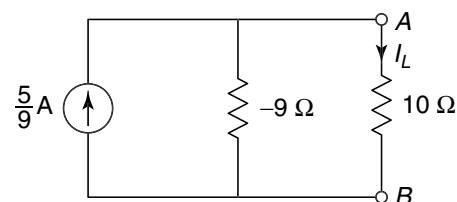
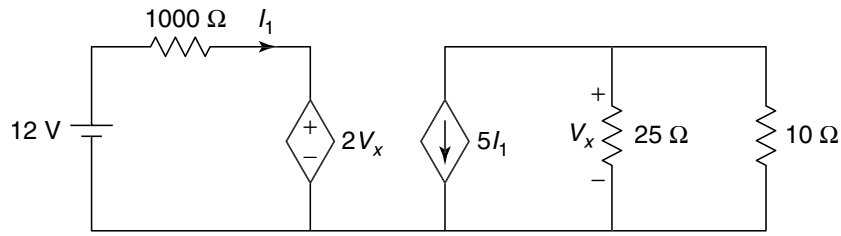


Fig. 3.343

Example 3.78Find the current through the $10\ \Omega$ resistor in the network shown in Fig. 3.344.**Fig. 3.344****Solution****Step I** Calculation of V_{Th} (Fig. 3.345)

From Fig. 3.345,

$$V_x = -25(5I_1) = -125I_1 \quad \dots(i)$$

Applying KVL to Mesh 1,

$$12 - 1000I_1 - 2V_x = 0$$

$$12 - 1000I_1 - 2(-125I_1) = 0 \quad \dots(ii)$$

$$I_1 = 0.016\text{ A}$$

$$V_x = -125I_1 = -125(0.016) = -2\text{ V}$$

Writing the V_{Th} equation,

$$V_{Th} = V_x = -2\text{ V}$$

Step II Calculation of I_N (Fig. 3.346)

From Fig. 3.346,

$$V_x = 0$$

The dependent source of $2V_x$ depends on the controlling variable V_x . When $V_x = 0$, the dependent source vanishes, i.e. $2V_x = 0$ as shown in Fig. 3.347.

$$I_1 = \frac{12}{1000} = 0.012\text{ A}$$





$$I_N = -5I_1 = -5(0.012) = -0.06\text{ A}$$


Step III Calculation of R_N

$$R_N = \frac{V_{Th}}{I_N} = \frac{-2}{-0.06} = 33.33\ \Omega$$

Step IV Calculation of I_L (Fig. 3.348)

$$I_L = -0.06 \times \frac{33.33}{33.33 + 10} = -0.046\text{ A}$$

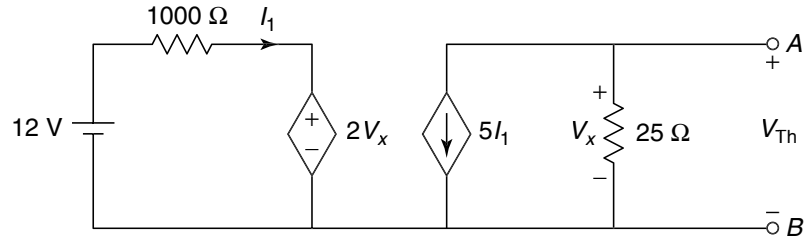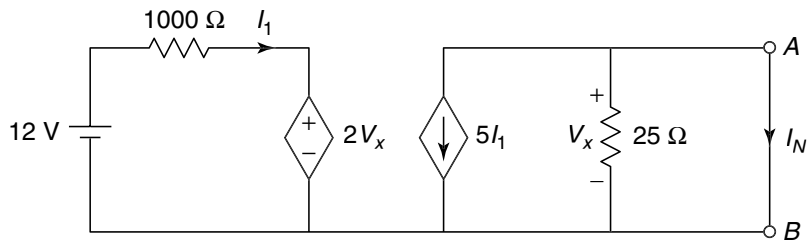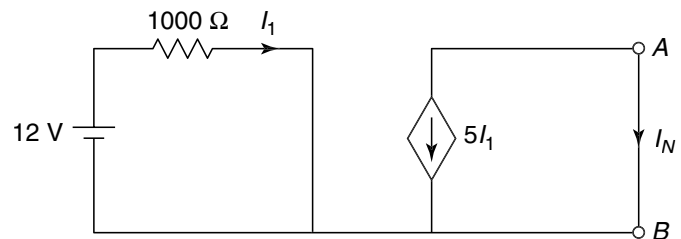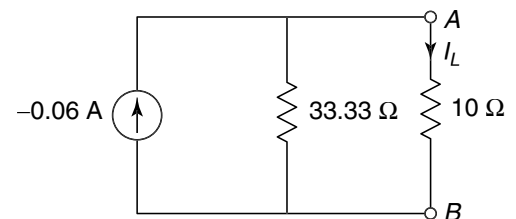**Fig. 3.345****Fig. 3.346****Fig. 3.347****Fig. 3.348**

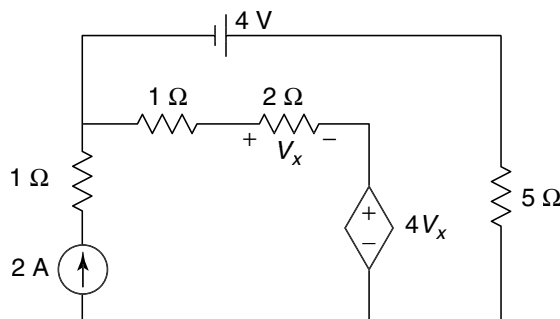Example 3.79Find the current through the $5\ \Omega$ resistor for the network of Fig. 3.349.**Fig. 3.349****Solution****Step I** Calculation of V_{Th} (Fig. 3.350)

From Fig. 3.350,

$$V_x = 2I$$

For the mesh,

$$I = 2$$

$$V_x = 2(2) = 4\text{ V}$$

Writing the V_{Th} equation,

$$4V_x + 2I + 1I + 4 - V_{Th} = 0$$

$$4(4) + 2(2) + 2 + 4 - V_{Th} = 0$$

$$V_{Th} = 26\text{ V}$$

Step II Calculation of I_N (Fig. 3.351)

From Fig. 3.351,

$$V_x = 2(I_1 - I_2) \quad \dots(i)$$

For Mesh 1,

$$I_1 = 2 \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$4V_x - 2(I_2 - I_1) - 1(I_2 - I_1) + 4 = 0$$

$$4[2(I_1 - I_2)] - 2I_2 + 2I_1 - I_2 + I_1 + 4 = 0$$

$$11I_1 - 11I_2 = -4 \quad \dots(iii)$$

Solving Eqs (ii) and (iii),

$$I_1 = 2\text{ A}$$

$$I_2 = 2.36\text{ A}$$




$$I_N = I_2 = 2.36\text{ A}$$


Step III Calculation of R_N

$$R_N = \frac{V_{Th}}{I_N} = \frac{26}{2.36} = 11.02\ \Omega$$

Step IV Calculation of I_L (Fig. 3.352)

$$I_L = 2.36 \times \frac{11.02}{11.02 + 5} = 1.62\text{ A}$$

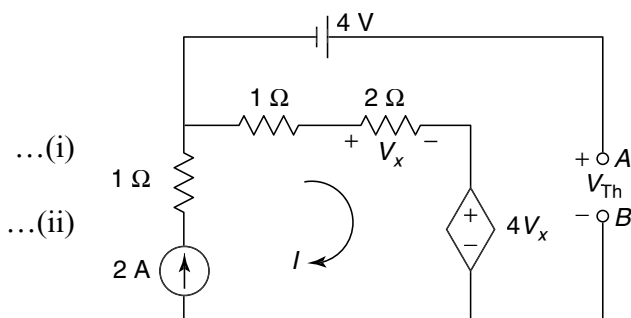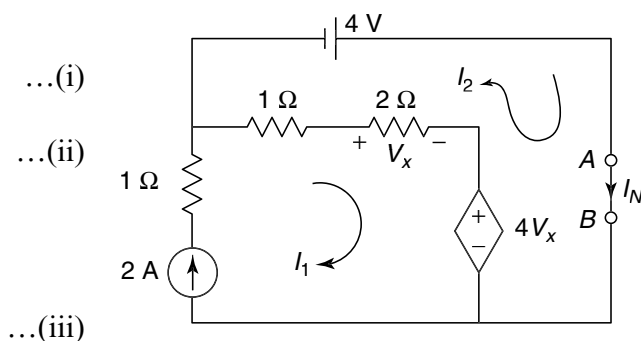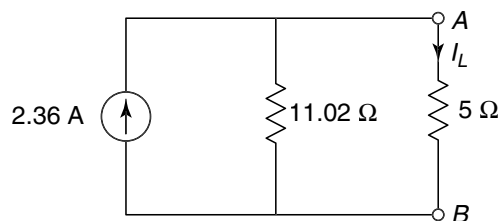**Fig. 3.350****Fig. 3.351****Fig. 3.352**

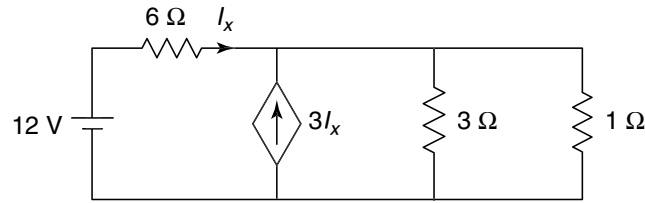Example 3.80Find the current through the $1\ \Omega$ resistor in the network of Fig. 3.353.**Fig. 3.353****Solution****Step I** Calculation of V_{Th} (Fig. 3.354)

From Fig. 3.354,

$$I_x = I_1 \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh.

Writing the current equation for the supermesh,

$$I_2 - I_1 = 3I_x = 3I_1$$

$$4I_1 - I_2 = 0 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$12 - 6I_1 - 3I_2 = 0$$

$$6I_1 + 3I_2 = 12 \quad \dots(iii)$$

Solving Eqs (ii) and (iii),

$$I_1 = 0.67\text{ A}$$

$$I_2 = 2.67\text{ A}$$

Writing the V_{Th} equation,

$$3I_2 - V_{Th} = 0$$

$$3(2.67) - V_{Th} = 0$$

$$V_{Th} = 8\text{ V}$$

Step II Calculation of I_N (Fig. 3.355)When a short circuit is placed across a $3\ \Omega$ resistor, it gets shorted as shown in Fig. 3.356.

From Fig. 3.356,

$$I_x = I_1 \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh.

Writing the current equation for the supermesh,




$$I_2 - I_1 = 3I_x = 3I_1$$

$$4I_1 - I_2 = 0 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$12 - 6I_1 = 0$$

$$I_1 = 2 \quad \dots(iii)$$

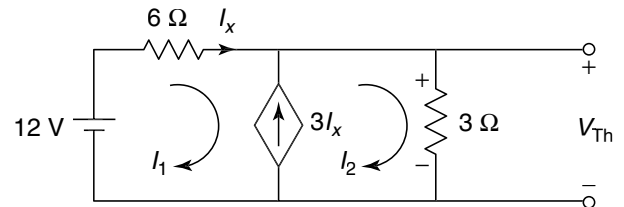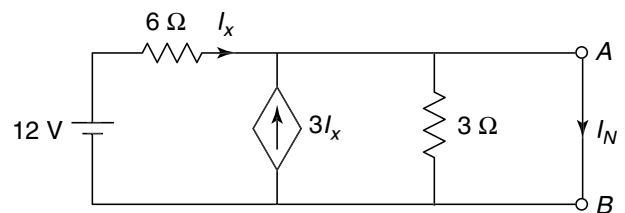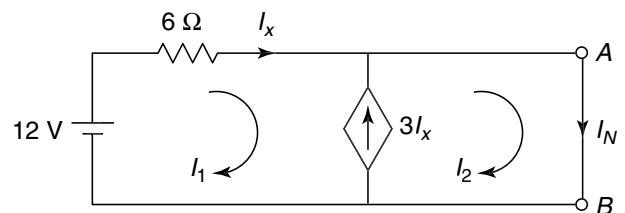**Fig. 3.354****Fig. 3.355****Fig. 3.356**

3.90 Network Analysis and Synthesis

Solving Eqs (ii) and (iii),

$$I_1 = 2 \text{ A}$$

$$I_2 = 8 \text{ A}$$

$$I_N = I_2 = 8 \text{ A}$$

Step III Calculation of R_N

$$R_N = \frac{V_{Th}}{I_N} = \frac{8}{8} = 1 \Omega$$

Step IV Calculation of I_L (Fig. 3.357)

$$I_L = 8 \times \frac{1}{1+1} = 4 \text{ A}$$

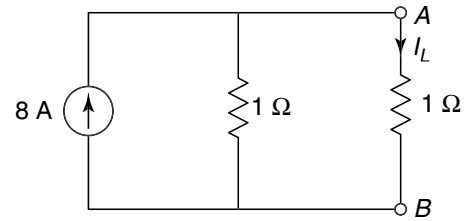


Fig. 3.357

Example 3.81

Find the current through the 1.6Ω resistor in the network of Fig. 3.358.

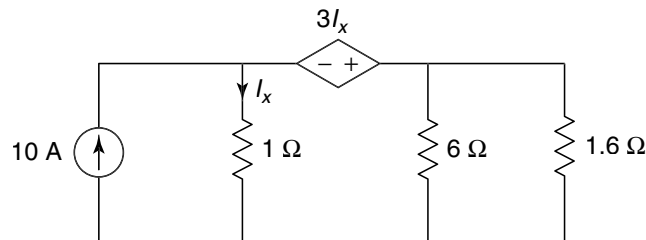


Fig. 3.358

Solution

Step I Calculation of V_{Th} (Fig. 3.359)

From Fig. 3.359,

$$I_x = I_1 - I_2 \dots(i)$$

For Mesh 1,

$$I_1 = 10 \dots(ii)$$

Applying KVL to Mesh 2,

$$-1(I_2 - I_1) + 3I_x - 6I_2 = 0$$

$$-I_2 + I_1 + 3(I_1 - I_2) - 6I_2 = 0$$

$$4I_1 - 10I_2 = 0$$

...(iii)

Solving Eqs (ii) and (iii),

$$I_1 = 10 \text{ A}$$

$$I_2 = 4 \text{ A}$$

Writing the V_{Th} equation,

$$6I_2 - V_{Th} = 0$$

$$6(4) - V_{Th} = 0$$

$$V_{Th} = 24 \text{ V}$$

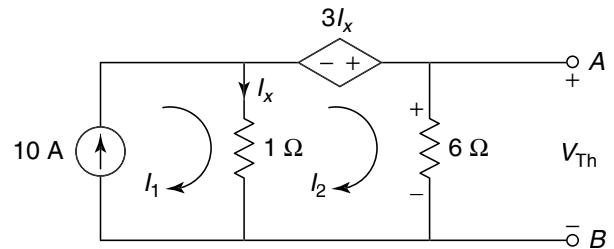


Fig. 3.359

Step II Calculation of I_N (Fig. 3.360)

When a short circuit is placed across the $3\ \Omega$ resistor, it gets shorted as shown in Fig. 3.361.

From Fig. 3.361,

$$I_x = I_1 - I_2 \quad \dots(i)$$

For Mesh 1,

$$I_1 = 10 \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$-1(I_2 - I_1) + 3I_x = 0$$

$$-I_2 + I_1 + 3(I_1 - I_2) = 0$$

$$4I_1 - 4I_2 = 0 \quad \dots(iii)$$

Solving Eqs (ii) and (iii),

$$I_1 = 10\text{ A}$$

$$I_2 = 10\text{ A}$$

$$I_N = I_2 = 10\text{ A}$$

Step III Calculation of R_N

$$R_N = \frac{V_{Th}}{I_N} = \frac{24}{10} = 2.4\ \Omega$$

Step IV Calculation of I_L (Fig. 3.362)

$$I_L = 10 \times \frac{2.4}{2.4 + 1.6} = 6\text{ A}$$

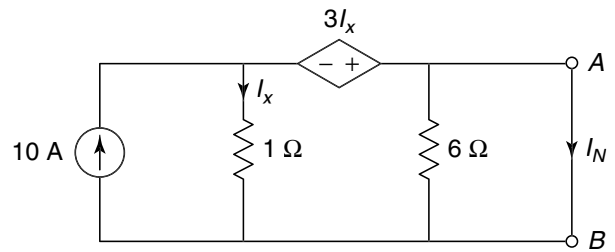


Fig. 3.360

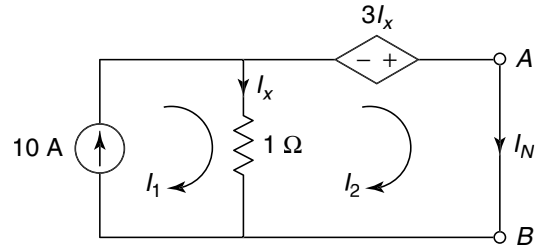


Fig. 3.361

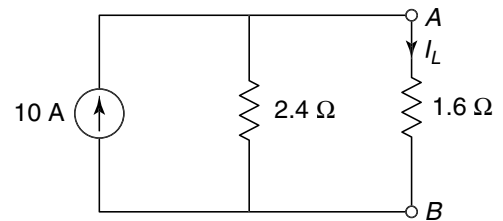


Fig. 3.362

3.5 MAXIMUM POWER TRANSFER THEOREM

It states that ‘the maximum power is delivered from a source to a load when the load resistance is equal to the source resistance.’

Proof From Fig. 3.363,

$$I = \frac{V}{R_s + R_L}$$

$$\text{Power delivered to the load } R_L = P = I^2 R_L = \frac{V^2 R_L}{(R_s + R_L)^2}$$

To determine the value of R_L for maximum power to be transferred to the load,

$$\begin{aligned} \frac{dP}{dR_L} &= 0 \\ \frac{dP}{dR_L} &= \frac{d}{dR_L} \frac{V^2}{(R_s + R_L)^2} R_L \\ &= \frac{V^2 [(R_s + R_L)^2 - (2R_L)(R_s + R_L)]}{(R_s + R_L)^4} \end{aligned}$$

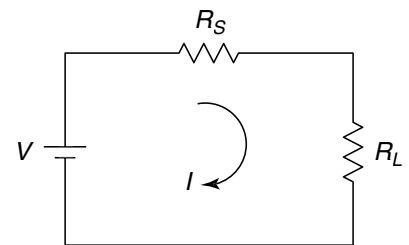


Fig. 3.363 Network illustrating maximum power transfer theorem

$$(R_s + R_L)^2 - 2 R_L (R_s + R_L) = 0$$

$$R_s^2 + R_L^2 + 2 R_s R_L - 2 R_L R_s - 2 R_L^2 = 0$$

$$R_s = R_L$$

Hence, the maximum power will be transferred to the load when load resistance is equal to the source resistance.

Steps to be followed in Maximum Power Transfer Theorem

1. Remove the variable load resistor R_L .
2. Find the open circuit voltage V_{Th} across points A and B .
3. Find the resistance R_{Th} as seen from points A and B .
4. Find the resistance R_L for maximum power transfer.

$$R_L = R_{Th}$$

5. Find the maximum power (Fig. 3.364).

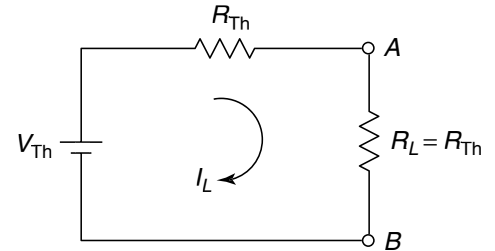


Fig. 3.364 Thevenin's equivalent network

$$I_L = \frac{V_{Th}}{R_{Th} + R_L} = \frac{V_{Th}}{2R_{Th}}$$

$$P_{max} = I_L^2 R_L = \frac{V_{Th}^2}{4R_{Th}^2} \times R_{Th} = \frac{V_{Th}^2}{4R_{Th}}$$

Example 3.82 Find the value of resistance R_L in Fig. 3.365 for maximum power transfer and calculate maximum power.

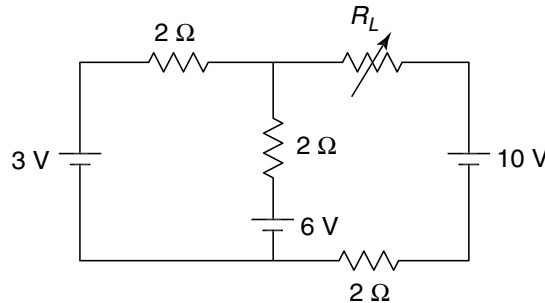


Fig. 3.365

Solution

Step I Calculation of V_{Th} (Fig. 3.366)

Applying KVL to the mesh,

$$3 - 2I - 2I - 6 = 0$$

$$I = -0.75 \text{ A}$$

Writing the V_{Th} equation,

$$6 + 2I - V_{Th} - 10 = 0$$

$$V_{Th} = 6 + 2I - 10 = 6 + 2(-0.75) - 10 = -5.5 \text{ V}$$

$$= 5.5 \text{ V (terminal B is positive w.r.t A)}$$

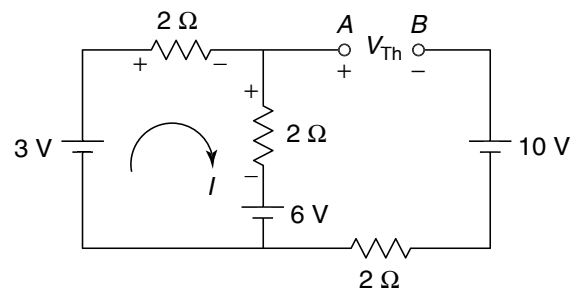


Fig. 3.366

Step II Calculation of R_{Th} (Fig. 3.367)

$$R_{Th} = (2 \parallel 2) + 2 = 3 \Omega$$

Step III Calculation of R_L
For maximum power transfer,

$$R_L = R_{Th} = 3 \Omega$$

Step IV Calculation of P_{max} (Fig. 3.368)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(5.5)^2}{4 \times 3} = 2.52 \text{ W}$$

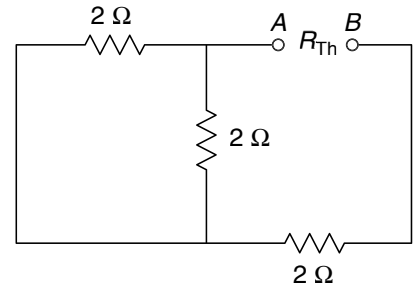


Fig. 3.367

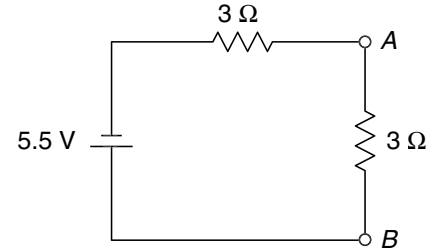


Fig. 3.368

Example 3.83 Find the value of resistance R_L in Fig. 3.369 for maximum power transfer and calculate maximum power.

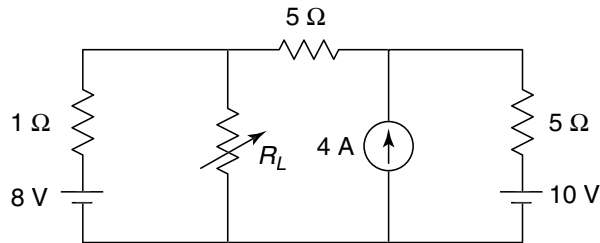


Fig. 3.369

Solution

Step I Calculation of V_{Th} (Fig. 3.370)

$$I_2 - I_1 = 4$$

Applying KVL to the outer path,

$$8 - 1I_1 - 5I_1 - 5I_2 - 10 = 0$$

$$-6I_1 - 5I_2 = 2$$

Solving Eqs (i) and (ii),

$$I_1 = -2 \text{ A}$$

$$I_2 = 2 \text{ A}$$

Writing the V_{Th} equation,

$$8 - 1I_1 - V_{Th} = 0$$

$$V_{Th} = 8 - I_1 = 8 - (-2) = 10 \text{ V}$$

Step II Calculation of R_{Th} (Fig. 3.371)

$$R_{Th} = 10 \parallel 1 = 0.91 \Omega$$

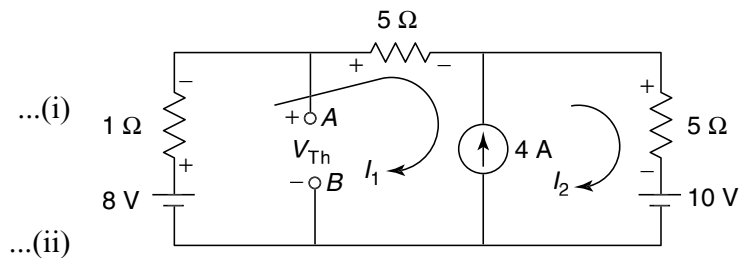


Fig. 3.370

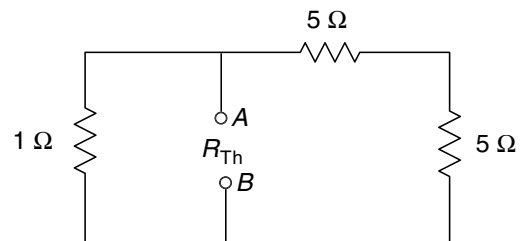


Fig. 3.371

3.94 Network Analysis and Synthesis

Step III Calculation of R_L

For maximum power transfer,

$$R_L = R_{Th} = 0.91 \Omega$$

Step IV Calculation of P_{max}

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(10)^2}{4 \times 0.91} = 27.47 \text{ W}$$

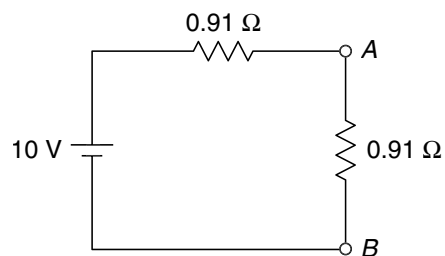


Fig. 3.372

Example 3.84 Find the value of the resistance R_L in Fig. 3.373 for maximum power transfer and calculate the maximum power.

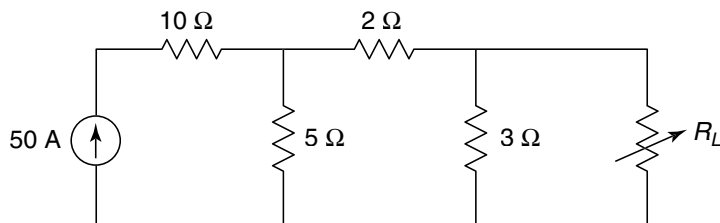


Fig. 3.373

Solution

Step I Calculation of V_{Th} (Fig. 3.374)

For Mesh 1,

$$I_1 = 50$$

Applying KVL to Mesh 2,

$$-5(I_2 - I_1) - 2I_2 - 3I_2 = 0$$

$$5I_1 - 10I_2 = 0$$

$$I_1 = 2I_2$$

$$I_2 = 25 \text{ A}$$

$$V_{Th} = 3I_2 = 3(25) = 75 \text{ V}$$

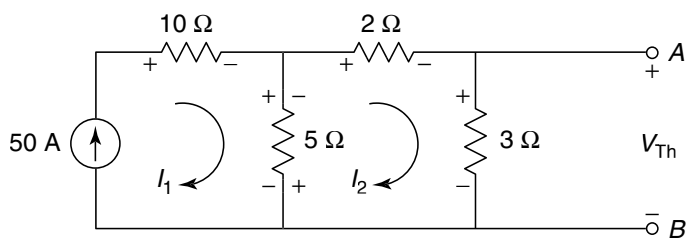


Fig. 3.374

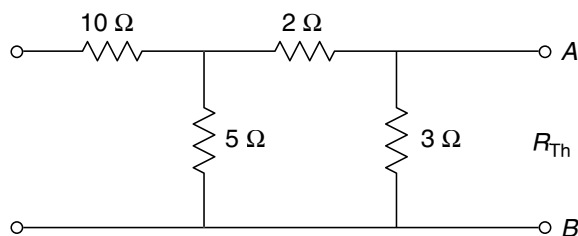


Fig. 3.375

Step II Calculation of R_{Th} (Fig. 3.375)

$$R_{Th} = (5 + 2) \parallel 3 = 2.1 \Omega$$

Step III Calculation of R_L

For maximum power transfer,

$$R_L = R_{Th} = 2.1 \Omega$$

Step IV Calculation of P_{max} (Fig. 3.376)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(75)^2}{4 \times 2.1} = 669.64 \text{ W}$$

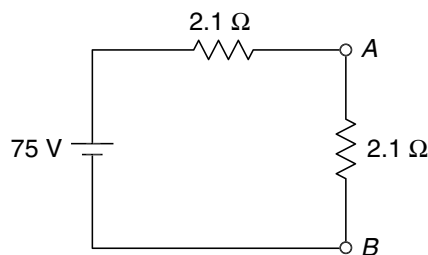


Fig. 3.376

Example 3.85 Find the value of resistance R_L in Fig. 3.377 for maximum power transfer and calculate maximum power.

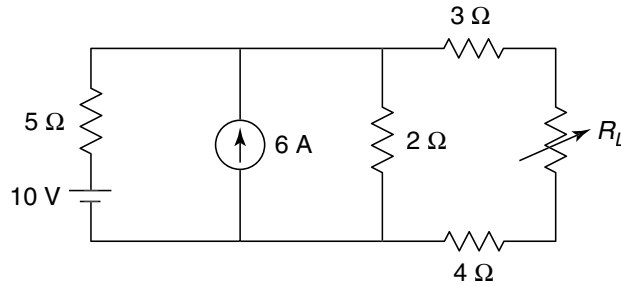


Fig. 3.377

Solution

Step I Calculation of V_{Th} (Fig. 3.378)

Writing the current equation for the supermesh,

$$I_2 - I_1 = 6$$

Applying KVL to the supermesh,

$$10 - 5I_1 - 2I_2 = 0$$

$$5I_1 + 2I_2 = 10$$

Solving Eqs (i) and (ii),

$$I_1 = -0.29 \text{ A}$$

$$I_2 = 5.71 \text{ A}$$

Writing the V_{Th} equation,

$$V_{Th} = 2I_2 = 11.42 \text{ V}$$

Step II Calculation of R_{Th} (Fig. 3.379)

$$R_{Th} = (5 \parallel 2) + 3 + 4 = 8.43 \Omega$$

Step III Calculation of R_L

For maximum power transfer,

$$R_L = R_{Th} = 8.43 \Omega$$

Step IV Calculation of P_{max} (Fig. 3.380)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(11.42)^2}{4 \times 8.43} = 3.87 \text{ W}$$

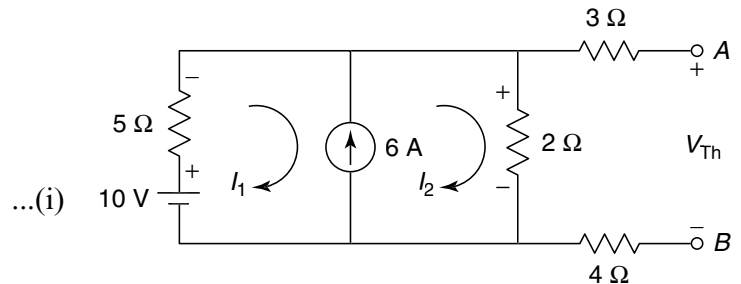


Fig. 3.378

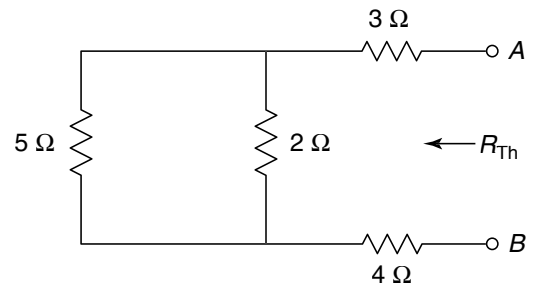


Fig. 3.379

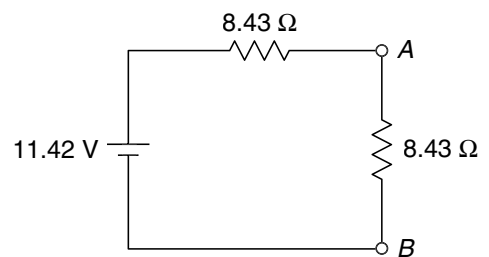


Fig. 3.380

Example 3.86 Find the value of resistance R_L in Fig. 3.381 for maximum power transfer and calculate the maximum power.

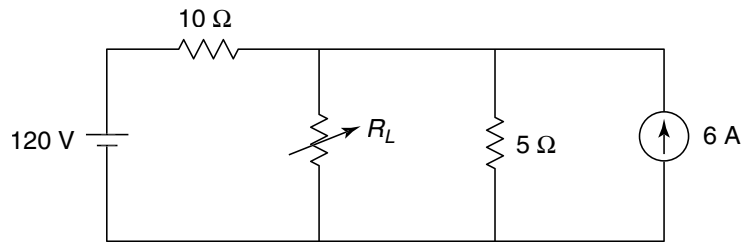


Fig. 3.381

Solution

Step I Calculation of V_{Th} (Fig. 3.382)

Applying KVL to Mesh 1,

$$120 - 10I_1 - 5(I_1 - I_2) = 0$$

$$15I_1 - 5I_2 = 120 \quad \dots(i)$$

Writing current equation for Mesh 2,

$$I_2 = -6 \quad \dots(ii)$$

Solving Eqs (i) and (ii),

$$I_1 = 6 \text{ A}$$

Writing the V_{Th} equation,

$$120 - 10I_1 - V_{Th} = 0$$

$$V_{Th} = 120 - 10(6) = 60 \text{ V}$$

Step II Calculation of R_{Th} (Fig. 3.383)

$$R_{Th} = 10 \parallel 5 = 3.33 \Omega$$

Step III Calculation of R_L

For maximum power transfer,

$$R_L = R_{Th} = 3.33 \Omega$$

Step IV Calculation of P_{max} (Fig. 3.384)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(60)^2}{4 \times 3.33} = 270.27 \text{ W}$$

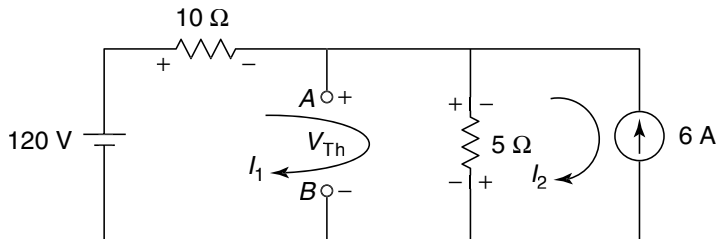


Fig. 3.382

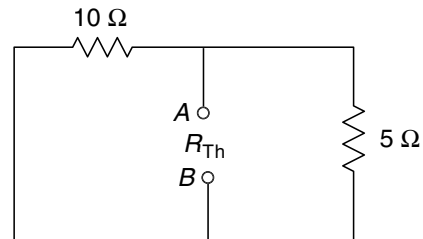


Fig. 3.383

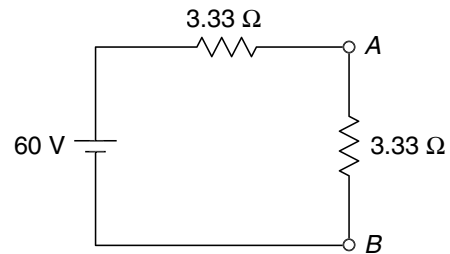


Fig. 3.384

Example 3.87 Find the value of resistance R_L in Fig. 3.385 for maximum power transfer and calculate the maximum power.

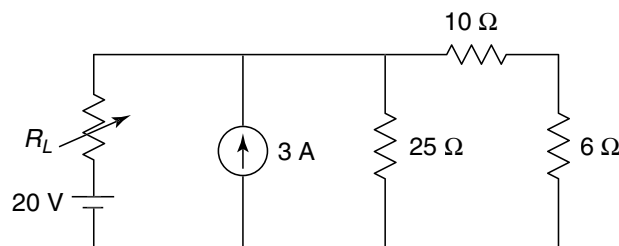


Fig. 3.385

Solution**Step I** Calculation of V_{Th} (Fig. 3.386)

$$I_1 = 3$$

Applying KVL to Mesh 2,

$$-25(I_2 - I_1) - 10I_2 - 6I_2 = 0$$

$$-25I_1 + 41I_2 = 0$$

Solving Eqs (i) and (ii),

$$I_2 = 1.83 \text{ A}$$

Writing the V_{Th} equation,

$$20 + V_{Th} - 10I_2 - 6I_2 = 0$$

$$V_{Th} = -20 + 10(1.83) + 6(1.83) = 9.28 \text{ V}$$

Step II Calculation of R_{Th} (Fig. 3.387)

$$R_{Th} = 25 \parallel (10 + 6) = 9.76 \Omega$$




Step III Calculation of R_L

For maximum power transfer,



$$R_L = R_{Th} = 9.76 \Omega$$

Step IV Calculation of P_{max} (Fig. 3.388)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(9.28)^2}{4 \times 9.76} = 2.21 \text{ W}$$

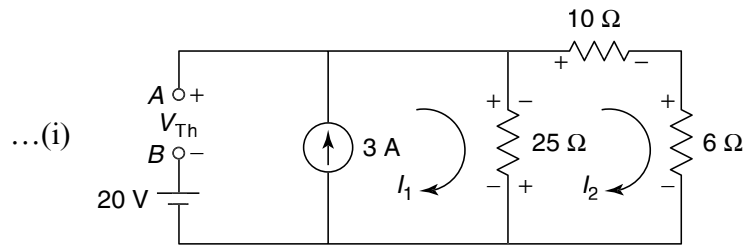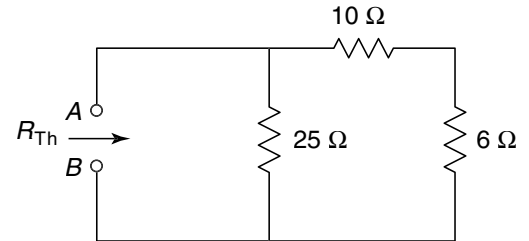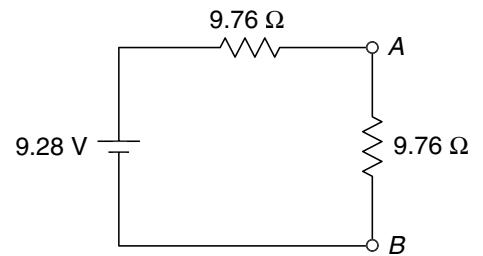**Fig. 3.386****Fig. 3.387****Fig. 3.388**

Example 3.88 Find the value of resistance R_L in Fig. 3.389 for maximum power transfer and calculate maximum power.

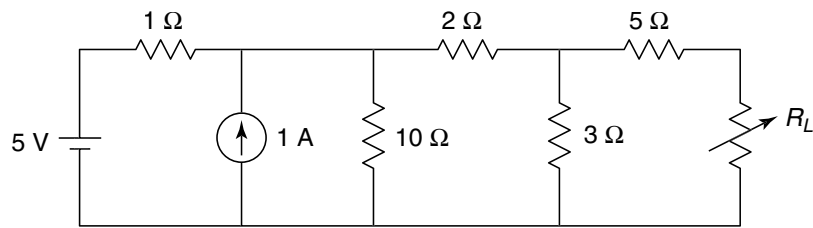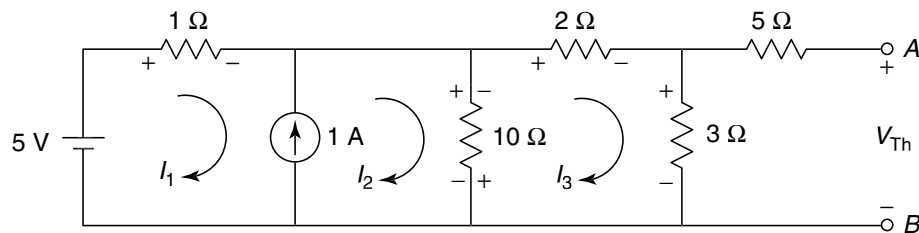**Fig. 3.389****Solution****Step I** Calculation of V_{Th} (Fig. 3.390)**Fig. 3.390**

3.98 Network Analysis and Synthesis

Meshes 1 and 2 will form a supermesh.

Writing the current equation for the supermesh,

$$I_2 - I_1 = 1 \quad \dots(i)$$

Writing the voltage equation for the supermesh,

$$5 - 1I_1 - 10(I_2 - I_3) = 0 \quad \dots(ii)$$

$$I_1 + 10I_2 - 10I_3 = 5$$

Applying KVL to Mesh 3,

$$-10(I_3 - I_2) - 2I_3 - 3I_3 = 0 \quad \dots(iii)$$

$$-10I_2 + 15I_3 = 0$$

Solving Eqs (i), (ii) and (iii),

$$I_1 = 0.38 \text{ A}$$

$$I_2 = 1.38 \text{ A}$$

$$I_3 = 0.92 \text{ A}$$

Writing the V_{Th} equation,

$$V_{Th} = 3I_3 = 2.76 \text{ V}$$

Step II Calculation of R_{Th} (Fig. 3.391)

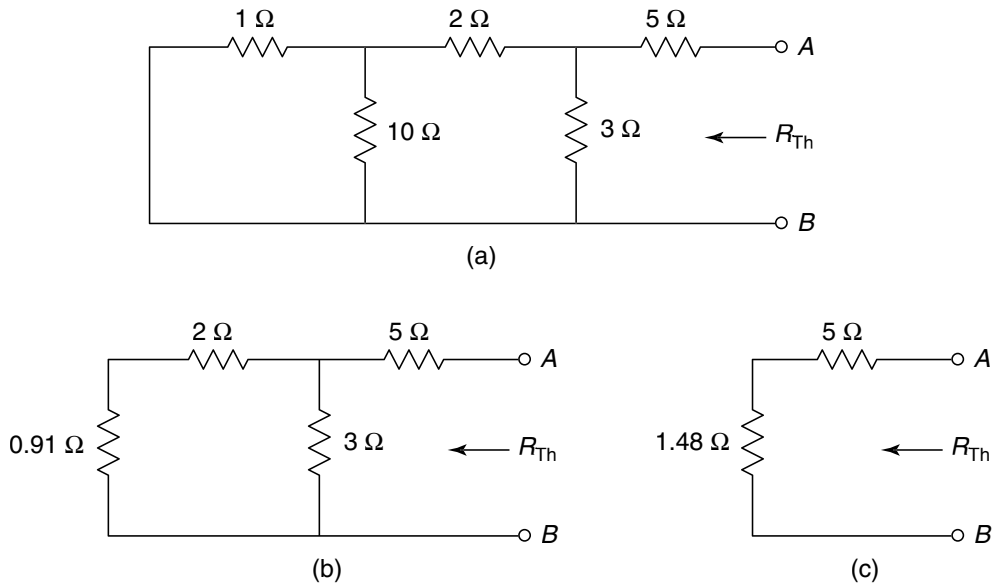


Fig. 3.391

$$R_{Th} = 6.48\ \Omega$$

Step III Calculation of R_L

For maximum power transfer,

$$R_L = R_{Th} = 6.48\ \Omega$$

Step IV Calculation of P_{max} (Fig. 3.392)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(2.76)^2}{4 \times 6.48} = 0.29 \text{ W}$$

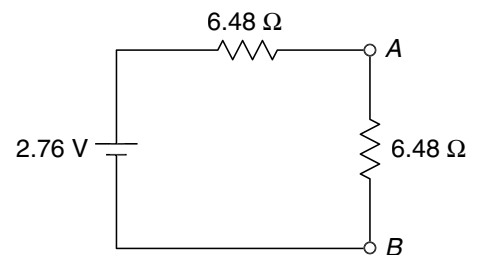


Fig. 3.392

Example 3.89 For the network shown in Fig. 3.393, find the value of the resistance R_L for maximum power transfer and calculate the maximum power.

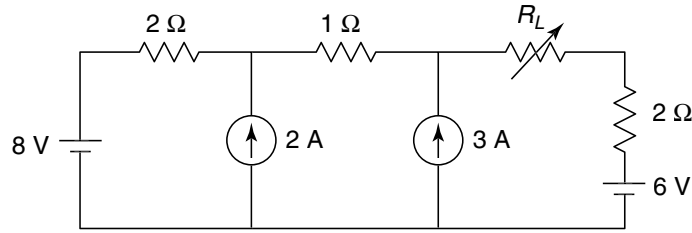


Fig. 3.393

Solution

Step I Calculation of V_{Th} (Fig. 3.394)

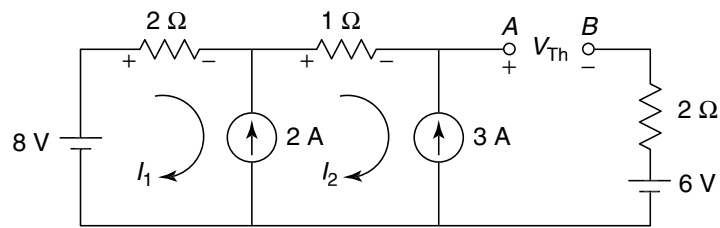


Fig. 3.394

$$I_2 - I_1 = 2 \quad \dots(i)$$

$$I_2 = -3 \text{ A} \quad \dots(ii)$$

Solving Eqs (i), and (ii),

$$I_1 = -5 \text{ A}$$

Writing the V_{Th} equation,

$$8 - 2I_1 - 1I_2 - V_{Th} - 6 = 0$$

$$V_{Th} = 8 - 2(-5) - (-3) - 6 = 15 \text{ V}$$

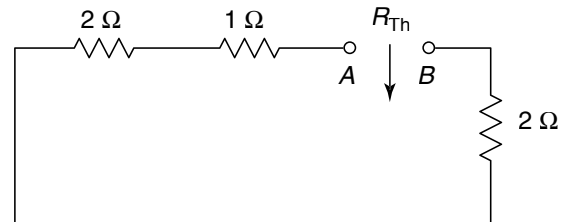


Fig. 3.395

Step II Calculation of R_{Th} (Fig. 3.395)

$$R_{Th} = 5 \Omega$$

Step III Calculation of R_L

For maximum power transfer,

$$R_L = R_{Th} = 5 \Omega$$

Step IV Calculation of P_{max} (Fig. 3.396)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(15)^2}{4 \times 5} = 11.25 \text{ W}$$

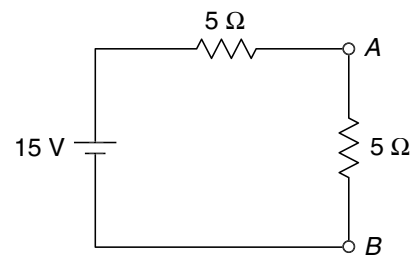


Fig. 3.396

Example 3.90 For the value of resistance R_L in Fig. 3.397 for maximum power transfer and calculate the maximum power.

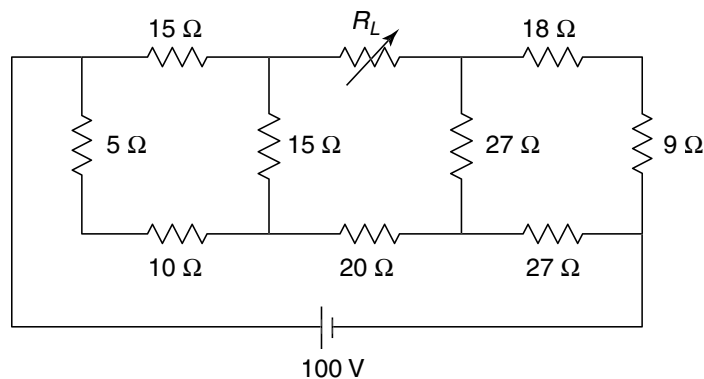


Fig. 3.397

Solution

Step I Calculation of V_{Th} (Fig. 3.398)

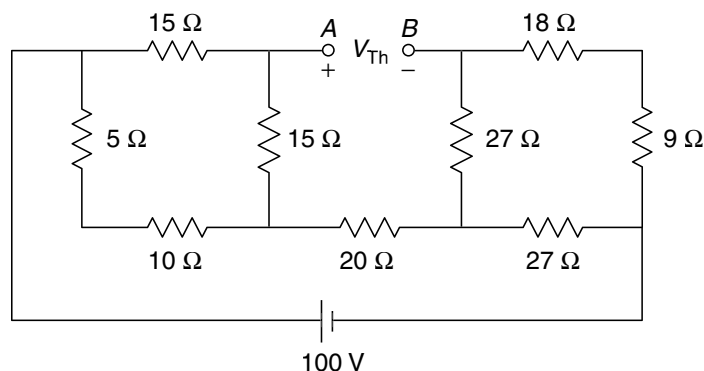


Fig. 3.398

By star-delta transformation (Fig. 3.399),

$$I = \frac{100}{5 + 5 + 20 + 9 + 9} = 2.08 \text{ A}$$

Writing the V_{Th} equation,

$$\begin{aligned} 100 - 5I - V_{Th} - 9I &= 0 \\ V_{Th} &= 100 - 14I \\ &= 100 - 14(2.08) \\ &= 70.88 \text{ V} \end{aligned}$$

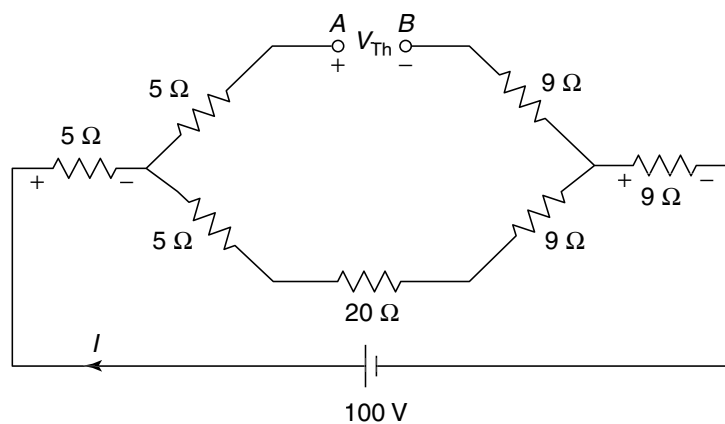


Fig. 3.399

Step II Calculation of R_{Th} (Fig. 3.400)

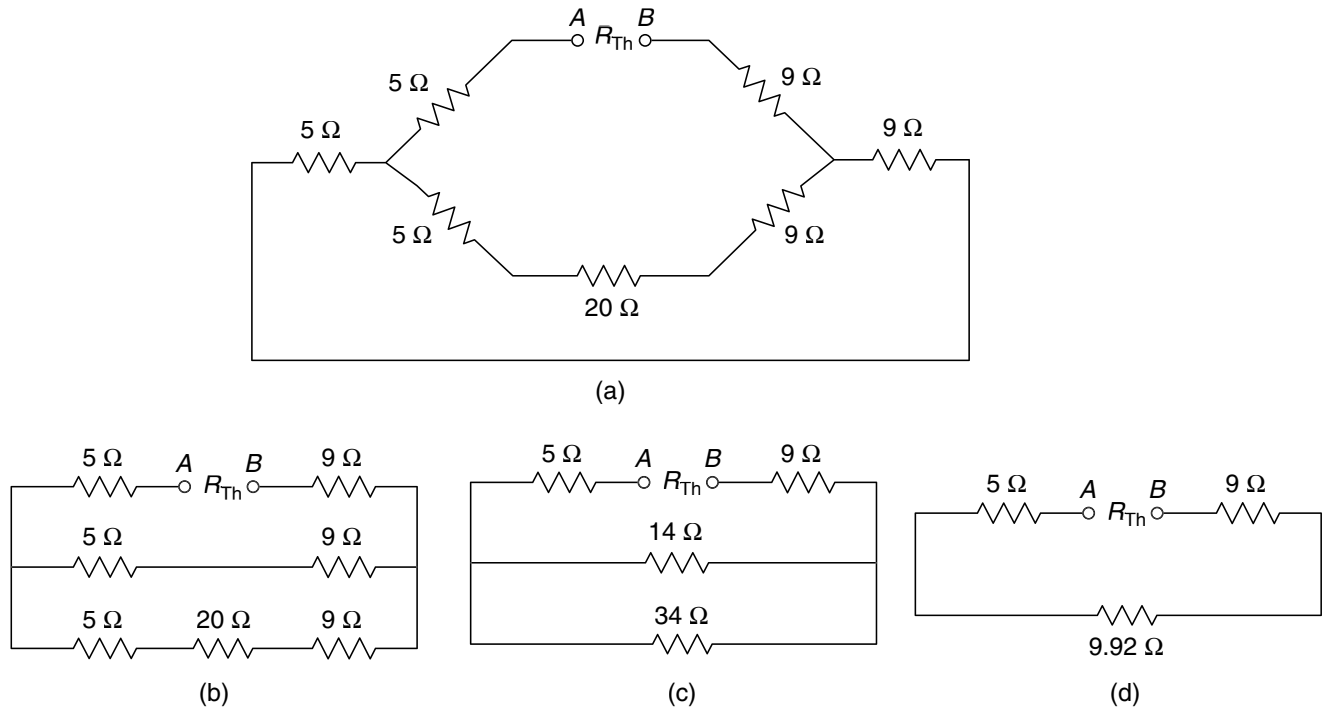


Fig. 3.400

$$R_{Th} = 23.92 \, \Omega$$

Step III Calculation of R_L
For maximum power transfer,

$$R_L = R_{Th} = 23.92 \, \Omega$$

Step IV Calculation of P_{max} (Fig. 3.401)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(70.88)^2}{4 \times 23.92} = 52.51 \, \text{W}$$

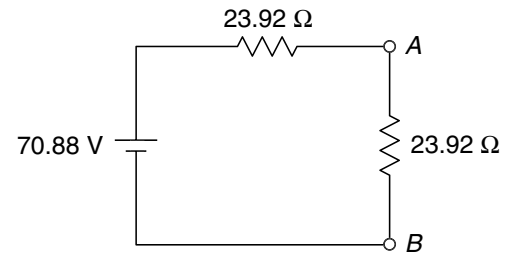


Fig. 3.401

Example 3.91 For the value of resistance R_L in Fig. 3.402 for maximum power transfer and calculate the maximum power.

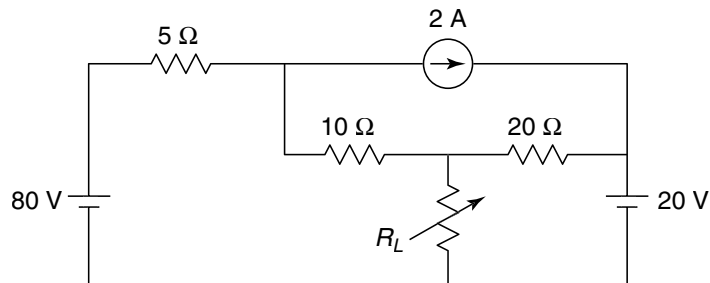


Fig. 3.402

Solution

Step I Calculation of V_{Th} (Fig. 3.403)

Applying KVL to Mesh 1,

$$80 - 5I_1 - 10(I_1 - I_2) - 20(I_1 - I_2) - 20 = 0$$

$$35I_1 - 30I_2 = 60 \quad \dots(i)$$

Writing the current equation for Mesh 2,

$$I_2 = 2 \quad \dots(ii)$$

Solving Eqs (i) and (ii),

$$I_1 = 3.43 \text{ A}$$

Writing the V_{Th} equation,

$$V_{Th} - 20(I_1 - I_2) - 20 = 0$$

$$V_{Th} = 20(3.43 - 2) + 20 = 48.6 \text{ V}$$

Step II Calculation of R_{Th} (Fig. 3.404)

$$R_{Th} = 15 \parallel 20 = 8.57 \Omega$$

Step III Calculation of R_L

For maximum power transfer,

$$R_L = R_{Th} = 8.57 \Omega$$

Step IV Calculation of P_{max} (Fig. 3.405)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(48.6)^2}{4 \times 8.57} = 68.9 \text{ W}$$

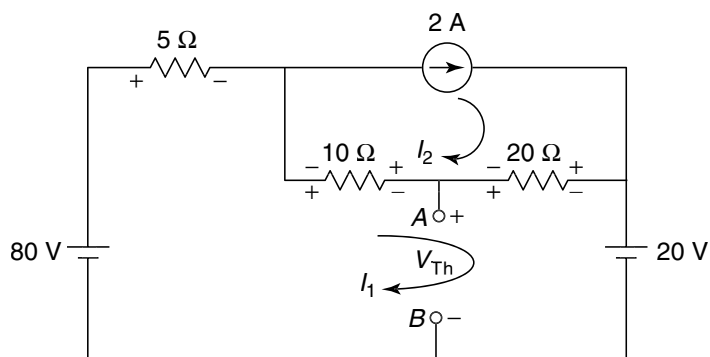


Fig. 3.403

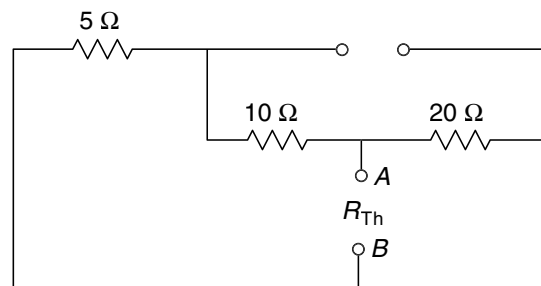


Fig. 3.404

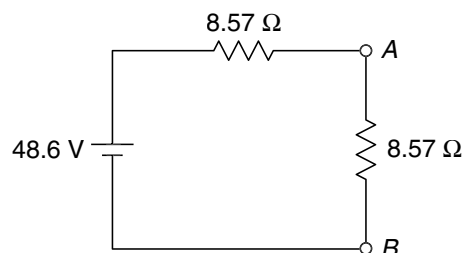


Fig. 3.405

Example 3.92 For the value of resistance R_L in Fig. 3.406 for maximum power transfer and calculate the maximum power.

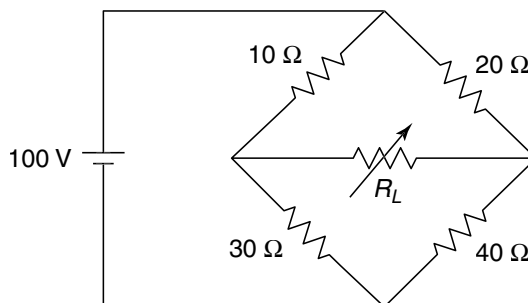


Fig. 3.406

Solution**Step I** Calculation of V_{Th} (Fig. 3.407)


$$I_1 = \frac{100}{10 + 30} = 2.5 \text{ A}$$

$$I_2 = \frac{100}{20 + 40} = 1.66 \text{ A}$$

Writing the V_{Th} equation,


$$V_{Th} + 10 I_1 - 20 I_2 = 0$$

$$V_{Th} = 20 I_2 - 10 I_1 = 20(1.66) - 10(2.5) = 8.2 \text{ V}$$

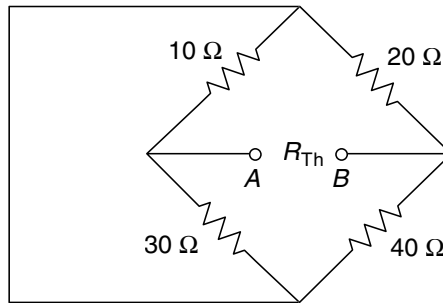Step II Calculation of R_{Th} (Fig. 3.408)**Fig. 3.408**

Redrawing the network (Fig. 3.409),

$$R_{Th} = (10 \parallel 30) + (20 \parallel 40) = 20.83 \Omega$$

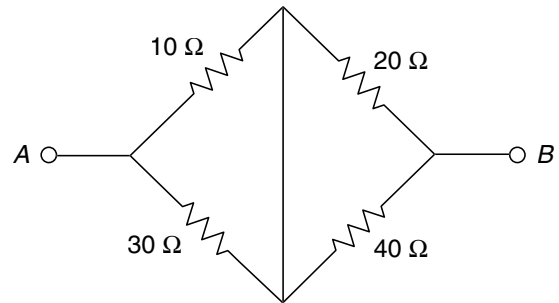
**Fig. 3.409****Step III** Value of R_L

For maximum power transfer,

$$R_L = R_{Th} = 20.83 \Omega$$

Step IV Calculation of P_{max} (Fig. 3.410)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(8.2)^2}{4 \times 20.83} = 0.81 \text{ W}$$

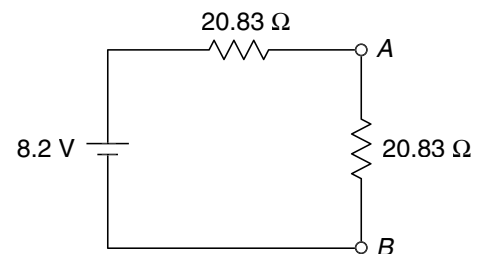**Fig. 3.410**

Example 3.93 For the value of resistance R_L in Fig. 3.411 for maximum power transfer and calculate the maximum power.

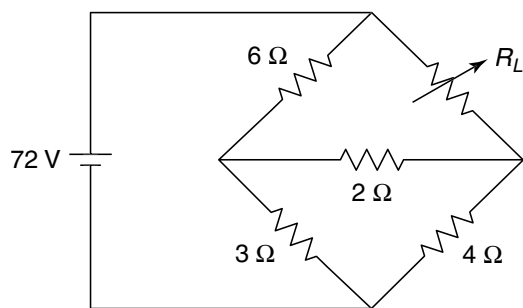


Fig. 3.411

Solution

Step I Calculation of V_{Th} (Fig. 3.412)

Applying KVL to Mesh 1,

$$\begin{aligned} 72 - 6I_1 - 3(I_1 - I_2) &= 0 \\ 9I_1 - 3I_2 &= 72 \quad \dots(i) \end{aligned}$$

Applying KVL to Mesh 2,

$$\begin{aligned} -3(I_2 - I_1) - 2I_2 - 4I_2 &= 0 \\ -3I_1 + 9I_2 &= 0 \quad \dots(ii) \end{aligned}$$

Solving Eqs (i) and (ii),

$$I_1 = 9 \text{ A}$$

$$I_2 = 3 \text{ A}$$

Writing the V_{Th} equation,

$$\begin{aligned} V_{Th} - 6I_1 - 2I_2 &= 0 \\ V_{Th} &= 6I_1 + 2I_2 = 6(9) + 2(3) = 60 \text{ V} \end{aligned}$$

Step II Calculation of R_{Th} (Fig. 3.413)

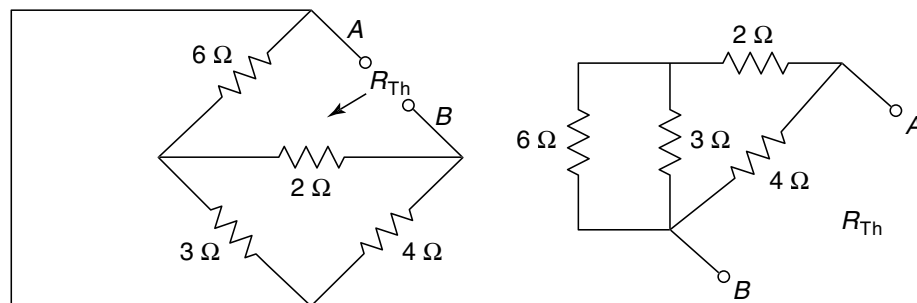


Fig. 3.413

$$R_{Th} = [(6 \parallel 3) + 2] \parallel 4 = 2 \Omega$$

Step III Calculation of R_L
For maximum power transfer,

$$R_L = R_{Th} = 2 \Omega$$

Step IV Calculation of $P_{\max}$ (Fig. 3.414)

$$P_{\max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(60)^2}{4 \times 2} = 450 \text{ W}$$

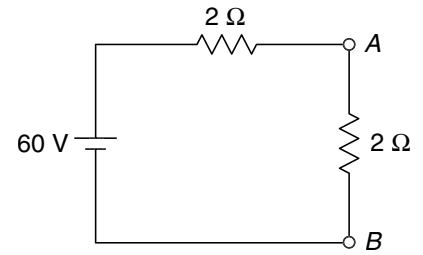


Fig. 3.414

Example 3.94 For the network shown in Fig. 3.415 find the value of the resistance R_L for maximum power transfer and calculate maximum power.

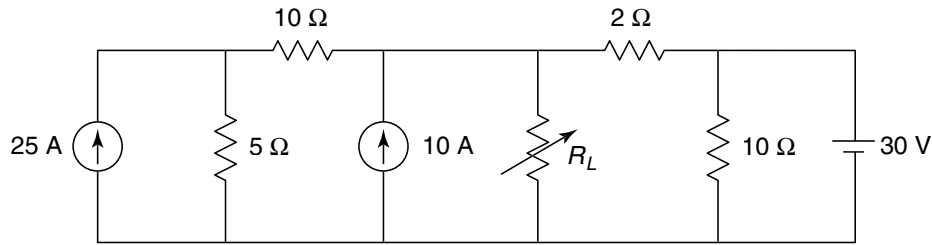


Fig. 3.415

Solution

Step I Calculation of V_{Th} (Fig. 3.416)

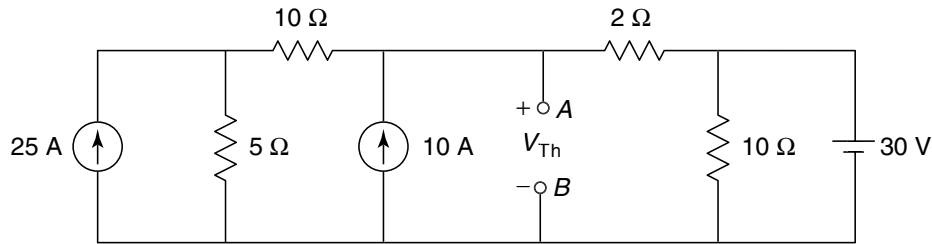


Fig. 3.416

By source transformation, the current source of 25 A and the 5 Ω resistor is converted into an equivalent voltage source of 125 V and a series resistor of 5 Ω. Also the voltage source of 30 V is connected across the 10 Ω resistor. Hence, the 10 Ω resistor becomes redundant (Fig. 3.417).

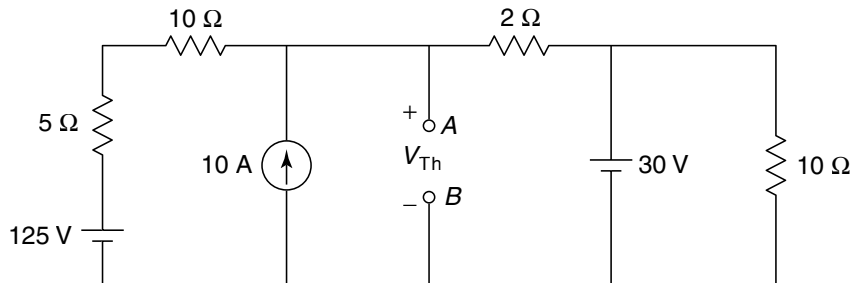


Fig. 3.417

3.106 Network Analysis and Synthesis

Applying KCL at the node,

$$\frac{V_{Th} - 125}{15} - 10 + \frac{V_{Th} - 30}{2} = 0$$

$$V_{Th} = 58.81 \text{ V}$$

Step II Calculation of R_{Th} (Fig. 3.418)

$$R_{Th} = 15 \parallel 2 = 1.76 \Omega$$

Step III Value of R_L

For maximum power transfer

$$R_L = R_{Th} = 1.76 \Omega$$

Step IV Calculation of P_{max} (Fig. 3.420)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(58.81)^2}{4 \times 1.76} = 491.28 \text{ W}$$

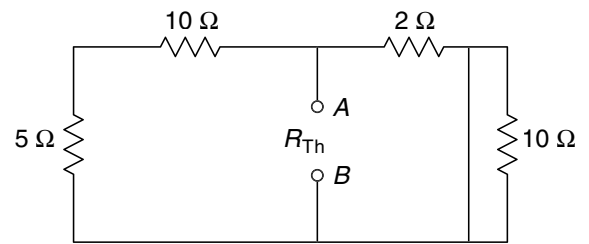


Fig. 3.418

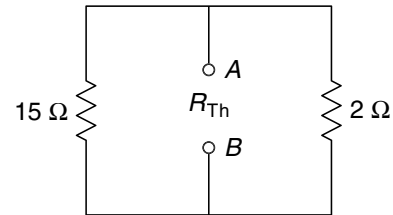


Fig. 3.419

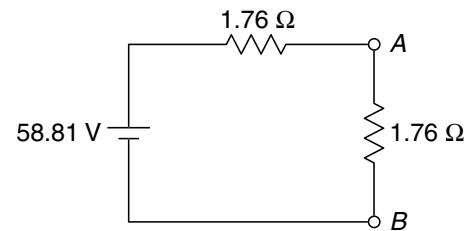


Fig. 3.420

Example 3.95

For the network shown in Fig. 3.421, find the value of the resistance R_L for maximum power transfer and calculate maximum power.

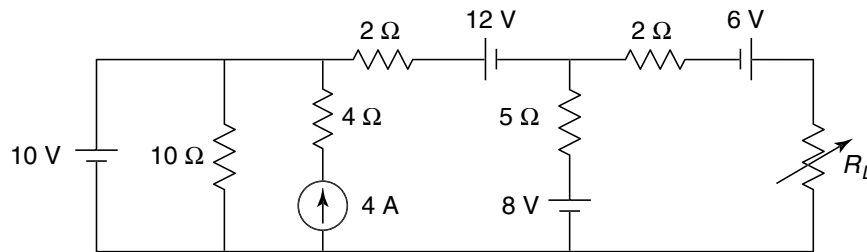


Fig. 3.421

Solution

Step I Calculation of V_{Th} (Fig. 3.422)

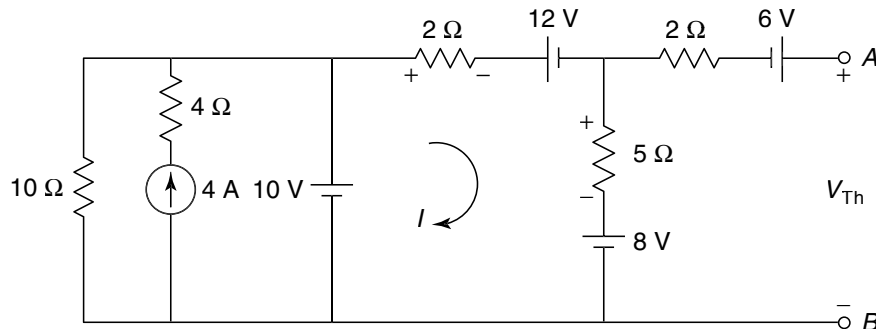


Fig. 3.422

Applying KVL to the outer path,

$$10 - 2I - 12 - 5I - 8 = 0$$

$$I = -\frac{10}{7} = -1.43 \text{ A}$$

Writing the V_{Th} equation,

$$8 + 5I + 6 - V_{Th} = 0$$

$$V_{Th} = 8 + 6 + 5I = 8 + 6 + 5(-1.43) = 6.85 \text{ V}$$

Step II Calculation of R_{Th} (Fig. 3.423)

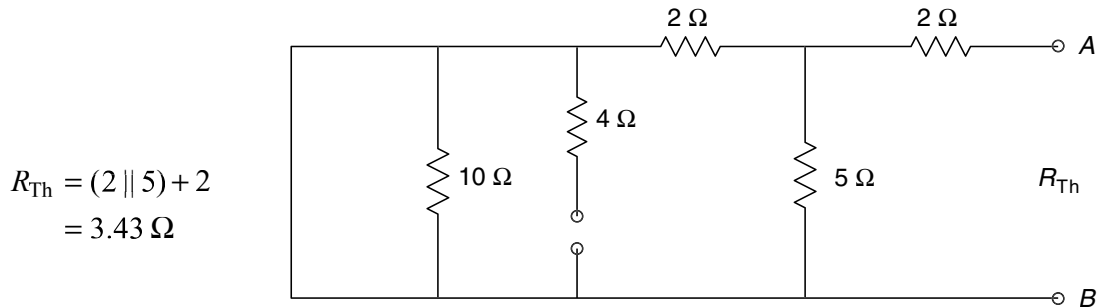


Fig. 3.423

Step III Value of R_L

For maximum power transfer,

$$R_L = R_{Th} = 3.43 \Omega$$

Step IV Calculation of P_{max} (Fig. 3.424)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(6.85)^2}{4 \times 3.43} = 3.42 \text{ W}$$

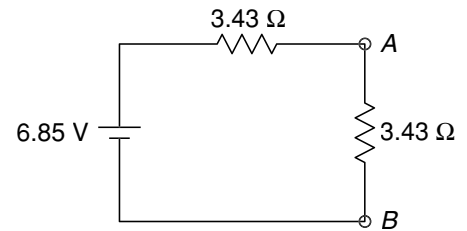


Fig. 3.424

EXAMPLES WITH DEPENDENT SOURCES

Example 3.96 For the network shown in Fig. 3.425, find the value of R_L for maximum power transfer. Also, calculate maximum power.

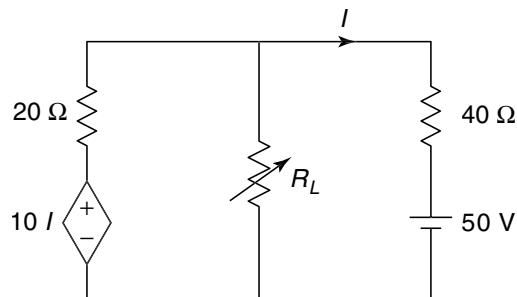


Fig. 3.425

Solution

Step I Calculation of V_{Th} (Fig. 3.426)

Applying KVL to the mesh,

$$10I - 20I - 40I - 50 = 0$$

$$I = -1 \text{ A}$$

Writing the V_{Th} equation,

$$V_{Th} - 40I - 50 = 0$$

$$V_{Th} - 40(-1) - 50 = 0$$

$$V_{Th} = 10 \text{ V}$$

Step II Calculation of I_N (Fig. 3.427)

From Fig. 3.427,

$$I = I_2 \quad \dots(i)$$

Applying KVL to Mesh 1,

$$10I - 20I_1 = 0$$

$$10I_2 - 20I_1 = 0 \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$-40I_2 - 50 = 0$$

$$I_2 = -1.25 \text{ A}$$

Solving Eqs (i), (ii) and (iii),

$$I_1 = -0.625 \text{ A}$$

$$I_N = I_1 - I_2 = -0.625 + 1.25 = 0.625 \text{ A}$$

Step III Calculation of R_N

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{10}{0.625} = 16 \Omega$$

Step IV Calculation of R_L

For maximum power transfer,

$$R_L = R_{Th} = 16 \Omega$$

Step V Calculation of P_{max} (Fig. 3.428)

$$P_{max} = \frac{V_{Th}^2}{4 R_{Th}} = \frac{(10)^2}{4 \times 16} = 1.56 \text{ W}$$

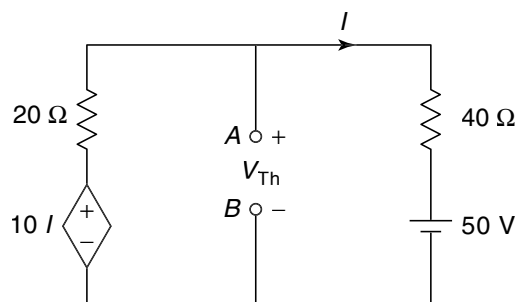


Fig. 3.426

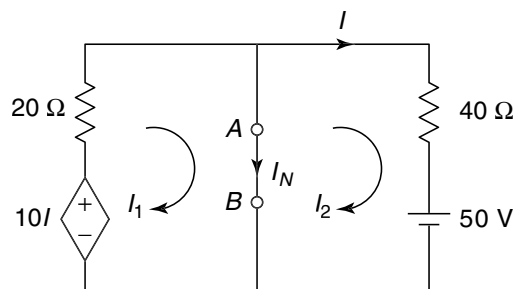


Fig. 3.427

... (iii)

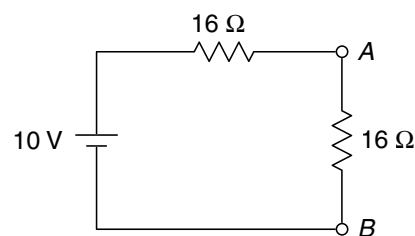


Fig. 3.428

Example 3.97 For the network shown in Fig. 3.429, calculate the maximum power that may be dissipated in the load resistor R_L .

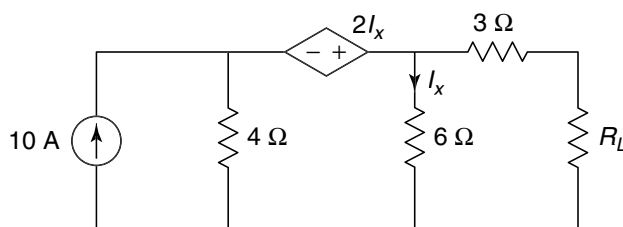


Fig. 3.429

Solution**Step I** Calculation of V_{Th} (Fig. 3.430)

From Fig. 3.430,

$$I_x = I_2$$

... (i)

For Mesh 1,

$$I_1 = 10$$

... (ii)

Applying KVL to Mesh 2,

$$-4(I_2 - I_1) + 2I_x - 6I_2 = 0$$

$$-4I_2 + 4I_1 + 2I_2 - 6I_2 = 0$$

$$4I_1 - 8I_2 = 0$$

... (iii)

Solving Eqs (ii) and (iii),

$$I_1 = 10 \text{ A}$$

$$I_2 = 5 \text{ A}$$

Writing the V_{Th} equation,

$$6I_2 - 0 - V_{Th} = 0$$

$$V_{Th} = 6I_2 = 6(5) = 30 \text{ V}$$

Step II Calculation of I_N (Fig. 3.431)

From Fig. 3.431,

$$I_x = I_2 - I_3$$

... (i)

For Mesh 1,

$$I_1 = 10$$

... (ii)

Applying KVL to Mesh 2,

$$-4(I_2 - I_1) + 2I_x - 6(I_2 - I_3) = 0$$

$$-4I_2 + 4I_1 + 2(I_2 - I_3) - 6I_2 + 6I_3 = 0$$

$$4I_1 - 8I_2 + 4I_3 = 0$$

... (iii)

Applying KVL to Mesh 3,

$$-6(I_3 - I_2) - 3I_3 = 0$$

$$6I_2 - 9I_3 = 0$$

... (iv)



Solving Eqs (ii), (iii) and (iv),

$$I_1 = 10 \text{ A}$$

$$I_2 = 7.5 \text{ A}$$

$$I_3 = 5 \text{ A}$$

$$I_N = I_3 = 5 \text{ A}$$

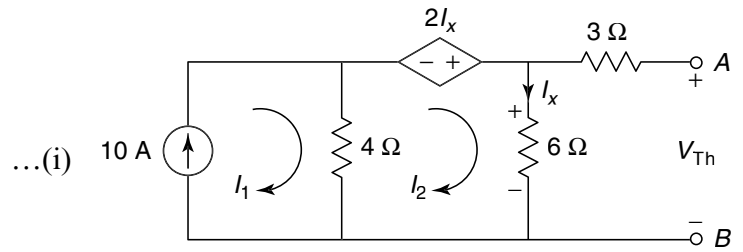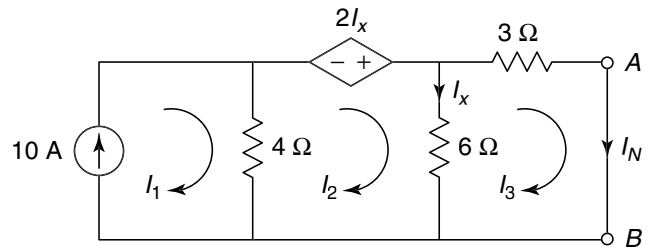**Fig. 3.430****Fig. 3.431**

Step III Calculation of R_{Th}

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{30}{5} = 6 \Omega$$

Step IV Calculation of R_L

For maximum power transfer,

$$R_L = R_{Th} = 6 \Omega$$

Step V Calculation of P_{max}

$$P_{max} = \frac{V_{Th}^2}{4 R_{Th}} = \frac{(30)^2}{4 \times 6} = 37.5 \text{ W}$$

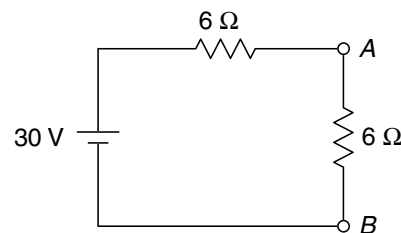


Fig. 3.432

Example 3.98 For the network shown in Fig. 3.433, find the value of R_L for maximum power transfer. Also, find maximum power.

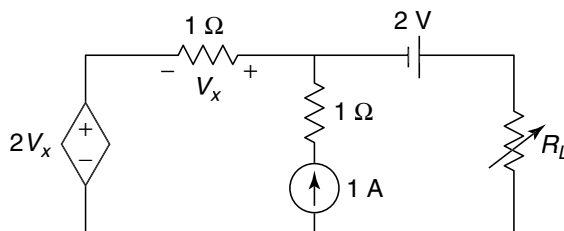


Fig. 3.433

Solution

Step I Calculation of V_{Th} (Fig. 3.434)

From Fig. 3.434,

$$V_x = -1I = -I \quad \dots(i)$$

For Mesh 1,

$$\begin{aligned} I &= -1 \\ V_x &= 1 \text{ V} \end{aligned} \quad \dots(ii)$$

Writing the V_{Th} equation,

$$\begin{aligned} 2V_x - 1I + 2 - V_{Th} &= 0 \\ 2(1) - (-1) + 2 - V_{Th} &= 0 \\ V_{Th} &= 5 \text{ V} \end{aligned}$$

Step II Calculation of I_N (Fig. 3.435)

From Fig. 3.435,

$$V_x = -1I_1 = -I_1 \quad \dots(i)$$

Meshes 1 and 2 will form a supermesh.

Writing the current equation for the supermesh,

$$I_2 - I_1 = 1 \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$\begin{aligned} 2V_x - 1I_1 + 2 &= 0 \\ 2(-I_1) - I_1 + 2 &= 0 \\ 3I_1 &= 0 \end{aligned}$$

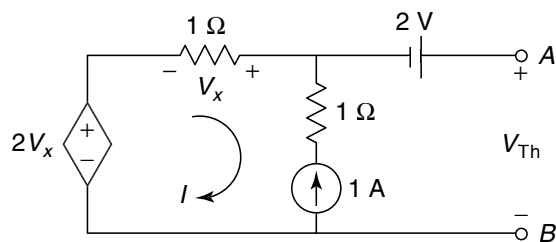


Fig. 3.434

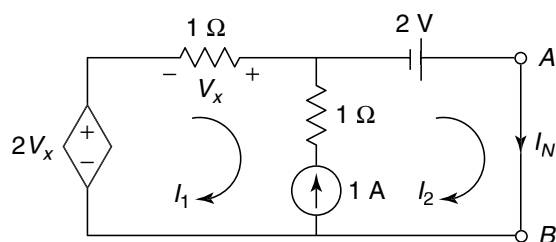


Fig. 3.435

$$\dots(iii)$$

Solving Eqs (ii) and (iii),

$$I_1 = 0.67 \text{ A}$$

$$I_2 = 1.67 \text{ A}$$

$$I_N = I_2 = 1.67 \text{ A}$$

Step III Calculation of R_{Th}

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{5}{1.67} = 3 \Omega$$

Step IV Calculation of R_L

For maximum power transfer,

$$R_L = R_{Th} = 3 \Omega$$

Step V Calculation of P_{max} (Fig. 3.436)

$$P_{max} = \frac{V_{Th}^2}{4 R_{Th}} = \frac{(5)^2}{4 \times 3} = 2.08 \text{ W}$$

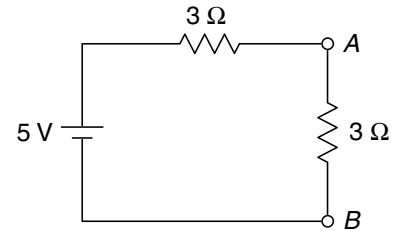


Fig. 3.436

Example 3.99 What will be the value of R_L in Fig. 3.437 to get maximum power delivered to it? What is the value of this power?

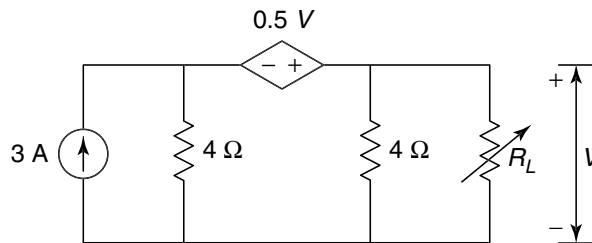


Fig. 3.437

Solution

Step I Calculation of V_{Th} (Fig. 3.438)

By source transformation,

From Fig. 3.438,

$$V_{Th} = 4I$$

Applying KVL to the mesh,

$$12 - 4I + 0.5 V_{Th} - 4I = 0$$

$$12 - V_{Th} + 0.5 V_{Th} - V_{Th} = 0$$

$$V_{Th} = 8 \text{ V}$$

Step II Calculation of I_N (Fig. 3.439)

If two terminals A and B are shorted, the 4Ω resistor gets shorted.

$$V = 0$$

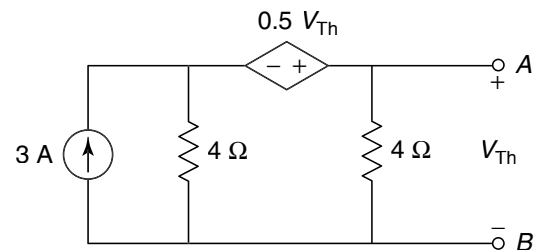


Fig. 3.438

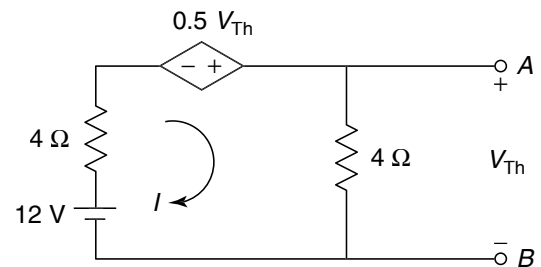


Fig. 3.439

3.112 Network Analysis and Synthesis

Dependent source $0.5 V$ depends on the controlling variable V . When $V = 0$, the dependent source vanishes, i.e. $0.5 V = 0$ as shown in Fig. 3.441.

$$I_N = \frac{12}{4} = 3 \text{ A}$$

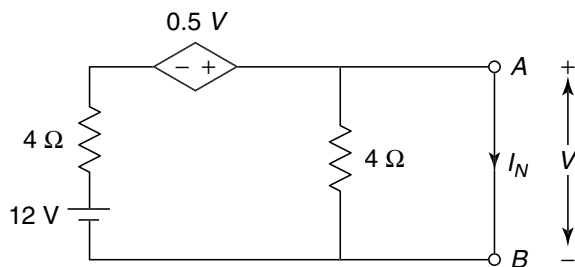


Fig. 3.440

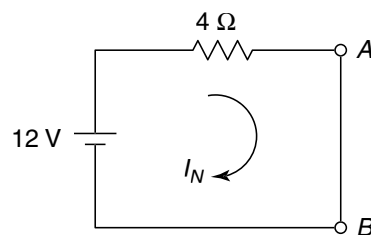


Fig. 3.441

Step III Calculation of R_{Th}

$$R_{Th} = \frac{V_{Th}}{I_N} = \frac{8}{3} = 2.67 \Omega$$

Step IV Calculation of R_L

For maximum power transfer,

$$R_L = R_{Th} = 2.67 \Omega$$

Step V Calculation of P_{max} (Fig. 3.442)

$$P_{max} = \frac{V_{Th}^2}{4R_{Th}} = \frac{(8)^2}{4 \times 2.67} = 6 \text{ W}$$

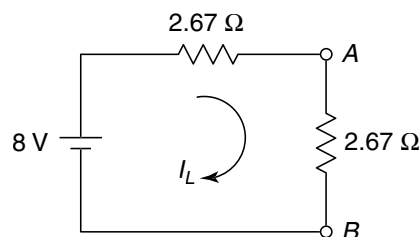


Fig. 3.442

3.6 RECIPROCITY THEOREM

It states that ‘in a linear, bilateral, active, single source network, the ratio of excitation to response remains same when the positions of excitation and response are interchanged.’

In other words, it may be stated as ‘if a single voltage source V_a in the branch ‘a’ produces a current I_b in the branch ‘b’ then if the voltage source V_a is removed and inserted in the branch ‘b’, it will produce a current I_b in branch ‘a’.

Explanation Consider a network shown in Fig. 3.443.

When the voltage source V is applied at the port 1, it produces a current I at the port 2. If the positions of the excitation (source) and response are interchanged, i.e., if the voltage source is applied at the port 2 then it produces a current I at the port 1.

The limitation of this theorem is that it is applicable only to a single-source network. This theorem is not applicable in the network which has a dependent source. This is applicable only in linear and bilateral networks. In the reciprocity theorem, position of any passive element (R, L, C) do not change. Only the excitation and response are interchanged.

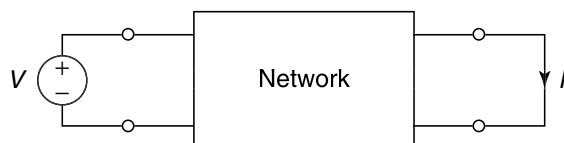


Fig. 3.443 Network

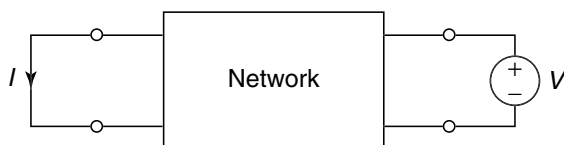



Fig. 3.444 Network when excitation and response are interchanged

Steps to be followed in Reciprocity Theorem

1. Identify the branches between which reciprocity is to be established.
2. Find the current in the branch when excitation and response are not interchanged.
3. Find the current in the branch when excitation and response are interchanged.

Example 3.100

Calculate current I and verify the reciprocity theorem for the network shown in Fig. 3.445.

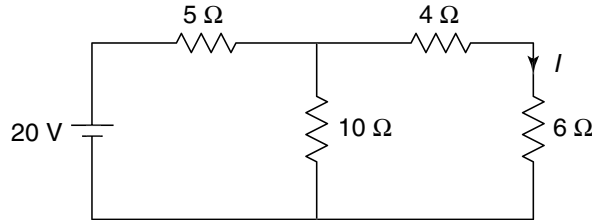**Fig. 3.445****Solution**

Case I Calculation of current I when excitation and response are not interchanged (Fig. 3.446)

Applying KVL to Mesh 1,


$$\begin{aligned} 20 - 5I_1 - 10(I_1 - I_2) &= 0 \\ 15I_1 - 10I_2 &= 20 \quad \dots(i) \end{aligned}$$

Applying KVL to Mesh 2,

$$\begin{aligned} -10(I_2 - I_1) - 4I_2 - 6I_2 &= 0 \\ -10I_1 + 20I_2 &= 0 \quad \dots(ii) \end{aligned}$$

Solving Eqs (i) and (ii),

$$\begin{aligned} I_1 &= 2 \text{ A} \\ I_2 &= 1 \text{ A} \\ I &= I_2 = 1 \text{ A} \end{aligned}$$

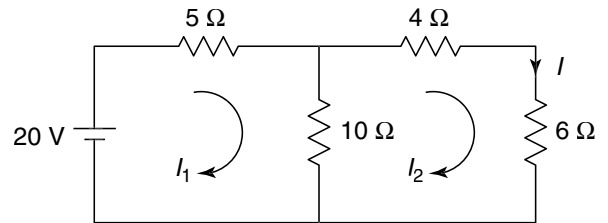**Fig. 3.446**

Case II Calculation of current I when excitation and response are interchanged (Fig. 3.447).

Applying KVL to Mesh 1,


$$\begin{aligned} -5I_1 - 10(I_1 - I_2) &= 0 \\ 15I_1 - 10I_2 &= 0 \quad \dots(i) \end{aligned}$$

Applying KVL to Mesh 2,


$$\begin{aligned} -10(I_2 - I_1) - 4I_2 - 20 - 6I_2 &= 0 \\ -10I_1 + 20I_2 &= -20 \quad \dots(ii) \end{aligned}$$

Solving Eqs (i) and (ii),

$$\begin{aligned} I_1 &= -1 \text{ A} \\ I_2 &= -1.5 \text{ A} \\ I &= -I_1 = 1 \text{ A} \end{aligned}$$

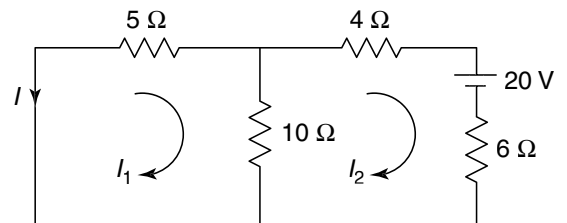**Fig. 3.447**

Since the current I remains the same in both the cases, reciprocity theorem is verified.

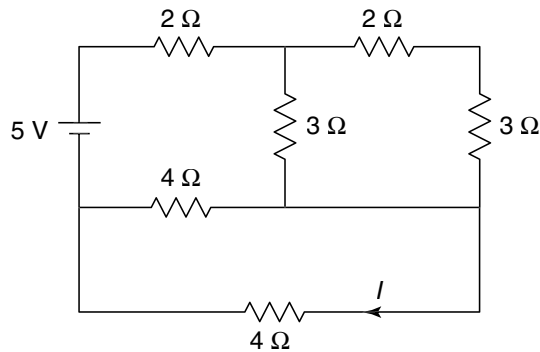Example 3.101Find the current I and verify reciprocity theorem for the network shown in Fig. 3.446.**Fig. 3.448****Solution****Case I** Calculation of the current I when excitation and response are not interchanged (Fig. 3.449)

Applying KVL to Mesh 1,

$$5 - 2I_1 - 3(I_1 - I_2) - 4(I_1 - I_3) = 0$$

$$9I_1 - 3I_2 - 4I_3 = 5 \quad \dots(i)$$

Applying KVL to Mesh 2,

$$-3(I_2 - I_1) - 2I_2 - 3I_2 = 0$$

$$-3I_1 + 8I_2 = 0 \quad \dots(ii)$$

Applying KVL to Mesh 3,

$$-4(I_3 - I_1) - 4I_3 = 0$$

$$-4I_1 + 8I_3 = 0 \quad \dots(iii)$$

Solving Eqs (i), (ii) and (iii),

$$I_1 = 0.85 \text{ A}$$

$$I_2 = 0.32 \text{ A}$$

$$I_3 = 0.43 \text{ A}$$

$$I = I_3 = 0.43 \text{ A}$$

Case II Calculation of current I when excitation and response are interchanged (Fig. 3.450).

Applying KVL to Mesh 1,



$$-2I_1 - 3(I_1 - I_2) - 4(I_1 - I_3) = 0$$

$$9I_1 - 3I_2 - 4I_3 = 0 \quad \dots(i)$$

Applying KVL to Mesh 2,

$$-3(I_2 - I_1) - 2I_2 - 3I_2 = 0$$

$$-3I_1 + 8I_2 = 0 \quad \dots(ii)$$

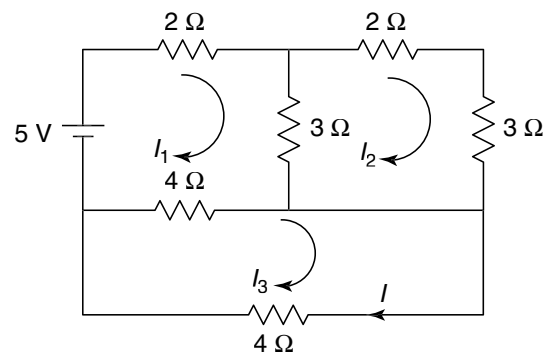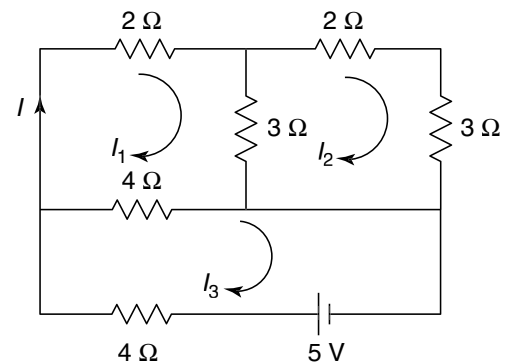**Fig. 3.449****Fig. 3.450**

Applying KVL to Mesh 3,

$$-4(I_3 - I_1) + 5 - 4I_3 = 0$$

$$-4I_1 + 8I_3 = 5 \quad \dots(\text{iii})$$

Solving Eqs (i), (ii) and (iii),

$$I_1 = 0.43 \text{ A}$$

$$I_2 = 0.16 \text{ A}$$

$$I_3 = 0.84 \text{ A}$$

$$I = I_1 = 0.43 \text{ A}$$

Since the current I remains the same in both the cases, reciprocity theorem is verified.

Example 3.102 Find the voltage V and verify reciprocity theorem for the network shown in Fig. 3.451.

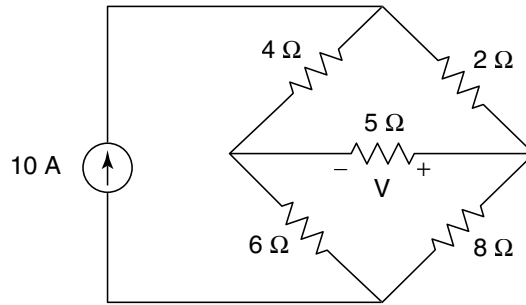


Fig. 3.451

Solution

Case I Calculation of the voltage V when excitation and response are not interchanged (Fig. 3.451)

For Mesh 1,

$$I_1 = 10 \quad \dots(\text{i})$$

Applying KVL to Mesh 2,

$$-4(I_2 - I_1) - 2I_2 - 5(I_2 - I_3) = 0$$

$$-4I_1 + 11I_2 - 5I_3 = 0 \quad \dots(\text{ii})$$

Applying KVL to Mesh 3,

$$-6(I_3 - I_1) - 5(I_3 - I_2) - 8I_3 = 0$$

$$-6I_1 - 5I_2 + 19I_3 = 0 \quad \dots(\text{iii})$$

Solving Eqs (i), (ii) and (iii),

$$I_1 = 10 \text{ A}$$

$$I_2 = 5.76 \text{ A}$$

$$I_3 = 4.67 \text{ A}$$

$$V = 5(I_2 - I_3) = 5(5.76 - 4.67) = 5.45 \text{ V}$$

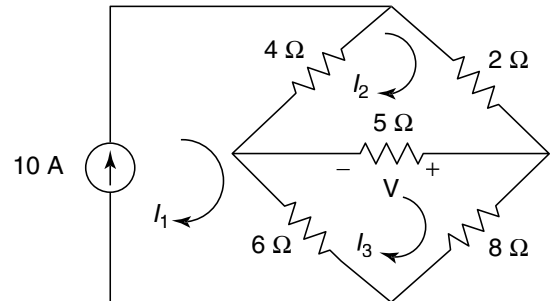


Fig. 3.452

Case II Calculation of voltage V when excitation and response are interchanged (Fig. 3.453).

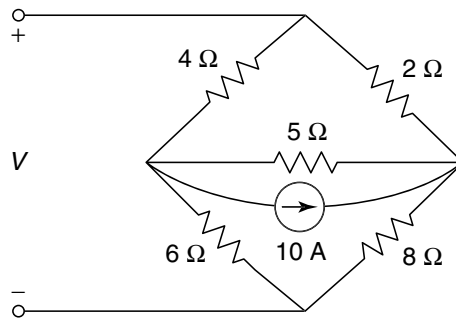


Fig. 3.453

By source transformation (Fig. 3.454),

Applying KVL to Mesh 1,

$$\begin{aligned} -4I_1 - 2I_1 - 50 - 5(I_1 - I_2) &= 0 \\ 11I_1 - 5I_2 &= -50 \quad \dots(i) \end{aligned}$$

Applying KVL to Mesh 2,

$$\begin{aligned} -6I_2 - 5(I_2 - I_1) + 50 - 8I_2 &= 0 \\ -5I_1 + 19I_2 &= 50 \quad \dots(ii) \end{aligned}$$

Solving Eqs (i) and (ii),

$$I_1 = -3.8 \text{ A}$$

$$I_2 = 1.63 \text{ A}$$

From Fig. 3.454,

$$V + 4I_1 + 6I_2 = 0$$

$$V + 4(-3.8) + 6(1.63) = 0$$

$$V = 5.42 \text{ V}$$

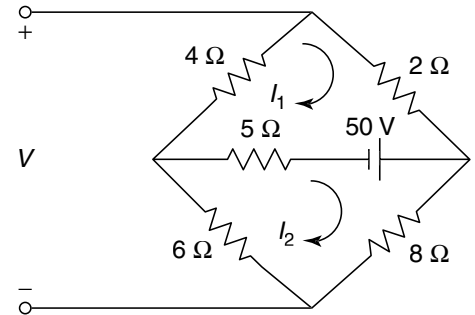


Fig. 3.454

Since the voltage V is same in both the cases, the reciprocity theorem is verified.

3.7 MILLMAN'S THEOREM

It states that 'if there are n voltage sources $V_1, V_2, \dots, V_n$ with internal resistances $R_1, R_2, \dots, R_n$ respectively connected in parallel then these voltage sources can be replaced by a single voltage source V_m and a single series resistance R_m ', (Fig. 3.455).

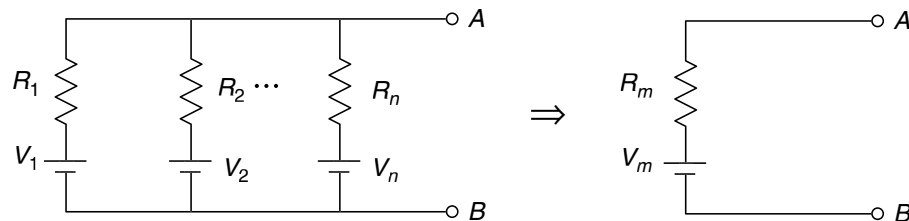


Fig. 3.455 Millman's network

where

$$V_m = \frac{V_1 G_1 + V_2 G_2 + \dots + V_n G_n}{G_1 + G_2 + \dots + G_n}$$

Exercises

Superposition Theorem

- 3.1 Find the current through the $10\ \Omega$ resistor in Fig. 3.490.

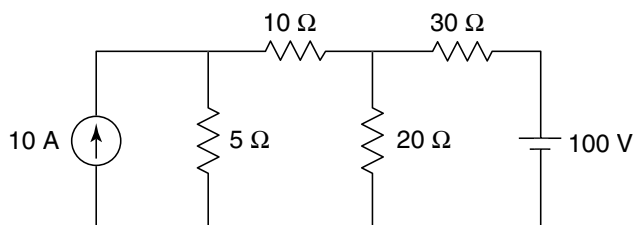


Fig. 3.490

[0.37 A]

- 3.2 Find the current through the $8\ \Omega$ resistor in Fig. 3.491.

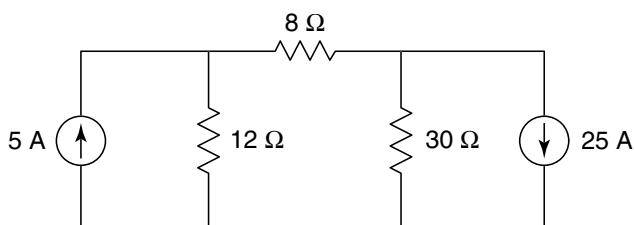


Fig. 3.491

[16.2 A]

- 3.3 Find the potential across the $3\ \Omega$ resistor in Fig. 3.492.

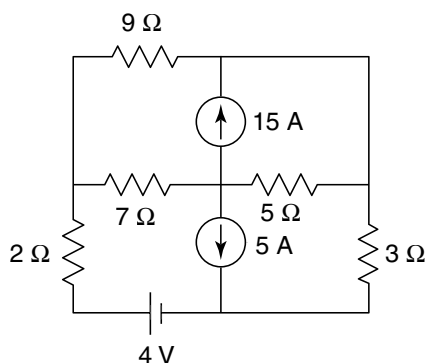


Fig. 3.492

[3.3 V]

- 3.4 Calculate the current through the $10\ \Omega$ resistor in Fig. 3.493.

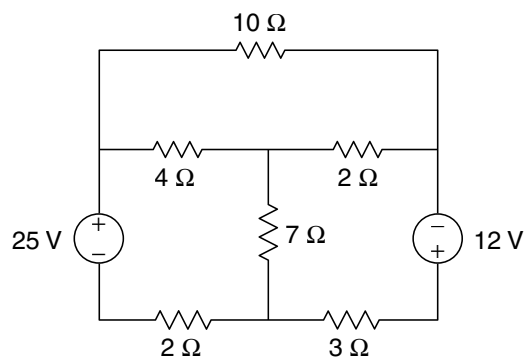


Fig. 3.493

[1.62 A]

- 3.5 Find the current through the $1\ \Omega$ resistor in Fig. 3.494.

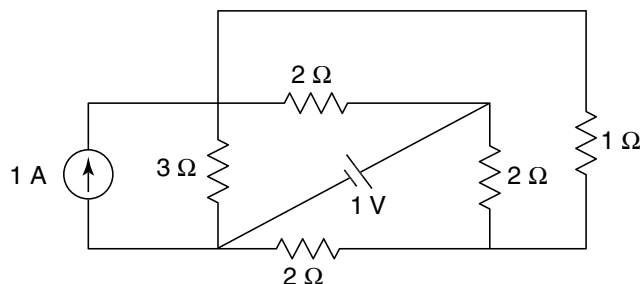


Fig. 3.494

[0.41 A]

- 3.6 Find the current through the $4\ \Omega$ resistor in Fig. 3.495.

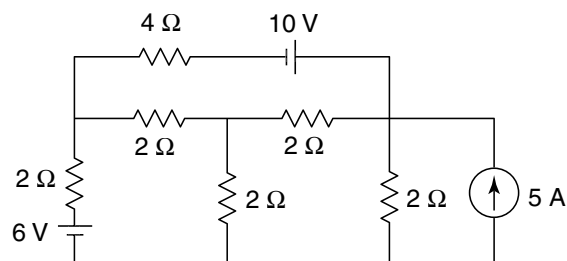


Fig. 3.495

[1.33 A]

3.7 Find the current I_x in Fig. 3.496.

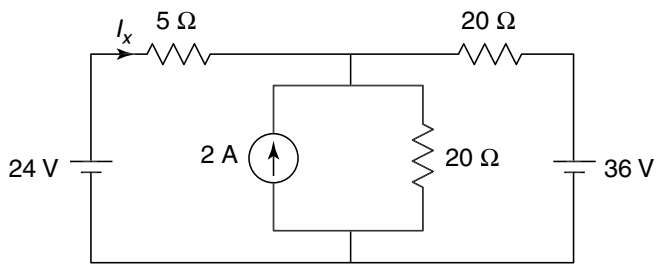


Fig. 3.496

[−1.143 A]

3.8 Find the voltage V_x in Fig. 3.497.

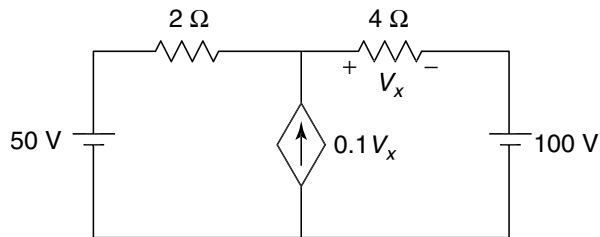


Fig. 3.497

[−38.5 V]

3.9 Determine the voltages V_1 and V_2 in Fig. 3.498.

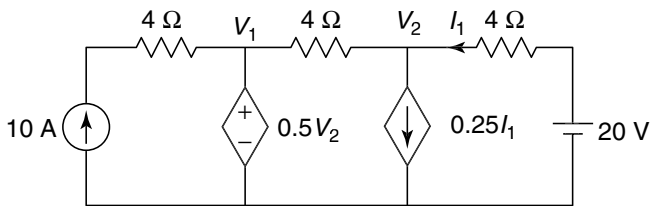


Fig. 3.498

[6 V, 12 V]

3.10 Find the voltage V_x in Fig. 3.499.

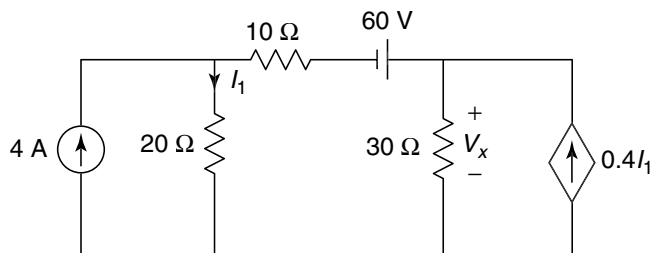


Fig. 3.499

[7.5 V]

Thevenin's Theorem

3.11 Find the current through the 5 Ω resistor in Fig. 3.500.

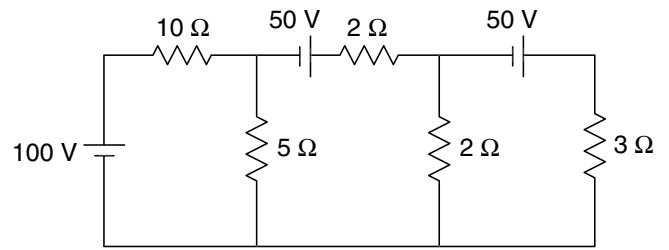


Fig. 3.500

[3.87 A]

3.12 Find the current through the 6 Ω resistor in Fig. 3.501.

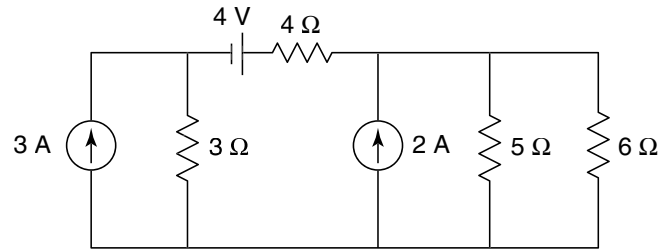


Fig. 3.501

[1.26 A]

3.13 Find the current through the 6 Ω resistor in Fig. 3.502.

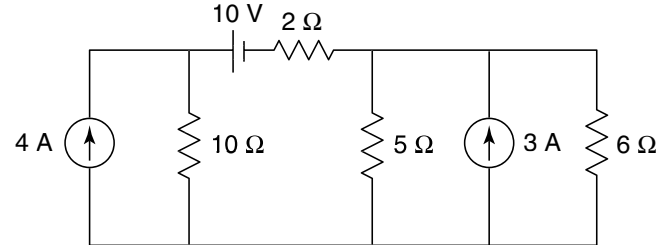


Fig. 3.502

[2.04 A]

3.14 Find the current through the 2 Ω resistor connected between terminals A and B in Fig. 3.503.

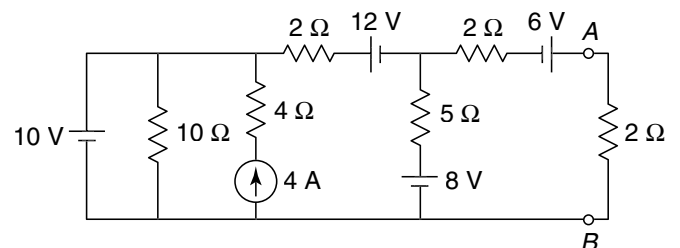


Fig. 3.503

[1.26 A]

3.15 Find the current through the $5\ \Omega$ resistor in Fig. 3.504.

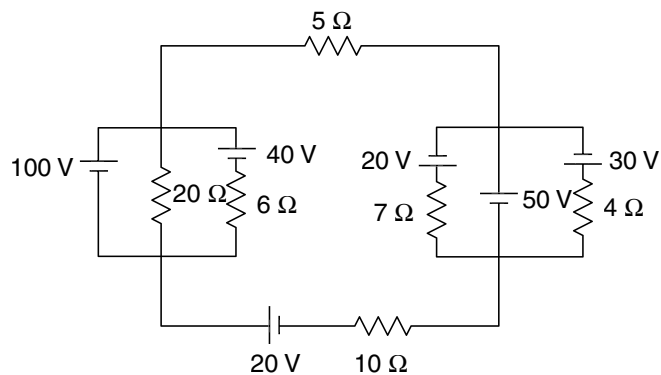


Fig. 3.504

3.16 Find the current through the $20\ \Omega$ resistor in Fig. 3.505.

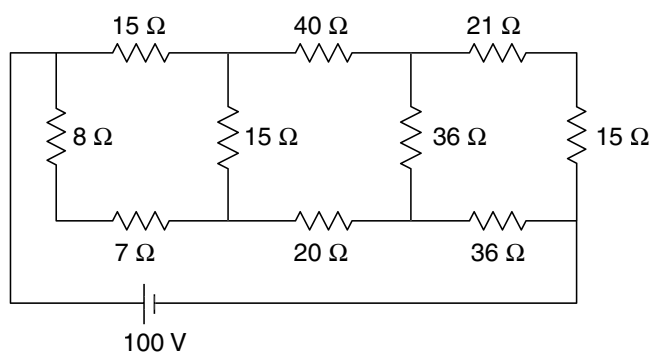


Fig. 3.505

3.17 Calculate the current through the $10\ \Omega$ resistor in Fig. 3.506.

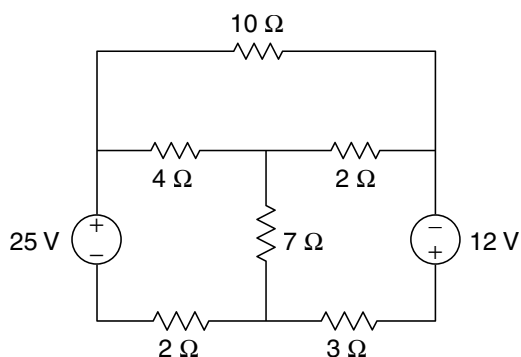


Fig. 3.506

3.18 Determine Thevenin's equivalent network for figures 3.507 to 3.510 shown below.

(i)

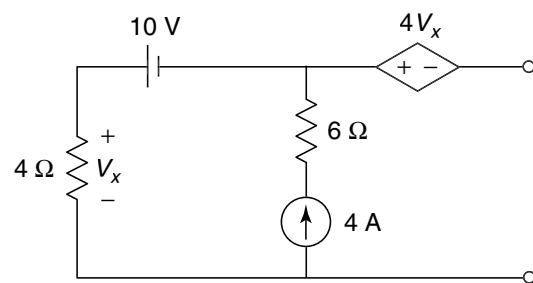


Fig. 3.507

$[-58\text{ V}, 12\ \Omega]$

(ii)

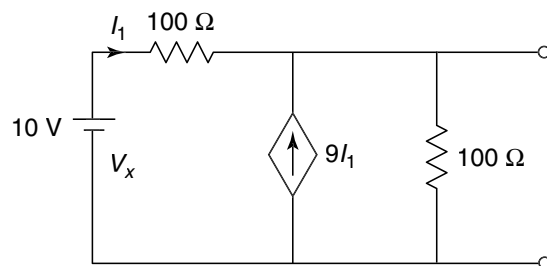


Fig. 3.508

$[9.09\text{ V}, 9.09\ \Omega]$

(iii)

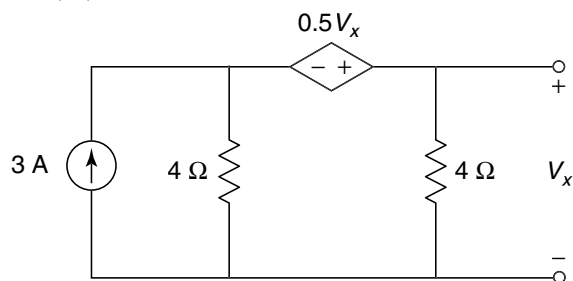


Fig. 3.509

$[8\text{ V}, 2.66\ \Omega]$

(iv)

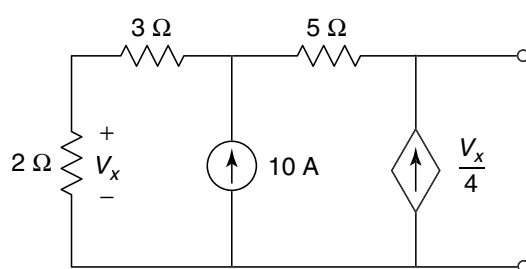


Fig. 3.510

$[150\text{ V}, 20\ \Omega]$

$[1.62\text{ A}]$

3.19 Find the current I_x in Fig. 3.511.

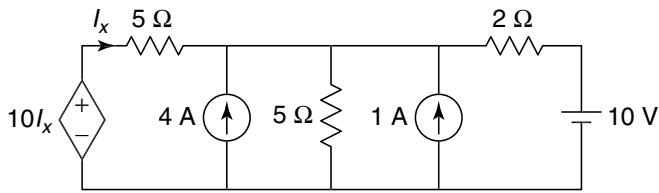


Fig. 3.511

[4 A]

3.20 Find the current in the 24 Ω resistor in Fig. 3.512.

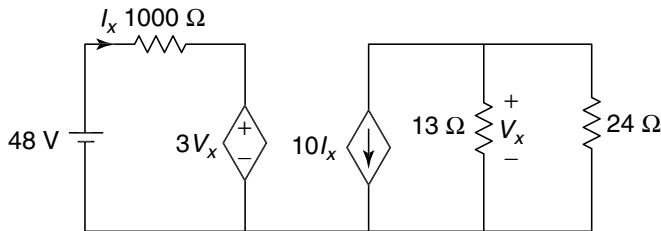


Fig. 3.512

[0.225 A]

Norton's Theorem

3.21 Find the current through the 10 Ω resistor in Fig. 3.513.

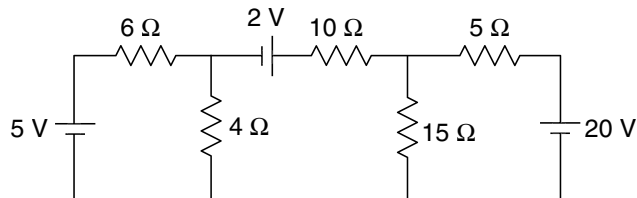


Fig. 3.513

[0.68 A]

3.22 Find the current through the 20 Ω resistor in Fig. 3.514.

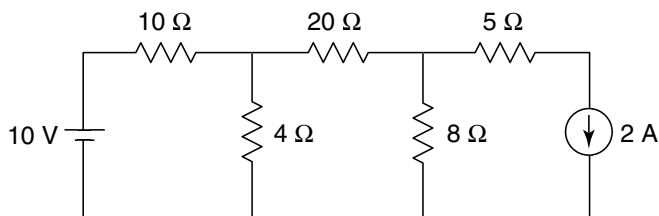


Fig. 3.514

[0.61 A]

3.23 Find the current through the 2 Ω resistor in Fig. 3.515.

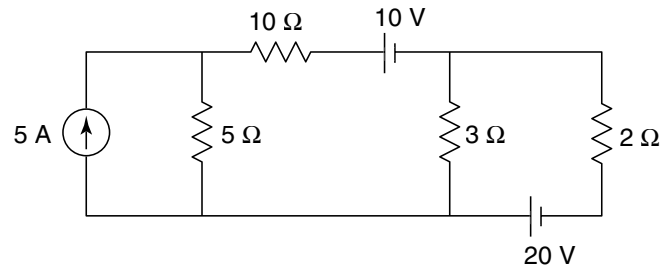


Fig. 3.515

[5 A]

3.24 Find the current through the 5 Ω resistor in Fig. 3.516.

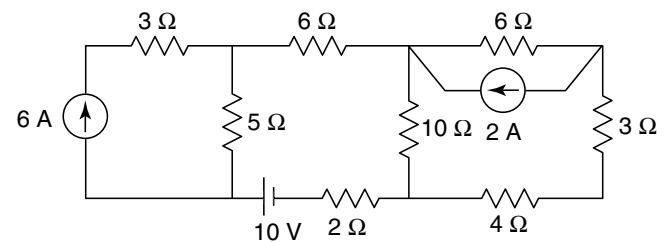


Fig. 3.516

[4.13 A]

3.25 Find Norton's equivalent circuit for the portion of network shown in Fig. 3.517 to the left of ab . Hence obtain the current in the 10 Ω resistor.

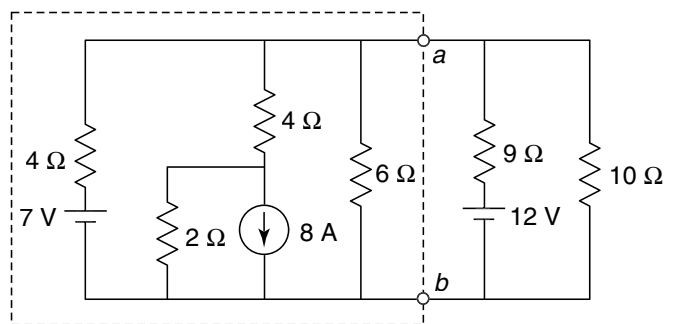


Fig. 3.517

[0.053 A]

3.26 Find Norton's equivalent network and hence find the current in the 10 Ω resistor in Fig. 3.518.

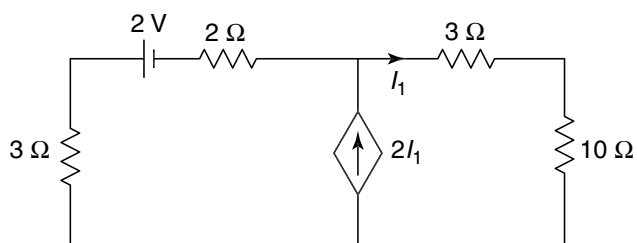


Fig. 3.518

[0.25 A]

3.27 Find Norton's equivalent network in Fig. 3.519.

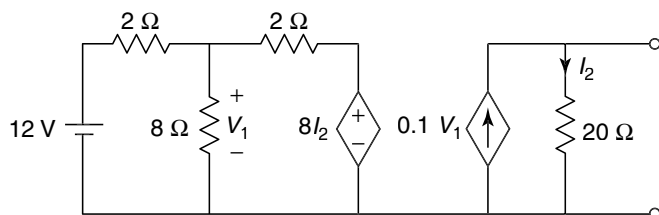


Fig. 3.519

[0.533 A, 31 W]

Maximum Power Transfer Theorem

3.28 Find the value of the resistance R_L in Fig. 3.520 for maximum power transfer and calculate the maximum power.

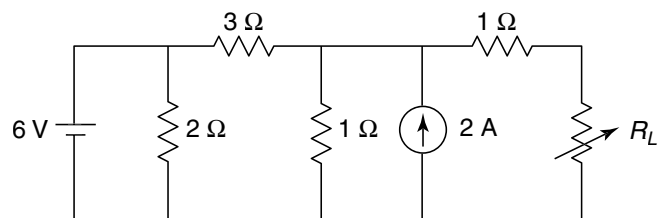


Fig. 3.520

[1.75 Ω, 1.29 W]

3.29 Find the value of the resistance R_L in Fig. 3.521 for maximum power transfer and calculate the maximum power.

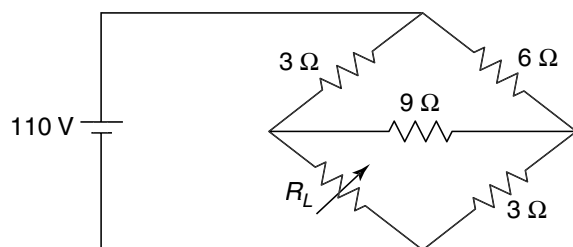


Fig. 3.521

[2.36 Ω, 940 W]

3.30 Find the value of the resistance R_L in Fig. 3.522 for maximum power transfer and calculate the maximum power.

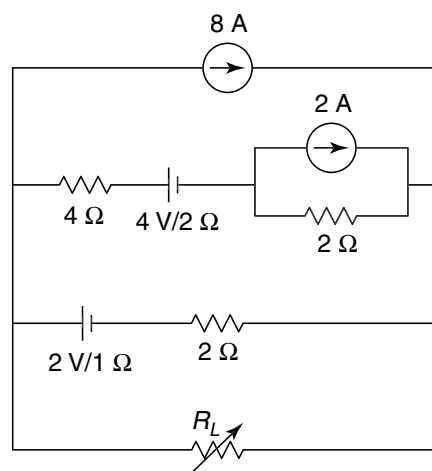


Fig. 3.522

[2.18 Ω, 29.35 W]

3.31 Find the value of the resistance R_L in Fig. 3.523 for maximum power transfer and calculate the maximum power.

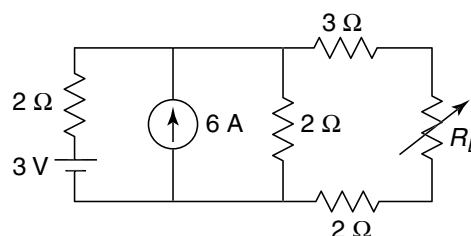


Fig. 3.523

[3 Ω, 2.52 W]

3.32 Find the value of the resistance R_L in Fig. 3.524 for maximum power transfer and calculate the maximum power.

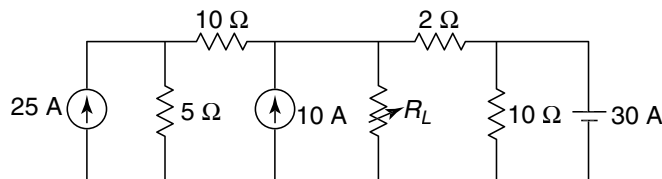


Fig. 3.524

[1.76 Ω, 490.187 W]

Objective-Type Questions

- 3.1 The value of the resistance R connected across the terminals A and B in Fig. 3.525, which will absorb the maximum power is

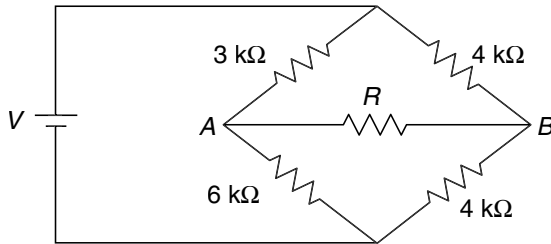


Fig. 3.525

- 3.2 Superposition theorem is not applicable to networks containing

- (a) nonlinear elements
- (b) dependent voltage source
- (c) dependent current source
- (d) transformers

- 3.3 The value of R required for maximum power transfer in the network shown in Fig. 3.526 is

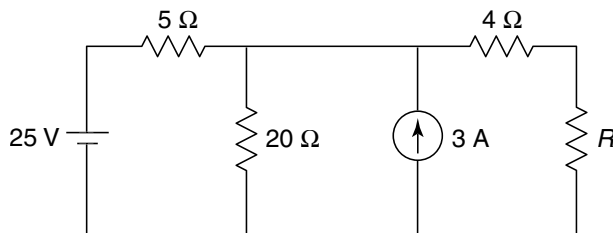


Fig. 3.526

- (a) $2\ \Omega$ (b) $4\ \Omega$ (c) $8\ \Omega$ (d) $16\ \Omega$
- 3.4 In the network of Fig. 3.527, the maximum power is delivered to R_L if its value is

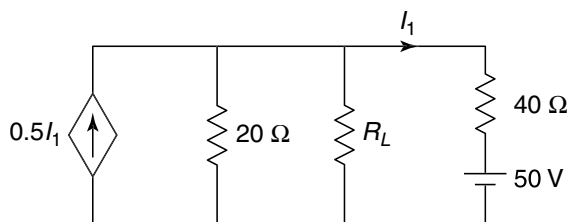


Fig. 3.527

- (a) $16\ \Omega$
- (b) $\frac{40}{3}\ \Omega$
- (c) $60\ \Omega$
- (d) $20\ \Omega$

- 3.5 The maximum power that can be transferred to the load R_L from the voltage source in Fig. 3.528 is

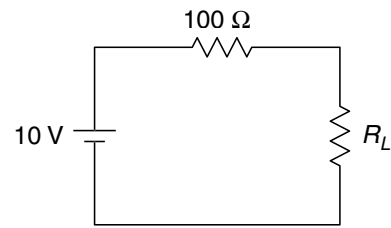


Fig. 3.528

- (a) 1 W
- (b) 10 W
- (c) 0.25 W
- (d) 0.5 W

- 3.6 For the circuit shown in Fig. 3.529, Thevenin's voltage and Thevenin's equivalent resistance at terminals $a-b$ is

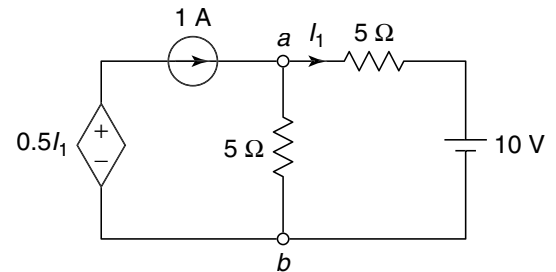


Fig. 3.529

- (a) 5 V and $2\ \Omega$
- (b) 7.5 V and $2.5\ \Omega$
- (c) 4 V and $2\ \Omega$
- (d) 3 V and $2.5\ \Omega$

- 3.7 The value of R_L in Fig. 3.530 for maximum power transfer is

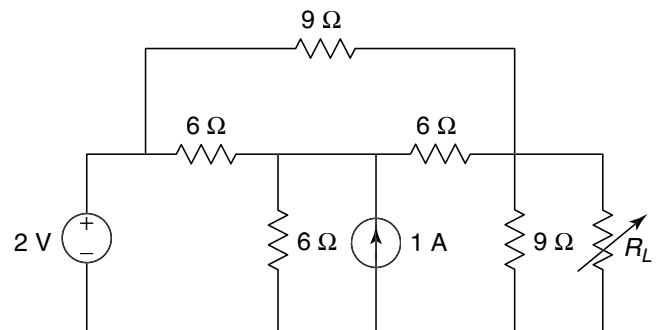


Fig. 3.530

- (a) $3\ \Omega$
- (b) $1.125\ \Omega$
- (c) $4.1785\ \Omega$
- (d) none of these

Network Theorems (Application to ac Circuits)

6.1 || INTRODUCTION

We have discussed the network theorems with reference to resistive load and dc sources. Now, all the theorems will be discussed when a network consists of ac sources, resistors, inductors and capacitors. All the theorems are also valid for ac sources.

6.2 || MESH ANALYSIS

Mesh analysis is useful if a network has a large number of voltage sources. In this method, currents are assigned in each mesh. We can write mesh equations by Kirchhoff's voltage law in terms of unknown mesh currents,

Example 6.1

Find mesh currents I_1 and I_2 in the network of Fig. 6.1.

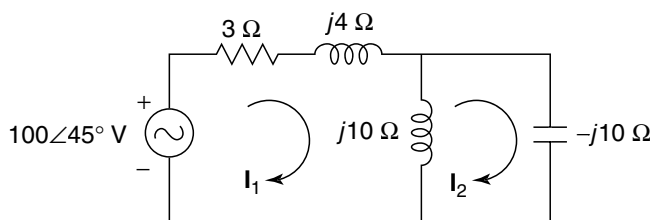


Fig. 6.1

Solution Applying KVL to Mesh 1,

$$100\angle 45^\circ - (3 + j4)I_1 - j10(I_1 - I_2) = 0$$

$$(3 + j14)I_1 - j10I_2 = 100\angle 45^\circ \quad \dots(i)$$

Applying KVL to Mesh 2,

$$-j10(I_2 - I_1) + j10(I_2) = 0$$


$$j10I_1 = 0 \quad \dots(ii)$$

$$I_1 = 0$$

Substituting I_1 in Eq. (i),

$$-j10I_2 = 100\angle 45^\circ$$

$$I_2 = \frac{100\angle 45^\circ}{-j10} = 10\angle 135^\circ \text{ A}$$

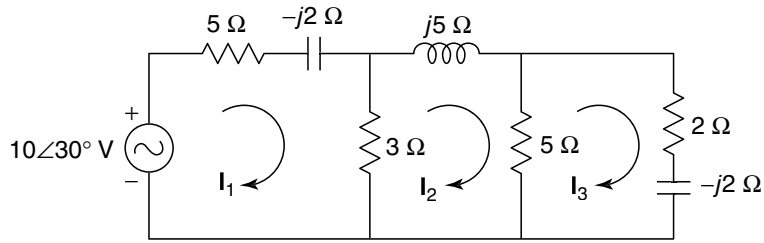Example 6.2Find mesh current $\mathbf{I}_1$, $\mathbf{I}_2$ and $\mathbf{I}_3$ in the network of Fig. 6.2.**Fig. 6.2****Solution** Applying KVL to Mesh 1,

$$10 \angle 30^\circ - (5 - j2) \mathbf{I}_1 - 3(\mathbf{I}_1 - \mathbf{I}_2) = 0$$

$$(8 - j2) \mathbf{I}_1 - 3 \mathbf{I}_2 = 10 \angle 30^\circ \quad \dots (i)$$

Applying KVL to Mesh 2,

$$-3(\mathbf{I}_2 - \mathbf{I}_1) - j5 \mathbf{I}_2 - 5(\mathbf{I}_2 - \mathbf{I}_3) = 0$$

$$-3 \mathbf{I}_1 + (8 + j5) \mathbf{I}_2 - 5 \mathbf{I}_3 = 0 \quad \dots (ii)$$

Applying KVL to Mesh 3,

$$-5(\mathbf{I}_3 - \mathbf{I}_2) - (2 - j2) \mathbf{I}_3 = 0$$

$$-5 \mathbf{I}_2 + (7 - j2) \mathbf{I}_3 = 0 \quad \dots (iii)$$

Writing Eqs (i), (ii) and (iii),

$$\begin{bmatrix} 8 - j2 & -3 & 0 \\ -3 & 8 + j5 & -5 \\ 0 & -5 & 7 - j2 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 10 \angle 30^\circ \\ 0 \\ 0 \end{bmatrix}$$

By Cramer's rule,

$$\mathbf{I}_1 = \frac{\begin{vmatrix} 10 \angle 30^\circ & -3 & 0 \\ 0 & 8 + j5 & -5 \\ 0 & -5 & 7 - j2 \end{vmatrix}}{\begin{vmatrix} 8 - j2 & -3 & 0 \\ -3 & 8 + j5 & -5 \\ 0 & -5 & 7 - j2 \end{vmatrix}} = 1.43 \angle 38.7^\circ \text{ A}$$

$$\mathbf{I}_2 = \frac{\begin{vmatrix} 8 - j2 & 10 \angle 30^\circ & 0 \\ -3 & 0 & -5 \\ 0 & 0 & 7 - j2 \end{vmatrix}}{\begin{vmatrix} 8 - j2 & -3 & 0 \\ -3 & 8 + j5 & -5 \\ 0 & -5 & 7 - j2 \end{vmatrix}} = 0.693 \angle -2.2^\circ \text{ A}$$

$$\mathbf{I}_3 = \frac{\begin{vmatrix} 8 - j2 & -3 & 10 \angle 30^\circ \\ -3 & 8 + j5 & 0 \\ 0 & -5 & 0 \end{vmatrix}}{\begin{vmatrix} 8 - j2 & -3 & 0 \\ -3 & 8 + j5 & -5 \\ 0 & -5 & 7 - j2 \end{vmatrix}} = 0.476 \angle 13.8^\circ \text{ A}$$

Example 6.3 In the network of Fig. 6.3, find the value of V_2 so that the current through $(2 + j3)$ ohm impedance is zero.

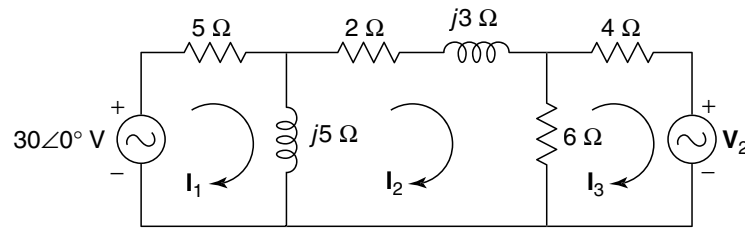


Fig. 6.3

Solution Applying KVL to Mesh 1,

$$\begin{aligned} 30\angle 0^\circ - 5\mathbf{I}_1 - j5(\mathbf{I}_1 - \mathbf{I}_2) &= 0 \\ (5 + j5)\mathbf{I}_1 - j5\mathbf{I}_2 &= 30\angle 0^\circ \end{aligned} \quad \dots(i)$$

Applying KVL to Mesh 2,

$$\begin{aligned} -j5(\mathbf{I}_2 - \mathbf{I}_1) - (2 + j3)\mathbf{I}_2 - 6(\mathbf{I}_2 - \mathbf{I}_3) &= 0 \\ -j5\mathbf{I}_1 + (8 + j8)\mathbf{I}_2 - 6\mathbf{I}_3 &= 0 \end{aligned} \quad \dots(ii)$$

Applying KVL to Mesh 3,

$$\begin{aligned} -6(\mathbf{I}_3 - \mathbf{I}_2) - 4\mathbf{I}_3 - \mathbf{V}_2 &= 0 \\ -6\mathbf{I}_2 + 10\mathbf{I}_3 &= -\mathbf{V}_2 \end{aligned} \quad \dots(iii)$$

Writing Eqs (i), (ii) and (iii) in matrix form,

$$\begin{bmatrix} 5 + j5 & -j5 & 0 \\ -j5 & 8 + j8 & -6 \\ 0 & -6 & 10 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 30\angle 0^\circ \\ 0 \\ -\mathbf{V}_2 \end{bmatrix}$$

By Cramer's rule,

$$\begin{aligned} \mathbf{I}_2 &= \frac{\begin{vmatrix} 5 + j5 & 30\angle 0^\circ & 0 \\ -j5 & 0 & -6 \\ 0 & -\mathbf{V}_2 & 10 \end{vmatrix}}{\begin{vmatrix} 5 + j5 & -j5 & 0 \\ -j5 & 8 + j8 & -6 \\ 0 & -6 & 10 \end{vmatrix}} = 0 \\ (5 + j5)(-6\mathbf{V}_2) - (30)(-j50) &= 0 \\ \mathbf{V}_2 &= \frac{j1500}{30 + j30} = 35.36\angle 45^\circ \text{ V} \end{aligned}$$

Example 6.4 Find the value of the current $\mathbf{I}_3$ in the network shown in Fig. 6.4.

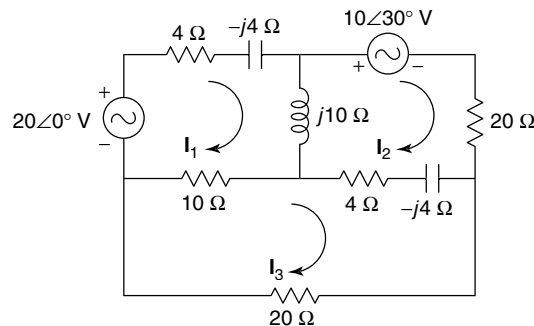


Fig. 6.4

6.4 Network Analysis and Synthesis

Solution Applying KVL to Mesh 1,

$$\begin{aligned} 20\angle 0^\circ - (4 - j4)\mathbf{I}_1 - j10(\mathbf{I}_1 - \mathbf{I}_2) - 10(\mathbf{I}_1 - \mathbf{I}_3) &= 0 \\ (14 + j6)\mathbf{I}_1 - j10\mathbf{I}_2 - 10\mathbf{I}_3 &= 20\angle 0^\circ \end{aligned} \quad \dots (i)$$

Applying KVL to Mesh 2,

$$\begin{aligned} -j10(\mathbf{I}_2 - \mathbf{I}_1) - 10\angle 30^\circ - 20\mathbf{I}_2 - (4 - j4)(\mathbf{I}_2 - \mathbf{I}_3) &= 0 \\ -j10\mathbf{I}_1 + (24 + j6)\mathbf{I}_2 - (4 - j4)\mathbf{I}_3 &= -10\angle 30^\circ \end{aligned} \quad \dots (ii)$$

Applying KVL to Mesh 3,

$$\begin{aligned} -10(\mathbf{I}_3 - \mathbf{I}_1) - (4 - j4)(\mathbf{I}_3 - \mathbf{I}_2) - 20\mathbf{I}_3 &= 0 \\ -10\mathbf{I}_1 - (4 - j4)\mathbf{I}_2 + (34 - j4)\mathbf{I}_3 &= 0 \end{aligned} \quad \dots (iii)$$

Writing Eqs (i), (ii) and (iii) in matrix form,

$$\begin{bmatrix} 14 + j6 & -j10 & -10 \\ -j10 & 24 + j6 & -(4 - j4) \\ -10 & -(4 - j4) & 34 - j4 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 20\angle 0^\circ \\ -10\angle 30^\circ \\ 0 \end{bmatrix}$$

By Cramer's rule,

$$\mathbf{I}_3 = \frac{\begin{vmatrix} 14 + j6 & -j10 & 20\angle 0^\circ \\ -j10 & 24 + j6 & -10\angle 30^\circ \\ -10 & -(4 - j4) & 0 \end{vmatrix}}{\begin{vmatrix} 14 + j6 & -10 & -10 \\ -j10 & 24 + j6 & -(4 - j4) \\ -10 & -(4 - j4) & 34 - j4 \end{vmatrix}} = 0.44\angle -14^\circ \text{ A}$$

Example 6.5

Find the voltage V_{AB} in the network of Fig. 6.5.

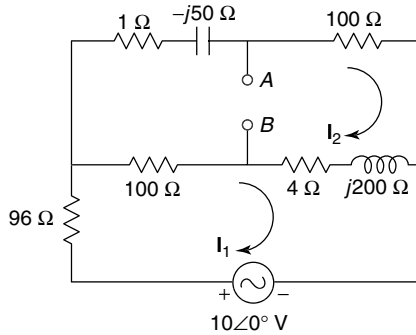


Fig. 6.5

Solution Applying KVL to Mesh 1,

$$\begin{aligned} -96\mathbf{I}_1 - (100 + 4 + j200)(\mathbf{I}_1 - \mathbf{I}_2) + 10\angle 0^\circ &= 0 \\ (200 + j200)\mathbf{I}_1 - (104 + j200)\mathbf{I}_2 &= 10\angle 0^\circ \end{aligned} \quad \dots (i)$$

Applying KVL to Mesh 2,

$$\begin{aligned} -(1 - j50 - 100)\mathbf{I}_2 - (100 + 4 + j200)(\mathbf{I}_2 - \mathbf{I}_1) &= 0 \\ -(104 + j200)\mathbf{I}_1 + (205 + j150)\mathbf{I}_2 &= 0 \end{aligned} \quad \dots (ii)$$

Writing Eqs (i) and (ii) in matrix form,

$$\begin{bmatrix} 200 + j200 & -(104 + j200) \\ -(104 + j200) & 205 + j150 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 10\angle 0^\circ \\ 0 \end{bmatrix}$$

By Cramer's rule,

$$\mathbf{I}_1 = \frac{\begin{vmatrix} 10\angle 0^\circ & -(104 + j200) \\ 0 & 205 + j150 \end{vmatrix}}{\begin{vmatrix} 200 + j200 & -(104 + j200) \\ -(104 + j200) & 205 + j150 \end{vmatrix}} = 0.051\angle 2.72 \times 10^{-3} \text{ }^\circ \text{ A}$$

$$\mathbf{I}_2 = \frac{\begin{vmatrix} 200 + j200 & 10\angle 0^\circ \\ -(104 + j200) & 0 \end{vmatrix}}{\begin{vmatrix} 200 + j200 & -(104 + j200) \\ -(104 + j200) & 205 + j150 \end{vmatrix}} = 0.045\angle 26.34^\circ \text{ A}$$

$$\begin{aligned} \mathbf{V}_{AB} &= 100\mathbf{I}_2 - (4 + j200)(\mathbf{I}_1 - \mathbf{I}_2) \\ &= 100(0.045\angle 26.34^\circ) - (4 + j200)(0.051\angle 2.72 \times 10^{-3} \text{ }^\circ - 0.045\angle 26.34^\circ) \\ &= 0.058\angle -92.65^\circ \text{ V} \end{aligned}$$

Example 6.6

For the network shown in Fig. 6.6, find the voltage across the capacitor.

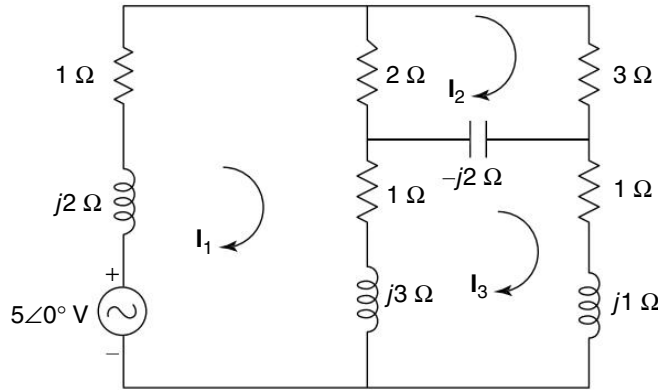


Fig. 6.6

Solution Applying KVL to Mesh 1,

$$\begin{aligned} 5\angle 0^\circ - (1 + j2)\mathbf{I}_1 - 2(\mathbf{I}_1 - \mathbf{I}_2) - (1 + j3)(\mathbf{I}_1 - \mathbf{I}_3) &= 0 \\ (4 + j5)\mathbf{I}_1 - 2\mathbf{I}_2 - (1 + j3)\mathbf{I}_3 &= 5\angle 0^\circ \end{aligned} \quad \dots(i)$$

Applying KVL to Mesh 2,

$$\begin{aligned} -2(\mathbf{I}_2 - \mathbf{I}_1) - 3\mathbf{I}_2 + j2(\mathbf{I}_2 - \mathbf{I}_3) &= 0 \\ -2\mathbf{I}_1 + (5 - j2)\mathbf{I}_2 + j2\mathbf{I}_3 &= 0 \end{aligned} \quad \dots(ii)$$

Applying KVL to Mesh 3,

$$\begin{aligned} -(1 + j3)(\mathbf{I}_3 - \mathbf{I}_1) + j2(\mathbf{I}_3 - \mathbf{I}_2) - (1 + j1)\mathbf{I}_3 &= 0 \\ -(1 + j3)\mathbf{I}_1 + j2\mathbf{I}_2 + (2 + j2)\mathbf{I}_3 &= 0 \end{aligned} \quad \dots(iii)$$

Writing Eqs (i), (ii) and (iii) in matrix form,

$$\begin{bmatrix} 4 + j5 & -2 & -(1 + j3) \\ -2 & 5 - j2 & j2 \\ -(1 + j3) & j2 & 2 + j2 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 5\angle 0^\circ \\ 0 \\ 0 \end{bmatrix}$$

6.6 Network Analysis and Synthesis

By Cramer's rule,

$$\mathbf{I}_2 = \frac{\begin{vmatrix} 4+j5 & 5\angle 0^\circ & -(1+j3) \\ -2 & 0 & j2 \\ -(1+j3) & 0 & 2+j2 \end{vmatrix}}{\begin{vmatrix} 4+j5 & -2 & -(1+j3) \\ -2 & 5-j2 & j2 \\ -(1+j3) & j2 & 2+j2 \end{vmatrix}} = 0.65\angle 130.51^\circ \text{ A}$$

$$\mathbf{I}_3 = \frac{\begin{vmatrix} 4+j5 & -2 & 5\angle 0^\circ \\ -2 & 5-j2 & 0 \\ -(1+j3) & j2 & 0 \end{vmatrix}}{\begin{vmatrix} 4+j5 & -2 & -(1+j3) \\ -2 & 5-j2 & j2 \\ -(1+j3) & j2 & 2+j2 \end{vmatrix}} = 0.91\angle -21.51^\circ \text{ A}$$

$$\mathbf{V}_c = (-j2)(\mathbf{I}_3 - \mathbf{I}_2) = (-j2)(0.91\angle -21.51^\circ - 0.65\angle 130.51^\circ) = 3.03\angle -123.12^\circ \text{ V}$$

Example 6.7

Find the voltage across the $2\ \Omega$ resistor in the network of Fig. 6.7.

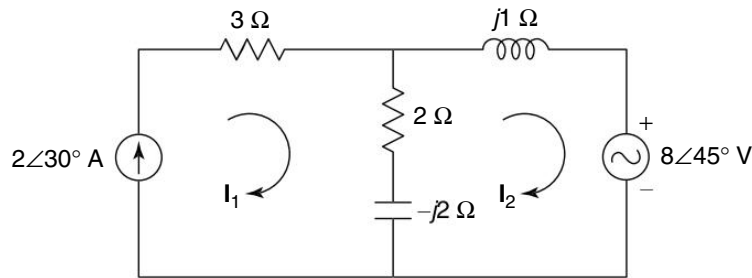


Fig. 6.7

Solution For Mesh 1,

$$\mathbf{I}_1 = 2\angle 30^\circ \quad \dots(i)$$


Applying KVL to Mesh 2,

$$\begin{aligned} -(2-j2)(\mathbf{I}_2 - \mathbf{I}_1) - j1\mathbf{I}_2 - 8\angle 45^\circ &= 0 \\ (2-j2)\mathbf{I}_1 - (2-j1)\mathbf{I}_2 &= 8\angle 45^\circ \quad \dots(ii) \end{aligned}$$

Substituting $\mathbf{I}_1$ in Eq. (i),

$$\begin{aligned} (2-j2)(2\angle 30^\circ) - (2-j1)\mathbf{I}_2 &= 8\angle 45^\circ \\ \mathbf{I}_2 &= \frac{-(8\angle 45^\circ) + (2-j2)(2\angle 30^\circ)}{2-j1} = 3.19\angle -65^\circ \text{ A} \end{aligned}$$

$$\mathbf{V}_{2\Omega} = 2(\mathbf{I}_1 - \mathbf{I}_2) = 2(2\angle 30^\circ - 3.19\angle -65^\circ) = 7.82\angle 84.37^\circ \text{ V}$$

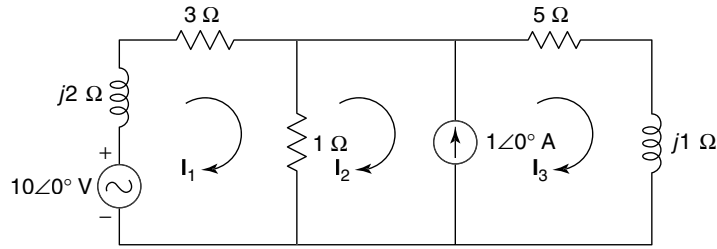Example 6.8Find the current through $3\ \Omega$ resistor in the network of Fig. 6.8.**Fig. 6.8****Solution** Applying KVL to Mesh 1,

$$10\angle 0^\circ - j2\mathbf{I}_1 - 3\mathbf{I}_1 - 1(\mathbf{I}_1 - \mathbf{I}_2) = 0$$

$$(4 + j2)\mathbf{I}_1 - \mathbf{I}_2 = 10\angle 0^\circ \quad \dots(i)$$

Meshes 2 and 3 will form a supermesh.

Writing current equation for the supermesh,

$$\mathbf{I}_3 - \mathbf{I}_2 = 1\angle 0^\circ \quad \dots(ii)$$

Applying KVL to the outer path of the supermesh,

$$-1(\mathbf{I}_2 - \mathbf{I}_1) - 5\mathbf{I}_3 - j1\mathbf{I}_3 = 0$$

$$\mathbf{I}_1 - \mathbf{I}_2 - (5 + j1)\mathbf{I}_3 = 0 \quad \dots(iii)$$


Writing Eqs (i), (ii) and (iii) in matrix form,

$$\begin{bmatrix} 4 + j2 & -1 & 0 \\ 0 & -1 & 1 \\ 1 & -1 & -(5 + j1) \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 10\angle 0^\circ \\ 1\angle 0^\circ \\ 0 \end{bmatrix}$$

By Cramer's rule,

$$\mathbf{I}_1 = \frac{\begin{vmatrix} 10\angle 0^\circ & -1 & 0 \\ 1\angle 0^\circ & -1 & 1 \\ 0 & -1 & -(5 + j1) \end{vmatrix}}{\begin{vmatrix} 4 + j2 & -1 & 0 \\ 0 & -1 & 1 \\ 1 & -1 & -(5 + j1) \end{vmatrix}} = 2.11\angle -28.01^\circ \text{ A}$$

$$\mathbf{I}_{3\ \Omega} = \mathbf{I}_1 = 2.11\angle -28.01^\circ \text{ A}$$

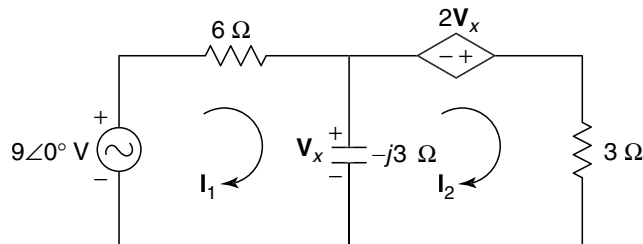Example 6.9Find the currents $\mathbf{I}_1$ and $\mathbf{I}_2$ in the network of Fig. 6.9.**Fig. 6.9**

6.8 Network Analysis and Synthesis

Solution From Fig. 6.9,

$$\mathbf{V}_x = -j3(\mathbf{I}_1 - \mathbf{I}_2) \quad \dots(i)$$

Applying KVL to Mesh 1,

$$\begin{aligned} 9\angle 0^\circ - 6\mathbf{I}_1 + j3(\mathbf{I}_1 - \mathbf{I}_2) &= 0 \\ (6 - j3)\mathbf{I}_1 + j3\mathbf{I}_2 &= 9\angle 0^\circ \end{aligned} \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$\begin{aligned} j3(\mathbf{I}_2 - \mathbf{I}_1) + 2\mathbf{V}_x - 3\mathbf{I}_2 &= 0 \\ j3\mathbf{I}_2 - j3\mathbf{I}_1 + 2[-j3(\mathbf{I}_1 - \mathbf{I}_2)] - 3\mathbf{I}_2 &= 0 \\ j9\mathbf{I}_1 + (3 - j9)\mathbf{I}_2 &= 0 \end{aligned} \quad \dots(iii)$$

Writing Eqs (ii) and (iii) in matrix form,

$$\begin{bmatrix} 6 - j3 & j3 \\ j9 & 3 - j9 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 9\angle 0^\circ \\ 0 \end{bmatrix}$$

By Cramer's rule,

$$\begin{aligned} \mathbf{I}_1 &= \frac{\begin{vmatrix} 9\angle 0^\circ & j3 \\ 0 & 3 - j9 \end{vmatrix}}{\begin{vmatrix} 6 - j3 & j3 \\ j9 & 3 - j9 \end{vmatrix}} = 1.3\angle 2.49^\circ \text{ A} \\ \mathbf{I}_2 &= \frac{\begin{vmatrix} 6 - j3 & 9\angle 0^\circ \\ j9 & 0 \end{vmatrix}}{\begin{vmatrix} 6 - j3 & j3 \\ j9 & 3 - j9 \end{vmatrix}} = 1.24\angle -15.95^\circ \text{ A} \end{aligned}$$

Example 6.10

Find the voltage across the $4\ \Omega$ resistor in the network of Fig. 6.10.

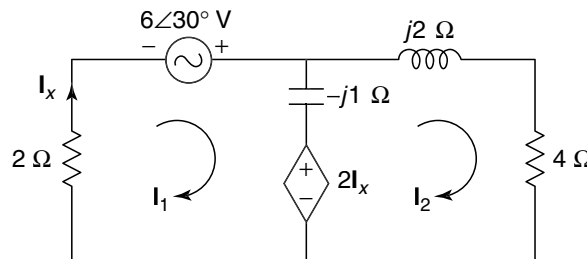


Fig. 6.10

Solution From Fig. 6.10,

$$\mathbf{I}_x = \mathbf{I}_1 \quad \dots(i)$$

Applying KVL to Mesh 1,

$$\begin{aligned} -2\mathbf{I}_1 + 6\angle 30^\circ + j1(\mathbf{I}_1 - \mathbf{I}_2) - 2\mathbf{I}_x &= 0 \\ -2\mathbf{I}_1 + 6\angle 30^\circ + j1\mathbf{I}_1 - j1\mathbf{I}_2 - 2\mathbf{I}_1 &= 0 \\ (4 - j1)\mathbf{I}_1 + j1\mathbf{I}_2 &= 6\angle 30^\circ \end{aligned} \quad \dots(ii)$$

Applying KVL to Mesh 2,

$$2\mathbf{I}_x + j1(\mathbf{I}_2 - \mathbf{I}_1) - j2\mathbf{I}_2 - 4\mathbf{I}_2 = 0$$

$$2\mathbf{I}_1 + j1\mathbf{I}_2 - j1\mathbf{I}_1 - j2\mathbf{I}_2 - 4\mathbf{I}_2 = 0$$

$$(2 - j1)\mathbf{I}_1 - (4 + j1)\mathbf{I}_2 = 0 \quad \dots(\text{iii})$$

Writing Eqs (ii) and (iii) in matrix form,

$$\begin{bmatrix} 4 - j1 & j1 \\ 2 - j1 & -(4 + j1) \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 6\angle 30^\circ \\ 0 \end{bmatrix}$$

By Cramer's rule,

$$\mathbf{I}_2 = \frac{\begin{vmatrix} 4 - j1 & 6\angle 30^\circ \\ 2 - j1 & 0 \end{vmatrix}}{\begin{vmatrix} 4 - j1 & j1 \\ 2 - j1 & -(4 + j1) \end{vmatrix}} = 0.74\angle -2.91^\circ \text{ A}$$

$$V_{4\Omega} = 4\mathbf{I}_2 = 4(0.74\angle -2.91^\circ) = 2.96\angle -2.91^\circ \text{ V}$$

6.3 || NODE ANALYSIS

Node analysis uses Kirchhoff's current law for finding currents and voltages in a network. For ac networks, Kirchhoff's current law states that the phasor sum of currents meeting at a point is equal to zero.

Example 6.11

In the network shown in Fig. 6.11, determine V_a and V_b .

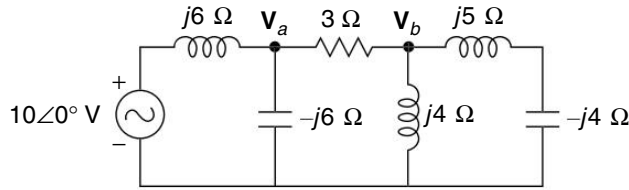


Fig. 6.11

Solution Applying KCL at Node a ,

$$\frac{V_a - 10\angle 0^\circ}{j6} + \frac{V_a}{-j6} + \frac{V_a - V_b}{3} = 0$$

$$\left(\frac{1}{j6} - \frac{1}{j6} + \frac{1}{3} \right) V_a - \frac{1}{3} V_b = \frac{10\angle 0^\circ}{j6}$$

$$0.33V_a - 0.33V_b = 1.67\angle -90^\circ \quad \dots(\text{i})$$

Applying KCL at Node b ,

$$\frac{V_b - V_a}{3} + \frac{V_b}{j4} + \frac{V_b}{j1} = 0$$

$$-\frac{1}{3}V_a + \left(\frac{1}{3} + \frac{1}{j4} + \frac{1}{j1} \right) V_b = 0$$

$$-0.33V_a + (0.33 - j1.25)V_b = 0 \quad \dots(\text{ii})$$

6.10 Network Analysis and Synthesis

Adding Eqs (i) and (ii),

$$-j1.25\mathbf{V}_b = 1.67\angle -90^\circ$$

$$\mathbf{V}_b = \frac{1.67\angle -90^\circ}{-j1.25} = 1.34\angle 0^\circ \text{ V}$$

Substituting $\mathbf{V}_b$ in Eq. (i),

$$0.33\mathbf{V}_a - 0.33(1.34\angle 0^\circ) = 1.67\angle -90^\circ$$

$$\mathbf{V}_a = \frac{1.73\angle 75.17^\circ}{0.33} = 5.24\angle -75.17^\circ \text{ V}$$

Example 6.12

For the network shown in Fig. 6.12, find the voltages $\mathbf{V}_1$ and $\mathbf{V}_2$.

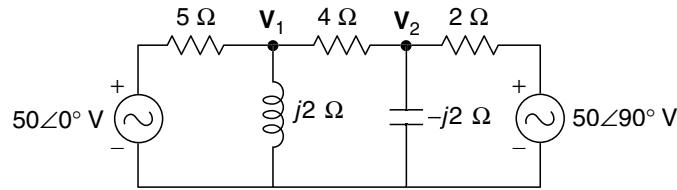


Fig. 6.12

Applying KCL at Node 1,

$$\frac{\mathbf{V}_1 - 50\angle 0^\circ}{5} + \frac{\mathbf{V}_1}{j2} + \frac{\mathbf{V}_1 - \mathbf{V}_2}{4} = 0$$

$$\left(\frac{1}{5} + \frac{1}{j2} + \frac{1}{4}\right)\mathbf{V}_1 - \frac{1}{4}\mathbf{V}_2 = 10\angle 0^\circ$$

$$(0.45 - j0.5)\mathbf{V}_1 - 0.25\mathbf{V}_2 = 10\angle 0^\circ \quad \dots(i)$$

Applying KCL at Node 2,

$$\frac{\mathbf{V}_2 - \mathbf{V}_1}{4} + \frac{\mathbf{V}_2}{-j2} + \frac{\mathbf{V}_2 - 50\angle 90^\circ}{2} = 0$$

$$-\frac{1}{4}\mathbf{V}_1 + \left(\frac{1}{4} + \frac{1}{-j2} + \frac{1}{2}\right)\mathbf{V}_2 = 25\angle 90^\circ$$

$$-0.25\mathbf{V}_1 + (0.75 + j0.5)\mathbf{V}_2 = 25\angle 90^\circ \quad \dots(ii)$$


Writing Eqs (i) and (ii) in matrix form,

$$\begin{bmatrix} 0.45 - j0.5 & -0.25 \\ -0.25 & 0.75 + j0.5 \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} 10\angle 0^\circ \\ 25\angle 90^\circ \end{bmatrix}$$

By Cramer's rule,

$$\mathbf{V}_1 = \frac{\begin{vmatrix} 10\angle 0^\circ & -0.25 \\ j25 & 0.75 + j0.5 \end{vmatrix}}{\begin{vmatrix} 0.45 - j0.5 & -0.25 \\ -0.25 & 0.75 + j0.5 \end{vmatrix}} = 24.7\angle 72.25^\circ \text{ V}$$

$$\mathbf{V}_2 = \frac{\begin{vmatrix} 0.45 - j0.5 & 10\angle 0^\circ \\ -0.25 & 25\angle 90^\circ \end{vmatrix}}{\begin{vmatrix} 0.45 - j0.5 & -0.25 \\ -0.25 & 0.75 + j0.5 \end{vmatrix}} = 34.34\angle 52.82^\circ \text{ V}$$

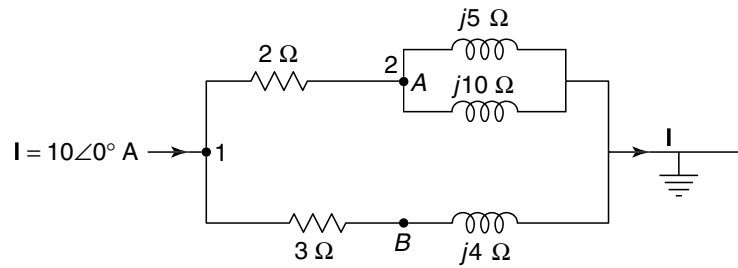Example 6.13Find the voltage V_{AB} in the network of Fig. 6.13.**Fig. 6.13****Solution** Applying KCL at Node 1,

$$10\angle 0^\circ = \frac{V_1 - V_2}{2} + \frac{V_1}{3 + j4}$$

$$\left(\frac{1}{2} + \frac{1}{3 + j4} \right) V_1 - \frac{1}{2} V_2 = 10\angle 0^\circ$$

$$(0.62 - j0.16)V_1 - 0.5V_2 = 10\angle 0^\circ \quad \dots(i)$$

Applying KCL at Node 2,

$$\frac{V_2 - V_1}{2} + \frac{V_2}{j5} + \frac{V_2}{j10} = 0$$

$$-\frac{1}{2}V_1 + \left(\frac{1}{2} + \frac{1}{j5} + \frac{1}{j10} \right) V_2 = 0$$

$$-0.5V_1 + (0.5 - j0.3)V_2 = 0 \quad \dots(ii)$$

Writing Eqs (i) and (ii) in matrix form,

$$\begin{bmatrix} 0.62 - j0.16 & -0.5 \\ -0.5 & 0.5 - j0.3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 10\angle 0^\circ \\ 0 \end{bmatrix}$$

By Cramer's rule,


$$V_1 = \frac{\begin{vmatrix} 10\angle 0^\circ & -0.5 \\ 0 & 0.5 - j0.3 \end{vmatrix}}{\begin{vmatrix} 0.62 - j0.16 & -0.5 \\ -0.5 & 0.5 - j0.3 \end{vmatrix}} = 21.8\angle 56.42^\circ \text{ V}$$

$$V_2 = \frac{\begin{vmatrix} 0.62 - j0.16 & 10\angle 0^\circ \\ -0.5 & 0 \end{vmatrix}}{\begin{vmatrix} 0.62 - j0.16 & -0.5 \\ -0.5 & 0.5 - j0.3 \end{vmatrix}} = 18.7\angle 87.42^\circ \text{ V}$$

$$V_A = V_2 = 18.7\angle 87.42^\circ \text{ V}$$

$$V_B = \frac{V_1}{3 + j4} (j4) = \frac{21.8\angle 56.42^\circ}{3 + j4} (j4) = 17.45\angle 93.32^\circ \text{ V}$$

$$V_{AB} = V_A - V_B = (18.7\angle 87.42^\circ) - (17.45\angle 93.32^\circ) = 2.23\angle 34.1^\circ \text{ V}$$

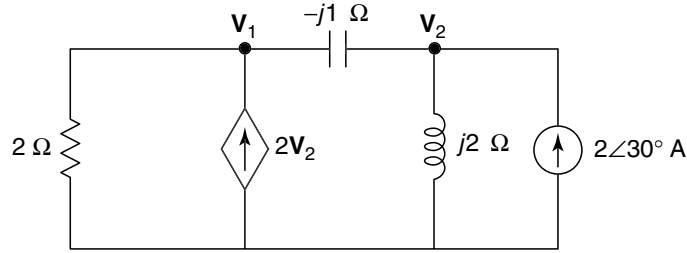Example 6.14Find the node voltages V_1 and V_2 in the network of Fig. 6.14.**Fig. 6.14****Solution** Applying KCL at Node 1,

$$\frac{V_1}{2} + \frac{V_1 - V_2}{-j1} = 2V_2$$

$$\left(\frac{1}{2} + \frac{1}{-j1}\right)V_1 - \left(2 - \frac{1}{j1}\right)V_2 = 0$$

$$(0.5 + j1)V_1 - (2 + j1)V_2 = 0 \quad \dots(i)$$

Applying KCL at Node 2,

$$\frac{V_2 - V_1}{-j1} + \frac{V_2}{j2} = 2\angle 30^\circ$$

$$\frac{1}{j1}V_1 + \left(\frac{1}{-j1} + \frac{1}{j2}\right)V_2 = 2\angle 30^\circ$$

$$-j1V_1 + j0.5V_2 = 2\angle 30^\circ \quad \dots(ii)$$


Writing Eqs (i) and (ii) in matrix form,

$$\begin{bmatrix} 0.5 + j1 & -(2 + j1) \\ -j1 & j0.5 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 0 \\ 2\angle 30^\circ \end{bmatrix}$$

By Cramer's rule,

$$V_1 = \frac{\begin{vmatrix} 0 & -(2 + j1) \\ 2\angle 30^\circ & j0.5 \end{vmatrix}}{\begin{vmatrix} 0.5 + j1 & -(2 + j1) \\ -j1 & j0.5 \end{vmatrix}} = 2.46\angle 130.62^\circ \text{ V}$$

$$V_2 = \frac{\begin{vmatrix} 0.5 + j1 & 0 \\ -j1 & 2\angle 30^\circ \end{vmatrix}}{\begin{vmatrix} 0.5 + j1 & -(2 + j1) \\ -j1 & j0.5 \end{vmatrix}} = 1.23\angle 167.49^\circ \text{ V}$$

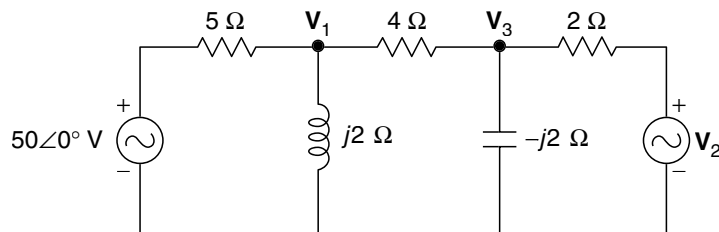Example 6.15In the network of Fig 6.15, find the voltage V_2 which results in zero current through $4\ \Omega$ resistor.**Fig. 6.15**

Solution Applying KCL at Node 1,

$$\begin{aligned}\frac{\mathbf{V}_1 - 50\angle 0^\circ}{5} + \frac{\mathbf{V}_1}{j2} + \frac{\mathbf{V}_1 - \mathbf{V}_3}{4} &= 0 \\ \left(\frac{1}{5} + \frac{1}{j2} + \frac{1}{4}\right)\mathbf{V}_1 - \frac{1}{4}\mathbf{V}_3 &= 10\angle 0^\circ \\ (0.45 - j0.5)\mathbf{V}_1 - 0.25\mathbf{V}_3 &= 10\angle 0^\circ\end{aligned}\quad \dots(i)$$

Applying KCL at Node 3,

$$\begin{aligned}\frac{\mathbf{V}_3 - \mathbf{V}_1}{4} + \frac{\mathbf{V}_3}{-j2} + \frac{\mathbf{V}_3 - \mathbf{V}_2}{2} &= 0 \\ -\frac{1}{4}\mathbf{V}_1 + \left(\frac{1}{4} + \frac{1}{-j2} + \frac{1}{2}\right)\mathbf{V}_3 &= 0.5\mathbf{V}_2 \\ -0.25\mathbf{V}_1 + (0.75 + j0.5)\mathbf{V}_3 &= 0.5\mathbf{V}_2\end{aligned}\quad \dots(ii)$$

Writing Eqs (i) and (ii) in matrix form,

$$\begin{bmatrix} 0.45 - j0.5 & -0.25 \\ -0.25 & 0.75 + j0.5 \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_3 \end{bmatrix} = \begin{bmatrix} 10\angle 0^\circ \\ 0.5\mathbf{V}_2 \end{bmatrix}$$

By Cramer's rule,

$$\mathbf{V}_1 = \frac{\begin{vmatrix} 10\angle 0^\circ & -0.25 \\ 0.5\mathbf{V}_2 & 0.75 + j0.5 \end{vmatrix}}{\begin{vmatrix} 0.45 - j0.5 & -0.25 \\ -0.25 & 0.75 + j0.5 \end{vmatrix}} = \frac{10(0.75 + j0.5) + 0.125\mathbf{V}_2}{0.55\angle -15.95^\circ}$$

$$\mathbf{V}_3 = \frac{\begin{vmatrix} 0.45 - j0.5 & 10\angle 0^\circ \\ -0.25 & 0.5\mathbf{V}_2 \end{vmatrix}}{\begin{vmatrix} 0.45 - j0.5 & -0.25 \\ -0.25 & 0.75 + j0.5 \end{vmatrix}} = \frac{0.5\mathbf{V}_2(0.45 - j0.5) + 2.5}{0.55\angle -15.95^\circ}$$

$$\mathbf{I}_{4\Omega} = \frac{\mathbf{V}_1 - \mathbf{V}_3}{4} = 0$$

$$\mathbf{V}_1 = \mathbf{V}_3$$

$$\frac{10(0.75 + j0.5) + 0.125\mathbf{V}_2}{0.55\angle -15.95^\circ} = \frac{0.5\mathbf{V}_2(0.45 - j0.5) + 2.5}{0.55\angle -15.95^\circ}$$

$$7.5 + 0.125\mathbf{V}_2 - j5 = 2.5 + 0.225\mathbf{V}_2 - j0.25\mathbf{V}_2$$

$$5 + j5 = \mathbf{V}_2(0.1 - j0.25)$$

$$\mathbf{V}_2 = \frac{5 + j5}{0.1 - j0.25} = 26.26\angle 113.2^\circ \text{ V}$$

Example 6.16

Find the voltage across the capacitor in the network of Fig. 6.16.

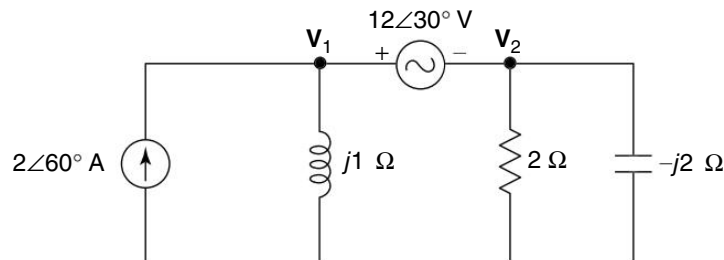


Fig. 6.16

6.14 Network Analysis and Synthesis

Solution Nodes 1 and 2 will form a supernode.

Writing the voltage equation for the supernode,

$$\mathbf{V}_1 - \mathbf{V}_2 = 12\angle 30^\circ \quad \dots(i)$$

Applying KCL to the supernode,

$$\frac{\mathbf{V}_1}{j1} + \frac{\mathbf{V}_2}{2} + \frac{\mathbf{V}_2}{-j2} = 2\angle 60^\circ$$

$$(-j1)\mathbf{V}_1 + (0.5 + j0.5)\mathbf{V}_2 = 2\angle 60^\circ \quad \dots(ii)$$

Writing Eqs (i) and (ii) in matrix form,

$$\begin{bmatrix} 1 & -1 \\ -j1 & 0.5 + j0.5 \end{bmatrix} \begin{bmatrix} \mathbf{V}_1 \\ \mathbf{V}_2 \end{bmatrix} = \begin{bmatrix} 12\angle 30^\circ \\ 2\angle 60^\circ \end{bmatrix}$$

By Cramer's rule,

$$\mathbf{V}_2 = \frac{\begin{vmatrix} 1 & 12\angle 30^\circ \\ -j1 & 2\angle 60^\circ \end{vmatrix}}{\begin{vmatrix} 1 & -1 \\ -j1 & 0.5 + j0.5 \end{vmatrix}} = 18.55\angle 157.42^\circ \text{ V}$$

$$\mathbf{V}_c = \mathbf{V}_2 = 18.55\angle 157.42^\circ \text{ V}$$

6.4 || SUPERPOSITION THEOREM

The superposition theorem can be used to analyse an ac network containing more than one source. The superposition theorem states that *in a network containing more than one voltage source or current source, the total current or voltage in any branch of the network is the phasor sum of currents or voltages produced in that branch by each source acting separately*. As each source is considered, all of the other sources are replaced by their internal impedances. This theorem is valid only for linear systems.

Example 6.17 Find the current through the $3 + j4$ ohm impedance.

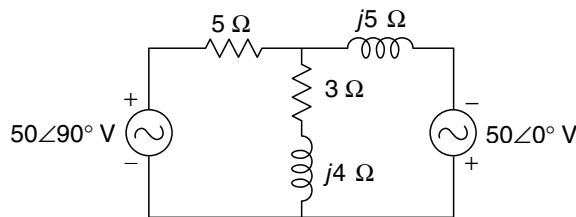


Fig. 6.17

Solution

Step I When the $50\angle 90^\circ$ V source is acting alone (Fig. 6.18)

$$\mathbf{Z}_T = 5 + \frac{(3 + j4)(j5)}{3 + j9} = 6.35\angle 23.2^\circ \Omega$$

$$\mathbf{I}_T = \frac{50\angle 90^\circ}{6.35\angle 23.2^\circ} = 7.87\angle 66.8^\circ \text{ A}$$

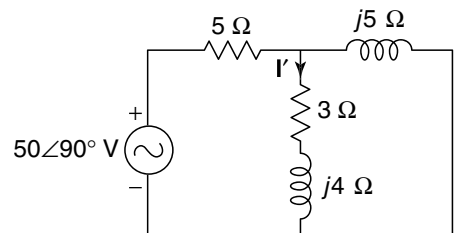


Fig. 6.18

By current division rule,

$$\mathbf{I}' = (7.87 \angle 66.8^\circ) \left(\frac{j5}{3 + j9} \right) = 4.15 \angle 85.3^\circ \text{ A} (\downarrow)$$

Step II When the $50 \angle 0^\circ \text{ V}$ source is acting alone (Fig. 6.19)

$$\mathbf{Z}_T = j5 + \frac{5(3 + j4)}{8 + j4} = 6.74 \angle 68.2^\circ \Omega$$

$$\mathbf{I}_T = \frac{50 \angle 0^\circ}{6.74 \angle 68.2^\circ} = 7.42 \angle -68.2^\circ \text{ A}$$

By current division rule,

$$\mathbf{I}'' = (7.42 \angle -68.2^\circ) \left(\frac{5}{8 + j4} \right) = 4.15 \angle -94.77^\circ \text{ A} (\uparrow) = 4.15 \angle 85.3^\circ \text{ A} (\downarrow)$$

Step III By superposition theorem,

$$\mathbf{I} = \mathbf{I}' + \mathbf{I}'' = 4.15 \angle 85.3^\circ + 4.15 \angle 85.3^\circ = 8.31 \angle 85.3^\circ \text{ A} (\downarrow)$$

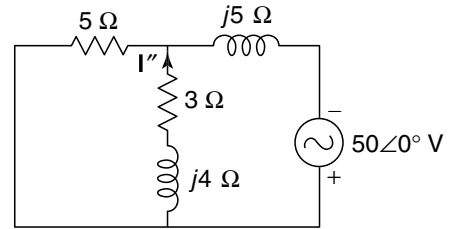


Fig. 6.19

Example 6.18

Determine the voltage across the $(2 + j5) \Omega$ impedance for the network shown in Fig. 6.20.

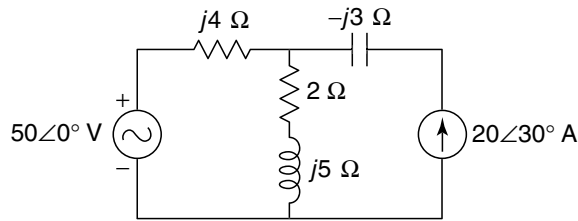


Fig. 6.20

Solution

Step I When the $50 \angle 0^\circ \text{ V}$ source is acting alone (Fig. 6.21)

$$\mathbf{I} = \frac{50 \angle 0^\circ}{2 + j4 + j5} = 5.42 \angle -77.47^\circ \text{ A}$$

Voltage across $(2 + j5) \Omega$ impedance

$$\mathbf{V}' = (2 + j5) (5.42 \angle -77.47^\circ) = 29.16 \angle -9.28^\circ \text{ V}$$

Step II When the $20 \angle 30^\circ \text{ A}$ source is acting alone (Fig. 6.22)

By current division rule,

$$\mathbf{I} = (20 \angle 30^\circ) \left(\frac{j4}{2 + j9} \right) = 8.68 \angle 42.53^\circ \text{ A}$$

Voltage across $(2 + j5) \Omega$ impedance

$$\mathbf{V}'' = (2 + j5) (8.68 \angle 42.53^\circ) = 46.69 \angle 110.72^\circ \text{ V}$$

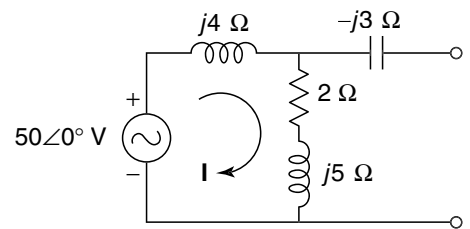


Fig. 6.21

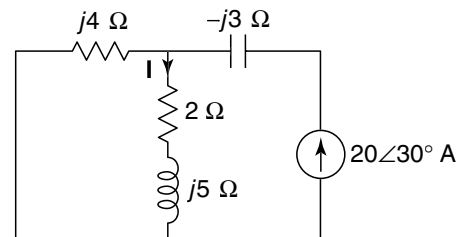


Fig. 6.22

6.16 Network Analysis and Synthesis

Step III By superposition theorem,

$$\mathbf{V} = \mathbf{V}' + \mathbf{V}'' = 29.16 \angle -9.28^\circ + 46.69 \angle 110.72^\circ = 40.85 \angle 72.53^\circ \text{ V}$$

Example 6.19

Determine the voltage V_{AB} for the network shown in Fig. 6.23.

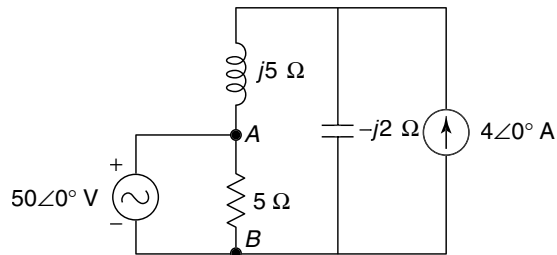


Fig. 6.23

Solution

Step I When the $50\angle 0^\circ \text{ V}$ source is acting alone (Fig. 6.24)

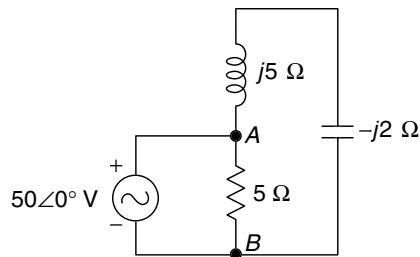


Fig. 6.24

$$\mathbf{V}'_{AB} = 50\angle 0^\circ \text{ V}$$

Step II When the $4\angle 0^\circ \text{ A}$ source is acting alone (Fig. 6.25)

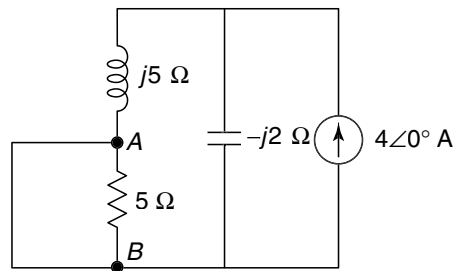
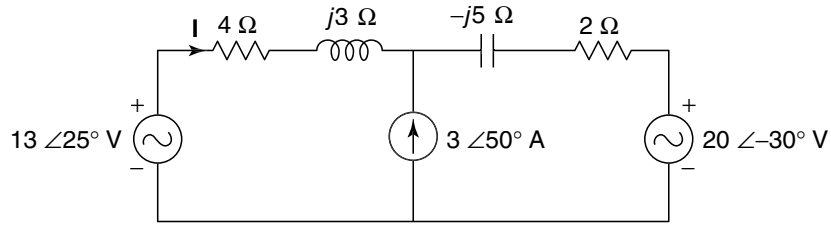
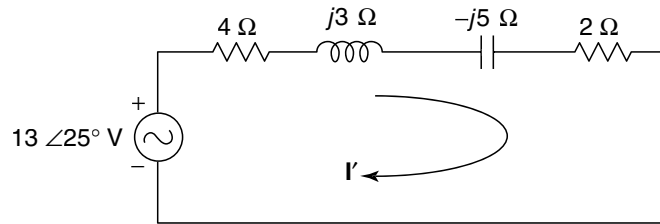


Fig. 6.25


$$\mathbf{V}''_{AB} = 0$$

Step III By superposition theorem,


$$\mathbf{V}_{AB} = \mathbf{V}'_{AB} + \mathbf{V}''_{AB} = 50\angle 0^\circ + 0 = 50\angle 0^\circ \text{ V}$$

Example 6.20Find the current I in the network shown in Fig. 6.26.**Fig. 6.26****Solution****Step I** When the $13\angle 25^\circ$ V source is acting alone (Fig. 6.27)**Fig. 6.27**

$$I' = \frac{13\angle 25^\circ}{6 - j2} = 2.057\angle 43.43^\circ \text{ A} \quad (\rightarrow)$$

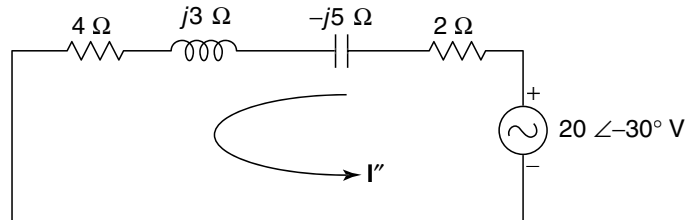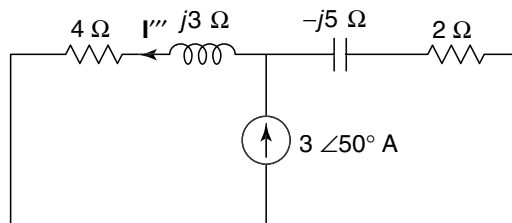Step II When the $20\angle -30^\circ$ V source is acting alone (Fig. 6.28)**Fig. 6.28**

$$I'' = \frac{20\angle -30^\circ}{6 - j2} = 3.16\angle -11.57^\circ \text{ A} (\leftarrow) = 3.16\angle 168.43^\circ \text{ A} (\rightarrow)$$

Step III When the $3\angle 50^\circ$ A source is acting alone (Fig. 6.29)**Fig. 6.29**

6.18 Network Analysis and Synthesis

By current division rule,

$$\mathbf{I}''' = 3\angle 50^\circ \times \frac{2-j5}{6-j2} = 2.56\angle 0.23^\circ \text{ A}(\leftarrow) = 2.56\angle -179.77^\circ \text{ A}(\rightarrow)$$

Step IV By superposition theorem,

$$\mathbf{I} = \mathbf{I}' + \mathbf{I}'' + \mathbf{I}''' = 2.057\angle 43.13^\circ + 3.16\angle 168.43^\circ + 2.56\angle -179.77^\circ \text{ A} = 4.62\angle 153.99^\circ \text{ A}(\rightarrow)$$

Example 6.21

Find the current through the $j3\ \Omega$ reactance in the network of Fig 6.30.

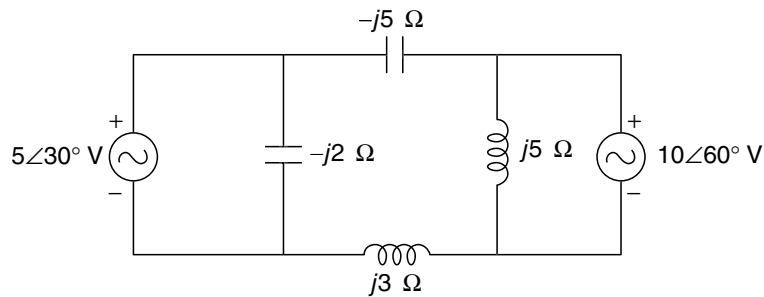


Fig. 6.30

Solution

Step I When the $5\angle 30^\circ \text{ V}$ source is acting alone (Fig. 6.31)

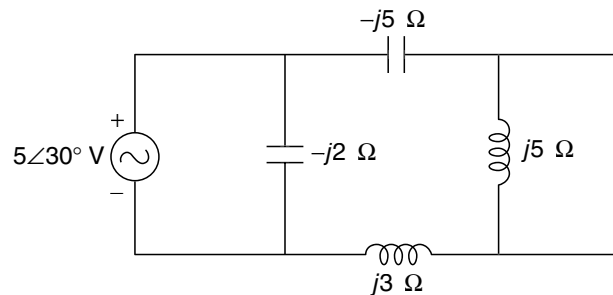


Fig. 6.31

When a short circuit is placed across $j15\ \Omega$ reactance, it gets shorted as shown in Fig 6.32.

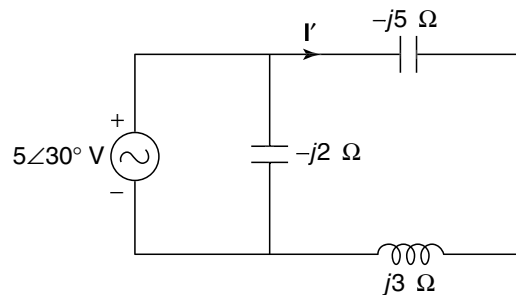


Fig. 6.32

$$\mathbf{I}' = \frac{5\angle 30^\circ}{-j5 + j3} = 2.5\angle 120^\circ \text{ A}(\leftarrow)$$

Step II When the $10\angle 60^\circ$ V source is acting alone (Fig. 6.33)

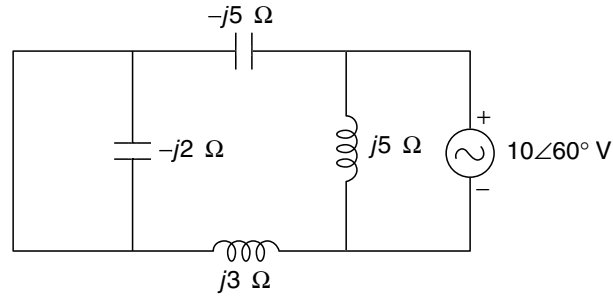


Fig. 6.33

When a short circuit is placed across the $-j2\ \Omega$ reactance, it gets shorted as shown in Fig. 6.34

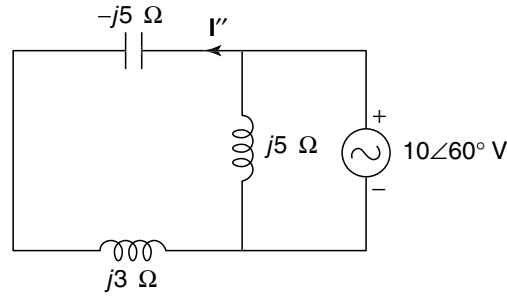


Fig. 6.34

$$\mathbf{I}'' = \frac{10\angle 60^\circ}{-j5 + j3} = 5\angle 150^\circ \text{ A } (\rightarrow) = 5\angle -30^\circ \text{ A } (\leftarrow)$$

Step III By superposition theorem,

$$\mathbf{I} = \mathbf{I}' + \mathbf{I}'' = 2.5\angle 120^\circ + 5\angle -30^\circ = 3.1\angle -6.21^\circ \text{ A } (\leftarrow)$$

Example 6.22

Find the current $\mathbf{I}_0$ in the network of Fig. 6.35.

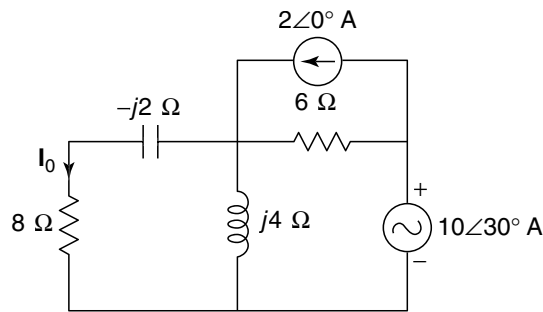


Fig. 6.35

Solution

Step I When the $10\angle 30^\circ$ V source is acting alone (Fig. 6.36)

$$\mathbf{Z}_T = 6 + \frac{j4(8 - j2)}{j4 + 8 - j2} = 8.64\angle 24.12^\circ \ \Omega$$

$$\mathbf{I}_T = \frac{10\angle 30^\circ}{8.64\angle 24.12^\circ} = 1.16\angle 5.88^\circ \text{ A}$$

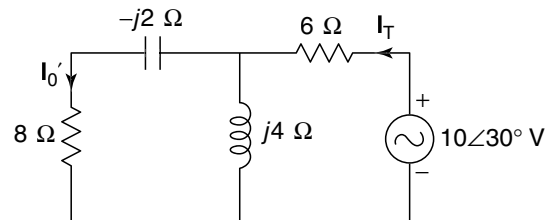


Fig. 6.36

By current division rule,

$$\mathbf{I}'_0 = 1.16 \angle 5.88^\circ \times \frac{j4}{8 - j2 + j4} = 0.56 \angle 81.84^\circ \text{ A } (\downarrow)$$

Step II When the $2 \angle 0^\circ$ A source is acting alone (Fig. 6.37)

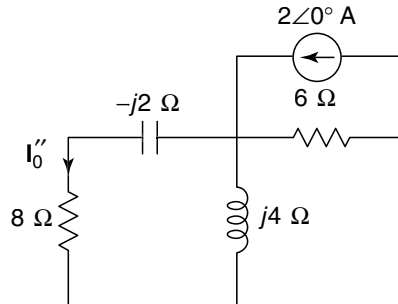


Fig. 6.37

The network can be redrawn as shown in Fig. 6.38.

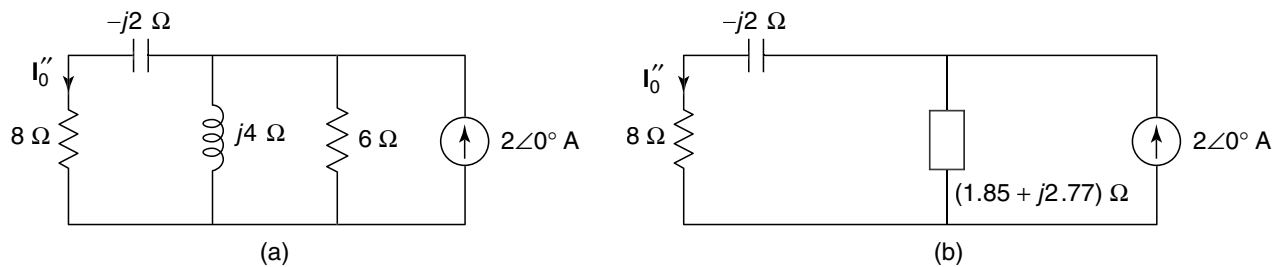


Fig. 6.38

By current division rule,

$$\mathbf{I}''_0 = 2 \angle 0^\circ \times \frac{1.85 + j2.77}{1.85 + j2.77 + 8 - j2} = 0.67 \angle 51.83^\circ \text{ A } (\downarrow)$$

Step III By superposition theorem,

$$\mathbf{I}_0 = \mathbf{I}'_0 + \mathbf{I}''_0 = 0.56 \angle 81.84^\circ + 0.67 \angle 51.83^\circ = 1.19 \angle 65.46^\circ \text{ A } (\downarrow)$$

Example 6.23

Find the current through the $j5 \Omega$ branch for the network shown in Fig. 6.39.

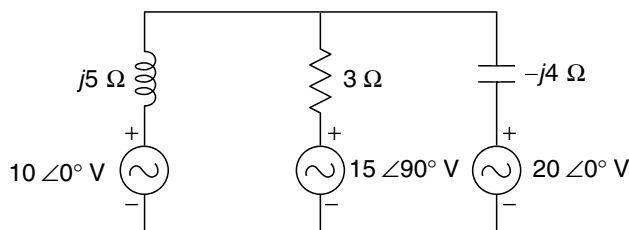
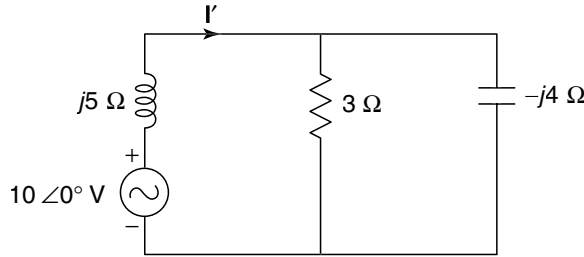


Fig. 6.39

Solution

Step I When the $10\angle 0^\circ$ V source is acting alone (Fig. 6.40)

**Fig. 6.40**


$$\mathbf{Z}_T = j5 + \frac{3(-j4)}{3 - j4} = 4.04\angle 61.66^\circ \Omega$$

$$\mathbf{I}' = \frac{10\angle 0^\circ}{4.04\angle 61.66^\circ} = 2.48\angle -61.66^\circ \text{ A} \quad (\rightarrow)$$

Step II When the $15\angle 90^\circ$ V source is acting alone (Fig. 6.41)

$$\mathbf{Z}_T = 3 + \frac{(j5)(-j4)}{j5 - j4} = 20.22\angle -81.47^\circ \Omega$$


$$\mathbf{I}_T = \frac{15\angle 90^\circ}{20.22\angle -81.47^\circ} = 0.74\angle 171.47^\circ \text{ A}$$

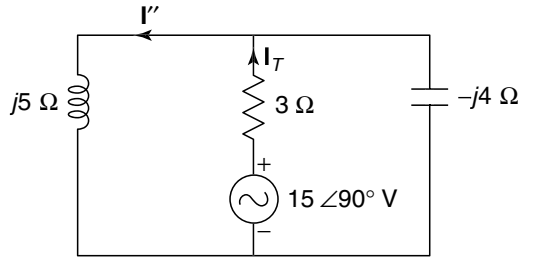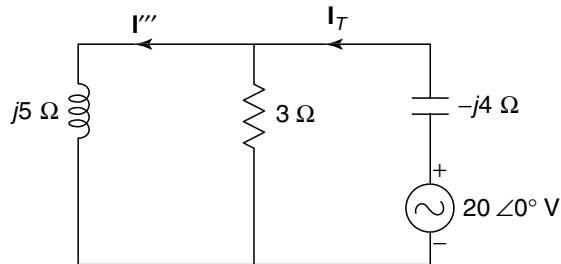**Fig. 6.41**

By current division rule,

$$\mathbf{I}'' = 0.74\angle 171.47^\circ \times \frac{-j4}{-j4 + j5} = 2.96\angle -8.53^\circ \text{ A} \quad (\leftarrow) = 2.96\angle 171.47^\circ \text{ A} \quad (\rightarrow)$$

Step III When the $20\angle 0^\circ$ V source is acting alone (Fig. 6.42)

**Fig. 6.42**

$$\mathbf{Z}_T = -j4 + \frac{3(j5)}{3 + j5} = 3.47\angle -50.51^\circ \Omega$$

$$\mathbf{I}_T = \frac{20\angle 0^\circ}{3.47\angle -50.51^\circ} = 5.76\angle 50.51^\circ \text{ A}$$

By current division rule,

$$\mathbf{I}''' = 5.76\angle 50.51^\circ \times \frac{3}{3 + j5} = 2.96\angle -8.53^\circ \text{ A} \quad (\leftarrow) = 2.96\angle 171.47^\circ \text{ A} \quad (\rightarrow)$$

6.22 Network Analysis and Synthesis

Step IV By superposition theorem,

$$\mathbf{I} = \mathbf{I}' + \mathbf{I}'' + \mathbf{I}''' = 2.48\angle -61.66^\circ + 2.96\angle 171.47^\circ + 2.96\angle 171.47^\circ = 4.86\angle -164.41^\circ \text{ A}$$

Example 6.24 Find the voltage drop across the capacitor for the network shown in Fig. 6.43.

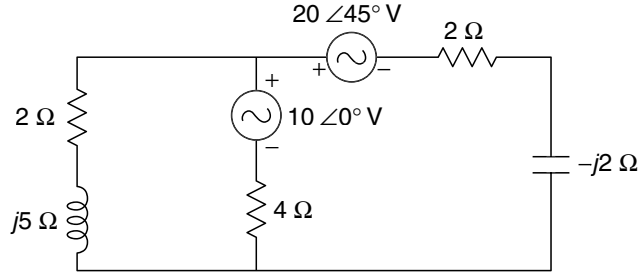


Fig. 6.43

Solution

Step I When the $10\angle 0^\circ \text{ V}$ source is acting alone (Fig. 6.44)

$$\mathbf{Z}_T = 4 + \frac{(2 + j5)(2 - j2)}{2 + j5 + 2 - j2}$$

$$= 7\angle -5.91^\circ \Omega$$

$$\mathbf{I}_T = \frac{10\angle 0^\circ}{7\angle -5.91^\circ} = 1.43\angle 5.91^\circ \text{ A}$$

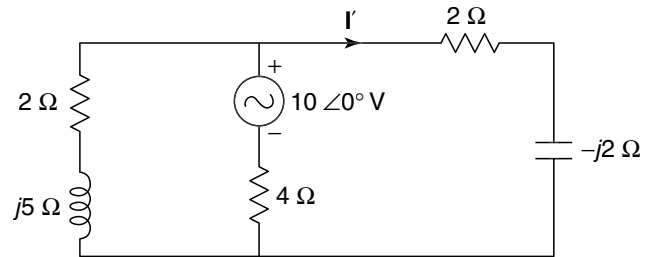


Fig. 6.44

By current division rule,

$$\mathbf{I}' = (1.43\angle 5.91^\circ) \left(\frac{2 + j5}{2 + j5 + 2 - j2} \right) = 1.54\angle 37.24^\circ \text{ A} \quad (\rightarrow)$$

Step II When the $20\angle 45^\circ \text{ V}$ source is acting alone (Fig. 6.45)

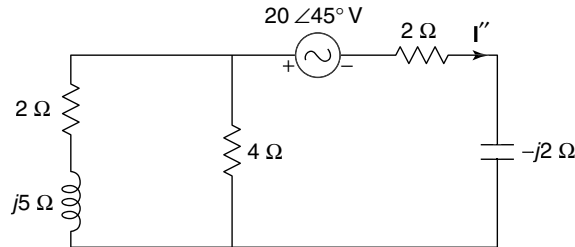


Fig. 6.45

$$\mathbf{Z}_T = (2 - j2) + \frac{4(2 + j5)}{4 + 2 + j5} = 4.48\angle -8.84^\circ \Omega$$

$$\mathbf{I}'' = \frac{20\angle 45^\circ}{4.48\angle -8.84^\circ} = 4.46\angle 53.84^\circ \text{ A} \quad (\leftarrow) = -4.46\angle 53.84^\circ \text{ A} \quad (\rightarrow)$$

Step III By superposition theorem,

$$\mathbf{I} = \mathbf{I}' + \mathbf{I}'' = 1.54 \angle 37.24^\circ - 4.46 \angle 53.84^\circ = 3.01 \angle -117.78^\circ \text{ A}$$

$$\mathbf{V}_c = (-j2)\mathbf{I} = (-j2)(3.01 \angle -117.78^\circ) = 6.02 \angle 152.22^\circ \text{ V}$$

Example 6.25

Find the node voltage V_2 in the network of Fig. 6.46.

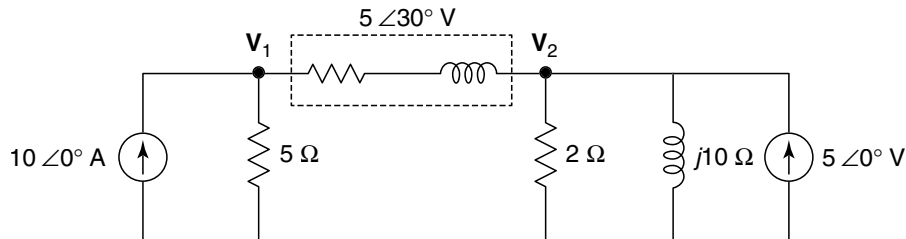


Fig. 6.46

Solution

Step I When the $10 \angle 0^\circ \text{ A}$ source is acting alone (Fig. 6.47)

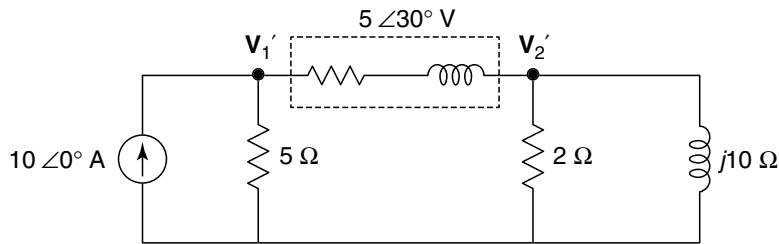


Fig. 6.47

Applying KCL at Node 1,

$$\frac{\mathbf{V}_1'}{5} + \frac{\mathbf{V}_1' - \mathbf{V}_2'}{5 \angle 30^\circ} = 10 \angle 0^\circ$$

$$\left(\frac{1}{5} + \frac{1}{5 \angle 30^\circ} \right) \mathbf{V}_1' - \frac{1}{5 \angle 30^\circ} \mathbf{V}_2' = 10 \angle 0^\circ$$

$$(0.37 - j0.1) \mathbf{V}_1' - (0.17 - j0.1) \mathbf{V}_2' = 10 \angle 0^\circ \quad \dots(i)$$

Applying KCL at Node 2,

$$\frac{\mathbf{V}_2' - \mathbf{V}_1'}{5 \angle 30^\circ} + \frac{\mathbf{V}_2'}{2} + \frac{\mathbf{V}_2'}{j10} = 0$$

$$-\frac{1}{5 \angle 30^\circ} \mathbf{V}_1' + \left(\frac{1}{5 \angle 30^\circ} + \frac{1}{2} + \frac{1}{j10} \right) \mathbf{V}_2' = 0$$

$$-(0.17 - j0.1) \mathbf{V}_1' + (0.67 - j0.2) \mathbf{V}_2' = 0 \quad \dots(ii)$$

6.24 Network Analysis and Synthesis

Writing Eqs (i) and (ii) in matrix form,

$$\begin{bmatrix} 0.37 - j0.1 & -(0.17 - j0.1) \\ -(0.17 - j0.1) & 0.67 - j0.2 \end{bmatrix} \begin{bmatrix} \mathbf{V}'_1 \\ \mathbf{V}'_2 \end{bmatrix} = \begin{bmatrix} 10 \angle 0^\circ \\ 0 \end{bmatrix}$$

By Cramer's rule,

$$\mathbf{V}'_2 = \frac{\begin{vmatrix} 0.37 - j0.1 & 10 \angle 0^\circ \\ -(0.17 - j0.1) & 0 \end{vmatrix}}{\begin{vmatrix} 0.37 - j0.1 & -(0.17 - j0.1) \\ -(0.17 - j0.1) & 0.67 - j0.2 \end{vmatrix}} = 8.57 \angle -3.36^\circ \text{ V}$$

Step II When the $5 \angle 0^\circ \text{ A}$ source is acting alone (Fig. 6.48)

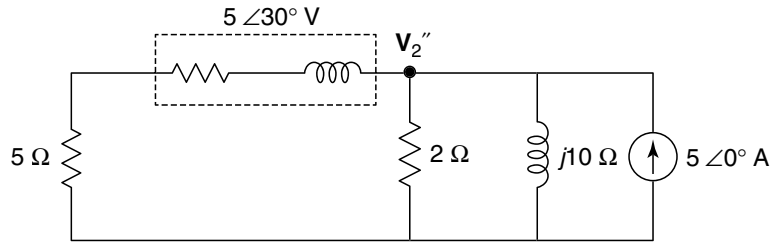


Fig. 6.48

$$\frac{\mathbf{V}_2''}{5 \angle 30^\circ + 5} + \frac{\mathbf{V}_2''}{2} + \frac{\mathbf{V}_2''}{j10} = 5 \angle 0^\circ$$

$$(0.61 \angle -11.93^\circ) \mathbf{V}_2'' = 5 \angle 0^\circ$$

$$\mathbf{V}_2'' = 8.2 \angle 11.93^\circ \text{ V}$$

Step III By superposition theorem,

$$\mathbf{V}_2 = \mathbf{V}_2' + \mathbf{V}_2'' = 8.57 \angle -3.36^\circ + 8.2 \angle 11.93^\circ = 16.62 \angle 4.12^\circ \text{ V}$$

Example 6.26

Find current through inductor in the network of Fig. 6.49.

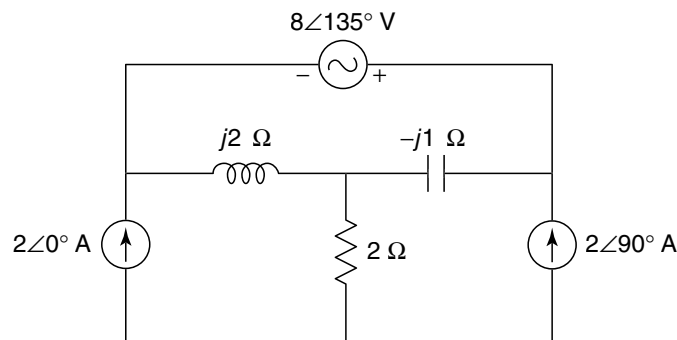


Fig. 6.49

Solution

Step I When the $8 \angle 135^\circ \text{ V}$ source is acting alone (Fig. 6.50)

Applying KVL to the mesh,

$$8 \angle 135^\circ - (-j1) \mathbf{I}' - j2 \mathbf{I}' = 0$$

$$\mathbf{I}' = \frac{8 \angle 135^\circ}{j1} = 8 \angle 45^\circ \text{ A } (\leftarrow) = 8 \angle -135^\circ \text{ A } (\rightarrow)$$

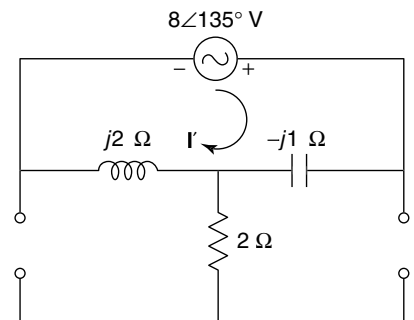


Fig. 6.50

Step II When the $2\angle 0^\circ$ A source is acting alone (Fig. 6.51)

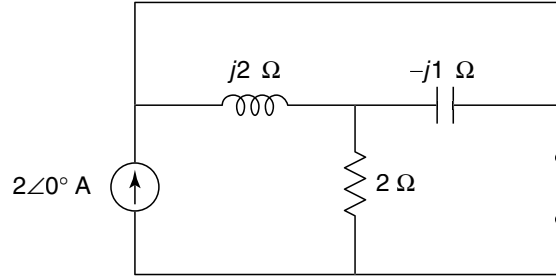


Fig. 6.51

The network can be redrawn as shown in Fig. 6.52.

By current division rule,

$$\mathbf{I}'' = 2\angle 0^\circ \left(\frac{-j1}{-j1 + j2} \right) = 2\angle 0^\circ \left(\frac{-j1}{j1} \right) = 2\angle 180^\circ \text{ A } (\rightarrow)$$

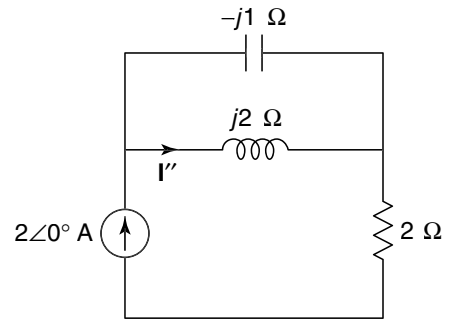


Fig. 6.52

Step III When the $2\angle 90^\circ$ A source is acting alone (Fig. 6.53)

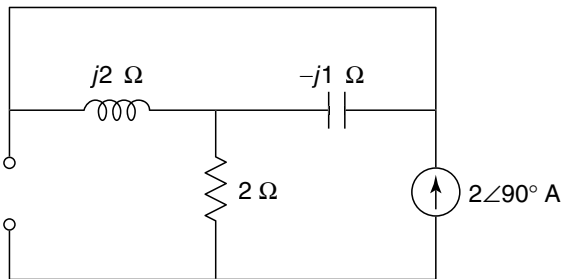


Fig. 6.53

The network can be redrawn as shown in Fig. 6.54.

By current division rule,

$$\mathbf{I}''' = 2\angle 90^\circ \left(\frac{-j1}{-j1 + j2} \right) = 2\angle -90^\circ \text{ A } (\leftarrow) = 2\angle 90^\circ \text{ A } (\rightarrow)$$

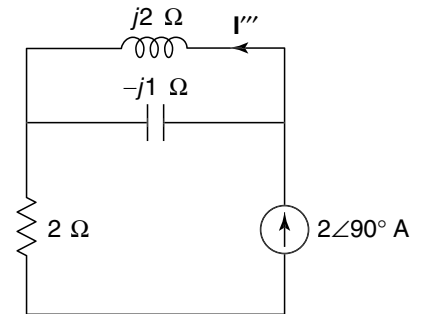


Fig. 6.54

Step III By superposition theorem,

$$\mathbf{I} = \mathbf{I}' + \mathbf{I}'' + \mathbf{I}''' = 8\angle -135^\circ + 2\angle 180^\circ + 2\angle 90^\circ = 8.49\angle -154.47^\circ \text{ A}$$

Example 6.27 Determine the source voltage V_s so that the current through $2\ \Omega$ resistor is zero in the network of Fig. 6.55.

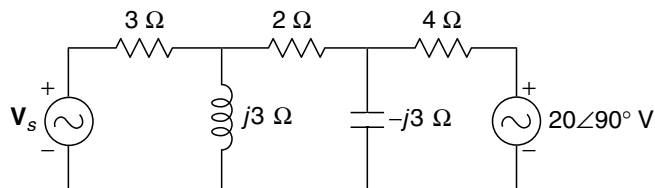
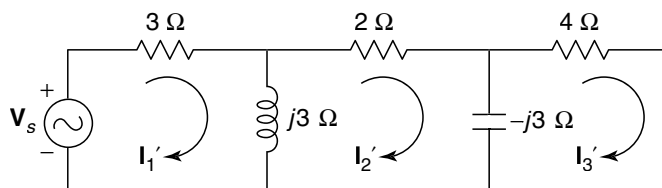


Fig. 6.55

Solution**Step I** When the voltage source V_s is acting alone (Fig. 6.56)**Fig. 6.56**

Applying KVL to Mesh 1,

$$\begin{aligned} V_s - 3I_1' - j3(I_1' - I_2') &= 0 \\ (3 + j3)I_1' - j3I_2' &= V_s \end{aligned} \quad \dots(i)$$

Applying KVL to Mesh 2,

$$\begin{aligned} -j3(I_2' - I_1') - 2I_2' + j3(I_2' - I_3') &= 0 \\ -j3I_1' + 2I_2' + j3I_3' &= 0 \end{aligned} \quad \dots(ii)$$

Applying KVL to Mesh 3,


$$\begin{aligned} -j3(I_3' - I_2') - 4I_3' &= 0 \\ j3I_2' + (4 - j3)I_3' &= 0 \end{aligned} \quad \dots(iii)$$

Writing Eqs (i), (ii) and (iii) in matrix form,

$$\begin{bmatrix} 3 + j3 & -j3 & 0 \\ -j3 & 2 & j3 \\ 0 & j3 & 4 - j3 \end{bmatrix} \begin{bmatrix} I_1' \\ I_2' \\ I_3' \end{bmatrix} = \begin{bmatrix} V_s \\ 0 \\ 0 \end{bmatrix}$$

By Cramer's rule,

$$I_2' = \frac{\begin{vmatrix} 3 + j3 & V_s & 0 \\ -j3 & 0 & j3 \\ 0 & 0 & 4 - j3 \end{vmatrix}}{\begin{vmatrix} 3 + j3 & -j3 & 0 \\ -j3 & 2 & j3 \\ 0 & j3 & 4 - j3 \end{vmatrix}} = \frac{(9 + j12)V_s}{\Delta}$$

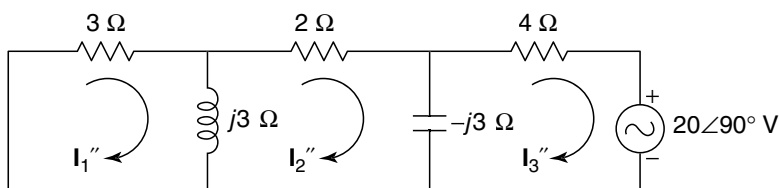Step II When the $20 \angle 90^\circ$ V source is acting alone (Fig. 6.57)**Fig. 6.57**

Applying KVL to Mesh 1,

$$\begin{aligned} -3I_1'' - j3(I_1'' - I_2'') &= 0 \\ (3 + j3)I_1'' - j3I_2'' &= 0 \end{aligned} \quad \dots(i)$$

Applying KVL to Mesh 2,

$$\begin{aligned} -j3(\mathbf{I}_2'' - \mathbf{I}_1'') - 2\mathbf{I}_2'' + j3(\mathbf{I}_2'' - \mathbf{I}_3'') &= 0 \\ -j3\mathbf{I}_1'' + 2\mathbf{I}_2'' + j3\mathbf{I}_3'' &= 0 \end{aligned} \quad \dots(\text{ii})$$

Applying KVL to Mesh 3,

$$\begin{aligned} j3(\mathbf{I}_3'' - \mathbf{I}_2'') - 4\mathbf{I}_3'' - 20\angle 90^\circ &= 0 \\ j3\mathbf{I}_2'' + (4 - j3)\mathbf{I}_3'' &= -20\angle 90^\circ \end{aligned} \quad \dots(\text{iii})$$

Writing Eqs (i), (ii) and (iii) in matrix form,

$$\begin{bmatrix} 3 + j3 & -j3 & 0 \\ -j3 & 2 & j3 \\ 0 & j3 & 4 - j3 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1'' \\ \mathbf{I}_2'' \\ \mathbf{I}_3'' \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ -20\angle 90^\circ \end{bmatrix}$$

By Cramer's rule,

$$\mathbf{I}_2'' = \frac{\begin{vmatrix} 3 + j3 & 0 & 0 \\ -j3 & 0 & j3 \\ 0 & -20\angle 90^\circ & 4 - j3 \end{vmatrix}}{\begin{vmatrix} 3 + j3 & -j3 & 0 \\ -j3 & 2 & j3 \\ 0 & j3 & 4 - j3 \end{vmatrix}} = \frac{-180 - j180}{\Delta}$$

Step III By superposition theorem,

$$\mathbf{I}_2 = \mathbf{I}_2' + \mathbf{I}_2'' = \frac{(9 + j12)\mathbf{V}_s + (-180 - j180)}{\Delta} = 0$$

$$(9 + j12)\mathbf{V}_s + (-180 - j180) = 0$$

$$(9 + j12)\mathbf{V}_s = 180 + j180$$

$$\mathbf{V}_s = 16.97\angle -8.13^\circ \text{ V}$$

6.5 THEVENIN'S THEOREM

Thevenin's theorem gives us a method for simplifying a network. In Thevenin's theorem, any linear network can be replaced by a voltage source $\mathbf{V}_{\text{Th}}$ in series with an impedance $\mathbf{Z}_{\text{Th}}$.

Example 6.28

Obtain Thevenin's equivalent network for the terminals A and B in Fig. 6.58.

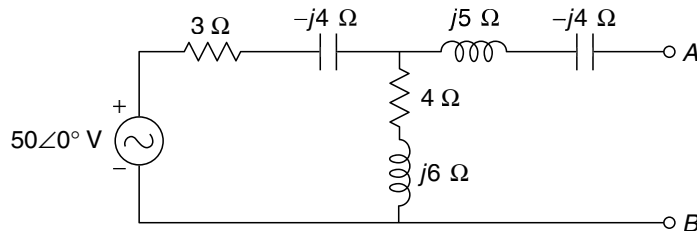


Fig. 6.58

6.28 Network Analysis and Synthesis

Solution

Step I Calculation of V_{Th} (Fig. 6.59)

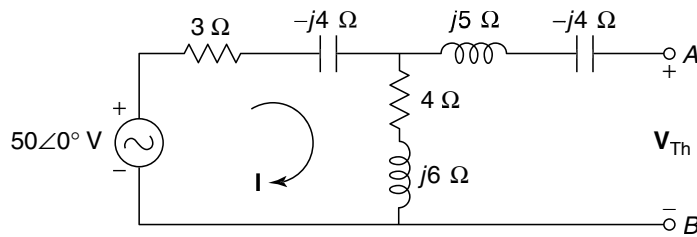


Fig. 6.59

Applying KVL to the mesh,

$$50 \angle 0^\circ - (3 - j4) \mathbf{I} - (4 + j6) \mathbf{I} = 0$$

$$\mathbf{I} = \frac{50 \angle 0^\circ}{(3 - j4) + (4 + j6)} = 6.87 \angle -15.95^\circ \text{ A}$$

$$\mathbf{V}_{Th} = (4 + j6) \mathbf{I} = (4 + j6) (6.87 \angle -15.95^\circ) = 49.5 \angle 40.35^\circ \text{ V}$$

Step II Calculation of Z_{Th} (Fig. 6.60)

$$\mathbf{Z}_{Th} = (j5 - j4) + \frac{(3 - j4)(4 + j6)}{(3 - j4) + (4 + j6)} = 4.83 \angle -1.13^\circ \Omega$$

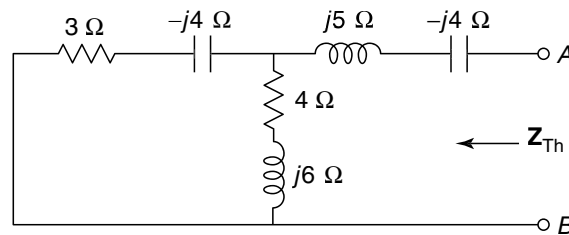


Fig. 6.60

Step III Thevenin's Equivalent Network (Fig. 6.61)

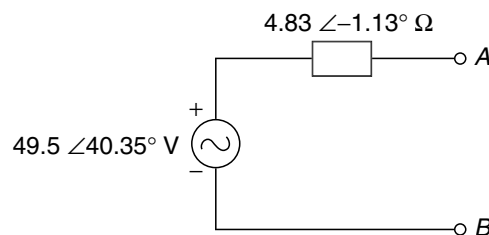


Fig. 6.61

Example 6.29

Find Thevenin's equivalent network for Fig. 6.62.

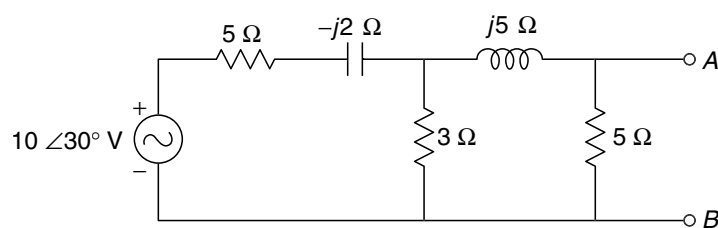
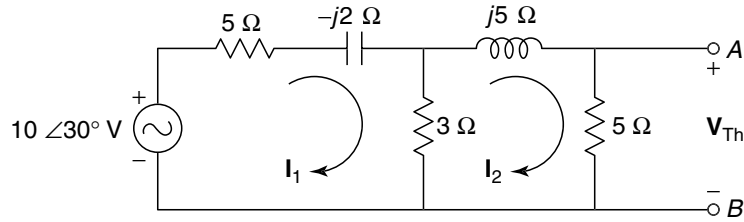


Fig. 6.62

Solution**Step I** Calculation of V_{Th} (Fig. 6.63)**Fig. 6.63**

Applying KVL to Mesh 1,

$$10 \angle 30^\circ - (5 - j2) I_1 - 3(I_1 - I_2) = 0$$

$$(8 - j2) I_1 - 3I_2 = 10 \angle 30^\circ \quad \dots(i)$$

Applying KVL to Mesh 2,

$$-3(I_2 - I_1) - j5 I_2 - 5 I_2 = 0$$

$$-3I_1 + (8 + j5) I_2 = 0 \quad \dots(ii)$$

Writing Eqs (i) and (ii) in matrix form;

$$\begin{bmatrix} 8 - j2 & -3 \\ -3 & 8 + j5 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 10 \angle 30^\circ \\ 0 \end{bmatrix}$$



By Cramer's rule,

$$I_2 = \frac{\begin{vmatrix} 8 - j2 & 10 \angle 30^\circ \\ -3 & 0 \end{vmatrix}}{\begin{vmatrix} 8 - j2 & -3 \\ -3 & 8 + j5 \end{vmatrix}} = 0.433 \angle 9.7^\circ \text{ A}$$

$$V_{Th} = 5I_2 = 5(0.433 \angle 9.7^\circ) = 2.16 \angle 9.7^\circ \text{ V}$$



Step II Calculation of Z_{Th} (Fig. 6.64)

$$\begin{aligned} Z_{Th} &= \left[\left\{ \frac{(5 - j2)3}{5 - j2 + 3} \right\} + j5 \right] \parallel 5 \\ &= [1.94 - j0.265 + j5] \parallel 5 = (1.94 + j4.735) \parallel 5 \\ &= \frac{(1.94 + j4.735)5}{6.94 + j4.735} = 3.04 \angle 33.4^\circ \Omega \end{aligned}$$

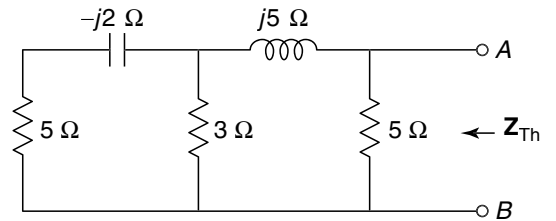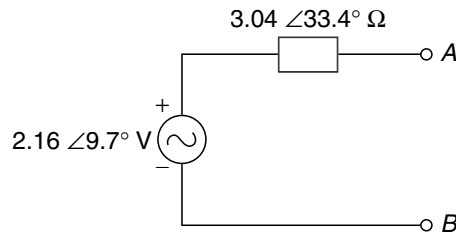**Fig. 6.64****Step III** Thevenin's equivalent Network (Fig. 6.65)**Fig. 6.65**

Example 6.30

Obtain Thevenin's equivalent network for Fig. 6.66.

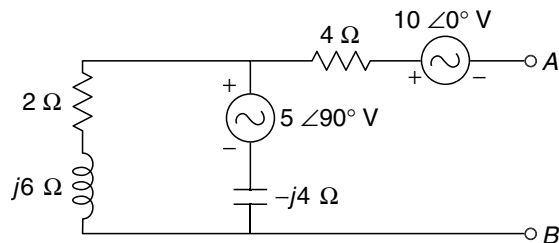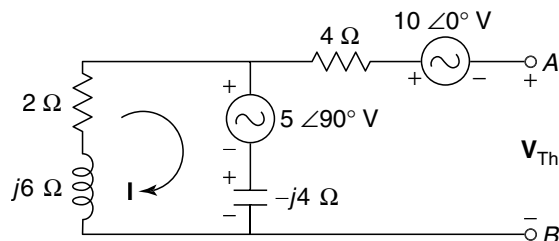
**Fig. 6.66****Solution****Step I** Calculation of V_{Th} **Fig. 6.67**

Applying KVL to the mesh,


$$(2 + j6 - j4)I - 5\angle 90^\circ = 0$$

$$I = \frac{5\angle 90^\circ}{2 + j2} = 1.77\angle 45^\circ \text{ A}$$

$$V_{Th} = (-j4)I + 5\angle 90^\circ - 10\angle 0^\circ = (4\angle -90^\circ)(1.77\angle 45^\circ) + 5\angle 90^\circ - 10\angle 0^\circ = 18\angle 146.31^\circ \text{ V}$$

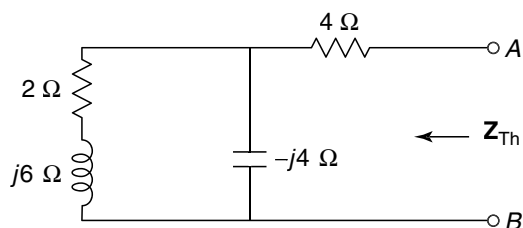
Step II Calculation of Z_{Th} (Fig. 6.67)**Fig. 6.68**

$$Z_{Th} = 4 + \frac{(2 + j6)(-j4)}{2 + j2} = 11.3\angle -44.93^\circ \Omega$$

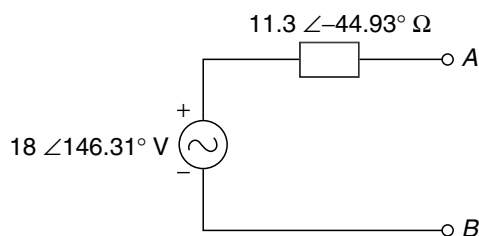Step III Thevenin's Equivalent Network**Fig. 6.69**

Example 6.31

Obtain Thevenin's equivalent network for Fig. 6.70.

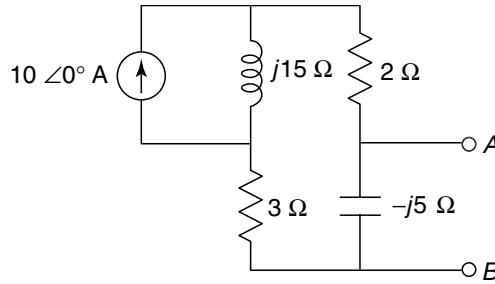**Fig. 6.70****Solution**

Step I Calculation of V_{Th} (Fig. 6.71)
By current division rule,




$$I = \frac{(10\angle 0^\circ)(j15)}{5 - j5 + j15} = 13.42\angle 26.57^\circ \text{ A}$$

$$V_{Th} = (-j5) I \\ = (5\angle -90^\circ)(13.42\angle 26.57^\circ) = 67.08\angle -63.43^\circ \text{ V}$$


Step II Calculation of Z_{Th} (Fig. 6.72)

$$Z_{Th} = \frac{(-j5)(5 + j15)}{-j5 + 5 + j15} = 7.07\angle -81.86^\circ \Omega$$

Step III Thevenin's Equivalent Network

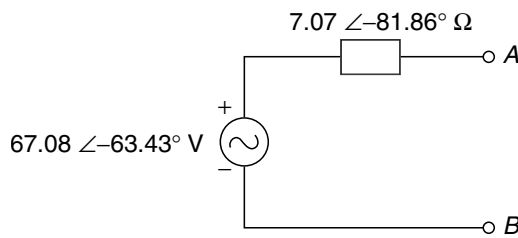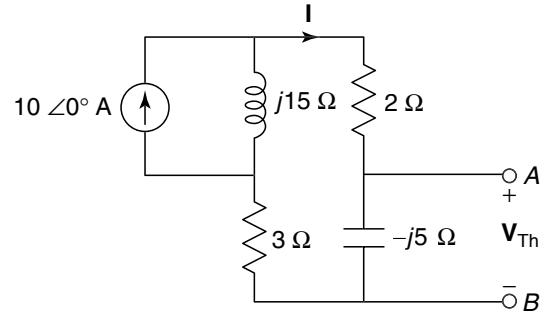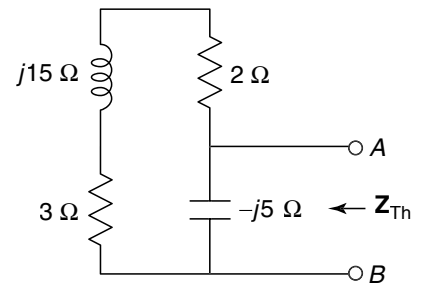**Fig. 6.73****Fig. 6.71****Fig. 6.72****Example 6.32**

Obtain Thevenin's equivalent network for Fig. 6.74.

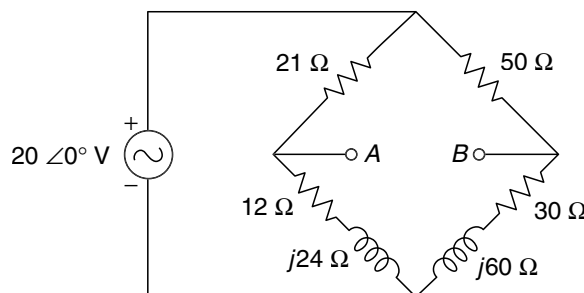**Fig. 6.74**

6.32 Network Analysis and Synthesis

Solution

Step I Calculation of V_{Th} (Fig 6.75)

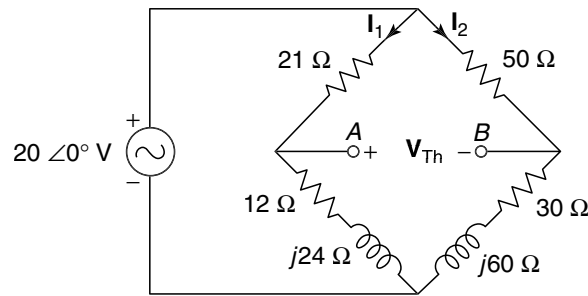


Fig. 6.75

$$I_1 = \frac{20\angle 0^\circ}{21 + 12 + j24} = 0.49\angle -36.02^\circ \text{ A}$$

$$I_2 = \frac{20\angle 0^\circ}{80 + j60} = 0.2\angle -36.86^\circ \text{ A}$$

$$\begin{aligned} V_{Th} &= (12 + j24) I_1 - (30 + j60) I_2 \\ &= (26.83 \angle 63.43^\circ) (0.49 \angle -36.02^\circ) - (67.08 \angle 63.43^\circ) (0.2 \angle -36.86^\circ) \\ &= 0.33 \angle 171.12^\circ \text{ V} \end{aligned}$$

Step II Calculation of Z_{Th} (Fig. 6.76)

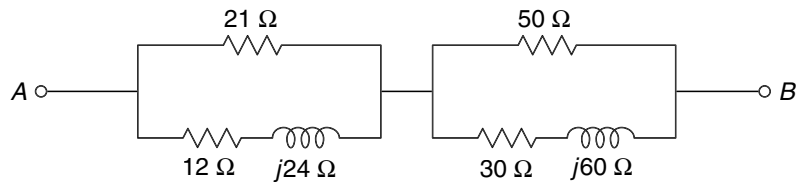


Fig. 6.76

$$Z_{Th} = \frac{21(12 + j24)}{33 + j24} + \frac{50(30 + j60)}{80 + j60} = 47.4\angle 26.8^\circ \Omega$$

Step III Thevenin's Equivalent Network

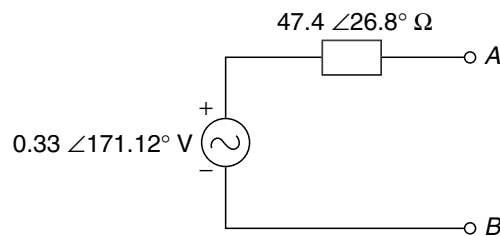
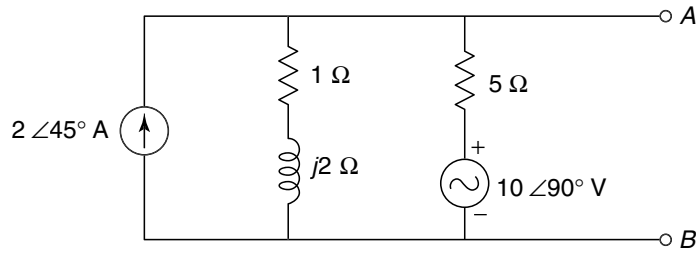


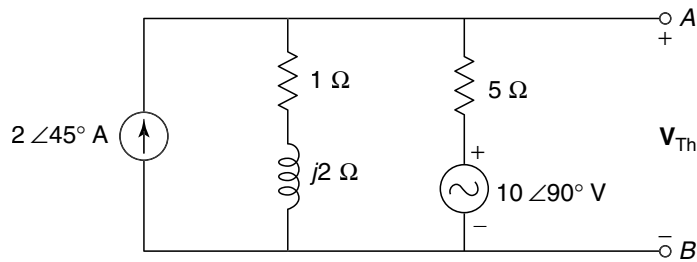
Fig. 6.77

Example 6.33

Find Thevenin's equivalent network across terminals A and B for Fig. 6.78.

**Fig. 6.78****Solution**

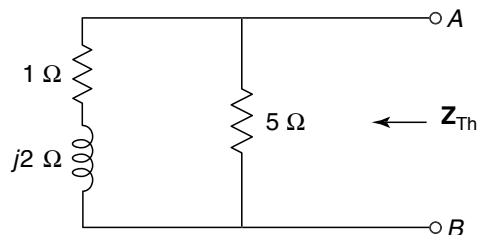
Step I Calculation of V_{Th} (Fig. 6.79)

**Fig. 6.79**

Applying KCL at the node,

$$\begin{aligned}\frac{V_{Th}}{1+j2} + \frac{V_{Th} - 10\angle 90^\circ}{5} &= 2\angle 45^\circ \\ \left(\frac{1}{1+j2} + \frac{1}{5} \right) V_{Th} &= 2\angle 45^\circ + 2\angle 90^\circ \\ (0.57\angle -45^\circ) V_{Th} &= 3.7\angle 67.5^\circ \\ V_{Th} &= 6.49\angle 112.5^\circ \text{ V}\end{aligned}$$

Step II Calculation of Z_{Th} (Fig. 6.80)

**Fig. 6.80**

$$Z_{Th} = \frac{5(1+j2)}{5+1+j2} = 1.77\angle 45^\circ \Omega$$

6.34 Network Analysis and Synthesis

Step III Thevenin's Equivalent Network (Fig. 6.81)

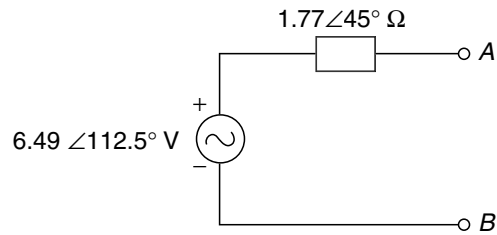


Fig. 6.81

Example 6.34

Find the current through the $(5 + j2) \Omega$ impedance in the network of Fig. 6.82.

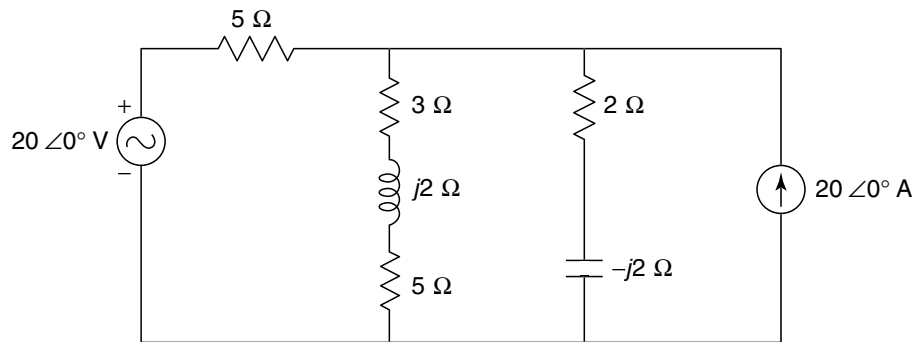


Fig. 6.82

Solution

Step I Calculation of V_{Th} (Fig. 6.83)

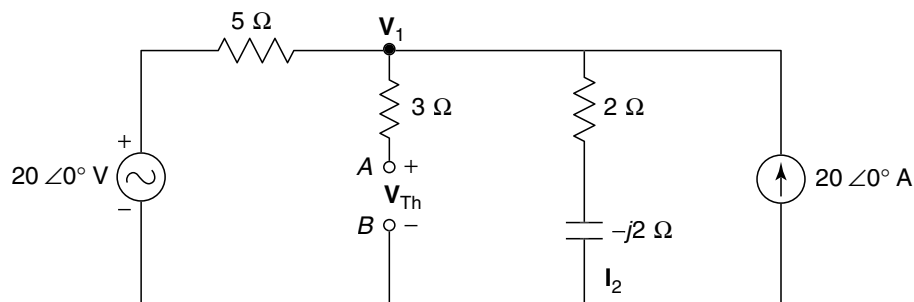


Fig. 6.83

Applying KCL at the node,

$$\begin{aligned} \frac{V_1 - 20 \angle 0^\circ}{5} + \frac{V_1}{2 - j2} &= 20 \angle 0^\circ \\ \left(\frac{1}{5} + \frac{1}{2 - j2} \right) V_1 &= 20 \angle 0^\circ + 4 \angle 0^\circ \\ 0.51 \angle 29.05^\circ V_1 &= 24 \angle 0^\circ \\ V_1 &= 47.06 \angle -29.05^\circ \text{ V} \\ V_{\text{Th}} = V_1 &= 47.06 \angle -29.05^\circ \text{ V} \end{aligned}$$

Step II Calculation of $\mathbf{Z}_{Th}$ (Fig. 6.84)

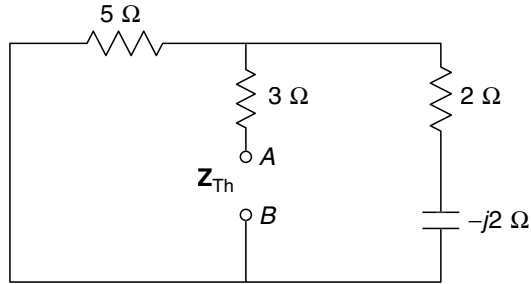


Fig. 6.84

$$\mathbf{Z}_{Th} = 3 + \frac{5(2 - j2)}{5 + 2 - j2} = 4.79 \angle -11.35^\circ \Omega$$

Step III Calculation of $\mathbf{I}_L$ (Fig. 6.85)

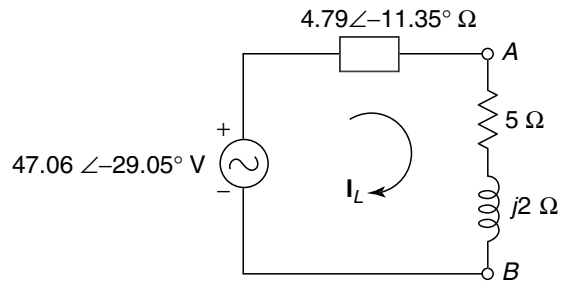


Fig. 6.85

$$\mathbf{I}_L = \frac{47.06 \angle -29.05^\circ}{4.79 \angle -11.35^\circ + 5 + j2} = 4.73 \angle -39.96^\circ \text{ A}$$

Example 6.35

Find the current through the 5Ω resistor in the network of Fig. 6.86.

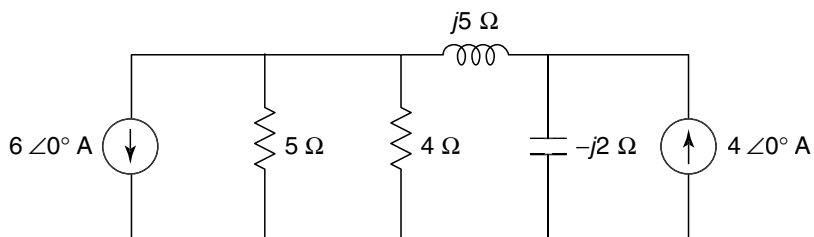


Fig. 6.86

Solution

Step I Calculation of $\mathbf{V}_{Th}$ (Fig. 6.87)

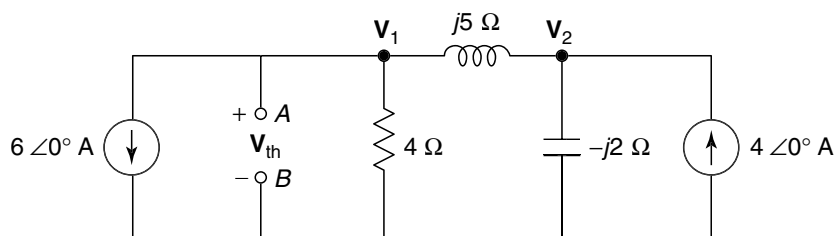


Fig. 6.87

6.36 Network Analysis and Synthesis

Applying KCL at Node 1,

$$\begin{aligned}\frac{V_1}{4} + \frac{V_1 - V_2}{j5} + 6\angle 0^\circ &= 0 \\ \left(\frac{1}{4} + \frac{1}{j5}\right)V_1 - \frac{1}{j5}V_2 &= -6\angle 0^\circ \\ (0.25 - j0.2)V_1 + j0.2V_2 &= -6\angle 0^\circ\end{aligned}\quad \dots(i)$$

Applying KCL at Node 2,

$$\begin{aligned}\frac{V_2 - V_1}{j5} + \frac{V_2}{-j2} &= 4\angle 0^\circ \\ \left(-\frac{1}{j5}\right)V_1 + \left(\frac{1}{j5} - \frac{1}{j2}\right)V_2 &= 4\angle 0^\circ \\ j0.2V_1 + j0.3V_2 &= 4\angle 0^\circ\end{aligned}\quad \dots(ii)$$

Writing Eqs (i) and (ii) in matrix form,

$$\begin{bmatrix} 0.25 - j0.2 & j0.2 \\ j0.2 & j0.3 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} -6\angle 0^\circ \\ 4\angle 0^\circ \end{bmatrix}$$

By Cramer's rule,

$$\begin{aligned}V_1 &= \frac{\begin{vmatrix} -6\angle 0^\circ & j0.2 \\ 4\angle 0^\circ & j0.3 \end{vmatrix}}{\begin{vmatrix} 0.25 - j0.2 & j0.2 \\ j0.2 & j0.3 \end{vmatrix}} = 20.8\angle -126.87^\circ \text{ V} \\ V_{Th} = V_1 &= 20.8\angle -126.87^\circ \text{ V}\end{aligned}$$

Step II Calculation of Z_{Th} (Fig. 6.88)

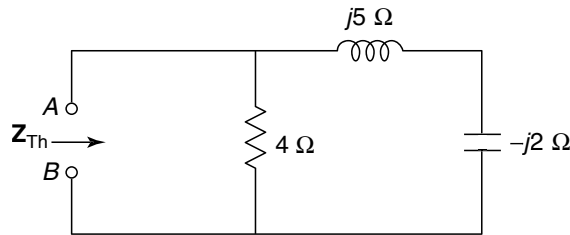


Fig. 6.88

$$Z_{Th} = \frac{4(-j2 + j5)}{4 - j2 + j5} = 2.4\angle 53.13^\circ \Omega$$

Step III Calculation of I_L (Fig. 6.89)

$$I_L = \frac{20.8\angle -126.87^\circ}{2.4\angle 53.13^\circ + 5} = 3.1\angle -143.47^\circ \text{ A}$$

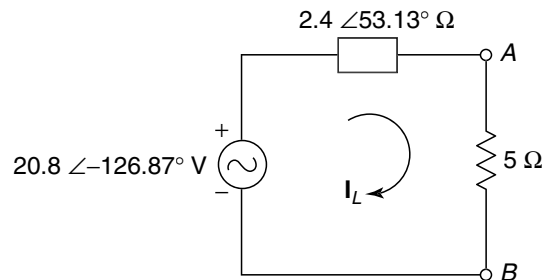
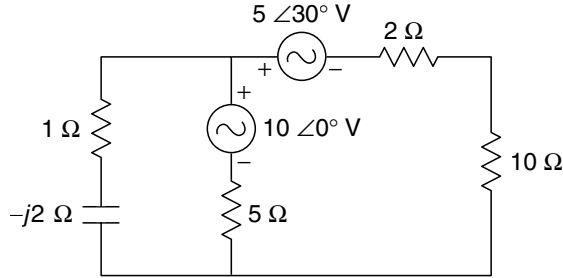


Fig. 6.89

Example 6.36

In the network of Fig. 6.90, find the current through the $10\ \Omega$ resistor.

**Fig. 6.90****Solution**

Step I Calculation of V_{Th} (Fig. 6.91)

Applying KVL to the mesh,

$$j2I - 1I - 10\angle 0^\circ - 5I = 0$$

$$(j2 - 6)I = 10\angle 0^\circ$$


$$I = 1.58\angle -161.57^\circ\text{ A}$$

Writing V_{Th} equation,

$$5I + 10\angle 0^\circ - 5\angle 30^\circ - 0 - V_{Th} = 0$$


$$5(1.58\angle -161.57^\circ) - 10\angle 0^\circ - 5\angle 30^\circ - V_{Th} = 0$$

$$V_{Th} = 5.32\angle -110.06^\circ\text{ V}$$

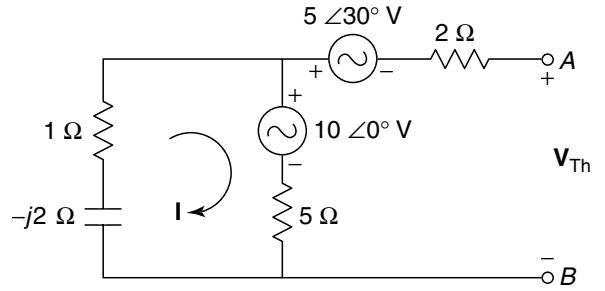
**Fig. 6.91**

Step II Calculation of Z_{Th} (Fig. 6.92)

$$Z_{Th} = 2 + \frac{5(1 - j2)}{5 + 1 - j2} = 3.48\angle -21.04^\circ\ \Omega$$

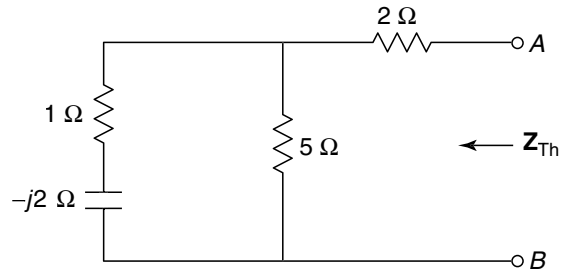**Fig. 6.92**

Step III Calculation of I_L (Fig. 6.93)

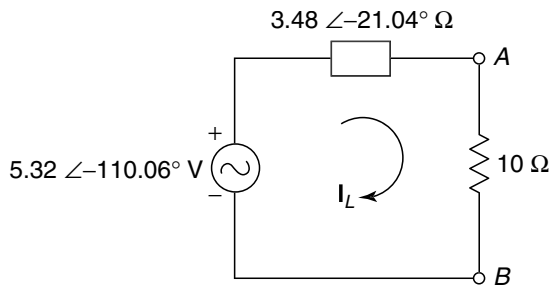**Fig. 6.93**

$$I_L = \frac{5.32\angle -110.06^\circ}{3.48\angle -21.04^\circ + 10} = 0.4\angle -104.67^\circ\text{ A}$$

Example 6.37 Find the current through $(4 + j6) \Omega$ impedance in the network of Fig. 6.94.

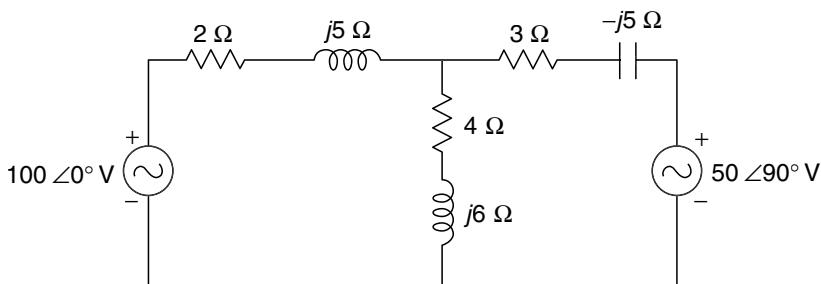


Fig. 6.94

Solution

Step I Calculation of V_{Th} (Fig. 6.95)

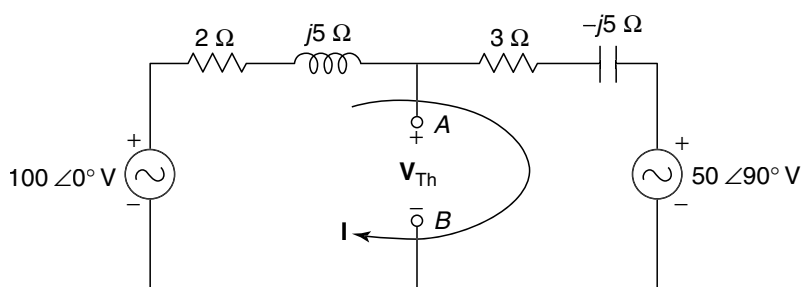


Fig. 6.95

Applying KVL to the mesh,

$$100\angle 0^\circ - 2I - j5I - 3I + j5I - 50\angle 90^\circ = 0$$

$$I = 22.36\angle -26.57^\circ \text{ A}$$

Writing V_{Th} equation,

$$V_{Th} - 3I + j5I - 50\angle 90^\circ = 0$$

$$V_{Th} - (3 - j5)(22.36\angle -26.57^\circ) - 50\angle 90^\circ = 0$$

$$V_{Th} = 80.61\angle -82.88^\circ \text{ V}$$

Step II Calculation of Z_{Th} (Fig. 6.96)

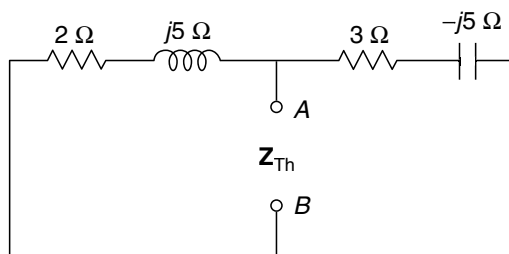


Fig. 6.96

$$Z_{Th} = \frac{(2 + j5)(3 - j5)}{2 + j5 + 3 - j5} = 6.28\angle 9.16^\circ \Omega$$

Step III Calculation of I_L (Fig. 6.97)

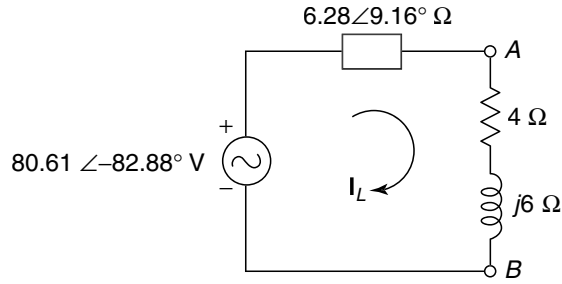


Fig. 6.97

$$I_L = \frac{80.61 \angle -82.88^\circ}{6.28 \angle 9.16^\circ + 4 + j6} = 6.52 \angle -117.34^\circ \text{ A}$$

Example 6.38

Obtain Thevenin's equivalent network across terminals A and B in Fig. 6.98.

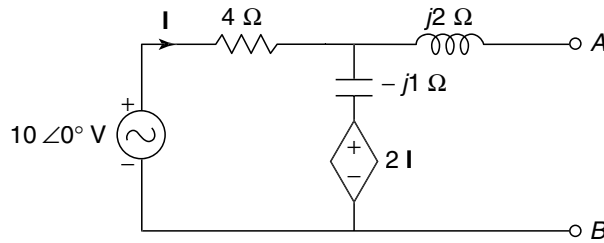


Fig. 6.98

Solution

Step I Calculation of V_{Th} (Fig. 6.99)

Applying KVL to the mesh,

$$10 \angle 0^\circ - 4I + j1I - 2I = 0$$

$$I = 1.64 \angle 9.46^\circ \text{ A}$$

Writing V_{Th} equation,

$$10 \angle 0^\circ - 4I - 0 - V_{Th} = 0$$

$$10 \angle 0^\circ - 4(1.64 \angle 9.46^\circ) - V_{Th} = 0$$

$$V_{Th} = 3.69 \angle -17^\circ \text{ V}$$

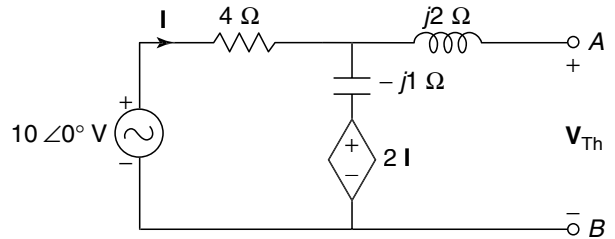


Fig. 6.99

Step II Calculation of I_N (Fig. 6.100)

From Fig. 6.100,

$$I = I_1$$

Applying KVL to Mesh 1,

$$10 \angle 0^\circ - 4I_1 + j1(I_1 - I_2) - 2I_1 = 0$$

$$10 \angle 0^\circ - 4I_1 + j1I_1 - j1I_2 - 2I_1 = 0$$

$$(6 - j1)I_1 + j1I_2 = 10 \angle 0^\circ \quad \dots(i)$$

Applying KVL to Mesh 2,

$$2I_1 + j1(I_2 - I_1) - j2I_2 = 0$$

$$2I_1 + j1I_2 - j1I_1 - j2I_2 = 0$$

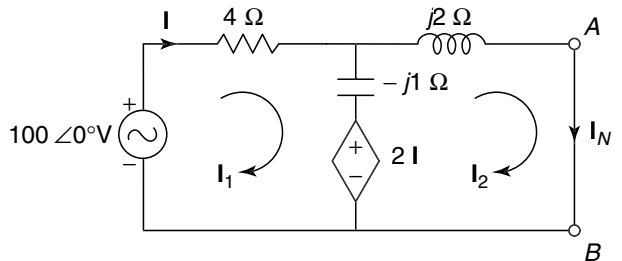


Fig. 6.100

$$(2 - j1)\mathbf{I}_1 - j1\mathbf{I}_2 = 0 \quad \dots(\text{ii})$$

Writing Eqs (i) and (ii) in matrix form,

$$\begin{bmatrix} 6 - j1 & j1 \\ 2 - j1 & -j1 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 10\angle 0^\circ \\ 0 \end{bmatrix}$$

By Cramer's rule,

$$\mathbf{I}_2 = \frac{\begin{vmatrix} 6 - j1 & 10\angle 0^\circ \\ 2 - j1 & 0 \end{vmatrix}}{\begin{vmatrix} 6 - j1 & j1 \\ 2 - j1 & -j1 \end{vmatrix}} = 2.71\angle -102.53^\circ \text{ A}$$

$$\mathbf{I}_N = \mathbf{I}_2 = 2.71\angle -102.53^\circ \text{ A}$$

Step III Calculation of $\mathbf{Z}_{Th}$

$$\mathbf{Z}_{Th} = \frac{\mathbf{V}_{Th}}{\mathbf{I}_N} = \frac{3.69\angle -17^\circ}{2.71\angle -102.53^\circ} = 1.36\angle 85.53^\circ \Omega$$

Step IV Thevenin's Equivalent Network (Fig. 6.101)

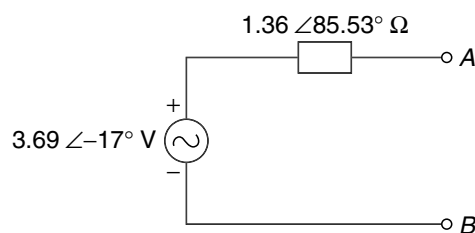


Fig. 6.101

Example 6.39

Find Thevenin's equivalent network across terminals A and B for Fig. 6.102.

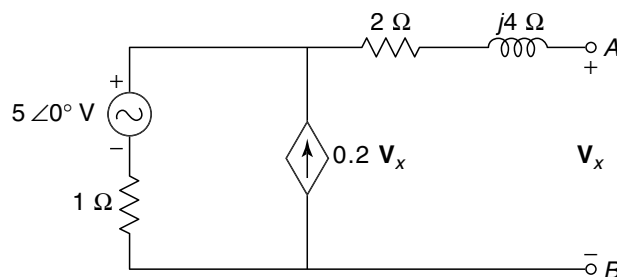


Fig. 6.102

Solution

Step I Calculation of $\mathbf{V}_{Th}$ (Fig. 6.103)

From Fig. 6.103,

$$\mathbf{I} = -0.2\mathbf{V}_x$$

Writing $\mathbf{V}_{Th}$ equation,

$$-\mathbf{I} + 5\angle 0^\circ - 0 - \mathbf{V}_x = 0$$

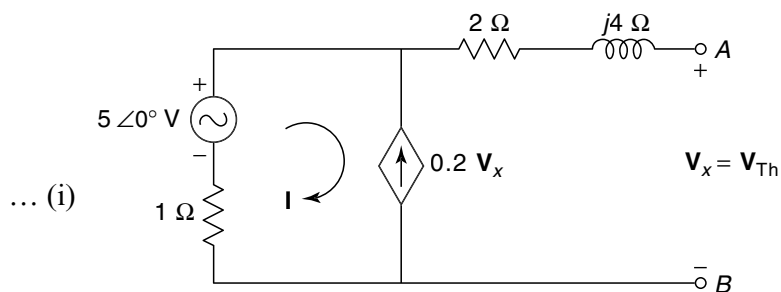


Fig. 6.103

$$0.2V_x + 5\angle 0^\circ - V_x = 0$$

$$V_x = 6.25\angle 0^\circ \text{ V}$$

$$V_{Th} = V_x = 6.25\angle 0^\circ \text{ V}$$

Step II Calculation of I_N (Fig. 6.104)

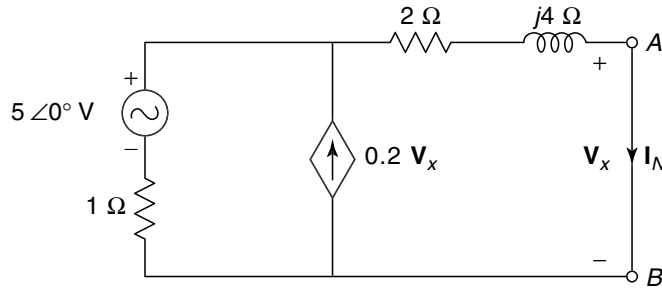


Fig. 6.104

From Fig. 6.104,

$$V_x = 0$$

The dependent source depends on the controlling variable V_x . When $V_x = 0$, the dependent source vanishes, i.e. $0.2V_x = 0$ as shown in Fig. 6.105.

$$I_N = \frac{5\angle 0^\circ}{1 + 2 + j4} = 1\angle -53.13^\circ \text{ A}$$

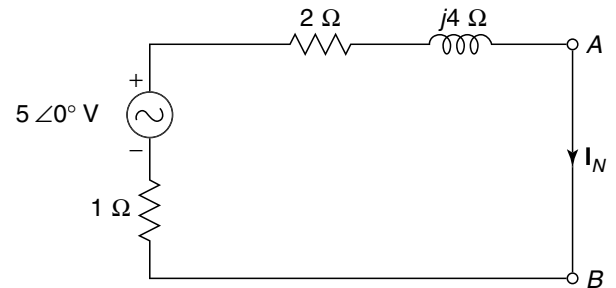


Fig. 6.105

Step III Calculation of Z_{Th}

$$Z_{Th} = \frac{V_{Th}}{I_N} = \frac{6.25\angle 0^\circ}{1\angle -53.13^\circ} = 6.25\angle 53.13^\circ \Omega$$

Step IV Thevenin's Equivalent Network (Fig. 6.106)

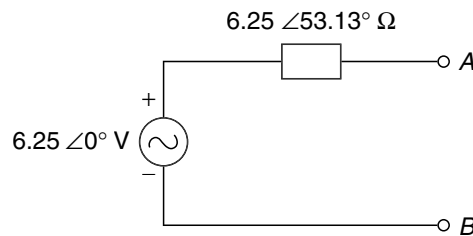


Fig. 6.106

6.6 || NORTON'S THEOREM

Norton's theorem states that *any linear network can be replaced by a current source I_N parallel with an impedance Z_N where I_N is the current flowing through the short-circuited path placed across the terminals.*

Example 6.40 Obtain Norton's equivalent network between terminals A and B as shown in Fig. 6.107.

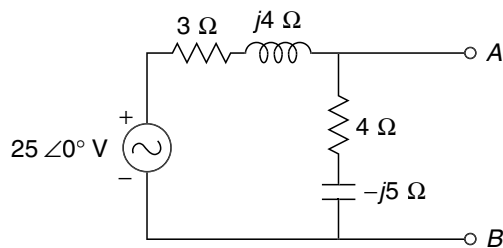


Fig. 6.107

Solution

Step I Calculation of I_N (Fig. 6.108)

When a short circuit is placed across $(4 - j4) \Omega$ impedance, it gets shorted as shown in Fig. 6.109.

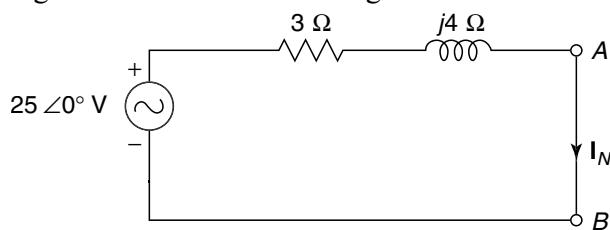


Fig. 6.109

$$I_N = \frac{25 \angle 0^\circ}{3 + j4} = 5 \angle -53.13^\circ \text{ A}$$

Step II Calculation of Z_N (Fig. 6.110)

$$Z_N = \frac{(3 + j4)(4 - j5)}{3 + j4 + 4 - j5} = 4.53 \angle 9.92^\circ \Omega$$

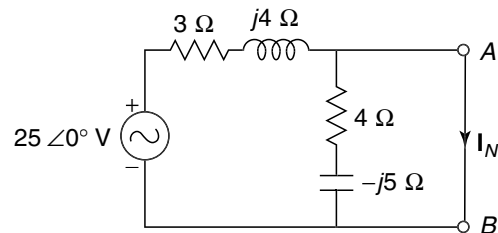


Fig. 6.108

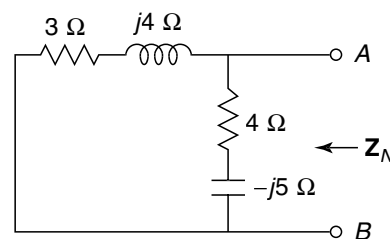


Fig. 6.110

Step III Norton's Equivalent Network

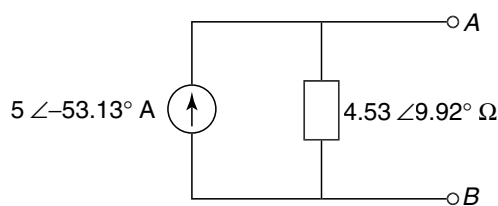


Fig. 6.111

Example 6.41 Obtain Norton's equivalent network at the terminals A and B in Fig. 6.112.

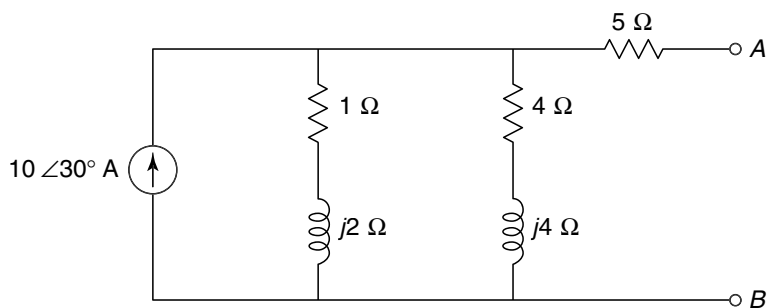
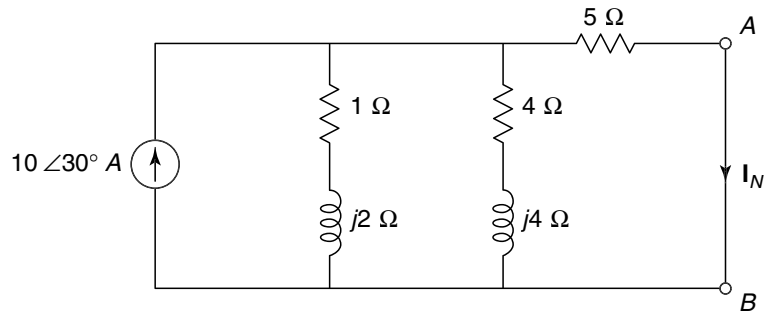
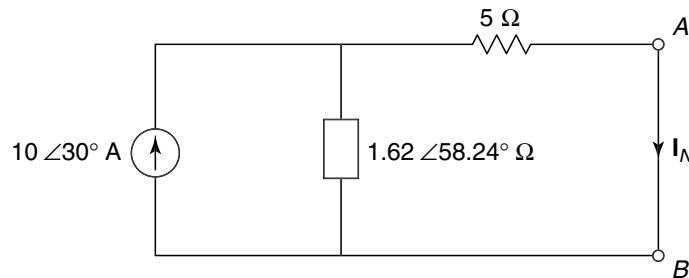



Fig. 6.112

Solution**Step I** Calculation of $\mathbf{I}_N$ (Fig. 6.113)**Fig. 6.113**

By series-parallel reduction technique (Fig. 6.114)

**Fig. 6.114**

$$\mathbf{I}_N = (10\angle 30^\circ) \left(\frac{1.62\angle 58.24^\circ}{1.62\angle 58.24^\circ + 5} \right) = 2.69\angle 75^\circ \text{ A}$$

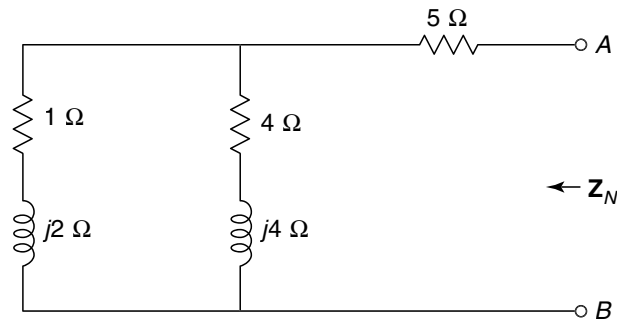Step II Calculation of $\mathbf{Z}_N$ (Fig. 6.115)**Fig. 6.115**

$$\mathbf{Z}_N = 5 + \frac{(1 + j2)(4 + j4)}{1 + j2 + 4 + j4} = 6.01\angle 13.24^\circ \Omega$$

6.44 Network Analysis and Synthesis

Step III Norton's Equivalent Network (Fig. 6.116)

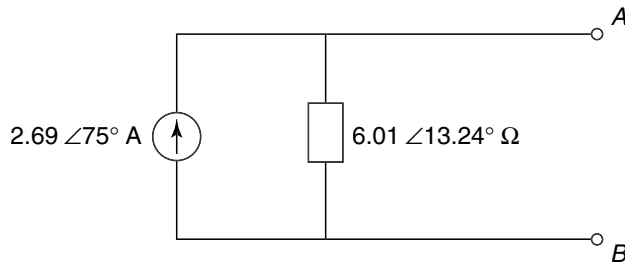


Fig. 6.116

Example 6.42

Find Norton's equivalent network across terminals A and B in Fig. 6.117.

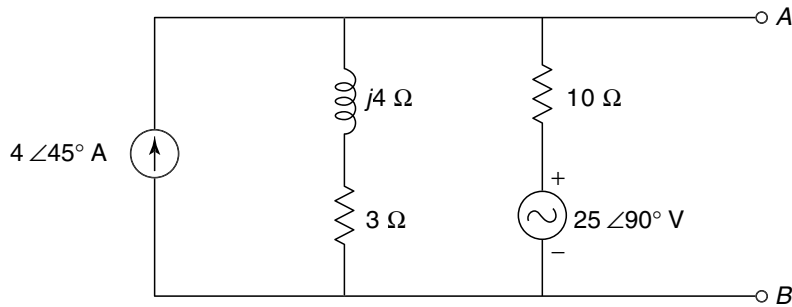


Fig. 6.117

Solution

Step I Calculation of I_N (Fig. 6.118)

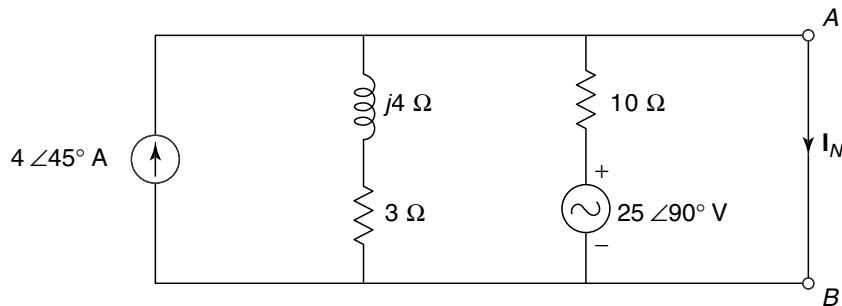


Fig. 6.118

When a short circuit is placed across the $(3 + j4) \Omega$ impedance, it gets shorted as shown in Fig. 6.119.

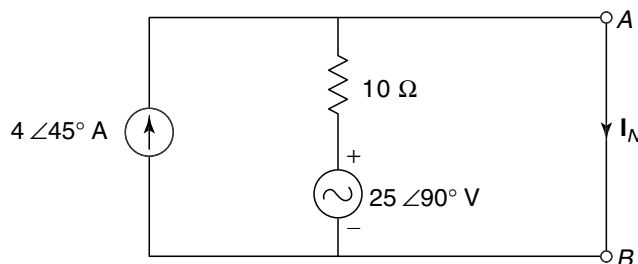


Fig. 6.119

By source transformation, the network is redrawn as shown in Fig. 6.120.

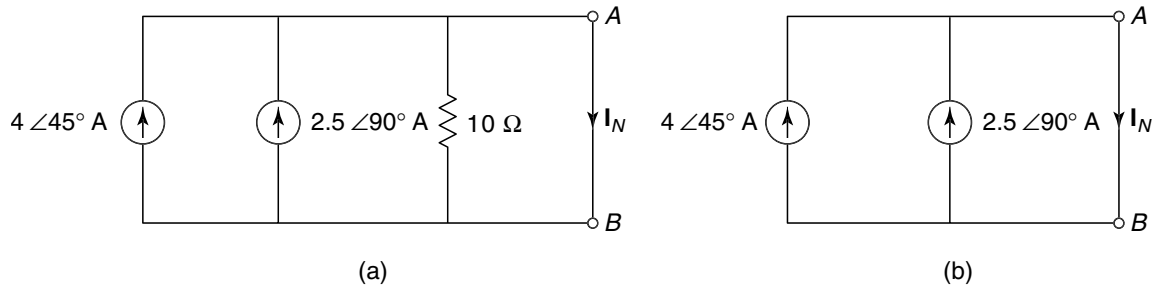


Fig. 6.120

$$I_N = 4\angle 45^\circ + 2.5\angle 90^\circ = 6.03\angle 62.04^\circ \text{ A}$$

Step II Calculation of Z_N (Fig. 6.121)

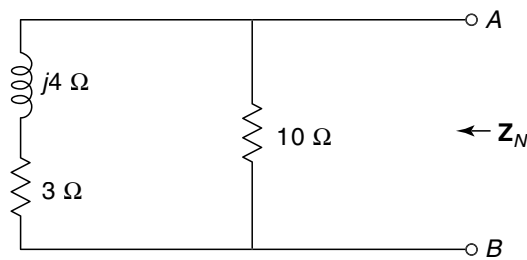


Fig. 6.121

$$Z_N = \frac{10(3 + j4)}{10 + 3 + j4} = 3.68\angle 36.03^\circ \Omega$$

Step III Norton's Equivalent Network (Fig. 6.122)

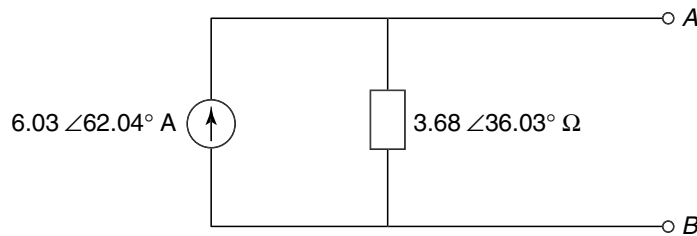


Fig. 6.122

Example 6.43

Obtain the Norton's equivalent network for Fig. 6.123.

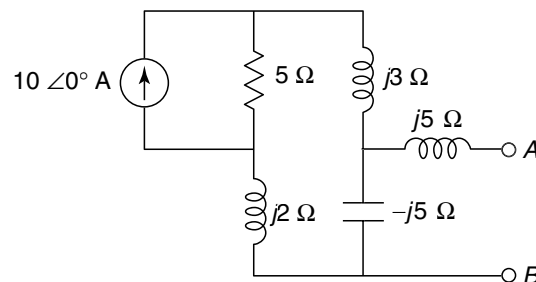


Fig. 6.123

6.46 Network Analysis and Synthesis

Solution

Step I Calculation of $\mathbf{I}_N$ (Fig. 6.124)

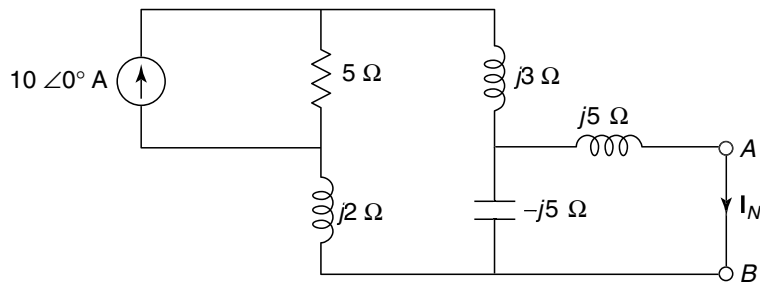


Fig. 6.124

By source transformation, the network can be redrawn as shown in Fig. 6.125.

Writing KVL equations in matrix form,

$$\begin{bmatrix} 5 & j5 \\ j5 & 0 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 50\angle 0^\circ \\ 0 \end{bmatrix}$$

By Cramer's rule,

$$\mathbf{I}_2 = \frac{\begin{vmatrix} 5 & 50\angle 0^\circ \\ j5 & 0 \end{vmatrix}}{\begin{vmatrix} 5 & j5 \\ j5 & 0 \end{vmatrix}} = 10\angle -90^\circ \text{ A}$$

$$\mathbf{I}_N = \mathbf{I}_2 = 10\angle -90^\circ \text{ A}$$

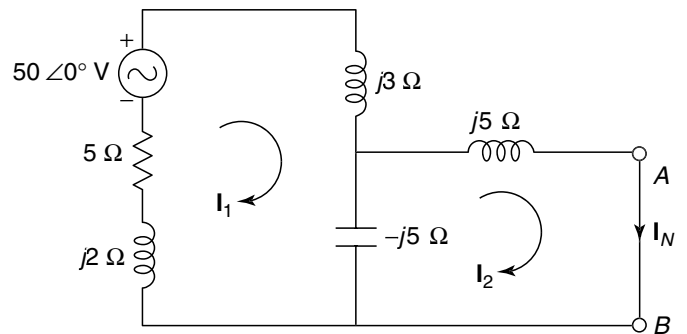


Fig. 6.125

Step II Calculation of $\mathbf{Z}_N$ (Fig. 6.126)

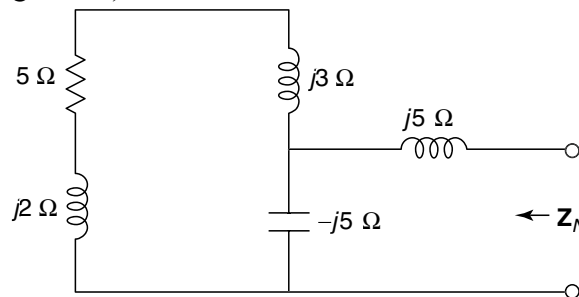


Fig. 6.126

$$\mathbf{Z}_N = j5 + \frac{(5 + j5)(-j5)}{5 + j5 - j5} = 5 \Omega$$

Step III Norton's Equivalent Network (Fig. 6.127)

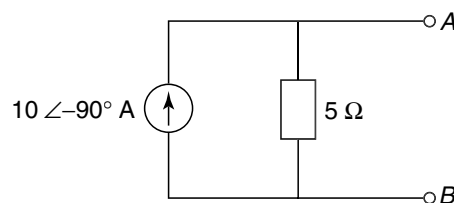
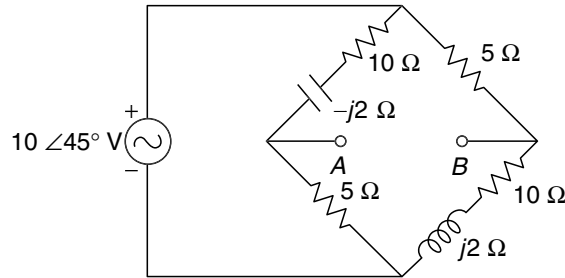


Fig. 6.127

Example 6.44

Obtain the Norton's equivalent network for Fig. 6.128.

**Fig. 6.128****Solution****Step I** Calculation of $\mathbf{I}_N$ (Fig. 6.129)

Writing KVL equations in matrix form,



$$\begin{bmatrix} 15 - j2 & -10 + j2 & -5 \\ -10 + j2 & 15 - j2 & 0 \\ -5 & 0 & 15 + j2 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 10\angle 45^\circ \\ 0 \\ 0 \end{bmatrix}$$

By Cramer's rule,


$$\mathbf{I}_2 = \frac{\begin{vmatrix} 15 - j2 & 10\angle 45^\circ & -5 \\ -10 + j2 & 0 & 0 \\ -5 & 0 & 15 + j2 \end{vmatrix}}{\begin{vmatrix} 15 - j2 & -10 + j2 & -5 \\ -10 + j2 & 15 - j2 & 0 \\ -5 & 0 & 15 + j2 \end{vmatrix}} = 1\angle 41.28^\circ \text{ A}$$

$$\mathbf{I}_3 = \frac{\begin{vmatrix} 15 - j2 & -10 + j2 & 10\angle 45^\circ \\ -10 + j2 & 15 - j2 & 0 \\ -5 & 0 & 0 \end{vmatrix}}{\begin{vmatrix} 15 - j2 & -10 + j2 & -5 \\ -10 + j2 & 15 - j2 & 0 \\ -5 & 0 & 15 + j2 \end{vmatrix}} = 0.49\angle 37.41^\circ \text{ A}$$

$$\mathbf{I}_N = \mathbf{I}_3 - \mathbf{I}_2 = 0.49\angle 37.41^\circ - 1\angle 41.28^\circ = 0.51\angle -135^\circ \text{ A}$$

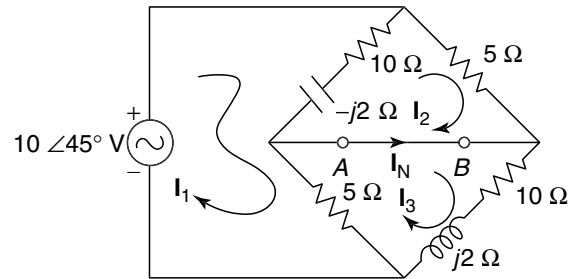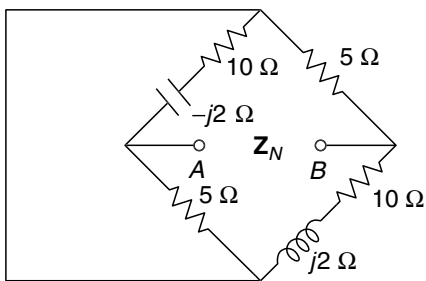**Fig. 6.129****Step II** Calculation of $\mathbf{Z}_N$ (Fig. 6.130)

(a)

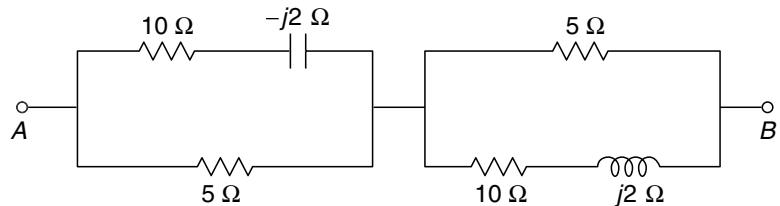

(b)

Fig. 6.130

$$\mathbf{Z}_N = \frac{5(10 - j2)}{5 + 10 - j2} + \frac{5(10 + j2)}{5 + 10 + j2} = 6.72 \, \Omega$$

Step III Norton's Equivalent Network (Fig. 6.131)

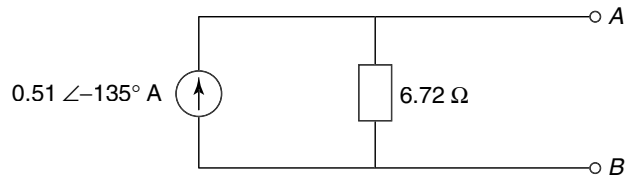


Fig. 6.131

Example 6.45

Find the current through the $8 \, \Omega$ resistor in the Network of Fig. 6.132.

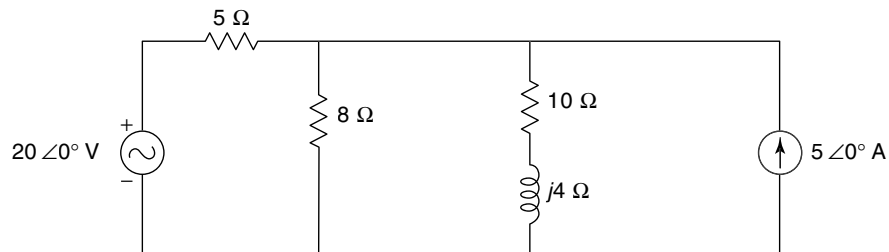


Fig. 6.132

Solution

Step I Calculation of $\mathbf{I}_N$ (Fig. 6.133)

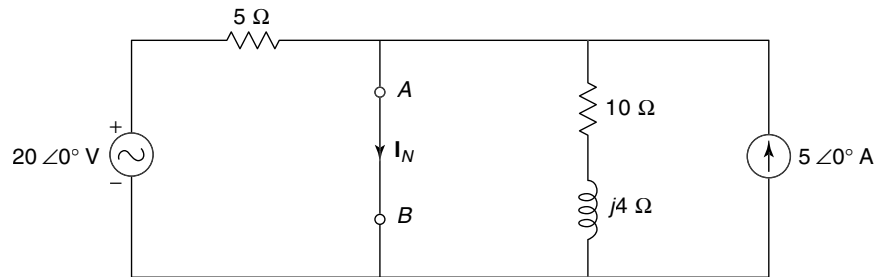


Fig. 6.133

When a short circuit is placed across the $(10 + j4) \, \Omega$ impedance, it gets shorted as shown in fig. 6.134.

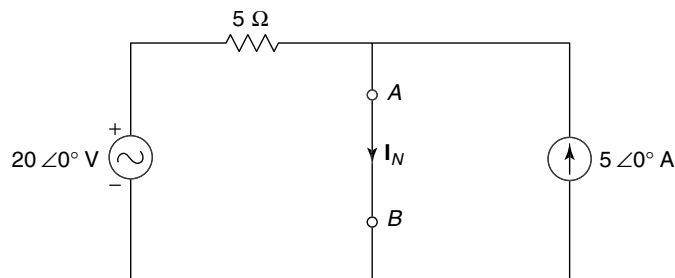


Fig. 6.134

By source transformation, the network is redrawn as shown in Fig. 6.135.

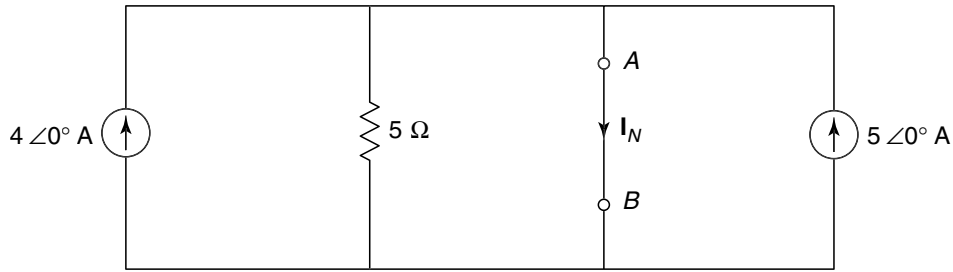


Fig. 6.135

$$\mathbf{I}_N = 4\angle 0^\circ + 5\angle 0^\circ = 9\angle 0^\circ \text{ A}$$

Step II Calculation of $\mathbf{Z}_N$ (Fig. 6.136)

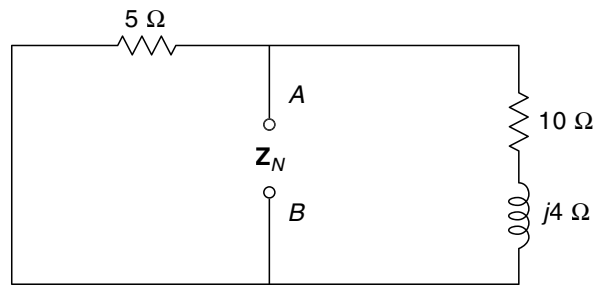


Fig. 6.136

$$\mathbf{Z}_N = \frac{5(10 + j4)}{5 + 10 + j4} = 3.47\angle 6.87^\circ \Omega$$

Step III Calculation of $\mathbf{I}_L$ (Fig. 6.137)

$$\mathbf{I}_L = \frac{9\angle 0^\circ}{3.47\angle 6.87^\circ + 8} = 0.79\angle -2.08^\circ \text{ A}$$

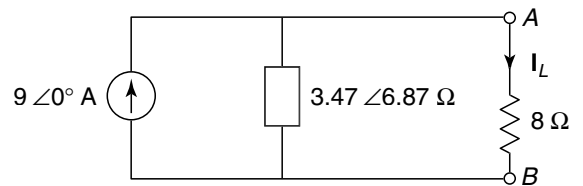


Fig. 6.137

Example 6.46

Obtain Norton's equivalent network across the terminals A and B in Fig. 6.138.

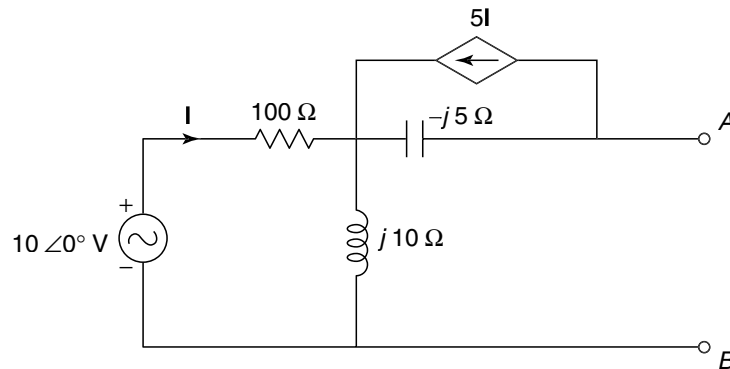


Fig. 6.138

6.50 Network Analysis and Synthesis

Solution

Step I Calculation of V_{Th} (Fig. 6.139)

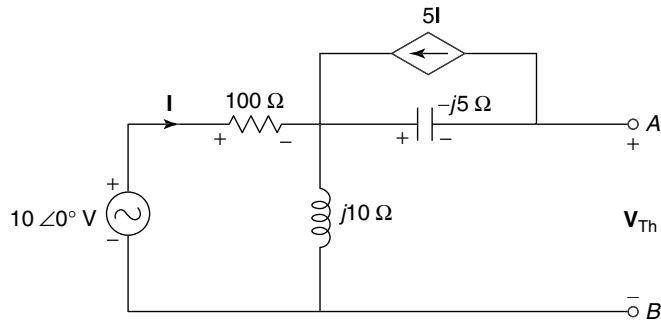


Fig. 6.139

$$\mathbf{I} = \frac{10\angle 0^\circ}{100 + j10} = 0.1\angle -5.71^\circ \text{ A}$$

Writing V_{Th} equation,

$$10\angle 0^\circ - 100\mathbf{I} - (-j5)(5\mathbf{I}) - V_{Th} = 0$$

$$10\angle 0^\circ - 100(0.1\angle -5.71^\circ) + (j5)(5)(0.1\angle -5.71^\circ) - V_{Th} = 0$$

$$V_{Th} = 3.5\angle 85.1^\circ \text{ V}$$

Step II Calculation of I_N (Fig. 6.140)

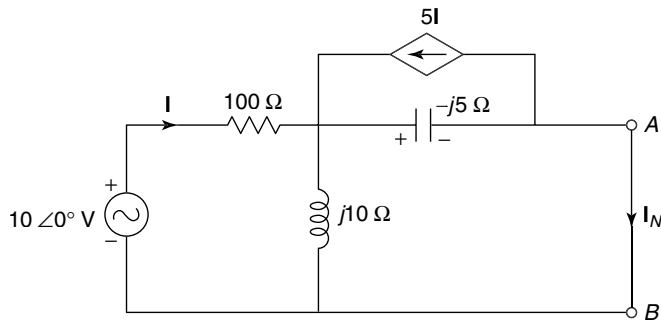


Fig. 6.140

By source transformation, the network is redrawn as shown in Fig. 6.141.

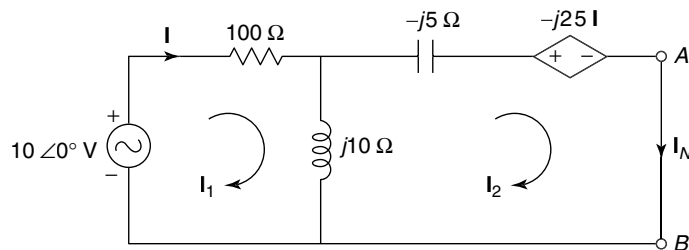


Fig. 6.141

From Fig. 6.141,

$$\mathbf{I} = \mathbf{I}_1 \quad \dots(i)$$

Applying KVL to Mesh 1,

$$\begin{aligned} 10\angle 0^\circ - 100\mathbf{I}_1 - j10(\mathbf{I}_1 - \mathbf{I}_2) &= 0 \\ (100 + j10)\mathbf{I}_1 - j10\mathbf{I}_2 &= 10\angle 0^\circ \end{aligned} \quad \dots(\text{ii})$$

Applying KVL to Mesh 2,

$$\begin{aligned} -j10(\mathbf{I}_2 - \mathbf{I}_1) + j5\mathbf{I}_2 + j25\mathbf{I} &= 0 \\ -j10\mathbf{I}_2 + j10\mathbf{I}_1 + j5\mathbf{I}_2 + j25\mathbf{I}_1 &= 0 \\ j35\mathbf{I}_1 - j5\mathbf{I}_2 &= 0 \end{aligned}$$

Writing Eqs (ii) and (iii) in matrix form,

$$\begin{bmatrix} 100 + j10 & -j10 \\ j35 & -j5 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 10\angle 0^\circ \\ 0 \end{bmatrix}$$

By Cramer's rule,

$$\begin{aligned} \mathbf{I}_2 &= \frac{\begin{vmatrix} 100 + j10 & 10\angle 0^\circ \\ j35 & 0 \end{vmatrix}}{\begin{vmatrix} 100 + j10 & -j10 \\ j35 & -j5 \end{vmatrix}} = 0.6\angle 30.96^\circ \text{ A} \\ \mathbf{I}_N = \mathbf{I}_2 &= 0.6\angle 30.96^\circ \text{ A} \end{aligned}$$

Step III Calculation of $\mathbf{Z}_N$

$$\mathbf{Z}_N = \frac{\mathbf{V}_{Th}}{\mathbf{I}_N} = \frac{3.5\angle 85.1^\circ}{0.6\angle 30.96^\circ} = 5.83\angle 54.14^\circ \Omega$$

Step IV Norton's Equivalent Network (Fig. 6.142)

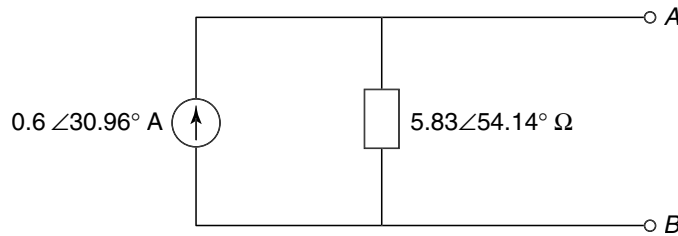


Fig. 6.142

6.7 || MAXIMUM POWER TRANSFER THEOREM

This theorem is used to determine the value of load impedance for which the source will transfer maximum power.

Consider a simple network as shown in Fig. 6.143.

There are three possible cases for load impedance $\mathbf{Z}_L$.

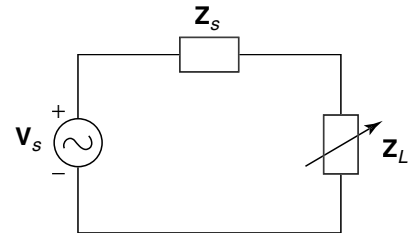


Fig. 6.143

6.52 Network Analysis and Synthesis

Case (i) When the load impedance is variable resistance (Fig. 6.144)

$$\mathbf{I}_L = \frac{\mathbf{V}_s}{\mathbf{Z}_s + \mathbf{Z}_L} = \frac{\mathbf{V}_s}{R_s + jX_s + R_L}$$

$$|\mathbf{I}_L| = \frac{|\mathbf{V}_s|}{\sqrt{(R_s + R_L)^2 + X_s^2}}$$

The power delivered to the load is

$$P_L = |\mathbf{I}_L|^2 R_L = \frac{|\mathbf{V}_s|^2 R_L}{\sqrt{(R_s + R_L)^2 + X_s^2}}$$

For power to be maximum,

$$\frac{dP_L}{dR_L} = 0$$

$$|\mathbf{V}_s|^2 \left[\frac{\{(R_s + R_L)^2 + X_s^2\} - 2R_L(R_s + R_L)}{[(R_s + R_L)^2 + X_s^2]^2} \right] = 0$$

$$(R_s + R_L)^2 + X_s^2 - 2R_L(R_s + R_L) = 0$$

$$R_s^2 + 2R_s R_L + R_L^2 + X_s^2 - 2R_L R_s - 2R_L^2 = 0$$

$$R_s^2 + X_s^2 - R_L^2 = 0$$

$$R_L^2 = R_s^2 + X_s^2$$

$$R_L = \sqrt{R_s^2 + X_s^2} = |\mathbf{Z}_s|$$

Hence, load resistance R_L should be equal to the magnitude of the source impedance for maximum power transfer.

Case (ii) When the load impedance is a complex impedance with variable resistance and variable reactance (Fig. 6.145)

$$\mathbf{I}_L = \frac{\mathbf{V}_s}{\mathbf{Z}_s + \mathbf{Z}_L}$$

$$|\mathbf{I}_L| = \frac{|\mathbf{V}_s|}{\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}}$$

The power delivered to the load is

$$P_L = |\mathbf{I}_L|^2 R_L = \frac{|\mathbf{V}_s|^2 R_L}{(R_s + R_L)^2 + (X_s + X_L)^2}$$

For maximum value of P_L , denominator of the equation should be small, ie. $X_L = -X_s$.

$$P_L = \frac{|\mathbf{V}_s|^2 R_L}{(R_s + R_L)^2}$$

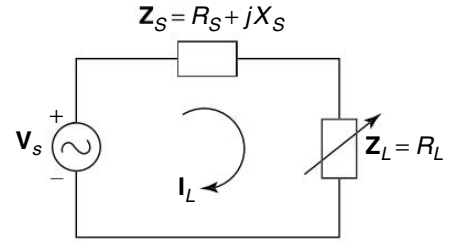


Fig. 6.144 Purely resistive load

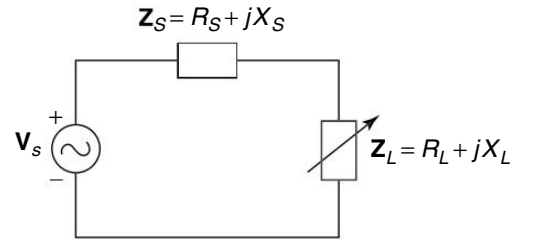


Fig. 6.145 Complex impedance load

Differentiating the above equation w.r.t. R_L and equating to zero,

$$\begin{aligned}\frac{dP_L}{dR_L} &= |\mathbf{V}_s|^2 \left[\frac{(R_s + R_L)^2 - 2 R_L (R_s + R_L)}{(R_s + R_L)^2} \right] = 0 \\ (R_s + R_L)^2 - 2 R_L (R_s + R_L) &= 0 \\ R_s^2 + 2 R_s R_L + R_L^2 - 2 R_L R_s - 2 R_L^2 &= 0 \\ R_s^2 - R_L^2 &= 0 \\ R_L^2 &= R_s^2 \\ R_L &= R_s\end{aligned}$$

Hence, load resistance R_L should be equal to source resistance R_s and load reactance X_L should be equal to negative value of source reactance for maximum power transfer.

$$\mathbf{Z}_L = \mathbf{Z}_s^* = R_s - jX_s$$

i.e. load impedance should be a complex conjugate of the source impedance.

Case (iii) When the load impedance is a complex impedance with variable resistance and fixed reactance (Fig. 6.146)

$$\begin{aligned}\mathbf{I}_L &= \frac{\mathbf{V}_s}{\mathbf{Z}_s + \mathbf{Z}_L} \\ |\mathbf{I}_L| &= \frac{|\mathbf{V}_s|}{\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}}\end{aligned}$$

The power delivered to the load is

$$P_L = |\mathbf{I}_L|^2 R_L = \frac{|\mathbf{V}_s|^2 R_L}{\sqrt{(R_s + R_L)^2 + (X_s + X_L)^2}}$$

For maximum power,

$$\begin{aligned}\frac{dP_L}{dR_L} &= 0 \\ |\mathbf{V}_s|^2 \left[\frac{(R_s + R_L)^2 + (X_s + X_L)^2 - 2 R_L (R_s + R_L)}{\{(R_s + R_L)^2 + (X_s + X_L)^2\}^2} \right] &= 0 \\ (R_s + R_L)^2 + (X_s + X_L)^2 - 2 R_L (R_s + R_L) &= 0 \\ R_s^2 + 2 R_s R_L + R_L^2 + (X_s + X_L)^2 - 2 R_L R_s - 2 R_L^2 &= 0 \\ R_s^2 + (X_s + X_L)^2 - R_L^2 &= 0 \\ R_L^2 &= R_s^2 + (X_s + X_L)^2 \\ R_L &= \sqrt{R_s^2 + (X_s + X_L)^2} \\ &= |R_s + j(X_s + X_L)| \\ &= |R_s + jX_s + jX_L| \\ &= |\mathbf{Z}_s + jX_L|\end{aligned}$$

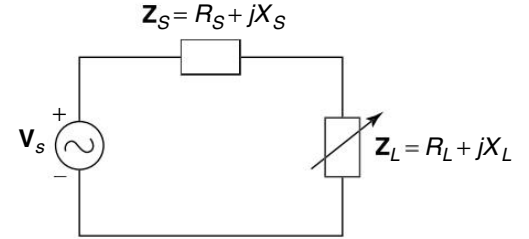


Fig. 6.146 Complex impedance load

6.54 Network Analysis and Synthesis

Hence, load resistance R_L should be equal to the magnitude of the impedance $\mathbf{Z}_s + jX_L$, i.e. $|\mathbf{Z}_s + jX_L|$ for maximum power transfer.

Example 6.47 For maximum power transfer, find the value of $\mathbf{Z}_L$ in the network of Fig. 6.147 if (i) $\mathbf{Z}_L$ is an impedance, and (ii) $\mathbf{Z}_L$ is pure resistance.

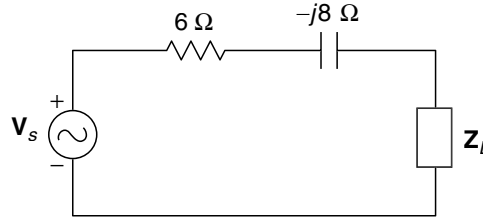


Fig. 6.147

Solution

$$\mathbf{Z}_s = (6 - j8) \Omega$$

(i) If $\mathbf{Z}_L$ is an impedance

For maximum power transfer, $\mathbf{Z}_L = \mathbf{Z}_s^* = (6 + j8) \Omega$

(ii) If $\mathbf{Z}_L$ is a resistance

For maximum power transfer, $\mathbf{Z}_L = |\mathbf{Z}_s| = |6 + j8| = 10 \Omega$

Example 6.48 For the maximum power transfer, find the value of $\mathbf{Z}_L$ in the network of Fig. 6.148 for the following cases:

(i) $\mathbf{Z}_L$ is variable resistance, (ii) $\mathbf{Z}_L$ is complex impedance, with variable resistance and variable reactance, and (iii) $\mathbf{Z}_L$ is complex impedance with variable resistance and fixed reactance of $j5 \Omega$.

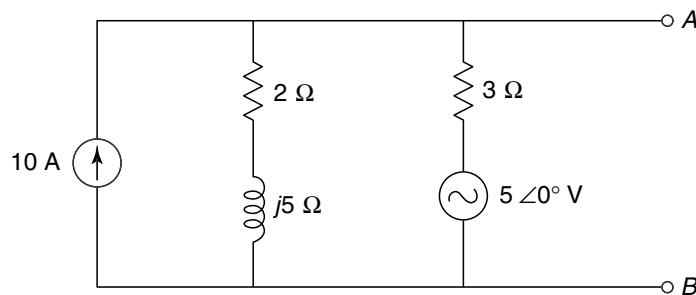


Fig. 6.148

Solution Thevenin's impedance can be calculated by replacing voltage source by a short circuit and current source by an open circuit.

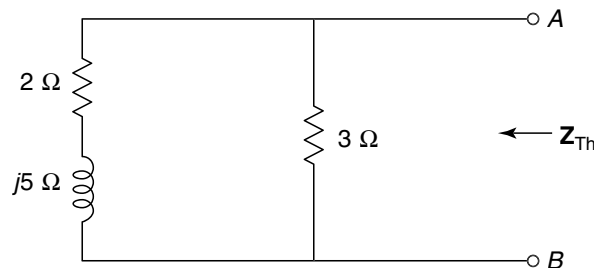


Fig. 6.149

$$\mathbf{Z}_{Th} = \frac{3(2 + j5)}{3 + 2 + j5} = (2.1 + j0.9) \Omega$$

For maximum power transfer, value of $\mathbf{Z}_L$ will be,

(i) $\mathbf{Z}_L$ is variable resistance

$$\mathbf{Z}_L = |\mathbf{Z}_{Th}| = |2.1 + j0.9| = 2.28 \Omega$$

(ii) $\mathbf{Z}_L$ is complex impedance with variable resistance and variable reactance

$$\mathbf{Z}_L = \mathbf{Z}_{Th}^* = (2.1 - j0.9) \Omega$$

(iii) $\mathbf{Z}_L$ is complex impedance with variable resistance and fixed reactance of $j5 \Omega$

$$\mathbf{Z}_L = |\mathbf{Z}_{Th} + j5| = |2.1 + j0.9 + j5| = 6.26 \Omega$$

Example 6.49 Find the impedance $\mathbf{Z}_L$ so that maximum power can be transferred to it in the network of Fig. 6.150. Find maximum power.

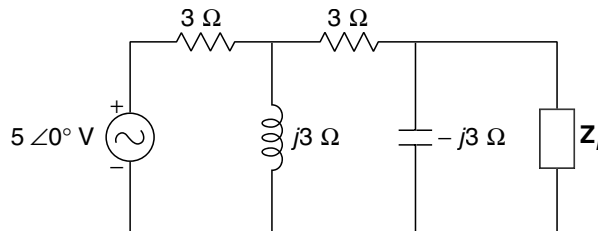


Fig. 6.150

Solution

Step I Calculation of $\mathbf{V}_{Th}$ (Fig. 6.151)

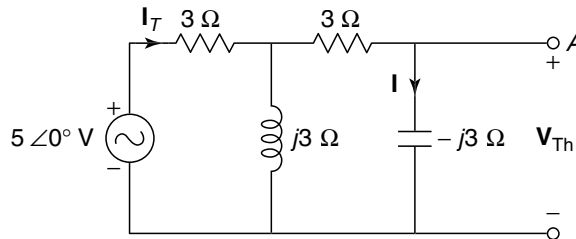


Fig. 6.151

$$\mathbf{Z}_T = 3 + \frac{j3(3 - j3)}{3 + j3 - j3} = 6.71 \angle 26.57^\circ \Omega$$

$$\mathbf{I}_T = \frac{5 \angle 0^\circ}{6.71 \angle 26.57^\circ} = 0.75 \angle -26.57^\circ \text{ A}$$

By current division rule,

$$\mathbf{I} = 0.75 \angle -26.57^\circ \times \frac{j3}{3 + j3 - j3} = 0.75 \angle 63.43^\circ \text{ A}$$

$$\mathbf{V}_{Th} = (-j3)(0.75 \angle 63.43^\circ) = 2.24 \angle -26.57^\circ \text{ V}$$

6.56 Network Analysis and Synthesis

Step II Calculation of $\mathbf{Z}_{Th}$ (Fig. 6.152)

$$\begin{aligned}\mathbf{Z}_{Th} &= [(3 \parallel j3) + 3] \parallel (-j3) \\ &= 3 \angle -53.12^\circ \Omega \\ &= (1.8 - j2.4) \Omega\end{aligned}$$

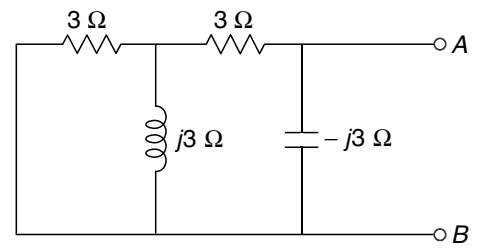


Fig. 6.152

Step III Calculation of $\mathbf{Z}_L$

For maximum power transfer, the load impedance should be a complex conjugate of the source impedance.

$$\mathbf{Z}_L = (1.8 + j2.4) \Omega$$

Step IV Calculation of P_{max} (Fig. 6.153)

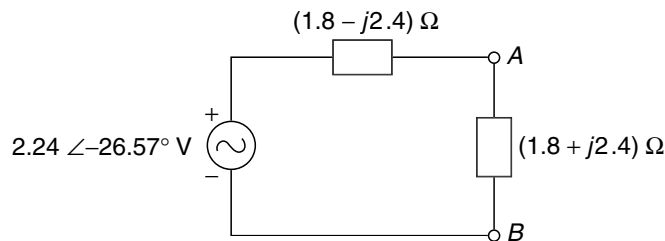


Fig. 6.153

$$P_{max} = \frac{|\mathbf{V}_{Th}|^2}{4R_L} = \frac{|2.24|^2}{4 \times 1.8} = 0.7 \text{ W}$$

Example 6.50

Find the value of $\mathbf{Z}_L$ for maximum power transfer in the network shown and find maximum power.

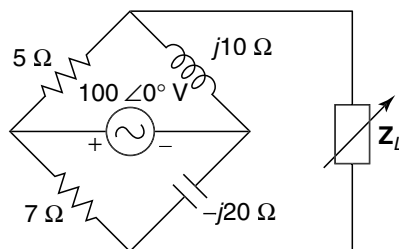


Fig. 6.154

Solution

Step I Calculation of $\mathbf{V}_{Th}$ (Fig. 6.155)

$$\mathbf{I}_1 = \frac{100 \angle 0^\circ}{5 + j10} = 8.94 \angle -63.43^\circ \text{ A}$$

$$\mathbf{I}_2 = \frac{100 \angle 0^\circ}{7 - j20} = 4.72 \angle 70.7^\circ \text{ A}$$

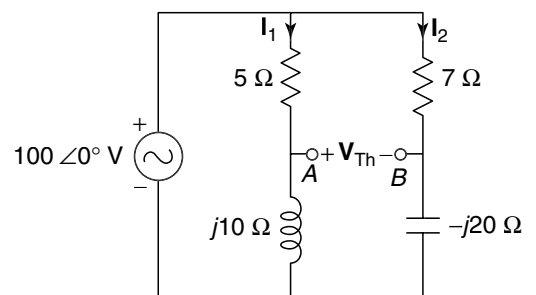


Fig. 6.155

$$\mathbf{V}_{\text{Th}} = \mathbf{V}_A - \mathbf{V}_B = (8.94 \angle -63.43^\circ)(j10) - (4.72 \angle 70.7^\circ)(-j20) = 71.76 \angle 97.3^\circ \text{ V}$$

Step II Calculation of $\mathbf{Z}_{\text{Th}}$ (Fig. 6.156)

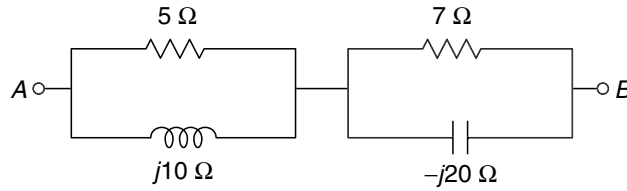


Fig. 6.156

$$\mathbf{Z}_{\text{Th}} = \frac{5(j10)}{5 + j10} + \frac{7(-j20)}{7 - j20} = \frac{50 \angle 90^\circ}{11.18 \angle 63.43^\circ} + \frac{140 \angle -90^\circ}{21.19 \angle -70.7^\circ} = (10.23 - j0.18) \Omega$$

Step III For maximum power transfer, the load impedance should be complex conjugate of the source impedance.

$$\mathbf{Z}_L = (10.23 + j0.18) \Omega$$

Step IV Calculation of P_{max} (Fig. 6.157)

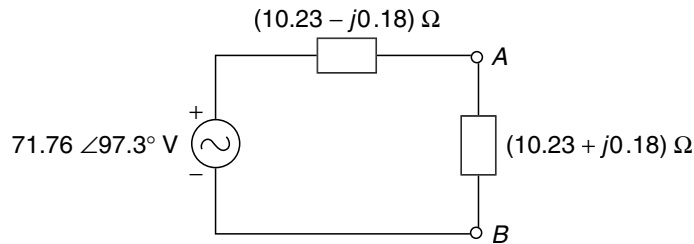


Fig. 6.157

$$P_{\text{max}} = \frac{|\mathbf{V}_{\text{Th}}|^2}{4R_L} = \frac{|71.76|^2}{4 \times 10.23} = 125.84 \text{ W}$$

Example 6.51 Find the value of load impedance $\mathbf{Z}_L$ so that maximum power can be transferred to it in the network of Fig. 6.158. Find maximum power.

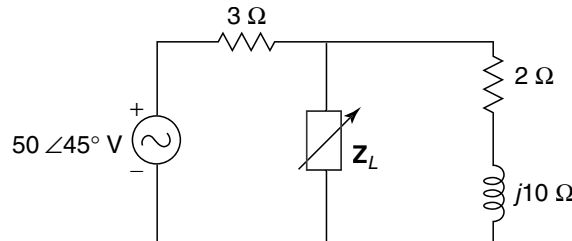


Fig. 6.158

6.58 Network Analysis and Synthesis

Solution

Step I Calculation of V_{Th} (Fig. 6.159)

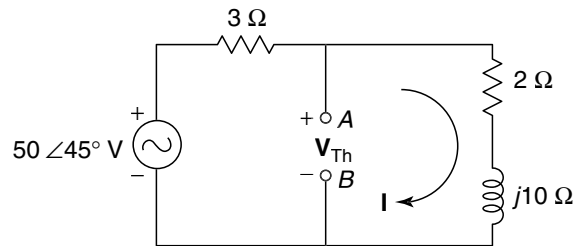


Fig. 6.159

$$I = \frac{50\angle 45^\circ}{3 + 2 + j10} = 4.47\angle -18.43^\circ \text{ A}$$

$$V_{Th} = (2 + j10) I = (2 + j10)(4.47\angle -18.43^\circ) = 45.6\angle 60.26^\circ \text{ V}$$

Step II Calculation of Z_{Th} (Fig. 6.160)

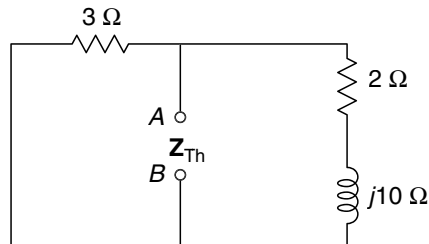


Fig. 6.160

$$Z_{Th} = \frac{3(2 + j10)}{3 + 2 + j10} = (2.64 + j0.72) \Omega$$

Step III Calculation of Z_L

For maximum power transfer, the load impedance should be complex conjugate of the source impedance.

$$Z_L = (2.64 - j0.72) \Omega$$

Step IV Calculation of P_{max} (Fig. 6.161)

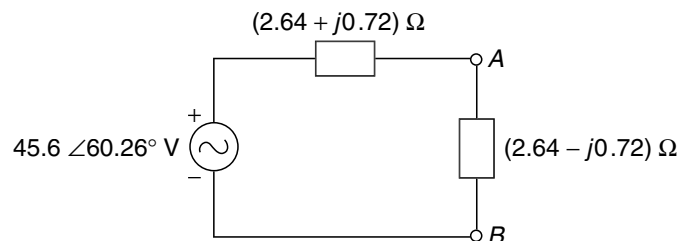


Fig. 6.161

$$P_{max} = \frac{|V_{Th}|^2}{4R_L} = \frac{|45.6|^2}{4 \times 2.64} = 196.91 \text{ W}$$

Example 6.52 Determine the load $\mathbf{Z}_L$ required to be connected in the network of Fig. 6.162 for maximum power transfer. Determine the maximum power drawn.

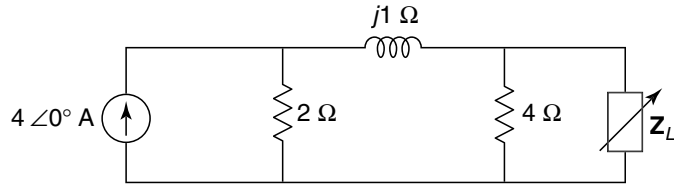


Fig. 6.162

Solution

Step I Calculation of $\mathbf{V}_{Th}$ (Fig. 6.163)

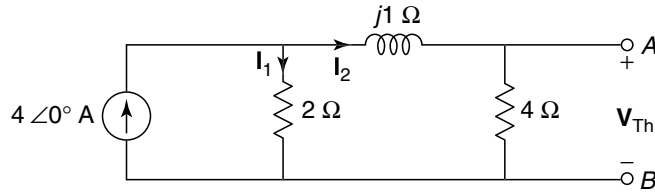


Fig. 6.163

$$\mathbf{I}_2 = 4\angle 0^\circ \times \frac{2}{6 + j1} = 1.315\angle -9.46^\circ \text{ A}$$

$$\mathbf{V}_{Th} = 4\mathbf{I}_2 = 4(1.315\angle -9.46^\circ) = 5.26\angle -9.46^\circ \text{ V}$$

Step II Calculation of $\mathbf{Z}_{Th}$ (Fig. 6.164)

$$\mathbf{Z}_{Th} = \frac{4(2 + j1)}{4 + 2 + j1} = 1.47\angle 17.1^\circ = (1.41 + j0.43) \Omega$$

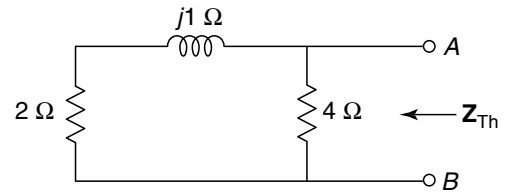


Fig. 6.164

Step III Calculation of $\mathbf{Z}_L$

For maximum power transfer, the load impedance should be the complex conjugate of the source impedance.

$$\mathbf{Z}_L = (1.41 - j0.43) \Omega$$

Step IV Calculation of P_{max} (Fig. 6.165)

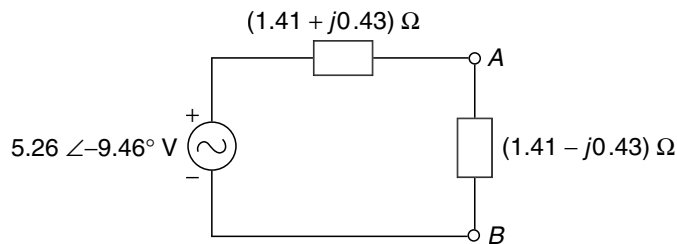


Fig. 6.165

$$P_{max} = \frac{|\mathbf{V}_{Th}|^2}{4R_L} = \frac{|5.26|^2}{4 \times 1.41} = 4.91 \text{ W}$$

Example 6.53 In the network shown in Fig. 6.166, find the value of Z_L for which the power transferred will be maximum. Also find maximum power.

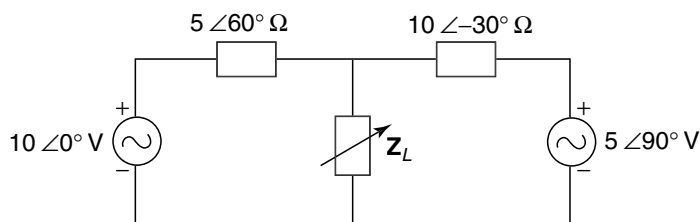


Fig. 6.166

Solution

Step I Calculation of V_{Th} (Fig. 6.167)

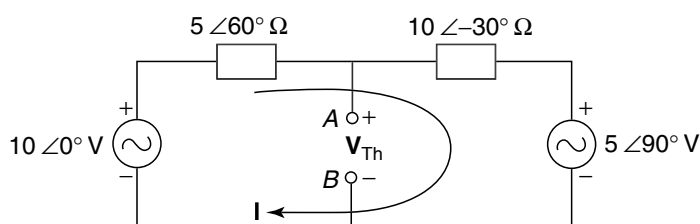


Fig. 6.167

Applying KVL to the mesh,

$$\begin{aligned} 10\angle 0^\circ - (5\angle 60^\circ)I - (10\angle -30^\circ)I - 5\angle 90^\circ &= 0 \\ 11.18\angle -26.57^\circ - (11.18\angle -3.43^\circ)I &= 0 \\ I &= 1\angle -23.14^\circ \text{ A} \end{aligned}$$

Writing V_{Th} equation,

$$\begin{aligned} 10\angle 0^\circ - (5\angle 60^\circ)I - V_{Th} &= 0 \\ 10\angle 0^\circ - (5\angle 60^\circ)(1\angle -23.14^\circ) - V_{Th} &= 0 \\ V_{Th} &= 6.71\angle -26.56^\circ \text{ V} \end{aligned}$$

Step II Calculation of Z_{Th} (Fig. 6.168)

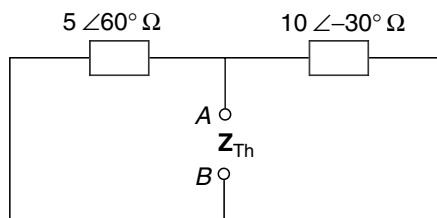



Fig. 6.168

$$Z_{Th} = \frac{(5\angle 60^\circ)(10\angle -30^\circ)}{5\angle 60^\circ + 10\angle -30^\circ} = 4.47\angle 33.43^\circ \Omega = (3.73 + j2.46) \Omega$$

Step III Calculation of Z_L

For maximum power transfer, the load impedance should be the complex conjugate of the source impedance.


$$Z_L = Z_{Th}^* = (3.73 - j2.46) \Omega$$

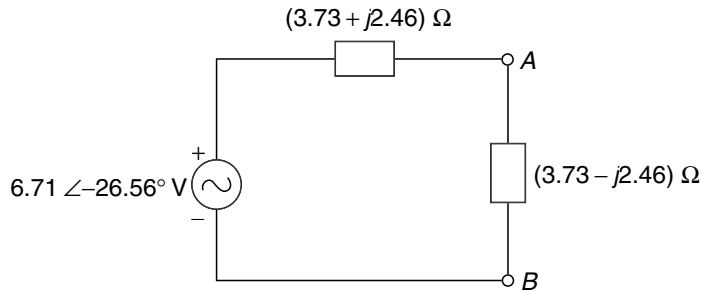Step IV Calculation of $P_{\max}$ (Fig. 6.169)**Fig. 6.169**

$$P_{\max} = \frac{|V_{Th}|^2}{4R_L} = \frac{(6.71)^2}{4 \times 3.73} = 3.02 \text{ W}$$

Example 6.54

In the network shown in Fig. 6.170, find the value of Z_L so that power transfer from the source is maximum. Also find maximum power.

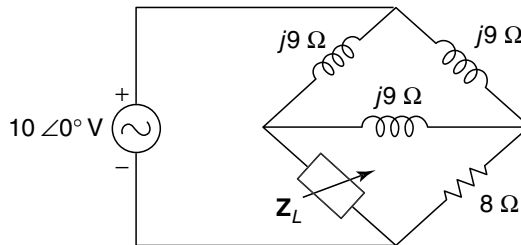
**Fig. 6.170****Solution****Step I** Calculation of V_{Th} (Fig. 6.171)

Applying Star-delta transformation (Fig. 6.172)

$$Z_1 = Z_2 = Z_3 = \frac{(j9)(j9)}{j9 + j9 + j9} = j3 \Omega$$

V_{Th} = Voltage drop across $(8 + j3) \Omega$ impedance

$$= (8 + j3) \frac{10 \angle 0^\circ}{8 + j3 + j3} = 8.54 \angle -16.31^\circ \text{ V}$$

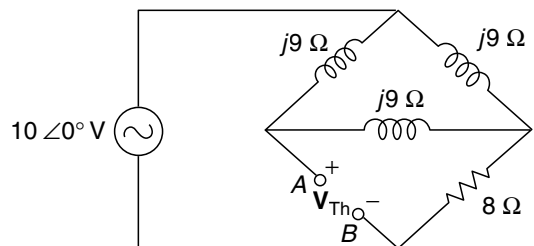**Fig. 6.171**

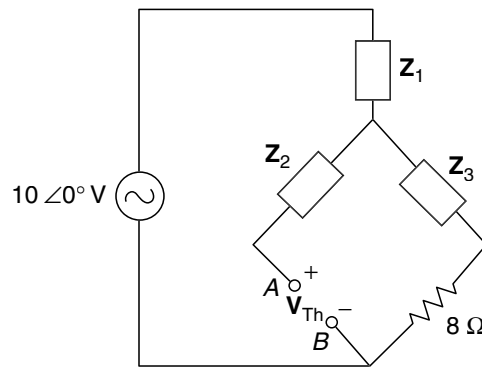


Fig. 6.172

Step II Calculation of Z_{Th} (Fig. 6.173)

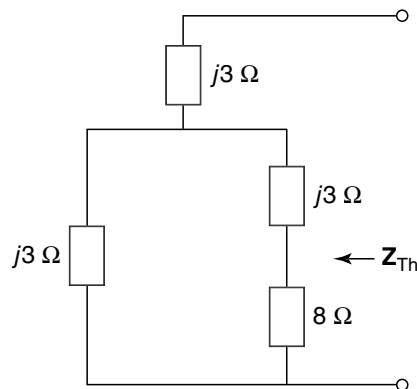


Fig. 6.173

$$Z_{Th} = j3 + \frac{j3(8 + j3)}{j3 + 8 + j3} = 5.51\angle 82.49^\circ \Omega = (0.72 + j5.46) \Omega$$

Step III Calculation of Z_L

For maximum power transfer, the load impedance should be the complex conjugate of the source impedance.

$$Z_L = Z_{Th}^* = (0.72 - j5.46) \Omega$$

Step IV Calculation of P_{max} (Fig. 6.174)

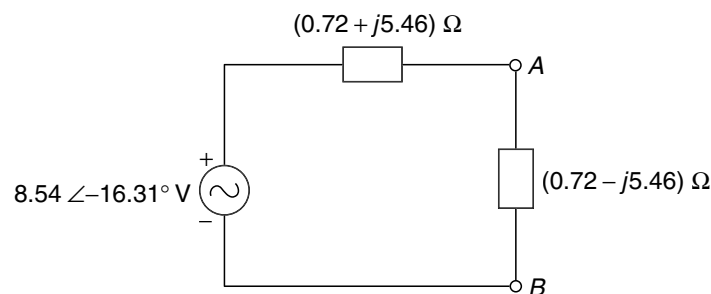


Fig. 6.174

$$P_{max} = \frac{|V_{Th}|^2}{4R_L} = \frac{(8.54)^2}{4 \times 0.72} = 25.32 \text{ W}$$

Example 6.55 For the network shown in Fig. 6.175, find the value of Z_L that will transfer maximum power from the source. Also find maximum power.

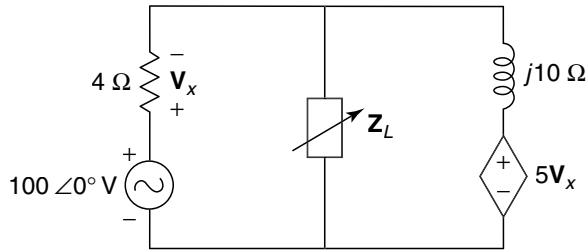


Fig. 6.175

Solution

Step I Calculation of V_{Th} (Fig. 6.176)

From Fig 6.176,

$$V_x = 4I$$

Applying KVL to the mesh,

$$100\angle 0^\circ - 4I - j10I - 5V_x = 0$$

$$100\angle 0^\circ - (4 + j10)I - 5(4I) = 0$$

$$I = \frac{100\angle 0^\circ}{24 + j10} = 3.85\angle -22.62^\circ \text{ A}$$

Writing V_{Th} equation,

$$100\angle 0^\circ - 4I - V_{Th} = 0$$

$$100\angle 0^\circ - 4(3.85\angle -22.62^\circ) - V_{Th} = 0$$

$$V_{Th} = 86\angle 3.95^\circ \text{ V}$$

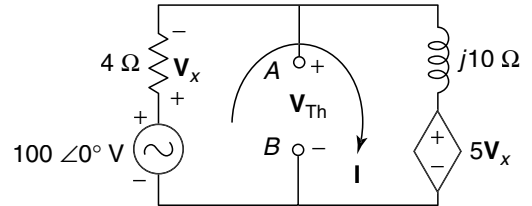


Fig. 6.176

Step II Calculation of I_N (Fig. 6.177)

From Fig. 6.177,

$$V_x = 4I_1$$

Applying KVL to Mesh 1,

$$100\angle 0^\circ - 4I_1 = 0$$

$$I_1 = 25 \text{ A}$$

Applying KVL to Mesh 2,

$$-j10I_2 - 5V_x = 0$$

$$-j10I_2 - 5(4I_1) = 0$$

$$-j10I_2 - 5(100) = 0$$

$$I_2 = 50\angle 90^\circ \text{ A}$$

$$I_N = I_1 - I_2 = 25 - 50\angle 90^\circ = 55.9\angle -63.43^\circ \text{ A}$$

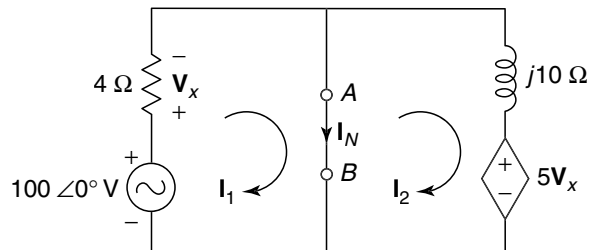


Fig. 6.177

Step III Calculation of Z_{Th}

$$Z_{Th} = \frac{V_{Th}}{I_N} = \frac{86\angle 3.95^\circ}{55.9\angle -63.43^\circ} = 1.54\angle 67.38^\circ \Omega = (0.59 + j1.42) \Omega$$

6.64 Network Analysis and Synthesis

Step IV Calculation of Z_L

For maximum power transfer, $Z_L = Z_{Th}^* = (0.59 - j1.42) \Omega$

Step V Calculation of $P_{\max}$ (Fig. 6.178)

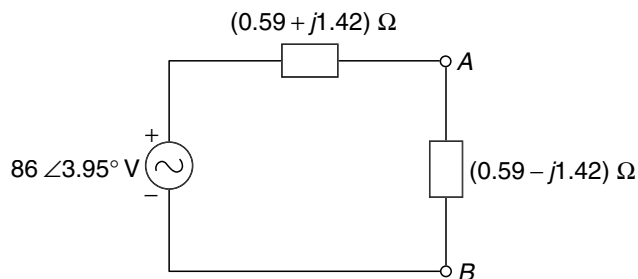


Fig. 6.178

$$P_{\max} = \frac{|V_{Th}|^2}{4R_L} = \frac{(86)^2}{4 \times 0.59} = 3133.9 \text{ W}$$

6.8 || RECIPROCITY THEOREM

The Reciprocity theorem states that ‘In a linear, bilateral, active, single-source network, the ratio of excitation to response remains same when the positions of excitation and response are interchanged.’

Example 6.56

Find the current through the 6Ω resistor and verify the reciprocity theorem.

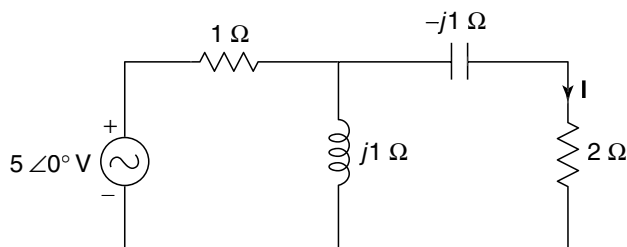


Fig. 6.179

Solution

Case I Calculation of current I when excitation and response are not interchanged (Fig. 6.180)

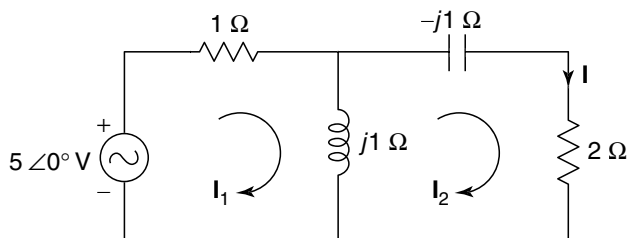


Fig. 6.180

Applying KVL to Mesh 1,

$$\begin{aligned} 5 \angle 0^\circ - 1I_1 - j1(I_1 - I_2) &= 0 \\ (1 + j1)I_1 - j1I_2 &= 5 \angle 0^\circ \end{aligned}$$

...(i)

Applying KVL to Mesh 2,

$$-j1(\mathbf{I}_2 - \mathbf{I}_1) + j1\mathbf{I}_2 - 2\mathbf{I}_2 = 0$$

$$-j1\mathbf{I}_1 + 2\mathbf{I}_2 = 0$$

...(ii)

Writing Eqs (i) and (ii) in matrix form,

$$\begin{bmatrix} 1+j1 & -j1 \\ -j1 & 2 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 5\angle 0^\circ \\ 0 \end{bmatrix}$$

By Cramer's rule,

$$\mathbf{I}_2 = \frac{\begin{vmatrix} 1+j1 & 5\angle 0^\circ \\ -j1 & 0 \end{vmatrix}}{\begin{vmatrix} 1+j1 & -j1 \\ -j1 & 2 \end{vmatrix}} = 1.39\angle 56.31^\circ \text{ A}$$

$$\mathbf{I} = \mathbf{I}_2 = 1.39\angle 56.31^\circ \text{ A}$$

Case II Calculation of current $\mathbf{I}$ when excitation and response are interchanged (Fig. 6.181)

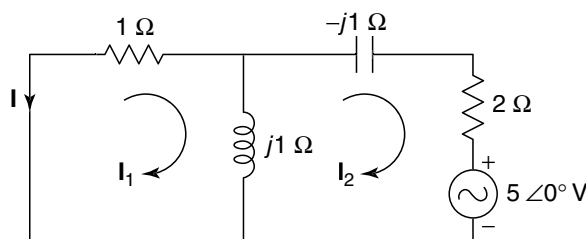


Fig. 6.181

Applying KVL to Mesh 1,

$$-1\mathbf{I}_1 - j1(\mathbf{I}_1 - \mathbf{I}_2) = 0$$

$$(1+j1)\mathbf{I}_1 - j1\mathbf{I}_2 = 0$$

...(i)

Applying KVL to Mesh 2,

$$-j1(\mathbf{I}_2 - \mathbf{I}_1) + j1\mathbf{I}_2 - 2\mathbf{I}_2 - 5\angle 0^\circ = 0$$

$$-j1\mathbf{I}_1 + 2\mathbf{I}_2 = -5\angle 0^\circ$$

...(ii)

Writing Eqs (i) and (ii) in matrix form,

$$\begin{bmatrix} 1+j1 & -j1 \\ -j1 & 2 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \end{bmatrix} = \begin{bmatrix} 0 \\ -5\angle 0^\circ \end{bmatrix}$$

By Cramer's rule,


$$\mathbf{I}_1 = \frac{\begin{vmatrix} 0 & -j1 \\ -5\angle 0^\circ & 2 \end{vmatrix}}{\begin{vmatrix} 1+j1 & -j1 \\ -j1 & 2 \end{vmatrix}} = 1.38\angle -123.69^\circ \text{ A}$$

$$\mathbf{I} = -\mathbf{I}_1 = 1.39\angle 56.31^\circ \text{ A}$$


Since the current $\mathbf{I}$ is same in both the cases, the reciprocity theorem is verified.

Example 6.57

In the network of Fig. 6.182, find the voltage V_x and verify the reciprocity theorem.

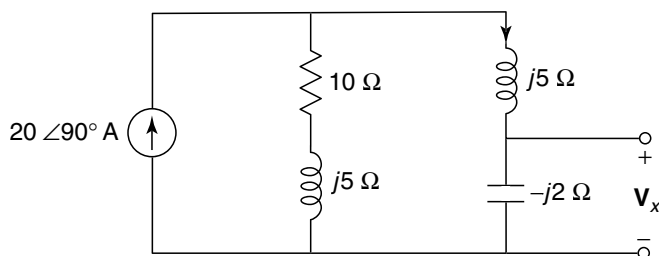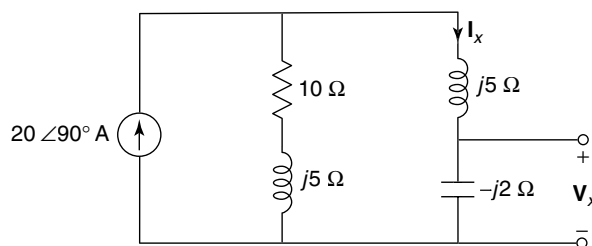**Fig. 6.182****Solution**

Case I Calculation of voltage V_x when excitation and response are interchanged. (Fig. 6.183)


**Fig. 6.183**

By current division rule,

$$I_x = (20\angle 90^\circ) \frac{(10 + j5)}{(10 + j5) + (j5 - j2)} = 17.46\angle 77.91^\circ \text{ A}$$

$$V_x = (-j2)I_x = (-j2)(17.46\angle 77.91^\circ) = 34.92\angle -12.09^\circ \text{ V}$$



Case II Calculation of voltage V_x when excitation and response are interchanged (Fig. 6.184)

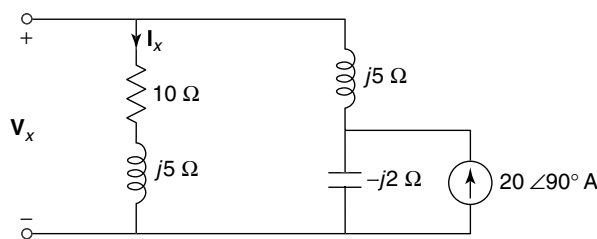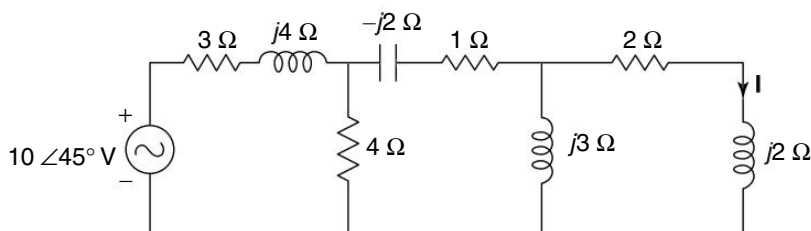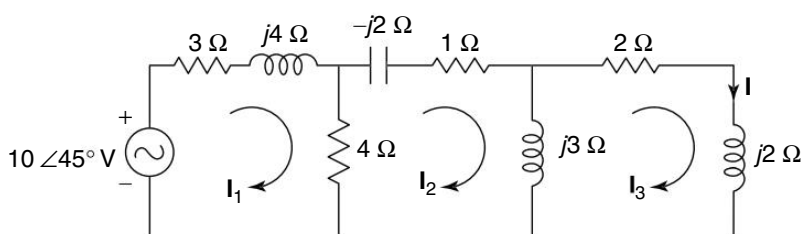**Fig. 6.184**

$$I_x = (20\angle 90^\circ) \frac{(-j2)}{(-j2) + (10 + j5 + j5)} = 3.12\angle -38.66^\circ \text{ A}$$

$$V_x = (10 + j5)I_x = (10 + j5)(3.12\angle -38.66^\circ) = 34.88\angle -12.09^\circ \text{ V}$$

Since the voltage V_x is same in both the cases, the reciprocity theorem is verified.

Example 6.58Find $\mathbf{I}$ and verify the reciprocity theorem for the network shown in Fig. 6.185.**Fig. 6.185****Solution****Case I** Calculation of $\mathbf{I}$ when excitation and response are not interchanged (Fig. 6.186)**Fig. 6.186**

Applying KVL to Mesh 1,

$$10\angle 45^\circ - (3 + j4)\mathbf{I}_1 - 4(\mathbf{I}_1 - \mathbf{I}_2) = 0$$

$$(7 + j4)\mathbf{I}_1 - 4\mathbf{I}_2 = 10\angle 45^\circ \quad \dots(i)$$

Applying KVL to Mesh 2,

$$-4(\mathbf{I}_2 - \mathbf{I}_1) - (1 - j2)\mathbf{I}_2 - j3(\mathbf{I}_2 - \mathbf{I}_3) = 0$$

$$-4\mathbf{I}_1 + (5 + j1)\mathbf{I}_2 - j3\mathbf{I}_3 = 0 \quad \dots(ii)$$

Applying KVL to Mesh 3,

$$-j3(\mathbf{I}_3 - \mathbf{I}_2) - 2\mathbf{I}_3 - j2\mathbf{I}_3 = 0$$

$$-j3\mathbf{I}_2 + (2 + j5)\mathbf{I}_3 = 0 \quad \dots(iii)$$

Writing Eqs (i), (ii) and (iii) in matrix form,

$$\begin{bmatrix} 7 + j4 & -4 & 0 \\ -4 & 5 + j1 & -j3 \\ 0 & -j3 & 2 + j5 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 10\angle 45^\circ \\ 0 \\ 0 \end{bmatrix}$$

By Cramer's rule,

$$\mathbf{I}_3 = \frac{\begin{vmatrix} 7 + j4 & -4 & 10\angle 45^\circ \\ -4 & 5 + j1 & 0 \\ 0 & -j3 & 0 \end{vmatrix}}{\begin{vmatrix} 7 + j4 & -4 & 0 \\ -4 & 5 + j1 & -j3 \\ 0 & -j3 & 2 + j5 \end{vmatrix}} = 0.704\angle 30.72^\circ \text{ A}$$

$$\mathbf{I} = \mathbf{I}_3 = 0.704\angle 30.72^\circ \text{ A}$$

Case II Calculation of $\mathbf{I}$ when excitation and response are interchanged (Fig. 6.187)

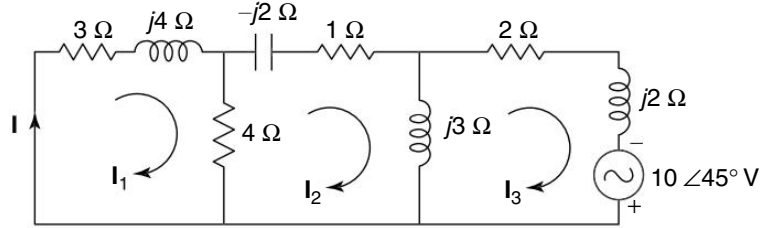


Fig. 6.187

Applying KVL to Mesh 1,

$$\begin{aligned} -(3 + j4)\mathbf{I}_1 - 4(\mathbf{I}_1 - \mathbf{I}_2) &= 0 \\ (7 + j4)\mathbf{I}_1 - 4\mathbf{I}_2 &= 0 \end{aligned} \quad \dots(i)$$

Applying KVL to Mesh 2,

$$\begin{aligned} -4(\mathbf{I}_2 - \mathbf{I}_1) - (1 - j2)\mathbf{I}_2 - j3(\mathbf{I}_2 - \mathbf{I}_3) &= 0 \\ -4\mathbf{I}_1 + (5 + j1)\mathbf{I}_2 - j3\mathbf{I}_3 &= 0 \end{aligned} \quad \dots(ii)$$

Applying KVL to Mesh 3,

$$\begin{aligned} -j3(\mathbf{I}_3 - \mathbf{I}_2) - 2\mathbf{I}_3 - j2\mathbf{I}_3 + 10\angle 45^\circ &= 0 \\ -j3\mathbf{I}_2 + (2 + j5)\mathbf{I}_3 &= 10\angle 45^\circ \end{aligned} \quad \dots(iii)$$

Writing Eqs (i), (ii) and (iii) in matrix form,

$$\begin{bmatrix} 7 + j4 & -4 & 0 \\ -4 & 5 + j1 & -j3 \\ 0 & -j3 & 2 + j5 \end{bmatrix} \begin{bmatrix} \mathbf{I}_1 \\ \mathbf{I}_2 \\ \mathbf{I}_3 \end{bmatrix} = \begin{bmatrix} 0 \\ 0 \\ 10\angle 45^\circ \end{bmatrix}$$

By Cramer's rule,

$$\mathbf{I}_1 = \frac{\begin{vmatrix} 0 & -4 & 0 \\ 10\angle 45^\circ & -j3 & 2 + j5 \end{vmatrix}}{\begin{vmatrix} 7 + j4 & -4 & 0 \\ -4 & 5 + j1 & -j3 \\ 0 & -j3 & 2 + j5 \end{vmatrix}} = 0.704\angle 30.72^\circ \text{ A}$$

$$\mathbf{I} = \mathbf{I}_1 = 0.704\angle 30.72^\circ \text{ A}$$


Since the current $\mathbf{I}$ is same in both the cases, the reciprocity theorem, is verified.

6.9 || MILLMAN'S THEOREM

Millman's theorem states that 'If there are n voltage sources $V_1, V_2, \dots, V_n$ with internal impedances $Z_1, Z_2, \dots, Z_n$ respectively connected in parallel then these voltage sources can be replaced by a single voltage source V_m and a single series impedance Z_m .

$$\mathbf{V}_m = \frac{\mathbf{V}_1 \mathbf{Y}_1 + \mathbf{V}_2 \mathbf{Y}_2 + \dots + \mathbf{V}_n \mathbf{Y}_n}{\mathbf{Y}_1 + \mathbf{Y}_2 + \dots + \mathbf{Y}_n}$$


$$\mathbf{Z}_m = \frac{1}{\mathbf{Y}_m} = \frac{1}{\mathbf{Y}_1 + \mathbf{Y}_2 + \dots + \mathbf{Y}_n}$$

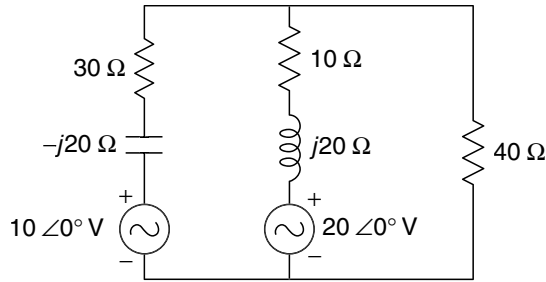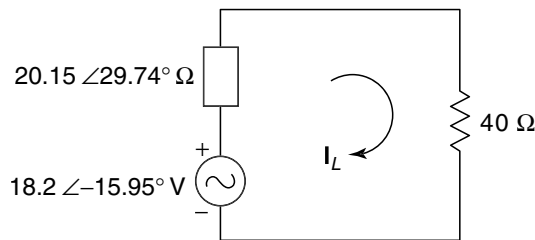Example 6.59Find the current through the $40\ \Omega$ resistor for the network shown in Fig. 6.188.**Fig. 6.188****Solution****Step I** Calculation of V_m


$$V_m = \frac{V_1 Y_1 + V_2 Y_2}{Y_1 + Y_2} = \frac{(10 \angle 0^\circ) \left(\frac{1}{30 - j20} \right) + (20 \angle 0^\circ) \left(\frac{1}{10 + j20} \right)}{\frac{1}{30 - j20} + \frac{1}{10 + j20}} = 18.2 \angle -15.95^\circ \text{ V}$$

Step II Calculation of Z_m

$$Z_m = \frac{1}{Y_m} = \frac{1}{Y_1 + Y_2} = \frac{1}{\frac{1}{30 - j20} + \frac{1}{10 + j20}} = 20.15 \angle 29.74^\circ \ \Omega$$

Step III Calculation of I_L (Fig. 6.189)**Fig. 6.189**

$$I_L = \frac{18.2 \angle -15.95^\circ}{20.15 \angle 29.74^\circ + 40} = 0.31 \angle -25.81^\circ \text{ A}$$

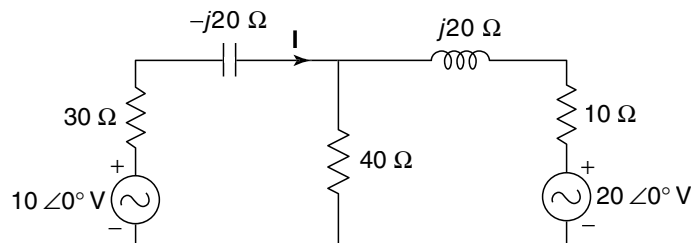Example 6.60Find the current I in the network shown in Fig. 6.190.**Fig. 6.190**

6.70 Network Analysis and Synthesis

Solution The network is redrawn as shown in Fig. 6.191.

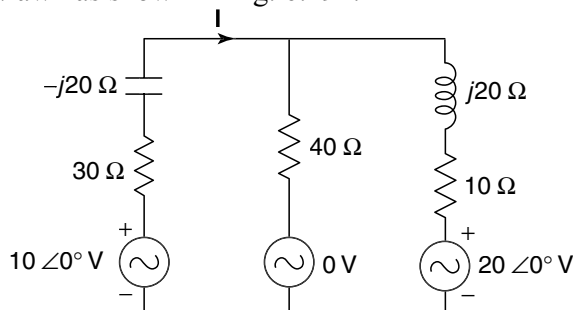


Fig. 6.191

Step I Calculation of V_m

$$V_m = \frac{V_1 Y_1 + V_2 Y_2}{Y_1 + Y_2} = \frac{0 \left(\frac{1}{40} \right) + (20 \angle 0^\circ) \left(\frac{1}{10 + j20} \right)}{\frac{1}{40} + \frac{1}{10 + j20}} = 14.86 \angle -21.8^\circ \text{ V}$$

Step II Calculation of Z_m

$$Z_m = \frac{1}{Y_m} = \frac{1}{Y_1 + Y_2} = \frac{1}{\frac{1}{40} + \frac{1}{10 + j20}} = 16.61 \angle 41.63^\circ \Omega$$

Step III Calculation of I (Fig. 6.192)

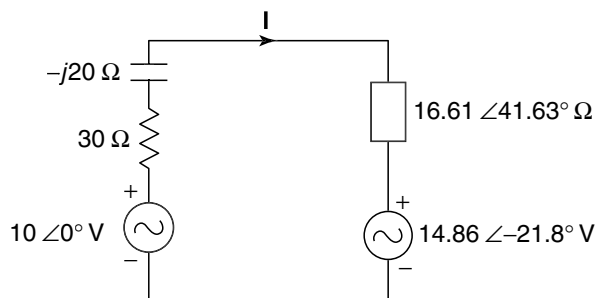


Fig. 6.192

$$I = \frac{10 - 14.86 \angle -21.8^\circ}{30 - j20 + 16.61 \angle 41.63^\circ} = 0.15 \angle 136.47^\circ \text{ A}$$

Example 6.61

Apply the dual Millman theorem and find the power loss in the $(2 + j2) \Omega$ impedance.

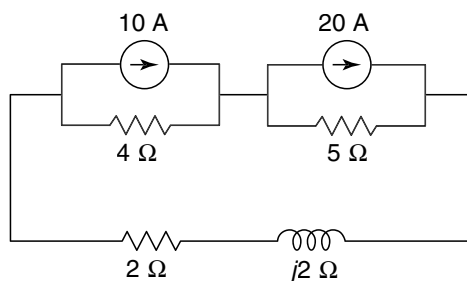



Fig. 6.193

Solution**Step I** Calculation of $\mathbf{I}_m$

$$\mathbf{I}_m = \frac{\mathbf{I}_1 \mathbf{Z}_1 + \mathbf{I}_2 \mathbf{Z}_2}{\mathbf{Z}_1 + \mathbf{Z}_2} = \frac{(10)(4) + (20)(5)}{4 + 5} = 15.56 \text{ A}$$

Step II Calculation of $\mathbf{Z}_m$

$$\mathbf{Z}_m = \mathbf{Z}_1 + \mathbf{Z}_2 = 4 + 5 = 9 \Omega$$

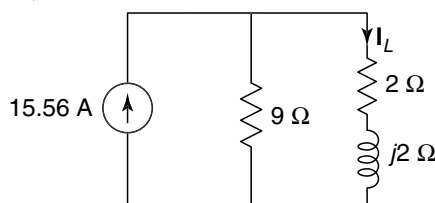Step III Calculation of P (Fig. 6.194)**Fig. 6.194**


By current division rule,

$$\mathbf{I}_L = 15.56 \times \frac{9}{9 + 2 + j2} = 12.53 \angle -10.3^\circ \text{ A}$$

$$P = \mathbf{I}_L^2 R_L = (12.53)^2 \times 2 = 314 \text{ W}$$

Example 6.62

In the network shown in Fig. 6.195, what load $\mathbf{Z}_L$ will receive the maximum power. Also find maximum power.

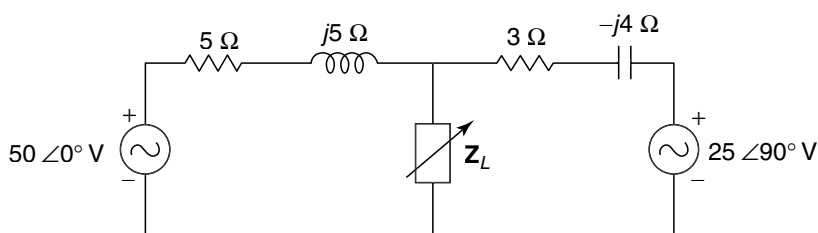**Fig. 6.195****Solution****Step I** Calculation of $\mathbf{V}_m$

$$\mathbf{V}_m = \frac{\mathbf{V}_1 \mathbf{Y}_1 + \mathbf{V}_2 \mathbf{Y}_2}{\mathbf{Y}_1 + \mathbf{Y}_2} = \frac{(50 \angle 0^\circ) \left(\frac{1}{5 + j5} \right) + (25 \angle 90^\circ) \left(\frac{1}{3 - j4} \right)}{\frac{1}{5 + j5} + \frac{1}{3 - j4}} = 9.81 \angle -78.69^\circ \text{ V}$$

Step II Calculation of $\mathbf{Z}_m$

$$\mathbf{Z}_m = \frac{1}{\mathbf{Y}_m} = \frac{1}{\mathbf{Y}_1 + \mathbf{Y}_2} = \frac{1}{\frac{1}{5 + j5} + \frac{1}{3 - j4}} = 4.39 \angle -15.26^\circ \Omega = (4.23 - j1.15) \Omega$$

Step II Calculation of change in current by compensation theorem

$$\delta Z = (1 + j1) - (5 + j2) = (-4 - j1) \Omega$$

$$V_c = I_L \delta Z = (1.44 \angle -25^\circ)(-4 - j1) = 5.94 \angle 169.04^\circ \text{ V}$$

The compensating network is shown in Fig. 6.208.

$$\begin{aligned} \delta I_L &= -\frac{5.94 \angle 169.04^\circ}{2.94 \angle -11.31^\circ + 5 + j2 - 4 - j1} \\ &= 1.52 \angle -17.18^\circ \text{ A} \end{aligned}$$

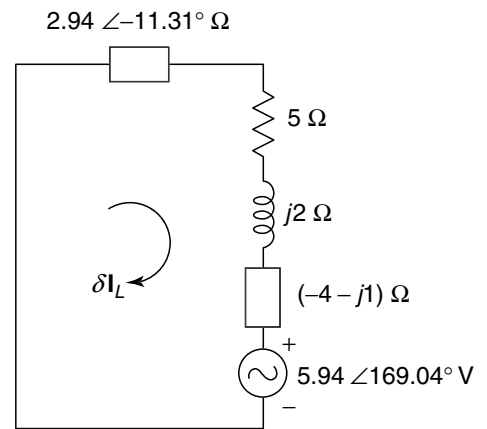


Fig. 6.208

Exercises

MESH ANALYSIS

- 6.1 Find the current through the $3 + j4 \Omega$ impedance in Fig. 6.209.

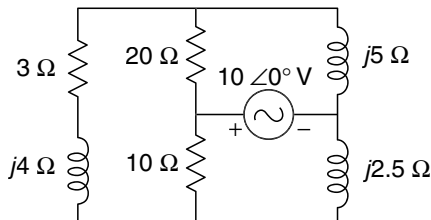


Fig. 6.209

- 6.2 In the network of Fig. 6.210, find V_0 .

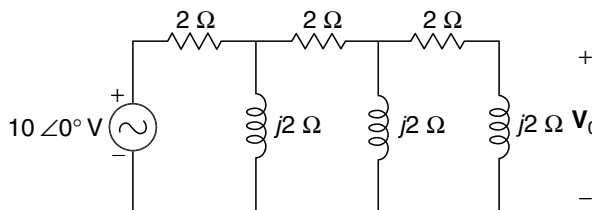


Fig. 6.210

[1.56 ∠ 128.7° V]

- 6.3 Find the current I_3 in the network of Fig. 6.211.

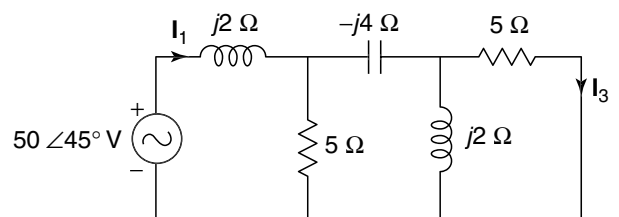


Fig. 6.211

[11.6 ∠ 113.2° A]

- 6.4 In the network of Fig. 6.212, find V_2 which results in zero current through the 4Ω resistor.

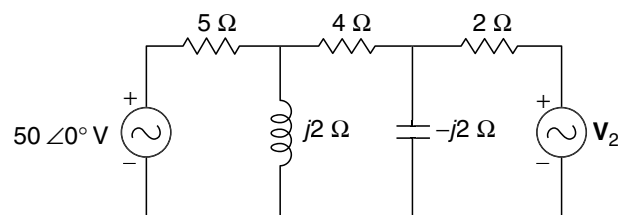
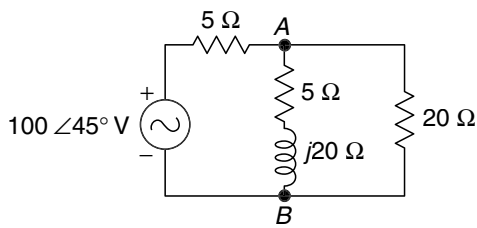


Fig. 6.212

[26.3 ∠ 113.2° V]


NODE ANALYSIS

- 6.5 For the network shown in Fig. 6.213, find the voltage V_{AB} .

**Fig. 6.213**


[75.4 ∠55.2° V]

- 6.6** Find the voltages at nodes 1 and 2 in the network of Fig. 6.214.

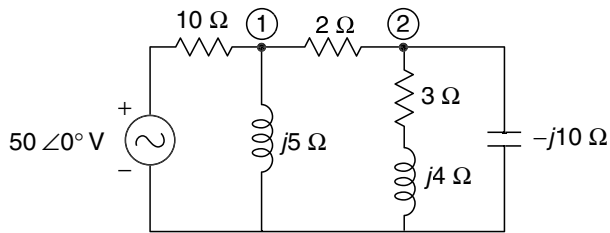**Fig. 6.214**

[15.95 ∠49.94° V, 12.9 ∠55.5° V]


- 6.7** In the network of Fig. 6.215, find the current in the 10 ∠30° V source.

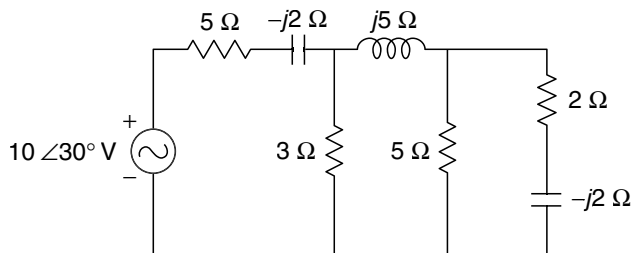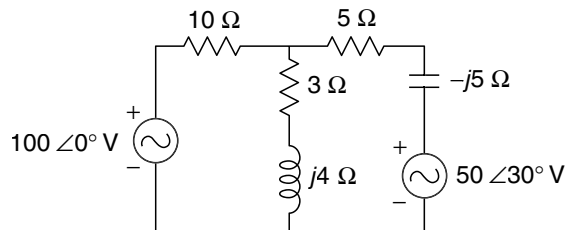**Fig. 6.215**

[1.44 ∠38.8° A]


SUPERPOSITION THEOREM

- 6.8** For the network shown in Fig. 6.216, find the current in the 10 Ω resistor.

**Fig. 6.216**

[73.4 ∠-21.84° A]


- 6.9** In the network of Fig. 6.217, find the current through capacitance.

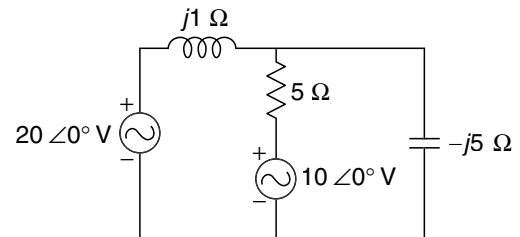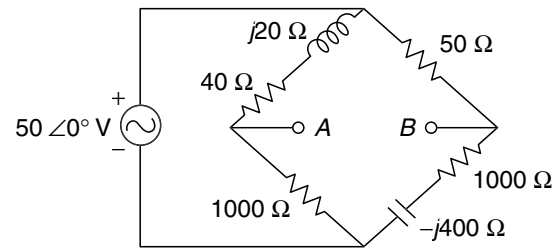**Fig. 6.217**

[4.86 ∠80.8° A]


THEVENIN'S THEOREM

- 6.10** Obtain Thevenin's equivalent network for the network shown in Fig. 6.218.

**Fig. 6.218**

[0.192 ∠-43.4° V, 88.7 ∠11.55° Ω]

- 6.11** Obtain Thevenin's equivalent network for Fig. 6.219.

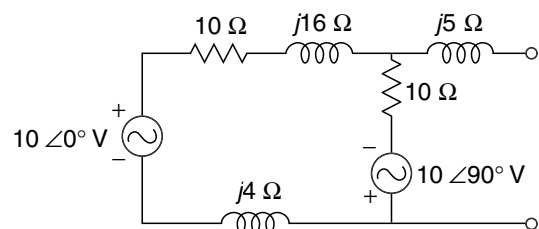**Fig. 6.219**

[11.17 ∠-63.4° V, 10.6 ∠45° Ω]

NORTON'S THEOREM

- 6.12** Find Norton's equivalent network for Fig. 6.220.

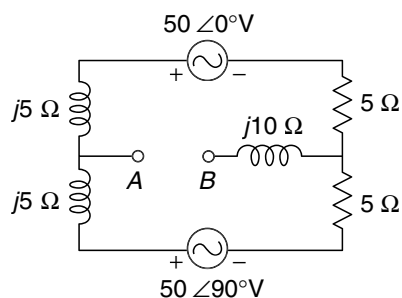


Fig. 6.220

[2.77 $\angle -33.7^\circ$ A, $2.5 + j12.5 \Omega$]

- 6.13 Find the current through the $(3 + j4) \Omega$ impedance in the network of Fig. 6.221.

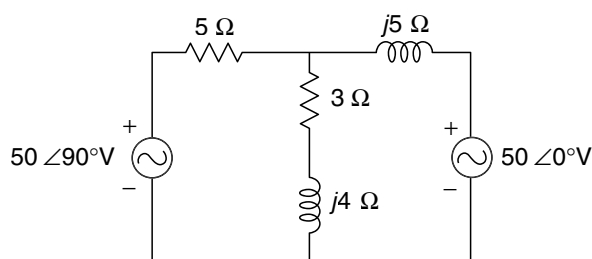


Fig. 6.221

[8.3 $\angle 85.2^\circ$ A]

MAXIMUM POWER TRANSFER THEOREM

- 6.14 Determine the maximum power delivered to the load in the network shown in Fig. 6.222.

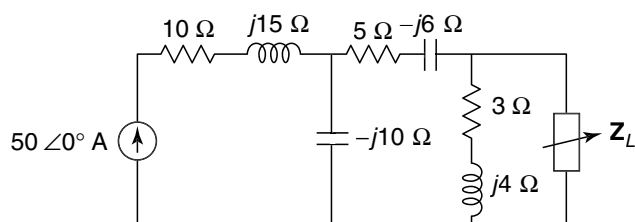


Fig. 6.222

[1032.35 W]

- 6.15 For the network shown in Fig. 6.223, find the value of Z_L that will receive the maximum power. Determine also this power.

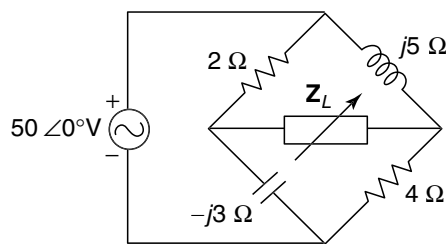


Fig. 6.223

[3.82 - j1.03 Ω , 54.5 W]

Objective-Type Questions

- 6.1 In Fig. 6.224, the equivalent impedance seen across terminals a, b , is

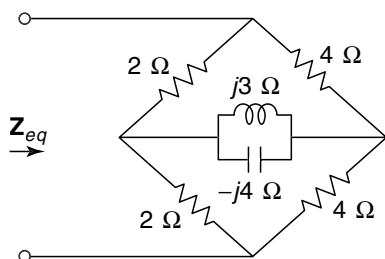


Fig. 6.224

- (a) $\frac{16}{3} \Omega$ (b) $\frac{8}{3} \Omega$
 (c) $\left(\frac{8}{3} + j12\right) \Omega$ (d) none of the above

- 6.2 The Thevenin equivalent voltage V_{Th} appearing between the terminals A and B of the network shown in Fig. 6.225 is given by

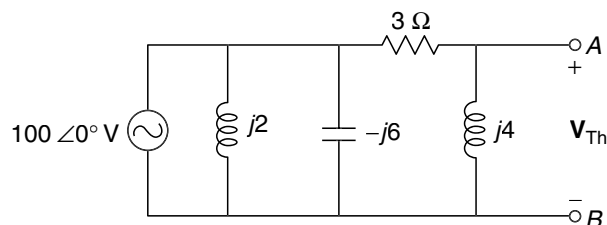


Fig. 6.225

- (a) $j16(3 - j4)$ (b) $j16(3 + j4)$
 (c) $16(3 + j4)$ (d) $16(3 - j4)$
 6.3 A source of angular frequency of 1 rad/s has a source impedance consisting of a 1 Ω resistance