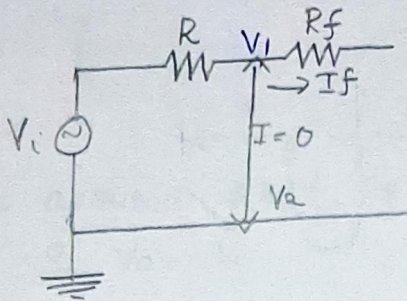


APPLICATIONS OF OP-AMP


VIRTUAL GROUND PROPERTY

This means the differential input voltage between inverting and non-inverting terminals essentially zero.



From the figure there is a virtual shot between 2 input terminals, but no current flows from input terminals to this ground. The 2 input terminals of OP-AMP are always at same potential w.r.t ground.

NON-INVERTING AMPLIFIER (SCALE CHANGER)

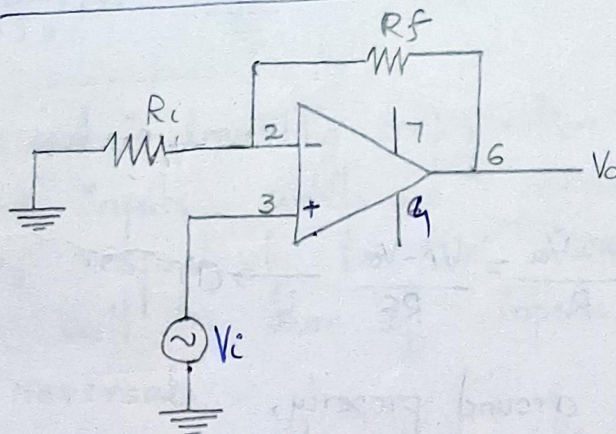


Voltage divider rule

$$V_i = V_o \times \frac{R_i}{R_i + R_f}$$


$$\frac{V_o}{V_i} = \frac{R_f + R_i}{R_i}$$

$$A_v = 1 + \frac{R_f}{R_i}, \text{ gain of non-inverting amplifier.}$$

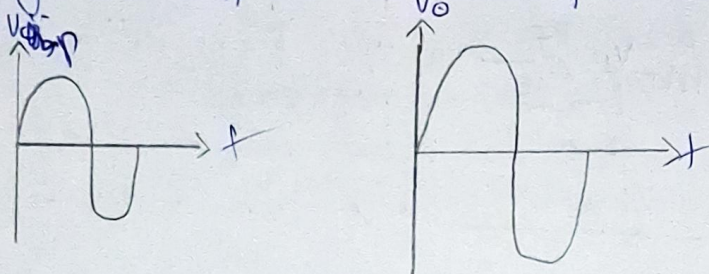On non-inverting amplifier the input is applied to the non-inverting input terminal and we will get the o/p which is in phase with input.



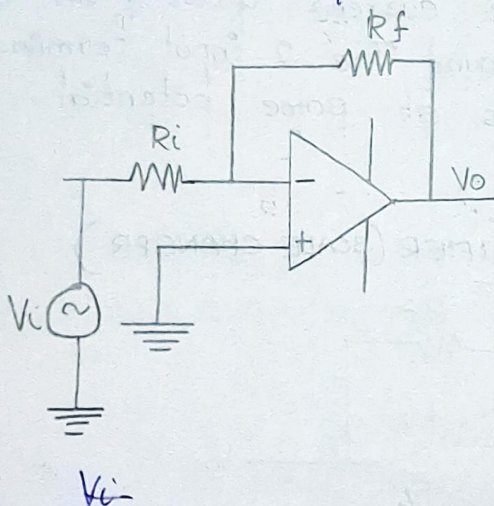INVERTING AMPLIFIER / ^{IGN}SCALE CHANGER



From figure $\frac{V_i - V_a}{R_i} = \frac{V_a - V_o}{R_f} \rightarrow (1)$


Due to virtual ground property,
 $V_i = 0$

Eqn (1) becomes

$$\frac{V_i}{R_i} = -\frac{V_o}{R_f}$$

$$\frac{V_o}{V_i} = \frac{-R_F}{R_i} = A_V, \text{ gain of inverting amplifier.}$$

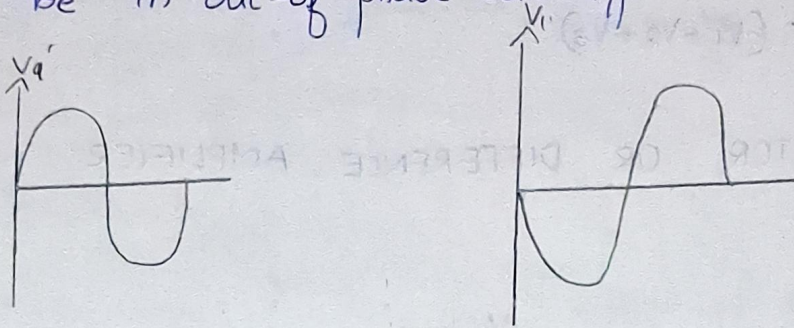
In the inverting amplifier, the input is given to inverting terminal and so the op generated will be in out-of phase with i/p.



Let us assume $R_F = R_i$

$$\text{So } V_o = -V_i$$

Summing Amplifier or Adder Circuit

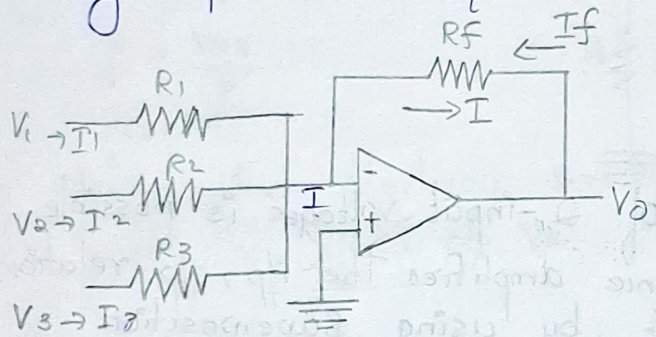

It is used in inverting configuration where V_1, V_2, V_3 are the inputs which are connected through R_1, R_2, R_3 respectively to the inverting terminal. The op will be sum of inputs, with the phase reversal.

From figure $I = I_1 + I_2 + I_3$

Since $I = -I_F$

$$-I_F = I_1 + I_2 + I_3$$


$$\frac{-V_o}{R_f} = \frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3}$$

9) $R_1 = R_2 = R_3 = R_f = R$


$$-V_o = V_1 + V_2 + V_3$$

$$V_o = -(V_1 + V_2 + V_3)$$

SUBTRACTOR OR DIFFERENCE AMPLIFIER

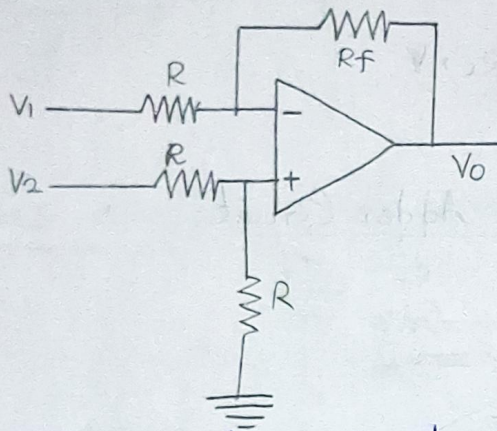

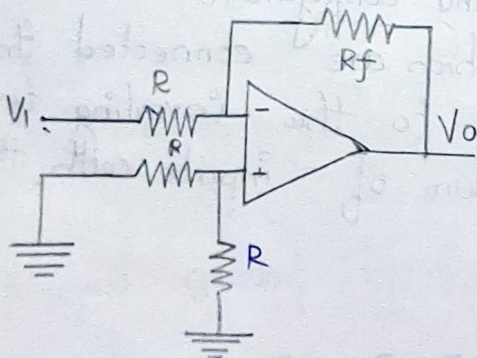
The subtraction of 2-input voltages is possible with using difference amplifiers. The i/p, o/p relation can be found out by using superposition theorem.



$$V_{o1} = -\frac{R_f}{R_i} \times V_1$$

$$\text{If } R_F = R$$

$$V_{O1} = -V_1$$

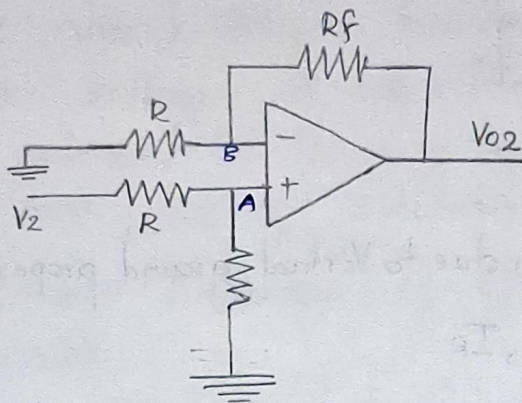

$$V_A = V_2 + \frac{R}{2R}$$

$$V_B = V_A = \frac{V_2}{2} \rightarrow (1)$$

V_A will couple to the -ve terminal of OP-AMP
So $V_B = V_A$

$$V_B = V_{O2} \times \frac{R}{2R} = \frac{V_{O2}}{2} \rightarrow (2)$$

Equate (1) eqn (1) and eqn (2)

$$\frac{V_2}{2} = \frac{V_{O2}}{2}$$

$$V_2 = V_{O2}$$

By taking the algebraic sum of V_{O1} and V_{O2} we can have the final op V_O

$$V_O = V_{O1} + V_{O2}$$


$$= -V_1 + V_2$$

$$\underline{V_O = V_2 - V_1}$$

INTEGRATOR

Integrator is a circuit whose op voltage is the integral of i/p voltage. An integrator without OP-AMP or transistor, is called passive Integrator.

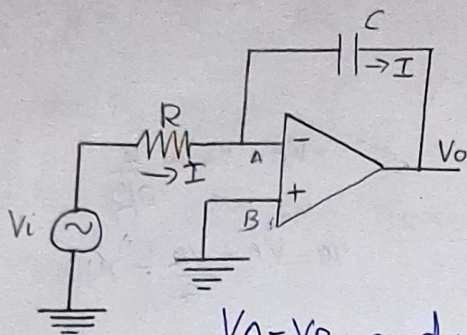While an integrator with OP-AMP active integrator



$V_A = V_B = 0$, due to Virtual ground property

Current through resistor, I_R

$$I_R = \frac{(V_i - V_A)}{R} = \frac{V_i}{R} \rightarrow (1)$$

Current through capacitor

$$I_C = C \cdot \frac{dV}{dt} = C \frac{d(V_A - V_O)}{dt}$$

$$I_C = -C \frac{dV_O}{dt}$$

$$I_C = -C \frac{dV_O}{dt} \rightarrow (2)$$

Since current through resistor = Current through capacitor

$$I_R = I_C$$

$$= \frac{V_i}{R} = -C \frac{dV_O}{dt}$$

Integrate both sides,

$$= \frac{1}{R} V_i - C \int \frac{dV_O}{dt}$$

$$= \frac{1}{R} \int V_i = -C V_O$$


$$\text{So } V_O = \frac{-1}{R_C} \int V_i dt$$

LIMITATIONS OF IDEAL INTEGRATOR

The OP-AMP has input offset voltage and input bias current. These two parameters produce an error voltage at output. This may cause OP-AMP to saturate. It is very difficult to pull fb, OP-AMP out of saturation.


Another limitation of ideal ^{OP-AMP} integrator is its low bandwidth.

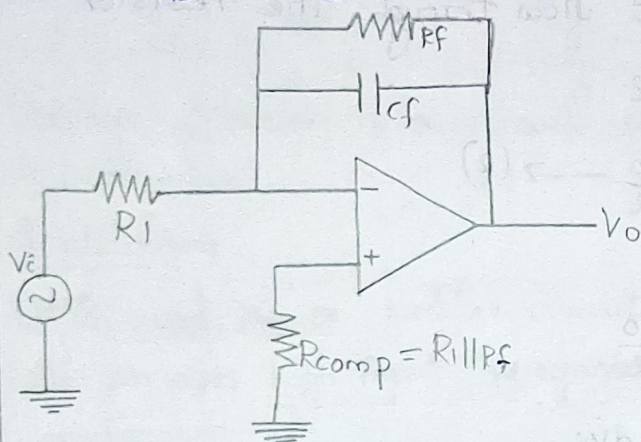Infinite gain at low frequencies, At DC C acts as an open circuit
PRactical Integrator Noise



Here the resistance R_{comp} or Compensation resistor R_s is used to overcome errors due to offset voltage and bias current and R_f reduces the voltage gain at low frequency and thereby preventing the OP-AMP from saturation.

DIFFERENTIATOR

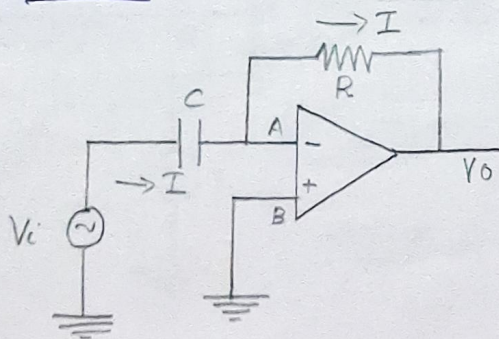

On this circuit the op is proportional to differential of input voltage. Here the terminal B is connected to ground and so the potential at B is will be coupled to terminal A

$$\therefore V_A = V_B = 0$$

Now the current through the capacitor,

$$I = C \frac{d}{dt} [V_i - V_A] \quad (V_A = 0)$$

$$I = C \frac{dV_i}{dt} \rightarrow (1)$$

The same current I flow through the resistor

$$I = \frac{V_A - V_o}{R}$$

$$I = \frac{-V_o}{R} \rightarrow (2)$$


Equate

Now eqn(1) and eqn(2)

$$C \frac{dV_i}{dt} = \frac{-V_o}{R}$$


$$V_o = -RC \frac{dV_i}{dt}$$

PRACTICAL DIFFERENTIATOR.

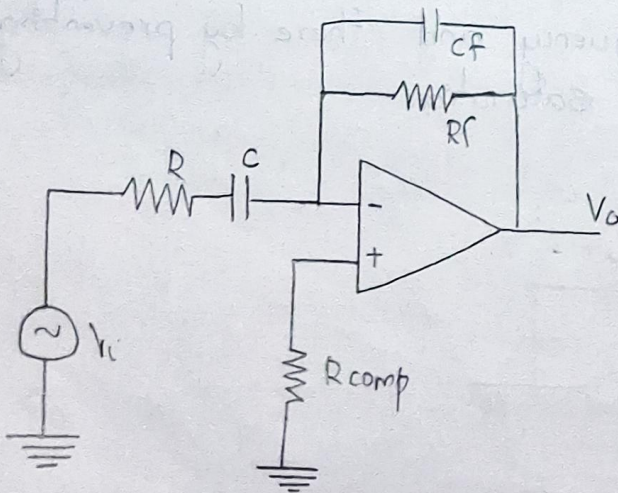

Through this circuit we can achieve, bias compensation, noise reduction and gain stability

VOLTAGE FOLLOWER

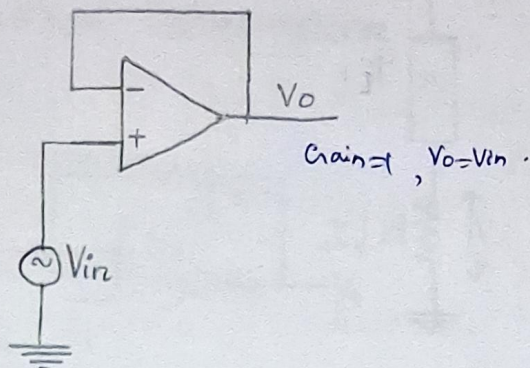

Voltage follower is a circuit whose gain is equal to 1 i.e., $V_o = V_{in}$.


Applications

- ★ It is used as a buffer circuit
- ★ It provides high input impedance for the amplifier.

VOLTAGE TO CURRENT AND CURRENT TO VOLTAGE CONVERTERS


V TO I CONVERTER

V to I converter with floated load

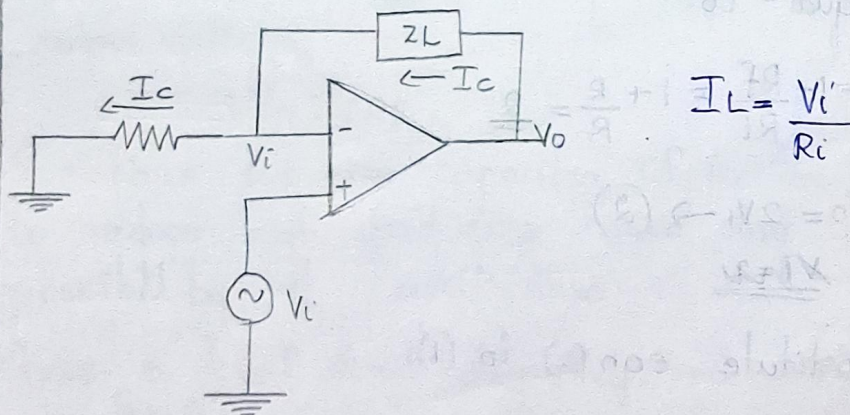


With floating load voltage to current converter
the expression for load current, I_L

$$I_L = \frac{V_i}{R_i}$$

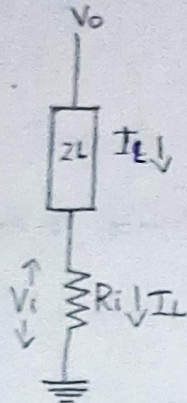

VTO I converter using grounded load.

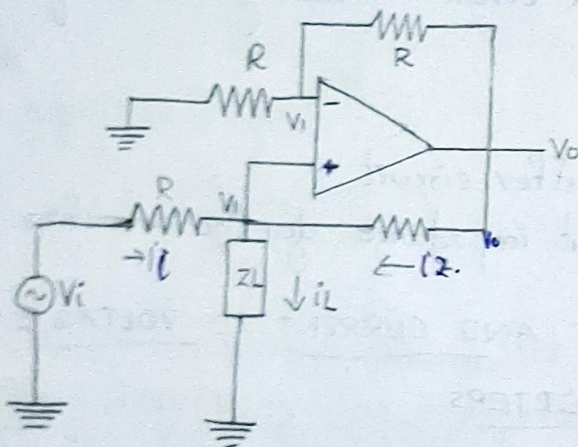

$$I_L = i_1 + i_2$$

$$I_L = \frac{V_i - V_1}{R} + \frac{V_o - V_1}{R}$$

$$I_L = \frac{V_i + V_o - 2V_1}{R} \rightarrow (1)$$

As it is configured in non-inverting type, the gain is equal to

$$\text{Gain} = 1 + \frac{R_f}{R_i} = 1 + \frac{R}{R} = 2$$

$$V_o = 2V_1 \rightarrow (2)$$


Ans

Then Substitute eqn (2) in (1)

$$i_L = \frac{V_i + 2V_i - 2V_i}{R}$$

$$i_L = \frac{V_i}{R}$$

CURRENT VOLTAGE CONVERTER

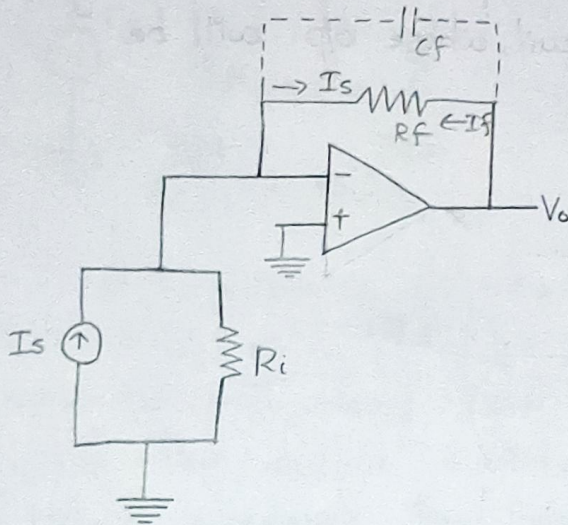

$$V_o = -I_s R_f$$

Photovoltaic cell, or photodiode etc gives an output current, which is directly proportional to incident energy or light. The current through the device can be converted into voltage by using current to voltage converter.

In figure, the entire source current I_s flows through feedback resistance R_f and expression for output voltage,

$$V_o = -I_s R_f$$


Sometimes we use capacitor C_f in the feedback to reduce high frequency noise and the possibility of oscillations.

- Q) Explain in detail about logarithmic and antilog amplifiers.
Fig, Eqn.


COMPARATORS

Comparator Circuit


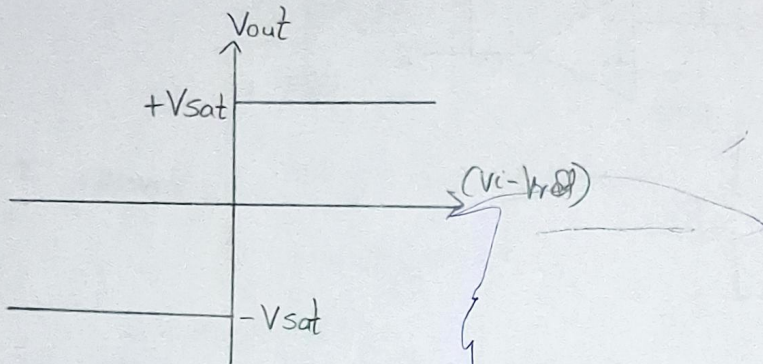
A comparator is a circuit which a signal voltage applied at one of the input with a non-reference voltage at the other input. It is basically an open-loop OP-AMP circuit, whose o/p will be $\pm V_{sat}$.



PRACTICAL CHARACTERISTICS


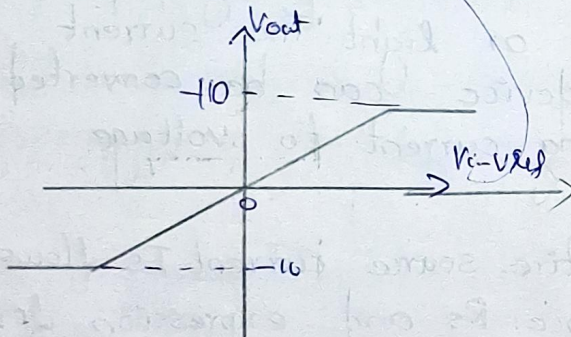


ZERO CROSSING DETECTOR

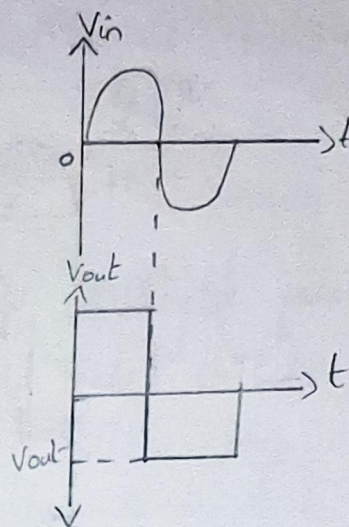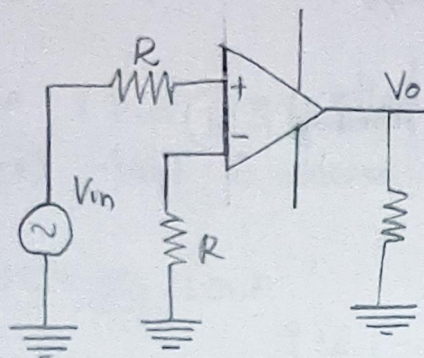



In a zero crossing detector, the reference voltage is set to zero. Figure shows a non-inverting zero crossing detector, where input is given to non-inverting terminal. The output switches between $+V_{sat}$ and $-V_{sat}$ whenever the input signal crosses the zero value. It is a sine wave to square wave converter.

SCHMITT TRIGGER

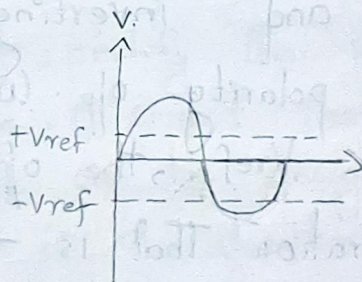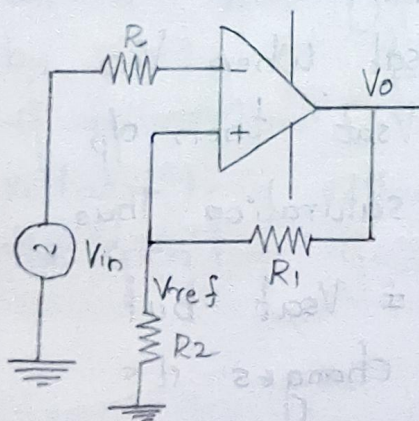

$$V_{ref} = +V_{sat} \times \frac{R_2}{R_1 + R_2}$$
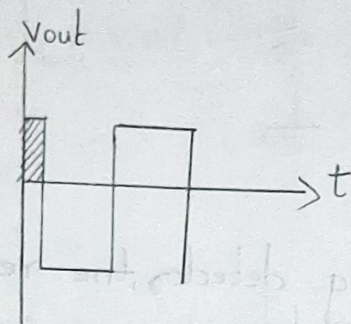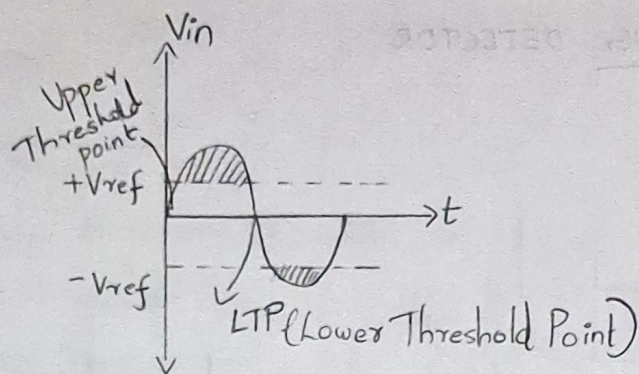
$$V_{ref} = -V_{sat} \times \frac{R_2}{R_1 + R_2}$$




Schmitt Trigger is a sine to square wave converter which uses a -ve feedback. Here the i/p applied to the inverting terminal and inverting mode produced opposite polarity o/p. When V_{in} is slightly more +ve than V_{ref} , the o/p gets driven into -ve saturation. That is $-V_{sat}$. When V_{in} becomes more -ve than $-V_{sat}$ then o/p gets driven into +ve saturation. Thus o/p voltage is always $\pm V_{sat}$ but voltage at which it changes its state can be controlled with R_1 and R_2 which forms voltage divider.

$$+V_{ref} = +V_{sat} \times \frac{R_2}{R_1 + R_2}$$

$$-V_{ref} = -V_{sat} \times \frac{R_2}{R_1 + R_2}$$

Here $+V_{ref}$ is called upper threshold point (UTP) $-V_{ref}$ is lower threshold point (LTP)


HYSTERESIS LOOP

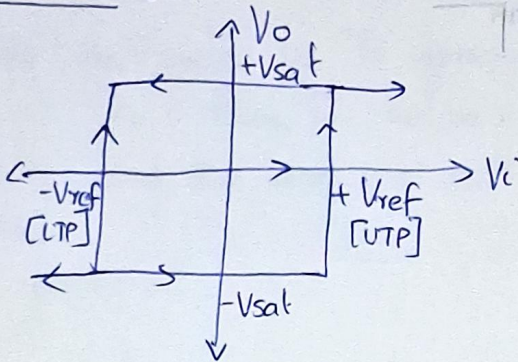


PRECISION RECTIFIER

The major function of a ordinary diode rectifier is that it cannot rectify the voltages below knee voltage. A circuit that acts as a ideal diode can be designed by placing a diode in the feedback loop of a OP-AMP where the cut in voltage (knee voltage) is decided by the open loop gain (A_{OL})

PRECISION HALF WAVE RECTIFIER

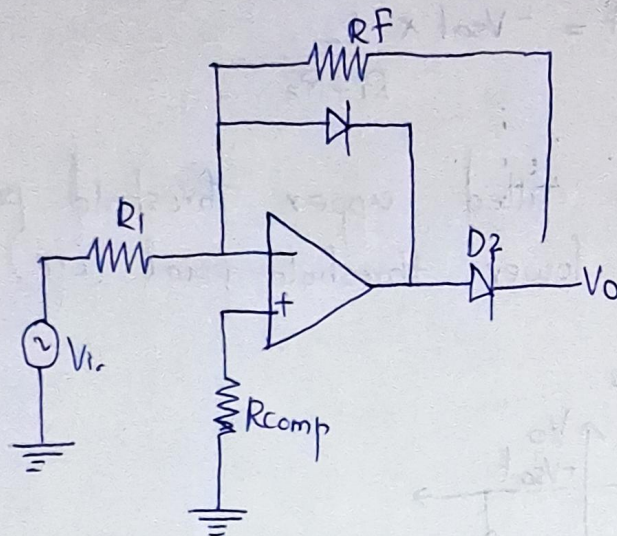


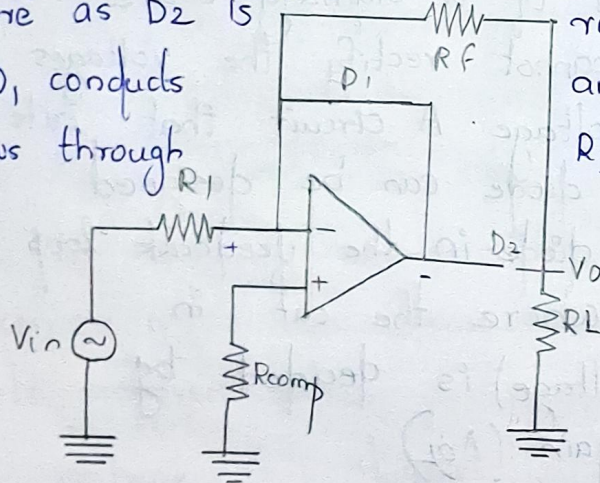During +ve half cycle diode D_1 become forward biased where as D_2 is reverse biased. $\therefore D_1$ conducts and practically no current flows through $R_F = 0$




So the o/p voltage $V_o = 0$


During -ve half cycle of input

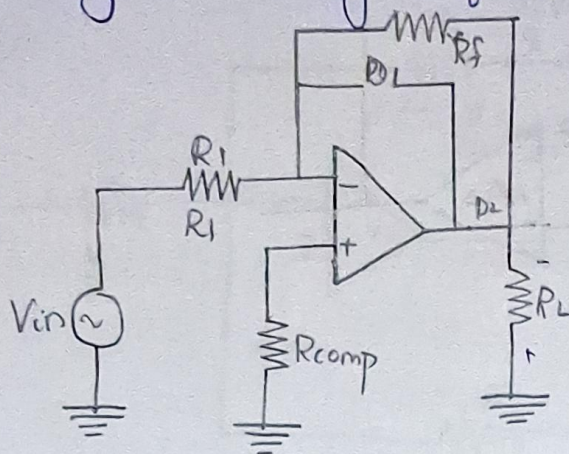

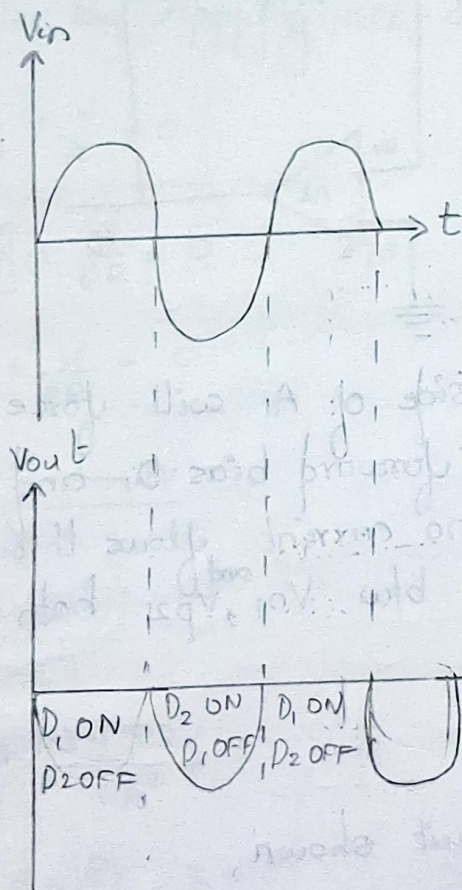
During -ve half cycle D_2 is forward biased at this time, the entire current flows through R_L and R_f and we will get an o/p voltage across R_L .



PRECISION FULLWAVE RECTIFIER

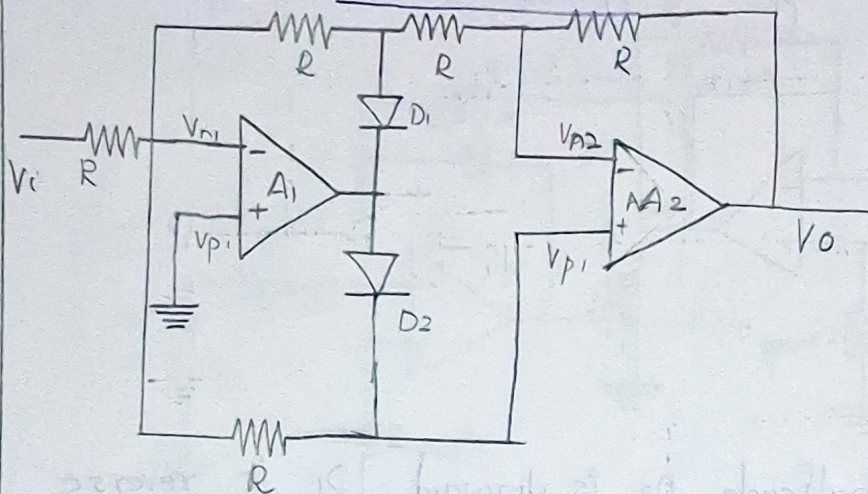

During +ve halfcycle, $V_{in} > 0$

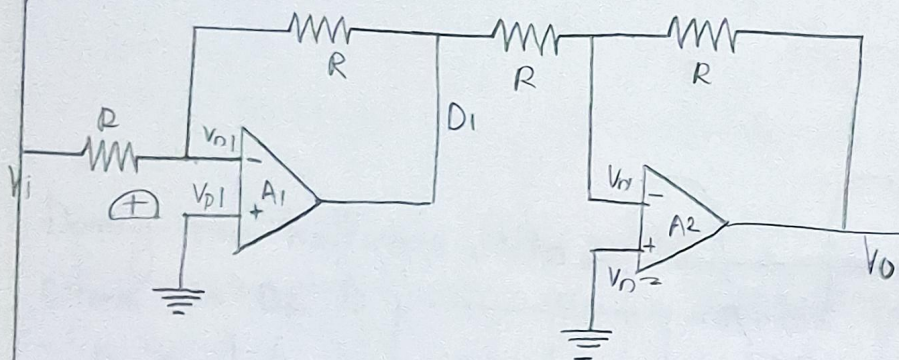

When $V_{in} > 0$, the inverting side of A_1 will force the o/p to swing -ve, thus forward bias D_1 and reverse bias D_2 . Since no current flows through resistance R connected b/w V_{in} and V_{p2} both are equipotential i.e;


$$\text{i.e., } V_{n1} = V_{p2} = 0$$

From the equivalent circuit shown,

$$V_o = V_{in} \left(\frac{-R}{R} \right) \times \left(\frac{-R}{R} \right)$$

$$V_o = V_{in}$$

During -ve half cycle

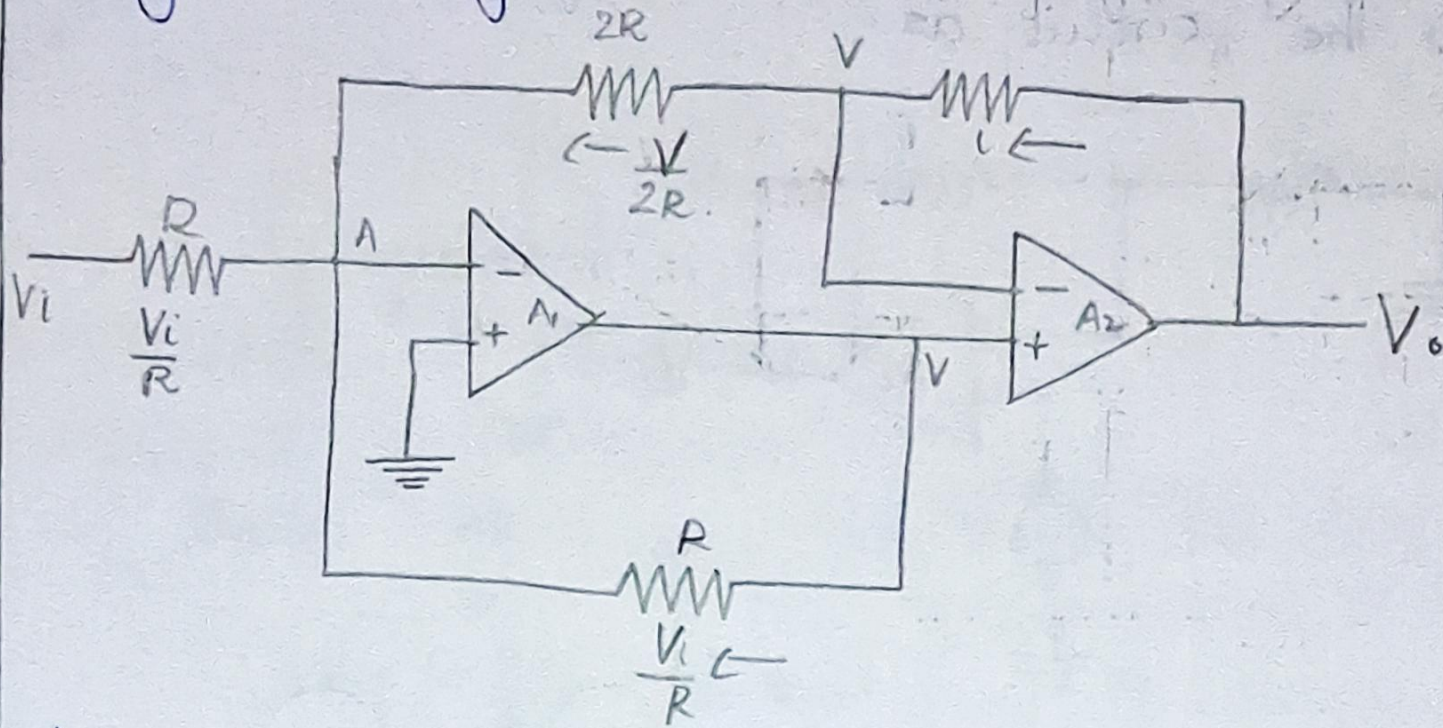

$\frac{V_i}{R}$ During -ve half cycle the op of A_1 swings to +ve making D_1 reverse biased and D_2 forward biased. So By Applying KCL at Node A


$$\frac{V_i}{R} + \frac{V}{2R} + \frac{V}{R} = 0$$

$$= \frac{V_i}{R} + \frac{RV + 2RV}{2R^2}$$

$$\frac{V_i}{R} + \frac{3RV}{3R^2} = 0$$

$$V = \underline{\underline{-\frac{2RV_i}{3}}}$$

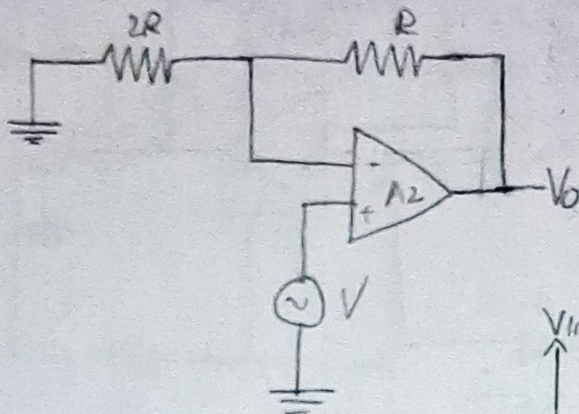In order to get final op in terms of V we will redraw the circuit as.



$$V_o = V \left[1 + \frac{R}{2R} \right]$$


$$= V \left[\frac{2R + R}{2R} \right]$$

$$= V \left[\frac{3R}{2R} \right]$$


$$V_o = V \times \frac{3}{2}$$

$$V_o = -\frac{2V_i}{3} \times \frac{3}{2}$$

$$\underline{V_o = -V_i}$$

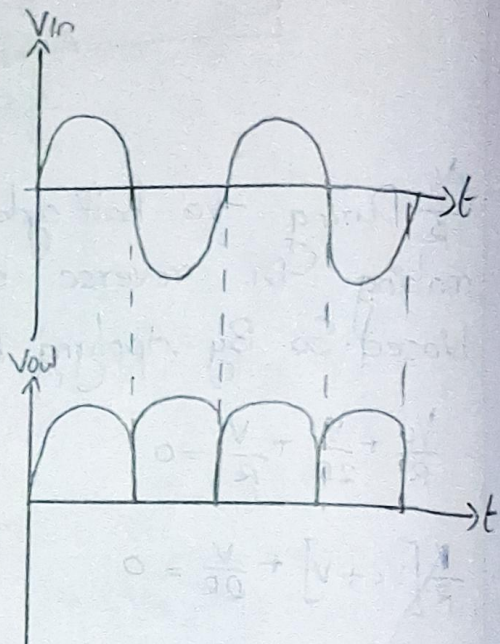

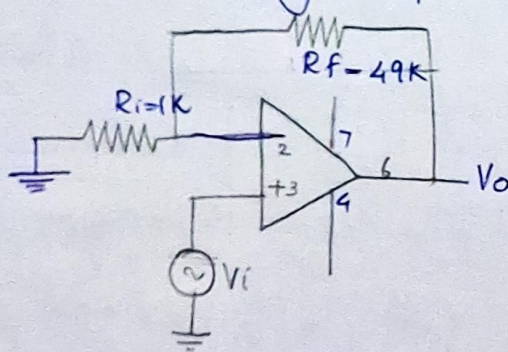? Design a non-inverting amplifier for a gain = 50



$$R_i = 1K$$

$$\text{Gain} = \frac{1 + R_f}{R_i}$$


$$50 = \frac{1 + R_f}{1 \cdot R_i}$$

$$50 = \frac{R_i + R_f}{R_i}$$

$$50 = 1 + R_f$$

$$50 - 1 = R_f, R_f = \underline{49K}$$

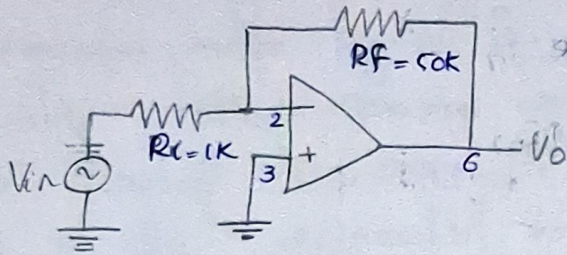2. Design an inverting Amplifier for gain 50



$$\text{Gain} = -\frac{R_F}{R_i}$$

$$50 = -\frac{R_F}{R_i} \quad R_F = 50K$$